FUNCTION GENERATOR EXPERIMENTS—BUILD A 2650 COMPUTER

$1.00 ■ MAY 1977

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

s programmable
IVIDE BY ANYTHING
equency divider

utomatic color TV
EATH PROGRAMMER
hanges channels for you

et your ears on
CB PREAMPLIFIER
oosts sensitivity

new radio rules
WARC '79
can affect you

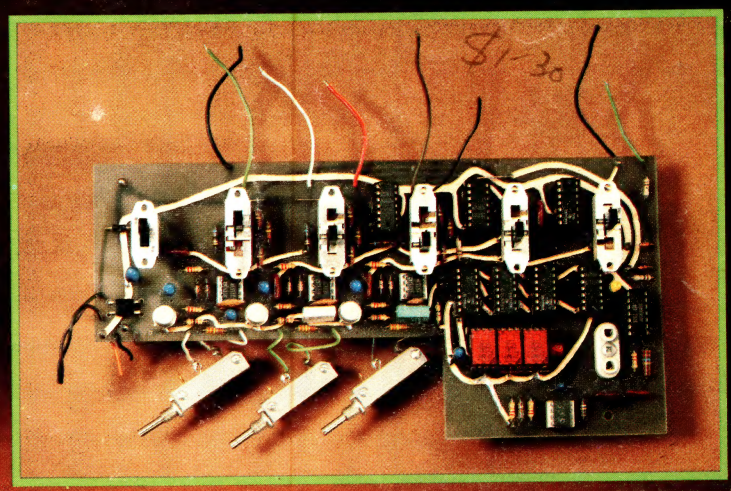

PLUS:

- ★ Hi-Fi Lab Test Reports
  - Nikko Amplifier
  - Heath Preamp
- ★ Jack Darr's Service Clinic
- ★ Komputer Korner
- ★ Equipment Reports
- ★ Step-By-Step Troubleshooting

A GERNSBACK PUBLICATION

Bally
FIREBALL!
PLAYERS
1 2 3 4
SCORE
293250
BALL IN PLAY
100
100
Bally

Pinball Computer

Your home, apartment or office can become an action entertainment center with America's first commercial-home pinball machine.

It's you against a computer. And the action and excitement from Fireball, your own computerized pinball machine, is nothing short of spectacular.

Fireball's computer replaces many of the mechanical, scoring, conventional electronics and sensing devices of a standard pinball machine. It's a dramatic change in pinball devices and the start of a new consumer electronics revolution.

DESIGNED FOR ACTION

Fireball contains flippers, bumpers, thumpers, flashing lights, sounds and a full-sized playfield. The glass covering the playfield is safe, shatterproof and specially tempered.

From one to four players can compete. Turn the unit on and simply program the computer with the number of players by pressing the start button up to four times. Each player's score is kept separately in a memory and appears on the display for each player's turn and at the end of the game.

The ball is automatically ejected and you pull the plunger to project it into action. The ball bounces from side to side from bumper to thumper. Lights flash and the scoring begins. You use the separately controlled flippers by pressing the flipper controls on the sides of the playfield which are low enough so that even a five year old can reach them.

Flip a switch and Fireball can be programmed for beginner or advanced skills although pinball is the only game everybody knows how to play within seconds after they step up to a machine.

"WE'RE IN THE MONEY"

The thrill of winning a bonus score or extra ball is enhanced by Fireball's songs and scoring tones. The computer's synthesizer plays seven songs—everything from "We're in the Money" when an extra ball is awarded to "The Party's Over" when the game ends. Various scores sound five additional tones making the game a total sight and sound experience. A volume control lets you keep it loud at a party or turned down in quieter surroundings.

COMMERCIAL PARTS AND FEATURES

Fireball contains the same heavy-duty devices and scoring features as a commercial pinball machine. The game has a tilt feature—tilt Fireball and a tilt sign glows and the scoring stops. The full-sized, full-color commercial playfield even has a special friction silk-screened surface so the ball will roll and not slide. Fireball differs from an arcade unit only by the start button which has replaced the coin slot and its new electronics. In fact, all future commercial machines will resemble Fireball within a year.

MANY NEW FEATURES

Fireball's computer is as powerful as the million dollar IBM computer sold in 1964. The solid-state LED scoreboard replaces the old electromechanical pinball scoring wheels so Fireball's backboard is thinner and its scoring more reliable. Its memory not only keeps track of everybody's score but the exact playfield configuration and extra bonus balls—something present arcade games can't do.

The American-made Bally Fireball—the first computer pinball machine designed for both home and office entertainment centers.

Although the playfield is just as large as the commercial machines, the entire unit has less weight, less bulk, and practically no service requirements making it ideal for the home or office. It takes up a space 2 feet by 4 feet and weighs 160 pounds.

HOW TO JUSTIFY PINBALL (TAKE THIS TEST)

If you paid more than $600 for either your TV set, stereo system or pool table—you should consider a pinball machine. You'll have more fun and action than watching TV, listening to your stereo or playing pool.

And when guests pop in, your Fireball will be the talk and highlight of their visit. Your TV and stereo are used primarily for private viewing or listening. Your pinball machine is for all times—from your personal family enjoyment to big parties. It's the great new idea in home entertainment.

TAX DEDUCTIBLE

Consider Fireball for your office as either an executive toy or a free new benefit for your office or factory employees during their breaks. You get both an investment tax credit and depreciation. Fireball combines participation, action and entertainment. A pinball machine is so intriguing that people pour dollars into them at arcades. It requires skill, sharpens responses and can become the single most talked about entertainment product in your home or office.

LASTING PLAY VALUE

Fireball, unlike the new TV games, is partially a game of chance and thus can never be mastered. Even an experienced professional can lose to a youngster. A daughter can beat her father, grandma can beat grandpa and the surprise of an upset is what adds to the long lasting play value. A professional pinball machine is an amusement game that you rarely get tired of—no matter how good you get, no matter how long you've played. Ask any arcade operator. His customers will tire of his video games which he continually rotates with newer models but his pinball machines are played and played and played.

Don't be confused. There are other games made by toy designers selling for one half the price. Fireball is not a toy and is built by a company that specializes in pinball machines. With all its sophistication it is the most service-free, quality pinball machine ever produced.

When you buy an expensive product you must be absolutely satisfied that you get the service and a solid company standing behind your purchase for many years to come. Fireball is backed by a substantial company, Bally—in business since 1931 and now the world's largest manufacturer of coin operated amusement games. JS&A is America's largest single source of space-age consumer products and also a substantial company—further assurances that your investment is well protected.

A FRANK DISCUSSION OF SERVICE

Fireball is a solid-state computer with its electronics condensed on integrated circuits—all hermetically sealed and all pre-tested for a lifetime of service. Fireball is also self-diagnostic. Let us say something goes wrong with the system. Simply press the test button on the back panel of your machine and the exact problem is displayed on your scoreboard in digits. Check the instruction booklet and simply remove the designated plug-in circuit board, light bulb or part and send it to the service department closest to you for a brand new replacement. Even your TV or stereo isn't that easy to repair.

Please don't think service requirements are common. They're not. But we wanted to assure you that service was such an important consideration in its design that Fireball practically repairs itself. And any defective component will be replaced free-of-charge during its one year limited warranty.

SHIPPING AND THE TRIAL PERIOD

Each Fireball comes in two sections with four metal legs. The two sections quickly bolt together with the top portion also plugging into the bottom to make all electrical connections. Within minutes after it arrives, your unit is ready to operate.

Attach the metal legs, plug it in and start playing. Don't even read the instructions on how to play it—you should know how within minutes. Then after you've played Fireball for awhile, go to your local arcade and play a standard $1500 pinball machine. It's only then that you'll realize how much more value you are getting with Fireball.

But let's be realistic. What if you don't like what you get? Simple. A toll-free call to JS&A and we'll arrange for the pick-up of your unit and we'll pay all the pick-up and return costs. And you can play Fireball for one month before you make up your mind.

A GUARANTEE OF SATISFACTION

The cost for your own pinball machine is $795 (Illinois residents add $39.75 sales tax) plus the freight which you pay upon receipt and which will run approximately $34 from our facilities in Northbrook to Los Angeles or less if you live closer. You can order Fireball with any major credit card by calling our toll-free number or you can send your check for $795 to the address shown below. We will then promptly ship your unit and advise you.

We back Fireball with an outstanding service program made possible by plug-in commercial components. We provide the opportunity to use Fireball for one month without obligation and if 1) it does not live up to every one of your expectations 2) for any reason you get tired of playing it, or 3) you don't find it more challenging after one month than when you first played it, give us a call and we'll pick it up at your door at our expense and refund your money. We provide fast service turnaround time should service ever be required and we have been in business for over a decade providing the same conscientious service that has built our company into America's largest single source of quality space-age products.

Why not let the fun and action of your very own pinball machine add to your home or office entertainment picture? We'll make just trying Fireball the best entertainment move you've ever made. Order one at no obligation today.

JS&A® NATIONAL SALES GROUP
Dept. RA One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-9000
CALL TOLL-FREE.... 800 323-6400
In Illinois call ..... (312) 498-6900
©JS&A Group, Inc., 1977

There's more to Realistic® 40-channel CB than just 17 added channels...

there's 17 years of know-how!

With so many new and unproven brands on the CB bandwagon, the reasons for buying Realistic are clearer than ever. Seventeen years' experience and sales of a million sets annually have shown us what it takes to be a leader:

Intelligent, reliable engineering. Easy-to-find sales and service — to the tune of 4800 Radio Shacks in the USA alone. And low prices that are possible only because Radio Shack is a do-it-yourself company, from factory to warehouse to sales counter.

Take a look at our new high-performance mobile transceiver, the TRC-467. Advanced phase-lock loop circuitry generates all 40 channels with an electronic precision far beyond the limits of the multi-crystal sets.

Three ceramic IF filters improve the selectivity for a whopping 80 dB of adjacent-channel rejection. An automatic noise limiter cuts pulse interference, and it's switchable for maximum clarity on stronger signals.

Illuminated signal strength/RF output meter and channel selector, LED modulation indicator — conveniences that make your CB easier and more fun to use. With dynamic plug-in microphone, adjustable mobile bracket, and power cables for any vehicle with 12 VDC positive or negative ground.

Come in today and see the TRC-467. Designed, manufactured and sold only by "the" CB experts — Radio Shack. Just 119.95*.

These two credit cards honored at most Radio Shacks.
*Prices may vary at individual stores and dealers.

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76107
OVER 5000 LOCATIONS IN NINE COUNTRIES

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

MAY 1977 Vol. 48 No. 5

BUILD ONE OF THESE

37 **Divide By Anything** (Cover Story)
It's a programmable frequency divider.
by George Baumgras

45 **Build A 2650 Microcomputer**
Part II: Troubleshooting and assembly.
by Jeff Roloff

60 **Make This Speaker Phone Yourself**
Easy project offers hands-off phone use.
by Jules Gilder

66 **Experiments With IC Function Generators**
Part III: More circuits using the XR-2206.
by R.M. Marston

70 **Boost Performance With This CB Preamp**
Simple solid-state unit plugs between your CB antenna and rig. Enhances receiver performance.
by George Sante

GENERAL ELECTRONICS

4 **Looking Ahead**
Tomorrow's news today. **by David Lachenbruch**

24 **Komputer Korner**
Microcomputer interfacing and internal registers within the 8080 chip.
by David Larsen, Jon Titus, and Peter Rony

30 **VIZ Pulse Generator (Equipment Report)**
We test the new VIZ WR-549A

77 **New Radio Rules**
Special report tells how WARC '79 can affect you.
by Stanly Leinwoll

HI-FI STEREO

42 **New Way To Room Equalization**
Shure equalization analyzer speeds setup of graphic equalizers for overall flat response.
by Len Feldman

56 **R-E Lab Tests Nikko Integrated Amplifier.**
Nikko TRM-750 rated "excellent" in overall sound quality.

58 **R-E Lab Tests Heath Preamp**
Heath AP-1615 earns a "very good" in our lab.

TELEVISION

49 **Heath Programmable Color TV**
Automatic circuitry changes channels for you. Digital program readout on the screen. Discover how it works.
by Art Kleiman

81 **Jack Darr's Service Clinic**
How does your service shop rate? **by Jack Darr**

87 **Reader Questions**
Radio-Electronics Service Editor helps solve reader problems.

DEPARTMENTS

98 **Advertising Index**
12 **Advertising Offices**
14 **Letters**
96 **Market Center**
7 **New & Timely**
88 **New Products**
92 **New Literature**
99 **Free Information Card**

ON THE COVER

Programmable divider provides a wide range of frequency division by using three cascaded 555-timer IC stages. The divisor is selected by three 10-turn potentiometers and indicated by an LED readout. Complete story starts on page 37 of this issue.

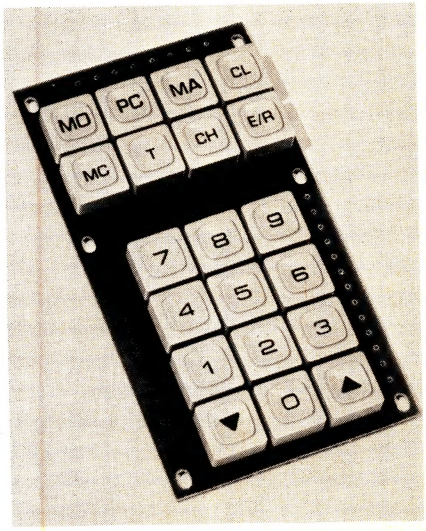

THIS KEYBOARD CONTROLS channel selection and programs a new TV set to automatically switch channels for you. It's an important part of Heath's programmer system. For full details turn to page 49.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, $8.75. Pan-American countries, $10.25. Other countries, $10.75. Single copies $1.00.

© 1977 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Microwaves and health: Government and private agencies are trying to determine what actually is a "safe" dose of microwaves—a subject in the spotlight since the discovery that the American Embassy in Moscow was being bombarded with low-intensity microwaves. The only existing standard today for safe exposure is 10 milliwatts-per-square-centimeter, established by the American National Standards Institute. Some tests indicate that this might be too high.

Is public health endangered by broadcast and other microwave transmissions? Initial results of studies indicate it is not. At ground level in immediate vicinity of broadcast transmitters at Mount Wilson, California (where the antennas of all Los Angeles TV stations are located), one study showed the maximum ambient radiation was four milliwatts and that the principal source of microwave radiation is UHF broadcast stations. If the safe level is found to be much lower than 10 mW, officials of the government's Office of Telecommunications Policy say some stations may be required to reduce their power. However, at present, experts feel that hazardous exposures are found only in occupational situations where people work on microwave-emitting equipment.

Backtalk on the cable: A major experiment in two-way cable TV will start this year in Columbus, Ohio. Warner Cable will offer the service to almost 100,000 homes there. It will feature a 7 × 6 × 2-inch home terminal that will permit subscribers to select programs, play interactive games, take tests, register their opinions instantly and "actually participate at home in TV programs and events." Warner Cable President Gustave Hauser says he expects to "see people participating in game shows, schools competing against other schools, communities against communities and so forth." Warner, which recently acquired video game producer Atari Inc., declined to give further details.

2-way game, 1-way cable: But you don't necessarily need a two-way cable system to play an interactive CATV game. Ralph Baer of Sanders Associates, who is regarded as the inventor of the video game, told a recent meeting of Gametronics in San Francisco that tests on cable TV systems in Boston and Akron showed several ways in which video games could interact with cable.

One experiment involved the CATV transmission of a colorful hockey playing field with four players moving at random—two goalies and two forwards. Game equipment developed by Sanders recognized the field and players, introduced them into the game logic circuitry and permitted interaction between the transmitted symbols and the viewer-manipulated locally generated players. He said CATV could also be used with microprocessor games, with digital data on game rules, character symbols and the like transmitted to storage equipment at the receiver terminal—in effect, programming the game via CATV. Another possibility would be viewer participation in quiz games sent over one-way cable.

Baer also forecast two-way game playing between homes by telephone connection and prerecorded home VTR or videodisc programs for interactive games. He predicted that game-playing capability would eventually be built into every home VTR or videodisc player.

CB stability promised: CB manufacturers and dealers are still reeling from the rough transition from 23- to 40-channel units, which caused severe dislocations and even a few bankruptcies. Now they're apprehensive that just when things get going again they'll be clobbered by new FCC efforts to move CB to a permanent home upstairs in the higher frequencies. But FCC Chief Engineer Ray Spence recently told the PC 77 trade show that the industry can "look forward to a period of stability with no new surprises." Other FCC spokesmen conceded the Commission was making long-range studies for new personal communication spectrum space, but said no action was planned which would eliminate the current 27-MHz band.

The FCC has proposed a ban on linear amplifiers in the 25–35-MHz band. These devices, designed for amateur radio, are being used illegally to boost power in CB equipment. The FCC has made no proposal to ban linear amplifiers in other ham bands, but it did propose a type-acceptance program for all amateur radio equipment, presumably to help block the manufacture of amplifiers that could easily be modified for CB use. The FCC proceedings are expected to be protracted, with amateur radio groups strongly opposed.

Another major problem faced by the CB industry is trying to convince prospective customers that 40-channel transceivers have as much "talk power" as the 23-channel transceivers. All manufacturers agree that rumors are rampant that the FCC rules make 40-channel transceivers less powerful. It's not true, but, like many rumors, it has some basis in fact. This is that some CB manufacturers lacking in engineering resources have reduced the percentage of modulation in order to meet the Commission's new tighter specifications. But the vast majority of well-known brands are said to provide full power and full modulation in their new transmitters. The entire problem—if you can call it a problem—undoubtedly has been exaggerated by dealers stuck with large quantities of 23-channel transceivers who have been bad-mouthing the 40-channel gear.

VTR fever rises: In a series of fast-breaking developments, the home videocassette recorder has taken a giant leap toward becoming the next major mass-market consumer electronic product in the United States, and the search for a "standard" system was sharply narrowed down:

continued on page 94

Convenience is only half the story.

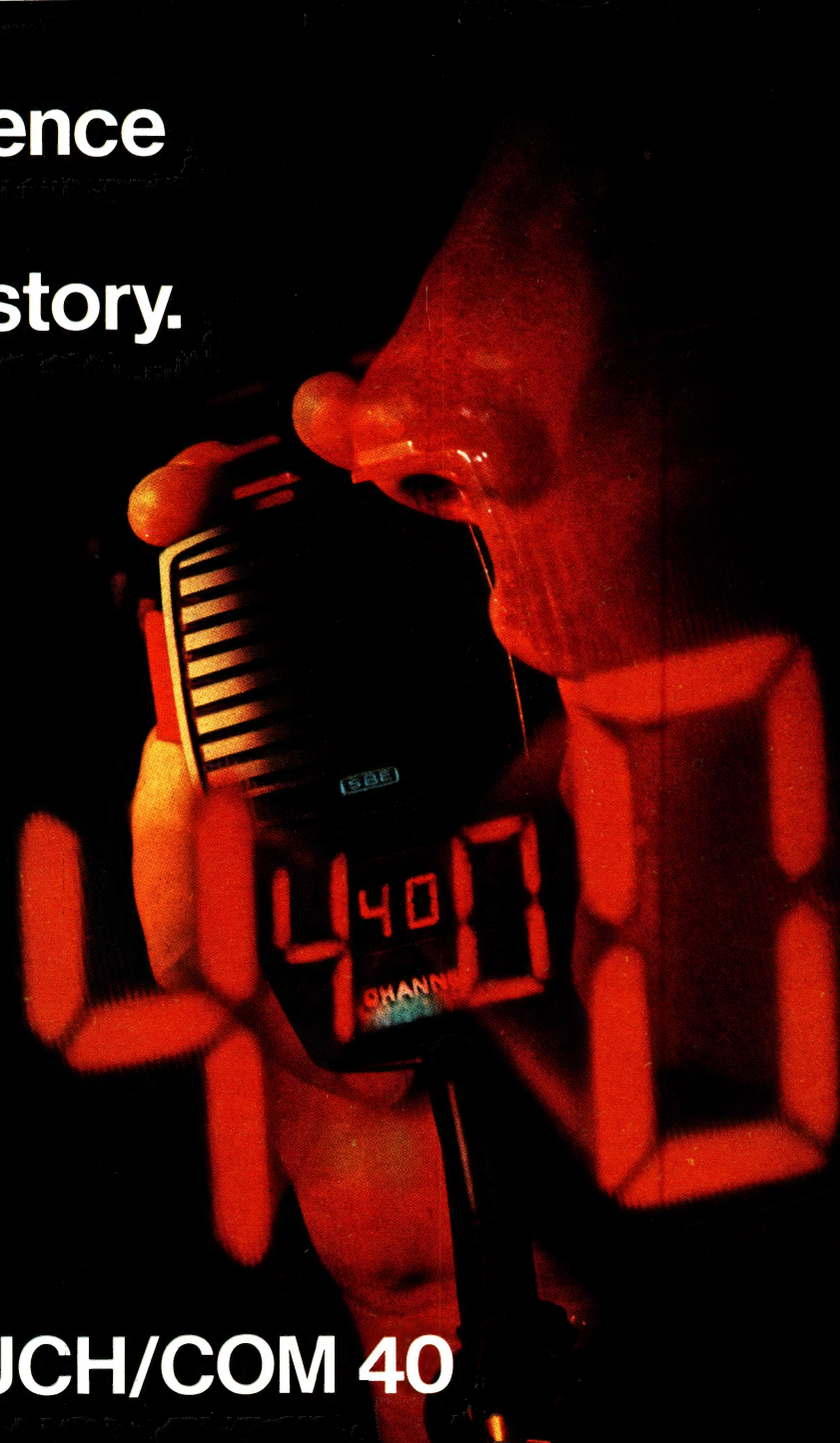

SBE TOUCH/COM 40

SBE adds the ultimate luxury to 40-channel operation: the convenience of microphone control that puts all CB functions right in the palm of your hand.

Quickly scan up or down through all 40 channels, or move channel by channel with the 2-speed channel selector. Identify your channel with the extra-large, high-intensity LED readout, clearly visible even in bright daylight. Adjust volume and squelch with the flick of a finger. And to transmit, simply push the "Press-to-Talk" control. It's all on the microphone.

But the convenience of TOUCH/COM 40 is only half the story. With such sophisticated features as SBE's "Speech Spander" voice-operated modulation level control, "Anti-Blast" audio burst protection circuit, 4-pole IF filter, delta tune, and MIC gain control, Touch/Com 40 offers top performance under the toughest operating conditions, plus dependability backed by 100 per cent quality control.

And that's the half of the story that is the most important to you.

SBE-43CB

SBE

Better Communications through Creative Technology

For complete information, visit your nearest SBE Dealer, or write SBE, Inc. 220 Airport Blvd., Watsonville, CA 95076

INTERNATIONAL OFFICES: E. S. Gould Marketing Co. Ltd., Montreal, Canada/Linear Systems S.A. Geneva 1, Switzerland

CIRCLE 28 ON FREE INFORMATION CARD

Digital Watch Breakthrough

There are several big changes taking place in digital watches. Here are all of them in one product.

Your digital watch is either too thick, uses up batteries quickly, has just a few functions or is hard to read under certain lighting conditions. You still have to press a button, flick your wrist, or hold your watch at just the right angle to read the time.

The digital watch industry has gone through four years of rapid change, but the disadvantages cited above have finally been resolved in one totally new product—the Sensor Laser 440 Digital. The Laser 440 is so different that it represents a dramatic departure from conventional digital watches.

NO BUTTON TO PRESS

There is no button to press since the display glows in the dark. A glass ampoule, charged with tritium and phosphor and sealed by a laser beam, is placed behind the new CDR (crystal diffusion reflection) display. When room lights dim, the self-contained tritium light source will compensate for the absence of light by glowing brightly and illuminating the display.

No matter when you wear your watch—day or night—just a glance will give you the correct time. There's no button to press, no special viewing angle required, and most important, you don't need two hands to read the time.

CHANGE YOUR OWN BATTERIES

The Laser 440 is only 8 millimeters thick—thinner than many of the so called thin digitals being advertised today. The new CDR display draws 100,000 times less current than an LED watch when displaying the time so your single commercially-available Union Carbide battery lasts years longer. In fact, part of our warranty includes all the batteries you'll ever need, free of charge, for five full years. To replace a battery, simply open up the battery hatch on the back of your watch, tap out the old battery and drop in the new one.

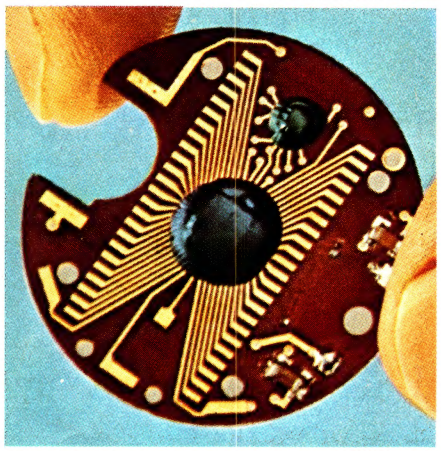

Most digital watches have dozens of electronic components. The Laser 440 has only six—two integrated circuits, a crystal and three microcapacitors. All components are bonded directly on the printed circuit board. By hermetically sealing the integrated circuits and using fewer components, the Laser 440 is considerably more reliable than other watches that do not yet have this complete integration.

The new Sensor Laser 440 digital watch glows in the dark so there's never a button to press to read the time in darkness or in sunlight.

THE ULTIMATE ACHIEVEMENT

Other manufacturers have devised unique ways to produce a watch you can read at a glance. The $300 LED Pulsar requires a snap of the wrist to turn on the display, but the Pulsar cannot be read in sunlight and its display uses 100,000 times the current of the Sensor display. The $400 Longine's Gemini combines both an LED and liquid crystal display. (Press a button at night for the LED display, and view it easily in sunlight with the liquid crystal display.) But you must still press a button to read the time. All these applications of existing technology still fail to produce the ultimate digital watch: one you can read under all light conditions without using two hands. Until the new Laser 440.

And if you've owned a digital watch for a year, chances are you've had it in for repair more than once—a very common consumer complaint. The Laser 440 is so service-free and has such high quality that it should rarely, if ever, require service. It is backed by a solid five-year warranty—your assurance of our commitment to this outstanding new product.

The Laser 440 has both time and stop watch functions. Six digits are on display—four large digits and two small ones. You choose between hours, minutes and seconds or hours, minutes and date by pressing a button. The Laser memory remembers the number of days in a month and resets automatically on the first day of the new month.

The 440 is also available in an 11 function chronograph (stop watch) and is truly the ultimate Laser timepiece. You can time two separate laps of a multilap race keeping one lap in memory. You can accumulate time; you can view the time of one lap while continuing to time a lap stored in memory. As a business executive, you can time long distance phone calls and interviews. Lawyers can keep track of their services, and doctors can time the vital signs of their patients. Even while the chronograph is functioning, you can still view the time—something even many of the expensive digital chronographs cannot do.

BUILT DIFFERENTLY

All wires have been replaced with circuitry printed on one single thin surface. On this same surface are two integrated circuits which use gold contacts and are hermetically sealed to protect their several thousand micro components. The American-made Laser is shock resistant and uses a tough mineral glass crystal to protect the rugged electronics from the everyday water and humidity tortures normally given any watch.

NEW QUARTZ BREAKTHROUGH

Digital watch accuracy depends on the quartz crystal. Even the best crystals change frequency with shock or age (especially when first produced). The Laser 440 uses the new and very expensive, tuning fork crystal. It is first aged to not shift frequency more than five parts per million per year (more accurate than most radio or TV time signals) so the extreme accuracy you expect is built into your watch from the first day you wear it. The crystal is cushioned and solidly bonded to the crystal carrier eliminating all fine wires that may break from shock. In short, the advanced design of the crystal will assure guaranteed accuracy greater than 5 seconds per month—year after year after year.

The Laser 440 is ideal for pilots because of its cockpit visibility and chronograph functions, perfect for the businessman who depends on his watch for split-second accuracy and the ultimate watch for anybody who wants unquestionably the finest digital watch ever offered at any price.

The Laser 440 is not only thin but is designed to conform to the contour of your wrist. A bulky digital watch can become annoying to wear—especially if you have a thin wrist.

HOW WE PROVIDE THE FINEST SERVICE

Can our company provide better service than even your local jeweler? We think so. If your Laser malfunctions during its unprecedented five-year warranty, just call us on our toll-free line. We have made arrangements with United Parcel Service to pick up your Laser at your door, at our expense, and we give you a loaner watch to use while your Laser is repaired. You pay nothing to have your watch serviced during its five-year warranty (that is if service is ever required) and we are as close as your phone or door.

WHO WILL BACK YOUR 5 YEAR LIMITED WARRANTY

Two solid companies are behind your new Laser. JS&A is America's largest single source of space-age products—a substantial company and a leader in electronics for over a decade. Our commitment to the consumer and to service is a matter of record. Check with the Better Business Bureau in your very own community, the Northbrook, Illinois Chamber of Commerce (312) 498-5555, or any of the 100 national magazines and newspapers in

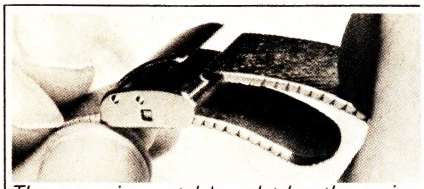

The expensive metal bracelet has the equivalent of 92 finely-hinged links and is completely adjustable. Simply slide the adjustment mechanism to the most comfortable position on the band for your wrist size and lock it into place. Then, whenever you have to put on your watch, simply hook the strap into the already pre-set adjustment mechanism and snap it shut. It's fast and simple and gives you the most comfortable fit of any watch by conforming exactly to the contour of your wrist.

which we advertise. We realize that a quality watch warranteed for five years is a serious investment and our reputation for service and customer satisfaction must be unsurpassed. Most important, check with our customers. For almost two years we have sold and serviced the Sensor watch. We are proud of our record and will gladly share it with anyone who inquires.

The Sensor Laser 440 is manufactured exclusively for JS&A by Micro Display Systems, a leader in the new emerging watch technology and a well-financed company backed by one of the world's major manufacturers.

STANDING BEHIND A PRODUCT

The Laser 440 is everything you would want in a digital watch: a major advance in digital watch technology, all the really important functions you'll need, a service contract so solid that you'll never have to leave your home if service is ever required, and a product of unsurpassed quality and accuracy. But it is only after you receive it that you will convince yourself of its beauty, its design, its fit and the accuracy of our claims. For that reason we give you a one month trial period. Wear the Laser 440 for one full month. Check its accuracy, its feel and show it to others. Compare it to all other digitals. If you are not totally convinced that the new Laser is the finest digital watch at any price, then return it for a prompt and courteous refund.

To order your Laser 440 for a personal trial, simply call our toll-free number below and give us your credit card number or send us your business or personal check. There are no postage or handling charges (Illinois residents add 5% sales tax) and it will be sent to you promptly by United Parcel Service unless you specify otherwise.

A REVOLUTION IN TECHNOLOGY

There is a revolution taking place in the watch industry. Some digitals are getting thinner, some have dozens of new functions and some claim exceptional visibility. None have all the features in one quality timepiece. The new Laser 440 does. Order yours at no obligation today.

White Gold With Time and Date $139
Gold-plated With Time and Date 159
White Gold With Chronograph 199
Gold-plated With Chronograph 219

JS&A ranked first among all watch manufacturers in total unit sales of quality digital watches during 1976.

JS&A® NATIONAL SALES GROUP

Dept. RA One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-9000

CALL TOLL-FREE. . . . 800 323-6400
In Illinois call . . . . . (312) 498-6900

©JS&A Group, Inc.,1977

new & timely

Zworykin elected to Inventors Hall of Fame

DR. VLADIMIR K. ZWORYKIN as he appeared when he invented the tube he is holding—the iconoscope that made our present television transmitting technology possible.

Dr. Vladimir Kosma Zworykin, television pioneer, has been elected to the National Inventors Hall of Fame, joining such notables in the communications world as Marconi, Bell, Morse, and Edison, and the three inventors of the transistor.

Vladimir Zworykin was graduated in 1912 from the St. Petersburg Institute of Technology, where he made his first contact with television as student-assistant to Professor Boris Rosing. Afterward he did post-graduate work at the College de France in Paris, returning to Russia at the outbreak of war in 1914.

Coming to the United States after World War I, he first worked for Westinghouse, and received his Ph.D in Physics from the University of Pittsburgh in 1926. In 1929 he joined RCA as director of the Electronic Research Laboratory. In 1947 he was elected a vice president and consultant for RCA Laboratories, and after his retirement in 1954 was made an honorary vice president and provided with an office at the David Sarnoff Research Center

Infrared light controls home slide projectors

In keeping with the trend toward the use of infrared light for remote control of electronic domestic equipment, Siemens says, they have come up with an idea for controlling home slide projectors. The simplicity of slide projectors makes circuitry much less complex than for, say, a TV set. Only four channels are needed, two to move the slide cassette forward and back, one for the projection lamp and one to control room lighting (a floor or table lamp is hooked into the circuit).

The Siemens device uses pulses transmitted sequentially on a fundamental frequency of 31.25 kHz. The pulse lengths, starting at 1.5 ms, are staggered by 0.5 ms from one channel to the next. Three infrared output diodes are driven by a Darlington circuit. Range is about 15 meters, and the low power consumption permits sending 30,000 instructions with a single 9-volt battery.

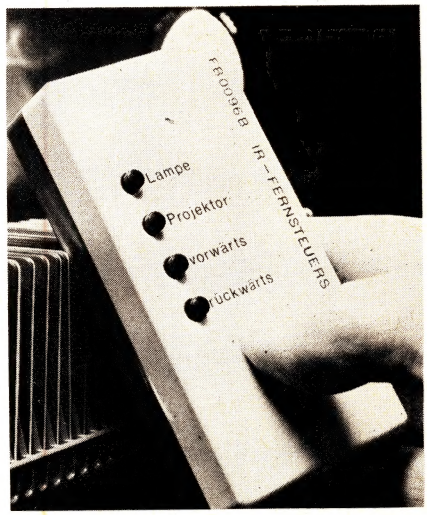

NEW INFRARED REMOTE CONTROL. Channels are *Lamp* (electric light for room illumination) *Projector, Forward* and *Back.*

In the receiver, a photodiode, a tuned circuit and transistor pick up the infrared signals and pass them to an integrated circuit that was originally developed as a video IF amplifier and is thus a low-priced item. A decoder then suppresses all pulses of less than 1 ms to clear out interference and noise. The individual signal lengths are then examined and allocated to their correct channels.

Engineering Consortorium offers computer courses

The 1977 Professional Growth in Engineering Spring Program of the National Engineering Consortorium features *Minicomputer, Microcomputer* and *Modern Signal Processing* as well as *Design and Production of Hybrid Circuits*. Eight programs are being presented during the week of May 22–27, 1977, at Pheasant Run Lodge, St. Charles, IL.

continued on page 12

Where do the pros get their training?

Almost half of the successful TV servicemen have home study training and with them, it's NRI 2 to 1.
It's a fact! Among men actually making their living repairing TV and audio equipment, more have taken training from NRI than any other home study school. More than twice as many!

A national survey*, performed by an independent research organization, showed that the pros named NRI most often as a recommended school and as the first choice by far among those who had taken home study courses from any school. Why? Perhaps NRI's 62-year record with over a million students . . . the solid training and value built into every NRI course . . . and the designed-for-learning equipment originated by NRI provide the answer. But send for your free NRI catalog and decide for yourself.

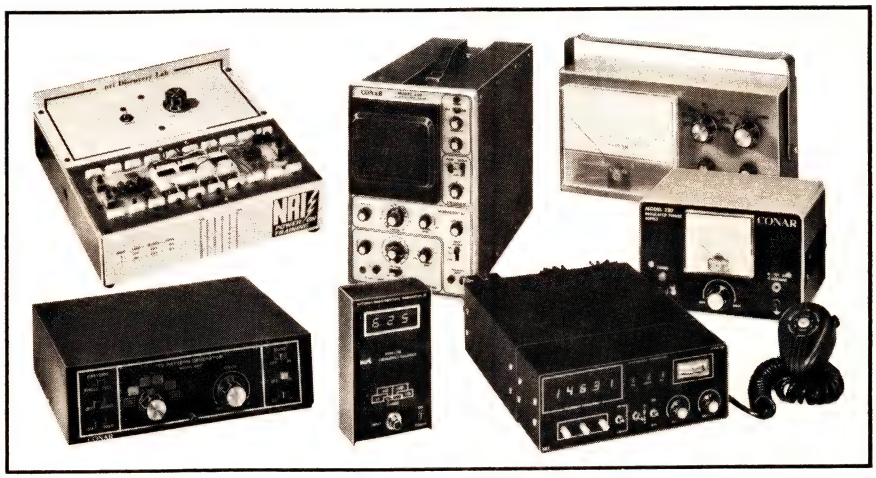

25" Diagonal Color TV... And 4-channel Quadraphonic Stereo.

As a part of NRI's Master Course in color TV/Audio servicing, you build a 25" diagonal solid state color TV with console cabinet. As you build it, you perform stage-by-stage experiments designed to give you actual bench experience. *And* you get a Quadraphonic system with 4 speakers. NRI's instruments are a cut above the average, including a transistorized volt ohmmeter, triggered sweep 5" oscilloscope, CMOS digital frequency counter and digital integrated circuit color TV pattern generator. They're top professional quality, designed to give you years of reliable service. You can pay hundreds of dollars more for a similar course and not get a nickel's worth extra in training and equipment.

Two Famous Educators... NRI and McGraw-Hill.

NRI is a part of McGraw-Hill, world's largest publishers of educational material. Together, they give you the kind of training that's geared for success . . . practical know-how aimed at giving you a real shot at a better job or a business of your own. You learn at home at your convenience, with "bite-size" lessons that ease learning and speed comprehension. Kits designed to give you practical bench experience also become first-class professional instruments you'll use in your work.

Widest Choice of Courses and Careers.

NRI doesn't stop with just one course in TV/Audio servicing. You can pick from five different courses (including an advanced color course for practicing technicians) so you can fit your training to your needs and your budget. Or, you can go into Computer Technology, learning on a real, digital computer you build yourself. Communications with your own 400 channel digitally-synthesized VHF transceiver. Aircraft or Marine Electronics. CB, Mobile Radio, and more.

Free Catalog... No Salesman Will Call.

Send the postage-paid card for our free color catalog showing details on all NRI electronics courses. Lesson plans, equipment, and career opportunities are fully described. Check card for information on G.I. benefits. No obligation, no salesman will call. Mail today and see for yourself why the pros select NRI two to one!

If card is missing, write,

*Summary of survey results upon request.

NRI McGraw Hill

NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016

new & timely

continued from page 7

Introduction to Micro/Minicomputers, May 22–24.

Microcomputer Basics and Programming, May 22–24.

Successful Design/Project Management of Micro/Minicomputer Systems, May 22–24.

Modern Signal Processing Design Techniques, May 22–24.

Microcomputer Architecture Interfaces and System Design, May 25–27.

Micro/Minicomputer Software Development and Systems Diagnostics, May 25–27.

Minicomputer Architecture, Interfaces Programming and Applications, May 25–27.

Design and Production of Hybrid Circuits, May 25–27.

The National Engineering Consortorium, Inc., is a nonprofit educational group serving the engineering community. Registration fee for each program is $395, for two programs $595. The registration fee includes the notes, lunch and dinner. Interested individuals may write the NEC Registrar, 1211 West 22nd St., Oak Brook, IL 60521, or phone (312) 325-5700.

INTERNATIONAL EXCHANGE OF IDEAS

AUSTRALIAN ABORIGINE, on visit to the University of Kansas, after demonstrating the art of the boomerang (and the ceremonial decoration required with it) to students of the William Allen White School of Journalism, learns something of American television technology using an Asian (Sony Videocorder) camera.

H. Potts, J. Peelee, R. Kulp are Gernsback Award winners

Harold R. Potts, Jr., John Peelee and Raymond B. Kulp, all correspondence students of the Capitol Radio Engineering Institute, are the Gernsback Award winners this month. The Gernsback Memorial Award is a check for $150 presented to an outstanding student in each of eight leading electronics home-study schools each year. Through the generosity of manufacturers, two supplemental awards of test instruments are given to the second-place and third-place student in each school.

Mr. Potts of Havelock, NC, says:

"My background goes back to my high school days. I was introduced to the world of electronics with a course in Basic Electricity. I enrolled in Electronics II the next year. But when I graduated, I realized I couldn't afford college right away. My alternative was to join the services, attend their schools and gain practical experience, then attend college under the GI Bill after my discharge. In 1974 I enlisted in the Marines with guaranteed training in electronics.

"Since then I have attended Basic Electronics classes for three weeks, and the Precision Measurement Equipment Calibration and Repair School in Denver, for 33 weeks. At my present duty station I have taken various classes on test equipment.

"I am currently involved with the core program of CREI and intend to go on to as many electives as I can. I receive technical training once a week at my laboratory and now I even instruct on some of them."

Mr. Peelee, of Springfield, VA, also started electronics as a freshman in high school, supplementing school courses with a night course in black-and-white and one in color TV repair, both given by the Fairfax Co. schools adult education division. At the end of his junior year, he worked part time for a local repair company. He started with CREI half way through his senior year, and on graduation started his own repair business. Now an electrical engineering student at the University of Virginia, he says "I am fixing electronic equipment this summer (1976), taking two electives at George Mason University, finishing CREI and getting a first class radiotelephone license. I will be graduated from UVA with a BSEE next May."

Raymond Kulp, second runner-up, works for Ford Aeroneutronics in Lansdale, PA. He reports:

"My CREI course has helped me in my work many times, especially the lessons on solid-state devices. An example is a problem we were having with a power supply. There was a Zener diode regulating a supply that always caused an FM oscillation problem. I found the Zeners used were the soft-knee type and the Zener point at the high end was right on the knee of the curve, giving little regulation on the high end. We have since gone to a sharp-knee Zener and the problem has virtually disappeared."

Mr. Potts receives the $150 Scholarship Award, Mr. Peelee a digital multimeter from B & K, and Mr. Kulp a Special Service Multimeter from VIZ.

Radio-Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, KOD-6694
editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Robert F. Scott, CET, W2PWG,
KXK-8533, technical editor
Arthur Kleiman, KTZ-3288,
managing editor
Jack Darr, CET service editor
Leonard Feldman
contributing high-fidelity editor
Karl Savon, semiconductor editor
David Lachenbruch, contributing editor
Rudolph F. Graf, contributing editor
George Whalen, contributing editor
Vincent P. Cicenia, production manager
Dale Allinson, production assistant
Harriet I. Matysko, circulation director
Sheila Wertling, circulation assistant
Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen
Cover photo by Walter Herstatt

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature.*

Radio-Electronics magazine is published by Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400

President: M. Harvey Gernsback

Vice President: Larry Steckler

Treasurer: Carol A. Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST
Stanley Levitan, KZA-5580
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.
Ralph Bergen, KXD-8396
Jim Reilly
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, IL 60646
(312) 792-3646

PACIFIC COAST
Mountain States
Jay Eisenberg, KYF-3277
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

SOUTHEAST
J.E. Publishers Representative Co.,
214-387-2424

Vaco.

Super Case

Vaco means value and variety.

Like our Super Case. A great value with great variety. 48 professional problem-solving tools from screwdrivers and nutdrivers to pliers, wrenches, crimping tools, and more! All right at hand. And all unconditionally guaranteed.

You'll find the Super Case and all the other fine Vaco tools in our exciting new 64-page Bicentennial Catalog. FREE for the asking! Just write:

Vaco Products Co., 510 N. Dearborn St., Chicago, Illinois 60610.

CIRCLE 64 ON FREE INFORMATION CARD

B&K-PRECISION COLOR GENERATORS

easy to use... reliable

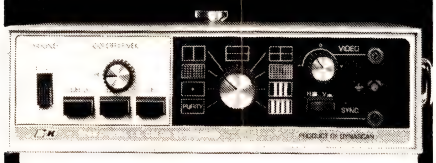

B&K-PRECISION
Model 1248-$175

Use it as a portable analyst

to localize TV problems at the customer's location. The 1248 has nine precise color patterns, with RF, IF, video, sync and sound outputs for signal substitution to let you locate the problem faster. Patterns are digitally generated. IF and RF outputs crystal-controlled. With carrying case.

B&K-PRECISION
Model 1230-$98

Compact and rugged!

Discrete TTL IC reliability and all metal case construction are just two of the ways the 1230 is built to last. Pattern quality compares with much larger generators. Generates 9 x 11 dots, 9 x 11 crosshatch, gated rainbow and purity. Just 1¾ x 5 x 7¾". AC powered.

Both available from your authorized distributor, or write for detailed specifications.

B&K PRECISION
DYNASCAN CORPORATION
6460 West Cortland Avenue
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Ontario
Intl. Sls: Empire Exp., 270 Newton, Plainview, N.J. 11803

CIRCLE 62 ON FREE INFORMATION CARD

letters

DIGITAL ALARM CLOCK

I built the "Digital Alarm Clock" that appeared in the November 1976 issue. Works fine and I am pleased. I used the complete kit of parts and "case" that were available.

I made a few changes that might interest you. They were improvements, naturally. I mounted a normally-open pushbutton on top in place of S2, the snooze switch. I mounted S1 and S3 on the rear of the PC board and added a 2 × 6 × 8-inch wooden base to hold the clock upright. I used the vacant space left by moving S2 to add a SPST switch (RUN-STOP) in series with the lowest position of S3 (FUNCTION). Now when I turn the alarm off, I don't accidentally put the clock in stop mode. Lastly, I found the display brightness excessive at night although the automatic brightness feature was working correctly. I added a switch in series with the + lead of C4, the +95 volt filter. Opening this produces some display flicker but greatly reduces the brightness by cutting the display duty-cycle even further. Hence I now have six brightness levels in two ranges.

Too bad the cost of this circuit is so high. It has all the features I wanted so I paid my money and got what I wanted; alarm, snooze, seconds display but smaller than the rest of the display, automatic brightness control, no LED's, and visible at night (no LCD). I may switch to a transformer for the +17-volt supply to cut the power consumption a bit.

The only gripe relates to the oxidized leads on the Mostek MK50252 chip and no socket. Either leads should be solderable or sockets should be used. A bit of sandpapering solved the problem, but not without fear of zapping the chip.

O. C. BARR
Richland, WA

AUTOMOBILE PROJECTS

As one of millions of tinkering hobbyists, I enjoy both automotive and electronic pursuits. I have been meaning to write you to thank you for the Electronic Ignition I found in your May 1976 issue.

However, that only whet my appetite! I began searching the library's stacks for digital speedometers, tachometers, etc., and came away disappointed. Available plans featured dissimilar displays, too few common parts and no common power supply seemed adaptable.

So, I have a suggestion for you! How about a series of construction articles for the following projects: Digital speedometer, digital tachometer, digital odometer, digital clock (with digital stopwatch, rally & race), water temperature gauge with LED display, transmission oil temperature with LED display, oil pressure gauge with LED display, ammeter with LED display, manifold vacuum gauge with LED display, LED display ignition monitor (displaying kV output from the coil), LED display digital dwell meter (unless you can arrange a diode and LED triggered replacement for the points in your ignition system), a central computer with exhaust emissions monitor to diagnose and troubleshoot problems.

The reason I mention a series of articles on these is simply that budget constraints preclude the purchase of all the parts in one lump sum. Monthly purchases would be most amiable.

An LED-tuned AM/FM Stereo and CB Monitor radio would be ideal as an addendum to these, especially with low-distortion op-amp construction.

As to construction techniques, I recommend Vector board, breadboarding and/or wire-wrapping followed by immersion in clear epoxy for heat sinking and vibration proofing.

You could continue the series with radar and laser speedtrap detection devices, anti-theft and alarm devices, (to protect our investments), navigation-type computers for us rally nuts, accelerometers for us drag racing nuts (accelerating and braking both), accelerometers to measure side G-forces, an on-board computer terminal, computer and microprocessor and the list is endless.

Pardon my verbosity but I want my own digital dashboard (and have wanted for so long) and the juices flow when I think too long on the subject.

JON CUMMINGS
Colorado Springs, CO

We agree! However, the one never-ending problem plaguing construction articles of this type is in the area of transducers. No one seems to be supplying transducers of this type to hobbyists. We would like to hear from any readers with ideas on this subject.—Editor

OOOOPS!

It was unfortunate to see our 23-channel CB Analyzer model GN-1375B in the New Products section of your February 1977 issue of **Radio-Electronics.**

Nikoltronix Co. was the first company to produce CB analyzers (1975) and the 23-channel CB Analyzer has established itself as the most compact, complete, and contemporary CB analyzer on the market. Since 1975, the 23-channel CB Analyzer has been continuously modified so as to meet the needs and requirements of the changing CB market; it is now equipped to service 40-channel CB radios since No-

continued on page 16

One Call.
Your Mallory distributor's got them all.

Take the search and wait out of your electronic parts finding.

Go straight to your Mallory distributor, by phone or in person.

Get to know the convenience and economy of simplified single-source buying. To deliver exactly what you want in parts, quality, and quantity. Immediately from stock on hand, or in most cases within 24 hours from the factory.

Your Mallory distributor goes all out for his Number 1 VIP . . . you. Get in touch with him soon. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Box 1284, Indianapolis, Indiana 46206. (317) 856-3731.

MALLORY

Capacitors • Controls • Fastening Devices • Resistors • Security Products • Semiconductors • Solderless Terminals • Switches

CIRCLE 60 ON FREE INFORMATION CARD

If your cartridge is more than three years old, don't replace your stylus!

Don't get us wrong. There is nothing worse than playing your records with a worn stylus. And no better way to restore your old unit to its original glory than a new diamond.

But frankly, there have been significant strides made recently in the phono cartridge field. And the new cartridges of today stand head and shoulders above even the finest of a few short years ago.

Here's the choice: Get fresh—but outdated—performance with a replacement stylus, or enjoy *all* the benefits of modern cartridge research and development for just a few dollars more. You'll find that you can update your system for far less than you might imagine. It's probably the *most dramatic single improvement* you can make.

For instance, Audio-Technica offers Universal™ cartridges equipped with a genuine Shibata stylus and our uniquely effective Dual Magnet™ system beginning at just $75.00 list. Or you can replace your present cartridge with a fresh new Audio-Technica cartridge with highly-polished elliptical tip for as little as $45.00 list.

AT11E	AT12Sa	AT13Ea	AT15Sa
$45.00	$75.00	$65.00	$125.00

Are these new models worth the difference? Absolutely. You'll be amazed at what you hear from *today's* generation of phono cartridges. Improved frequency response. Lower distortion. Better separation. Less record wear. Truly better sound.

A new Audio-Technica cartridge. Your best value in hi-fi.

audio-technica®
® INNOVATION □ PRECISION □ INTEGRITY

AUDIO-TECHNICA U.S., INC., Dept. 57E, 33 Shiawassee Avenue, Fairlawn, Ohio 44313
Available in Canada from Superior Electronics, Inc.

LETTERS

continued from page 14

vember 1976 (a photograph of the new 40 channel CB Analyzer model GN-1375B is enclosed).

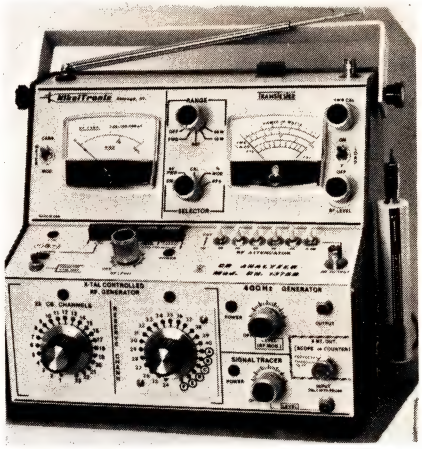

Thus, it is apparent that the 23-channel GN-1375B does not belong in the New Products section of your magazine.

Your mistake, although unintentional, has caused great confusion among those who are familiar with our products and reputation as the originator and leader in CB Analyzers.

Hopefully, we have eliminated the confusion and misunderstanding.

GEORGE D. NIKOL
Nikoltronix Co.
Chicago, IL

GI VIDEO GAME IC

I really enjoyed the article "IC Application of the Month" in the January 1977 issue. This was a very timely article as many of us would like to have a TV game but can't afford one of the commercial versions. Please publish more articles such as this one. Better yet, make it a regular feature.

However, there is one problem. Where can one purchase the AY-3-8500-1 IC? I've tried all the supply houses in the Colorado Springs and also in Denver, but no one has the IC nor does anyone know of a source for the IC. Would you please publish the price and the address of a source? Also, in the future please publish a source for some of the more difficult to get parts, please.

Keep up the great work.

KARL S. PERRY
Widefield, CO

Check the advertisements in the back of this issue for a supplier. We know James Electronics has some in stock. Check their ad for price and ordering information. There may be other suppliers as well.—Editor

BIC FORMULA

The article on the BIC Formula 7 Monitor Series Speaker in the February 1977 issue is of interest. I would hasten to

continued on page 22

HOBBY-WRAP WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)

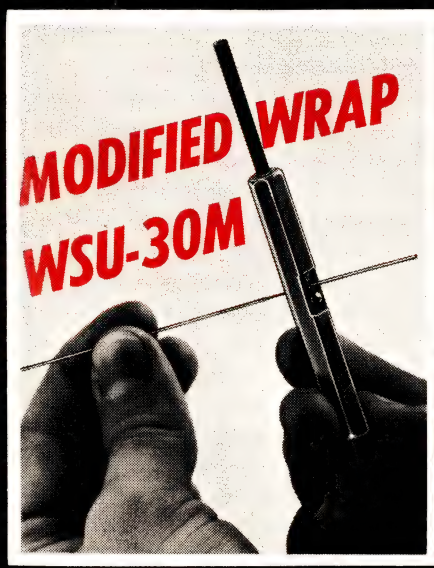

STRIP WRAP UNWRAP

REGULAR WRAP

PART No. WSU-30

TYPES OF WRAP

■ A "Regular" bit wraps the bare wire around the terminal. A "Modified" bit wraps a portion of insulation around the terminal in addition to the bare wire. This greatly increases the ability to withstand vibration.

MODIFIED WRAP

PART No. WSU-30M

HOBBY-WRAP WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)

STRIP WRAP UNWRAP

OK MACHINE & TOOL CORPORATION

3455 CONNER STREET, BRONX, NEW YORK, N.Y. 10475 U.S.A. • PHONE (212) 994-6600

TELEX: 125091 TELEX: 232395

CIRCLE 22 ON FREE INFORMATION CARD

Heathkit®

SPRING 1977

Heathkit products are known world-wide for quality, performance and VALUE. And no matter what your interest — there's a kit that's just right for you. Every Heathkit product comes with a thorough step-by-step assembly manual that leaves nothing to chance, and all our kits are backed by our famous "We won't let you fail" pledge. See all the exciting electronic products YOU CAN BUILD YOURSELF right here in this catalog.

New Electronic Circuits Self-Learning Course See page 93

New High-Performance Stereo Components See pages 29, 31 and 37

New Deluxe Timing Light with Advance Meter and Tach See page 17

New Aircraft Clock/Timer See page 24

New 3-Band VHF-UHF Automatic Scanning Monit... See page...

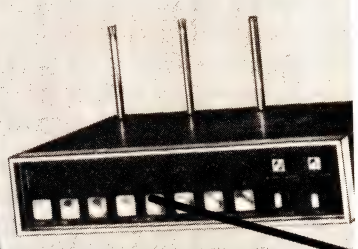

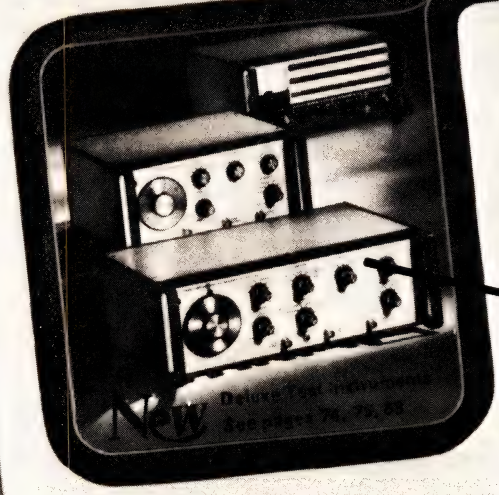

New Deluxe Test Instruments See pages 74, 75, 83

New Programmable Home Heating Control See page 44

New Amateur Radio Self-Learning Course See page 95

HI

MAIL ORDER CATA...

"Heath" and "Heathkit" are registered trademarks ...

©1977 Heath Company

See Index on page 3

Heath Company, Dept. 20-29
Benton Harbor, Michigan 49022

CIRCLE 100 ON FREE INFORMATION CARD

FREE!

Some of the most exciting electronic kits ever to come along are described in this NEW Heathkit Catalog.

NEW! AS-1348 deluxe Three-Way Speaker System

Our biggest and best speaker system is designed for use with the finest stereo components! Has a massive 15″ woofer for bass response all the way down to 20 Hz; dual 4½″ midrange speakers for twice the power handling at the important middle frequencies, and a three-tweeter array that maintains dispersion and stereo image throughout any listening area. The AS-1348 provides "live performance" sound levels at ALL audible frequencies.

NEW! Electronic Circuits Learn-at-Home Course

The latest in our series of programmed learning courses — the Electronic Circuits Course provides an explanation of most common circuits and gives you the "hands-on" experience you need for circuit design and development. Covers amplifiers, power supplies, oscillators, pulse circuits, modulation and demodulation with emphasis on integrated circuits. Includes text material, audio records and 110 electronic parts for 18 different experiments with the optional electronic trainer.

NEW! GR-1132 3-Band VHF/UHF Automatic Scanning Monitor

Listen to ALL the action — automatically! Covers any combination of 8 crystal-controlled channels in the 30-50 and 146-174 MHz VHF bands, and 450-500 MHz UHF band, for police, fire, ambulances, Amateur 2-meter FM, marine, emergency vehicles, U.S. Gov't weather stations and more. Has extra-large lighted channel indicators, priority channel feature and channel lockout buttons, built-in antenna for all three bands, provision for external antenna. Built-in speaker, volume and squelch controls.

NEW! CI-1096 Deluxe Auto Timing Light with built-in Tachometer and Advance

The fast, easy way to keep tabs on your car's engine timing and distributor advance functions for smoother operating and better fuel economy. Single, compact unit houses a timing light, advance meter and tachometer. Measures up to 60° mechanical or vacuum advance from 1500 to 4500 RPM and indicates engine speed to 4500 RPM. Bright xenon flash tube lets you set timing even in daylight. Inductive pickup snaps around #1 sparkplug wire for easy hookup.

NEW! Advanced Test and Service Equipment

Three new test instruments will bring advanced service capability to any test or hobby bench. The IG-1275 is a deluxe Swept-Function Lin/Log Generator. The IG-1273 is a voltage-controlled Lin/Log Generator, and the IG-1272 is a low-distortion audio frequency oscillator perfect for audio testing. All three offer professional performance and specifications at low kit-form prices.

PLUS nearly 400 other superb, easy-to-build, money-saving products. You'll find a complete line of digital electronic clocks and weather instruments, plus useful and unique items for your car, home or office.

Our learn-at-home courses are now in use by the thousands! A really effective and low-cost way to teach yourself about electronics for fun, for knowledge, or for profit. We also have a wide selection of popular books covering almost everything in electronics.

There are many more exciting products to read about too! Home convenience items like a practical freezer alarm, a touch-control light switch, intercoms and a unique programmable doorbell. Automotive instruments and accessories, marine equipment, model aircraft Radio Control gear, security systems and more. Plus our world-famous Amateur Radio equipment and test and service instruments.

These are among the nearly 400 quality, fun-to-build kits described in this new Heathkit catalog. Kits for every interest. All with the world-famous Heathkit assembly manual — a step-by-step instruction guide that makes kitbuilding easy and leaves nothing to chance. And all backed by our "We won't let you fail" promise. Find out about the satisfaction, savings and FUN of kitbuilding.

Send for your FREE copy today!

HEATH
Schlumberger

Heath Company, Dept. 20-29
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.
I am not on your mailing list.

Name_____

Address_____

City_____ State_____

Zip_____

CL-632

CIRCLE 100 ON FREE INFORMATION CARD

dynaco's sound starter

Learn what Dynakit's legendary sound quality and ease of assembly is all about. Save $100 in 3 or 4 evenings and hear the finest sounding low cost amp/preamp ever! Dynaco's SCA-50. Get the satisfaction of the famed PAT-5 and Stereo 150, at 50 watts power (though it seems much more) and a price that's even lower than that! Optional wood cabinet shown.

dynaco dynakit

Made in AMERICA

For free catalog, write Dept. A-2
Box 88, Blackwood, N.J. 08012

CIRCLE 31 ON FREE INFORMATION CARD

point out that an SPL meter in the actual sound field is inherently better than any built-in audio power monitoring system. Room effects such as the carpet, drapes, furniture, number of people, etc., all alter the developed SPL which cannot be estimated solely at the speaker terminals. Resonance effects play a large part as an elementary study of room acoustics will show.

Thus an SPL meter in the field is worth more than two audio power meters at the source (for stereo systems). Furthermore, a modern SPL meter can cost less than the electronics presented for the BIC system. While audio power level monitoring is generally a good idea to protect speaker systems and people from gross overdrive, a field SPL meter is cheaper in this case and provides a much better estimate of the amount of ear damage anticipated in the listening environment.

There is a great tendency these days to digitize everything in sight, including now, the speaker power-input level with blinking LED displays. A pointer reading VU meter and single op-amp driver can do the same job here cheaper and probably better.

RALPH W. BURHANS
Ohio University
Athens, OH

R-E

Treat yourself to a new direct reading DVM today.

DVM35

POCKET PORTABLE ANALOG REPLACEMENT

3-digit, 1% DCV, Battery or AC

Only $134

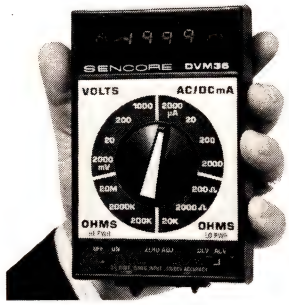

DVM36

LAB ACCURATE POCKET PORTABLE

3½ digit, .5% DCV, Battery or AC

Only $158

DVM32

BENCH & FIELD MASTER

3½ digit, .5% DCV, Battery or AC

Only $198

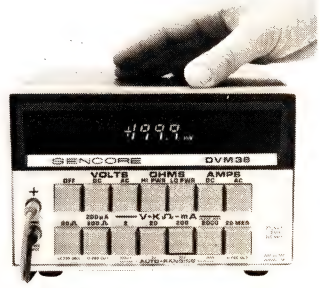

DVM38

"PRIME" STANDARD AT YOUR FINGERTIPS

3½ digit, .1% DCV, Auto-Ranging

Only $348

A COMPLETE LINE OF DVMs TO FILL YOUR EVERY NEED OR WANT.

You can be sure more times in more circuits, under more adverse conditions, with greater versatility, accuracy, and meter protection than any other digital multimeters on the market today; and for less money too. 10 Day Free Trial: Try any of these famous DVMs for 10 days. If the DVMs in use don't prove exactly what we say, return them to your Sencore FLPD Distributor.

Want more information? We would like to tell you all about the Sencore DVMs by sending you a 24-page Sencore News, a six-page brochure, and the name of your nearest Sencore Distributor today . . . simply write or circle reader's service number.

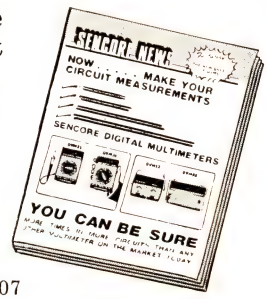

SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107

CIRCLE 14 ON FREE INFORMATION CARD

Tuner Service Corporation

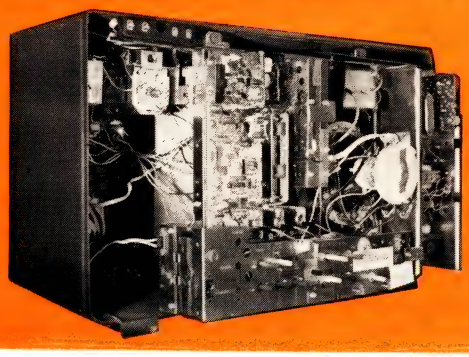

STILL ONLY

$10.95

U.S.A. ONLY

Major Parts and Shipping Charged at Cost

One Year Guarantee

MODULE REPAIRS

TSC has been repairing private brand TV modules for over 2 years.

Expanded facilities now include modules for

- RCA
- GE
- ZENITH
- W. T. GRANT
- J. C. PENNEY
- WESTERN AUTO
- GAMBLES

as well as Zenith IF subchassis.

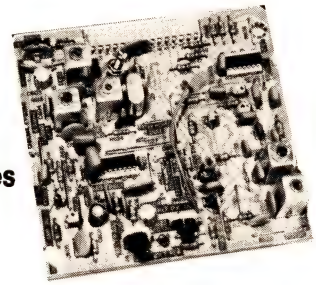

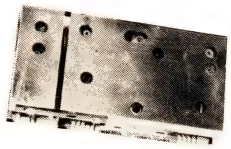

For free Price List and complete information write or phone;
TSC HEADQUARTERS, BLOOMINGTON, IND.
or any of the TSC locations listed below.

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

TUNER REPAIRS

VHF OR UHF ANY TYPE..... (U.S.A.) **$10.95**
UHF/VHF COMBINATION..... (U.S.A.) **$17.95**

MAJOR PARTS AND SHIPPING CHARGED AT COST

- **FAST, EFFICIENT SERVICE AT ANY OF THE CONVENIENTLY LOCATED SERVICE CENTERS LISTED BELOW.**
- ***ONLY ORIGINAL FACTORY PARTS USED***
- **All tuners ultrasonically cleaned, repaired and realigned.**

EXACT REPLACEMENT

- **Exact Replacement Tuners are available at a cost of $14.95 and up.** ..... (U.S.A. Only)
- **Send in your original tuner for comparison purposes to any of the Centers listed below.**

UNIVERSAL REPLACEMENT

- **UNIVERSAL REPLACEMENT TUNER $13.95**..... (U.S.A. Only)
- **This price buys you a complete new tuner built specifically for this purpose.**
- **All shafts have a maximum length of $10\frac{1}{2}$" which can be cut to $1\frac{1}{2}$".**
- **Specify heater type parallel and series 450 mA or 600 mA.**

FLASH

NOW AVAILABLE—TUNER SERVICE PARTS CATALOG
OF ALL SARKES TARZIAN VHF AND UHF TUNERS, INCLUDING EXPLODED VIEW DRAWINGS. OVER 200 PAGES. ORDER YOUR COPY TODAY.
SEND $2.50 WITH ORDER TO BLOOMINGTON HEAD OFFICE.

SAME DAY SERVICE — ONLY ORIGINAL FACTORY PARTS USED

TSC

WATCH US GROW

HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812/334-0411
ALABAMA	BIRMINGHAM, ALABAMA 35212	5623 1st Avenue, North	Tel. 205/592-9150
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213/769-2720
	SAN MATEO, CALIF. 94402	600 S. Amphlett Boulevard	Tel. 415/348-3292
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209/521-8051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813/253-0324
	FT. LAUDERDALE, FLORIDA 33309	3516 N.W. 10th Avenue	Tel. 305/566-4882
GEORGIA	ATLANTA, GEORGIA 30310	646 Evans Street S.W.	Tel. 404/758-2232
ILLINOIS	URBANA, ILLINOIS 61801	908 E Main Street	Tel. 217/384-2052
	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312/675-0230
INDIANA	INDIANAPOLIS, INDIANA 46204	112 West St. Clair Street	Tel. 317/632-3493
KENTUCKY	LOUISVILLE, KENTUCKY 40205	2244 Taylorsville Road	Tel. 502/452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	2423 Southern Ave.	Tel. 318/221-3027
MASSACHUSETTS	SPRINGFIELD, MASSACHUSETTS 01108	405 Dickinson Street	Tel. 413/788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	9577 Page Avenue	Tel. 314/429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue	Tel. 702/384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	1139 Pennsylvania Avenue	Tel. 609/393-0999
	JERSEY CITY, NEW JERSEY 07307	454 Central Avenue	Tel. 201/792-3730
NEW YORK	ROCHESTER, NEW YORK 14615	37 Pullman Avenue	Tel. 716/647-9180
NORTH CAROLINA	GREENSBORO, NORTH CAROLINA 27405	2914 East Market Street	Tel. 919/273-6276
OHIO	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216/741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Ave., P.O. Box 10141	Tel. 503/222-9059
PENNSYLVANIA	PITTSBURGH, PENNSYLVANIA 15209	515 Grant Avenue	Tel. 412/821-4004
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901/458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214/327-8413
CANADA	ST. LAURENT, QUEBEC H4N-2L7	305 Decarie Boulevard	Tel. 514/748-8803
	CALGARY, ALBERTA T2H-1Y3	P.O. Box 5823, Stn. "A"	Tel. 403/243-0971

If you want to branch out into the TV Tuner Repair Business write to the Bloomington Headquarters about a franchise.

FOR MODULE CIRCLE 25 ON FREE INFORMATION CARD

FOR TUNER CIRCLE 75 ON FREE INFORMATION CARD

INTRODUCING THE FAST WORKING COUNTERS FROM HICKOK.

Four affordable, deluxe counters—one for every need.

MODEL 380. 1 Hz to 80 MHz, 10 ppm **$269**
MODEL 380X. 1 Hz to 80 MHz, 1ppm **$419**
MODEL 385. 1 Hz to 512 MHz, 10ppm **$545**
MODEL 385X. 1 Hz to 512 MHz, 1ppm **$699**

Perfect for communications, CB, audio and digital work, servicing and laboratory applications.

Full 7-digit display with automatic decimal, full autoranging. SPEED READ mode updates display 5 times each second to aid tuning and adjustments.

Resolution is 1 Hz to 10 MHz, and 10 Hz to 80 MHz. Models 385, 385X feature a built-in prescaler to take you all the way to 512 MHz. Models 380X, 385X incorporate temperature compensated crystal oscillators with 1 ppm accuracy.

See these exciting new counters at your distributor now!

HICKOK
the value innovator
INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286
CIRCLE 12 ON FREE INFORMATION CARD

KOMPUTER KORNER

PETER R. RONY, DAVID G. LARSEN, and JONATHAN A. TITUS*

IN THIS COLUMN, WE WILL INTRODUCE YOU TO additional details concerning the operations of an 8080A-based microcomputer that are controlled by software. It is the software instructions, or steps, that actually indicate to the microcomputer the tasks that it must perform. Just as you may start the day with a list of things to be done and a sequence in which they should be accomplished, the microcomputer, too, must be provided with a sequential list of program steps.

In general, we may not be familiar with what each microcomputer instruction does within the microprocessor chip. This does not deter us, however, from using them in all of our programs. Many of us are not familiar with the inner workings of an internal combustion engine, an automatic transmission, or a Xerox machine; our lack of knowledge does not prevent us from using them daily.

All of our programs are stored in fast semiconductor memory, either read/write memory or programmable read-only memory. The microprocessor IC *fetches* an instruction byte from the memory and then executes it. Each software instruction requires at least one fetch-and-execute action. Software instructions that contain several instruction bytes require two or three sequential fetch-and-execute actions. Again, exactly what is done within the microprocessor IC is not of interest to us, only the overall effect. All software is executed sequentially, one step after another, unless we purposely transfer control to instruction bytes located elsewhere in memory.

To conveniently handle the large number of software instructions in the 8080A microprocessor instruction set, it is customary to group them into several instruction groups. The Intel *8080 Microcomputer Systems User's Manual* subdivides the instruction set into five groups:

- Data Transfer Group—these instructions move data between registers or between memory and registers
- Arithmetic Group—add, subtract, increment or decrement data in registers or in memory
- Logical Group—and, or, exclusive-or, compare, rotate or complement data in registers or in memory
- Branch Group—conditional and unconditional jump instructions, subroutine call instructions and return instructions
- Stack, I/O and Machine Control Group—includes I/O instruc-

continued on page 26

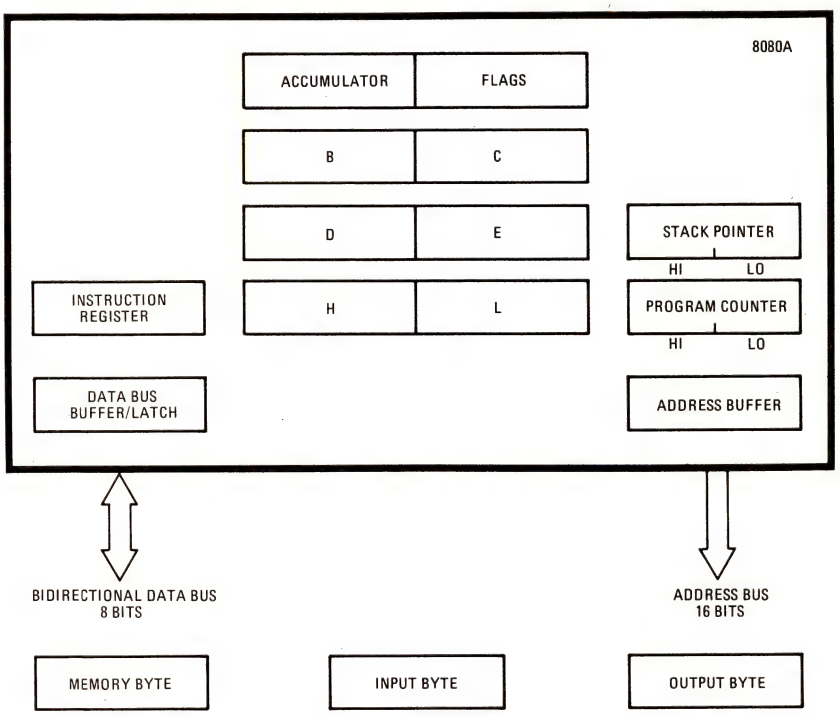

FIG 1

* Mr. Titus is president of Tychon, Inc., a microcomputer consulting firm in Blacksburg, Virginia. Dr. Rony, Department of Chemical Engineering, and Mr. Larsen, Department of Chemistry, are with the Virginia Polytechnic Institute & State University.

THE AGE OF CASTLE TIMESAVERS HAS ARRIVED!

TO A PROFESSIONAL TV SERVICE TECHNICIAN, A MAJOR KEY TO INCREASING PROFITS IS SAVING TIME. CASTLE'S ADVANCED TECHNOLOGY WILL HELP YOU!

MEZZER™ TV FIELD STRENGTH METERS
Put an End to Guessing About the Signal Level

VHF Field Strength Meter Model FSM-V
Range: 20 microvolts-100 millivolts
Attenuator: x1, x10, x100
Inputs: 75 ohms & 300 ohms
AC-DC (Batteries not included) net $137.95

SUBBER® TV SIGNAL CIRCUIT ANALYSTS
Analyze the Entire Signal Circuit of any TV Receiver

Master Subber® Model Mark V
Outputs at video IF, sound IF, video & audio
Built-in Monopole Antenna
Built-in Loudspeaker
Complete with 120 vac/wall plug-in transformer and matched test cables.
Video Carrier Level Meter
Battery Indicator Meter
net $169.95

CASTLE ELECTRONICS

5233 OLD HIGHWAY 37 S. BLOOMINGTON, IN. 47401
(812) 824-9791

For More Details and Specifications Contact
Your Nearest Castle Products Distributor
In Canada: Len Finkler Ltd; Ontario

CIRCLE 21 ON FREE INFORMATION CARD

continued from page 24

tions, as well as instructions for maintaining the stack and internal control flags

Before we can make much sense of these instructions, we must know more about the internal architecture within the 8080 itself. We shall present such information in steps, since it can be overwhelming if tackled all at once.

Shown in Fig. 1 is a schematic diagram that depicts the significant aspects of the internal architecture within an 8080 or 8080A IC. Our emphasis in the diagram has been an accessible 8-bit and 16-bit *registers* that store information within the IC. You should exclude from consideration the Data Bus Buffer/Latch and the Address Buffer, which we show here to make the point that these are internal circuits that interface the internal digital circuitry with the outside world, i.e., the 8-bit *bidirectional data bus* and the 16-bit *address bus.* As you learn about the 8080, you will be specially interested in the *accumulator, flags, program counter, stack pointer,* and *general purpose registers* that are designated B, C, D, E, H, and L.

We will not say much about the *instruction register,* since its function is automatic and we have little control over it. The function of the instruction register can be best understood with the aid of Fig. 2, which shows that it is an 8-bit register that temporarily stores the 8-bit instruction code for an instruction that is to be executed. Within the microprocessor IC, an instruction decoder converts the instruction code into a series of actions that, together, cause a microcomputer operation to occur. The individual actions are clocked by the ϕ_1 and ϕ_2 clock signals that are input at pins 22 and 15, respectively, on the 8080 IC.

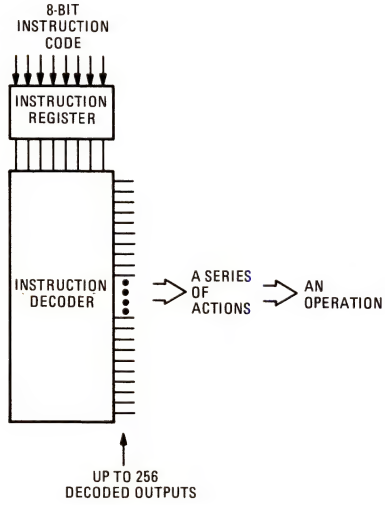

FIG 2

The general purpose registers B, C, D, E, H, and L are used for many varied purposes, *e.g.*, the storage of an 8-bit constant, the storage of a 16-bit pointer address, the storage of an intermediate result in an addition or subtraction, etc. Each general purpose register contains eight bits and can exchange data directly with the 8-bit external bidirectional data bus. Simple 8080 instructions permit you to transfer eight bits of data from one register to another; from a pair of registers to the program counter; from a register to the accumulator; and from a register to a memory location, and *vice versa.* You can use the contents of a register to perform addition, subtraction, and, or, exclusive-or, and compare operations with the contents of the accumulator. The contents of each register can be incremented or decremented. Register pairs, such as register H and register L, can be incremented or decremented as a 16-bit word.

The accumulator also acts as a general purpose register, but it has some special characteristics not possessed by the other six registers. The result of any arithmetic or logical operation is stored in the 8-bit accumulator. The I/O instructions (IN and OUT) transfer data only between the accumulator and external I/O devices. The contents of the accumulator can be transferred to any other general purpose register or to a memory location, and *vice versa.*

The five flags—zero, carry, parity, sign, and auxiliary carry—are flip-flops that indicate that certain conditions have arisen during the course of an arithmetic or logical instruction. Such flags are used by the microcomputer in making decisions, *i.e.*, with conditional jump, call, and return instructions; in multiple-precision arithmetic operations; and in logical masking operations.

The program counter is a 16-bit register in the 8080 IC that contains the address of the

continued on page 28

NEW

"FERRET" TV MINI-ANALYZER

FOR FAST STEP-BY-STEP TROUBLE SHOOTING

SUB TUNER

VHF AND UHF TUNER FOR RAPID TESTING OF ALL CHANNELS. CALIBRATED GAIN ADJUSTMENTS PROVIDE FOR SIGNAL STRENGTH COMPARISON.

DIGITAL GENERATOR

CRYSTAL CONTROLLED FOR GENERATING STABLE PATTERNS WHEN CONVERGING RED, GREEN AND BLUE GUNS. IDEAL FOR LINEARITY, PIN CUSHION, CENTERING, FOCUS AND ALL PICTURE ADJUSTMENTS.

40 MHz OUTPUTS

IF SIGNALS FROM DIGITAL GENERATOR AND SUB TUNER FOR STAGE-BY-STAGE ANALYZING AND TROUBLE SHOOTING.

SG 785 $99.95

GENERATOR SECTION

CROSS-HATCH

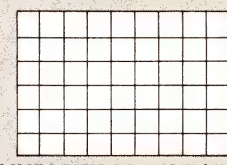

LINEARITY ADJUSTMENT

STANDARD FOR VERTICAL AND HORIZONTAL POSITIONING, PICTURE CONTRAST, IF BANDWITH TEST

DOT PATTERN

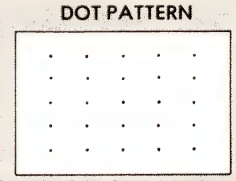

CONVERGENCE ADJUSTMENT

STATIC AND DYNAMIC CONVERGENCE, BEAM ADJUSTMENTS.

The VHF/UHF section of the Ferret allows direct substitution of the TV's tuner for fast, positive localizing of front end trouble.

The crystal controlled digital circuitry assures complete accuracy of both the vertical and horizontal frequencies. Accuracy is better than .005%. Output from the generator may be coupled thru the tuner section or directly to the IF-video stages. Resolution is limited only by the picture quality of the TV receiver. Operates from 105 to 125 volts 50-60Hz.

SOLD THRU DISTRIBUTORS ONLY

Please send me more information. F-5
Name _____
Address _____
_____ Code _____

TeleMatic 2849 FULTON STREET, BROOKLYN, NY 11207
PHONE: (212) 827-1500

CIRCLE 45 ON FREE INFORMATION CARD

THE CATS TO CATCH.

"Roar Power" puts these new 40-channel CB's from Pearce-Simpson out in front. The Lion 40™ and Tiger 40™. Built with all the power and prestige you'll ever need in the CB jungle. As well as some advanced Pearce-Simpson features that command real attention. Like HetroLock™, for zeroing in on the right frequency. Receiv-O-Slide™ tuning for the best reception and superior adjustment of signals (even from "off-freq."sets). And the Lion's bold new LED digital read-out.

Both sets are backed by Pearce-Simpson's over quarter-century of experience in personal two-way communications. And both are available right now. So stop by your Pearce-Simpson dealer today. He'll be glad to help you make the big cats roar.

For further information, write Pearce-Simpson, 4701 N.W. 77th Ave., Miami, FL 33166. In Canada, Scotcomm Radio, Inc., 4643 Levesque Blvd., Chomesday, Laval, Quebec.

LION 40

TIGER 40

PEARCE-SIMPSON
DIVISION OF GLADDING CORPORATION
THE CB RADIO • MARINE RADIO • ANTENNA PEOPLE.

CIRCLE 29 ON FREE INFORMATION CARD

TWO NEW GENERATORS FROM EICO®

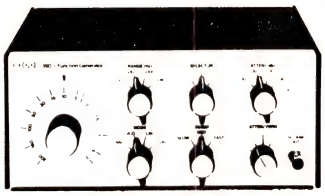

EICO 390 SWEEP/FUNCTION GENERATOR

- **.2 Hz to 200 KHz**
- **Sine, Square, Triangle**
- **Linear & Log Sweep**

Now you can afford a Function Generator that will meet all your signal requirements! The 390 generates discrete sine, square, and triangle waveforms over a very broad frequency range. You have a choice of either linear or logarithmic sweep with slow, medium, or fast rates. The 390 also allows for external frequency control through a rear panel input. With its 50-ohm output impedance and calibrated attenuator, the 390 can handle everything from checking the response of an audio amplifier to driving digital circuits.

Model 390 assembled **$169.95**

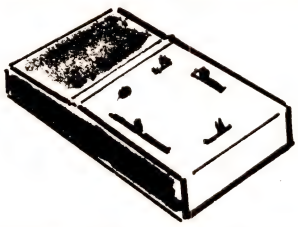

EICO 388 PORTABLE COLOR BAR PATTERN GENERATOR

- **Battery Operated with LED Indicator**
- **IC Digital Circuit Design**
- **RF Adjustable, Channels 2, 3, 4**

The 388 is truly the most advanced pocket-size portable color generator in the field today. A single MOS LSI IC provides 9 digitally controlled, stable patterns. The 388 operates by simply connecting its output cable to the TV's VHF terminals. Two matrix slide switches select any one of the 9 patterns. Crystal controlled chroma and timing oscillators assure precision, accuracy and stability. The 388 is powered by two 9-volt transistor batteries.

Model 388 assembled **$89.95**

FREE EICO CATALOG

For latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO-283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics since 1945.

CIRCLE 67 ON FREE INFORMATION CARD

KOMPUTER KORNER

continued from page 26

next instruction byte that must be executed in a program. You can load the program counter register either from a register pair or, more likely, from two instruction bytes in sequence located in memory.

The stack pointer is a 16-bit register that contains the address of the last byte that has been placed on the stack. The stack is a region of memory that is allocated for the storage of temporary information, usually the contents of the internal registers within the 8080 IC.

This summarizes our brief discussion of the internal architecture of the 8080 microprocessor. Keep in mind that there are seven 8-bit registers, two 16-bit registers and five flags, *the contents of which you can control using software.* Much of what an 8080 microcomputer does is to move 8-bit bytes from one location to another. This will become more apparent in subsequent columns. **R-E**

DEFINITIONS

accumulator—The register within a computer where the results of all arithmetic and logical operations are placed.

address bus—A unidirectional bus over which digital information appears to identify either a particular memory location or a particular I/O device.

bidirectional data bus—A data bus in which digital information can be transferred in either direction. With reference to an 8080A-based microcomputer, the bidirectional data path by which data is transferred between the microprocessor chip, memory, and input-output devices.

fetch—In a computer, the collective actions of acquiring a memory address and then an instruction or data byte from memory.

flag—A single flip-flop that indicates that a certain condition has arisen as, for example, during the course of an arithmetic or logical operation in a computer program.

general purpose registers—In the 8080 microprocessor, the 8-bit B, C, D, E, H, and L registers.

program counter—In a computer, the register that contains the address of the next instruction byte that must be executed in a computer program.

register—A short-term digital electronic storage circuit the capacity of which is usually one computer word or byte.

software—The totality of programs and routines used to extend the capabilities of computers. Examples include compilers, assemblers, narrators, routines, and subroutines.

stack—A region of memory that stores temporary information, usually the contents of the internal registers within a microprocessor chip.

stack pointer—A register that contains the address of the last byte that has been placed on the stack in an 8080 microcomputer.

Original operators celebrate 50 years of overseas phone

Two retired overseas telephone operators commemorated a half century of transatlantic telephone service with a call placed January 7, 1977, exactly 50 years after the first overseas phone call got through.

Ms. Rose de Palma, 73, one of the four original transatlantic operators for AT&T's Long Lines, called Ms. Isabel Ivy Baker, with whom she had worked from the earliest days of the transatlantic telephone. Ms. de Palma, brought from Florida to make the historic call, had retired from the Bell System in 1966 after 46 years of service. Ms. Baker, now 74 years old, left the British Post Office in 1940 and now lives in Thornton Heath, Surrey, England.

The two old-time operators reminisced before turning the phones over to dignitaries of AT&T in New York and its opposite number, the British Post Office in London.

The 1977 call was dialled by International Direct Distance Dialing, a service that permits one-fourth of all Bell System subscribers to dial direct to as many as 36 countries. There have been a few other changes in 50 years. The cost of a three-minute call in 1927 was $75 (equivalent to about $250 in 1977 dollars). The same three-minute call can be placed today for $4.05.

Computers now made useful for small-business man

Altair Software Distribution Co. is putting out software packages to fit the needs of retail stores, small wholesale distribution centers, industrial users and professional firms, among others. Altair is a subsidiary of MITS, microcomputer manufacturer of Albuquerque, NM.

The packages are designed to allow a purchaser to select the components of a system that will fit his needs closely. The accounting system, for example, is composed of four packages, *General Ledger, Payroll, Receivables* and *Payables*. The *Word Processing* package is a flexible text editor system that allows contracts or other lengthy documents to be stored, edited and printed. Documents can call for inserts from other files, making repetitive letters, etc., easy to produce.

The *Inventory Management* package is a flexible data-base management system that allows a business to keep complete inventory records "on line." In its off-the-shelf form, it is structured for a typical retail store whose inventory reorder policy is based on minimum reorder points. **R-E**

An Extraordinary Offer to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

take any **3** of these unique electronics books (value to $62.70) for only **99¢** each

with a Trial Membership in the Book Club that guarantees to save you 25% to 75% on a wide selection of electronics books

All 2- and 3-book sets count as only one of your 3 Selections.

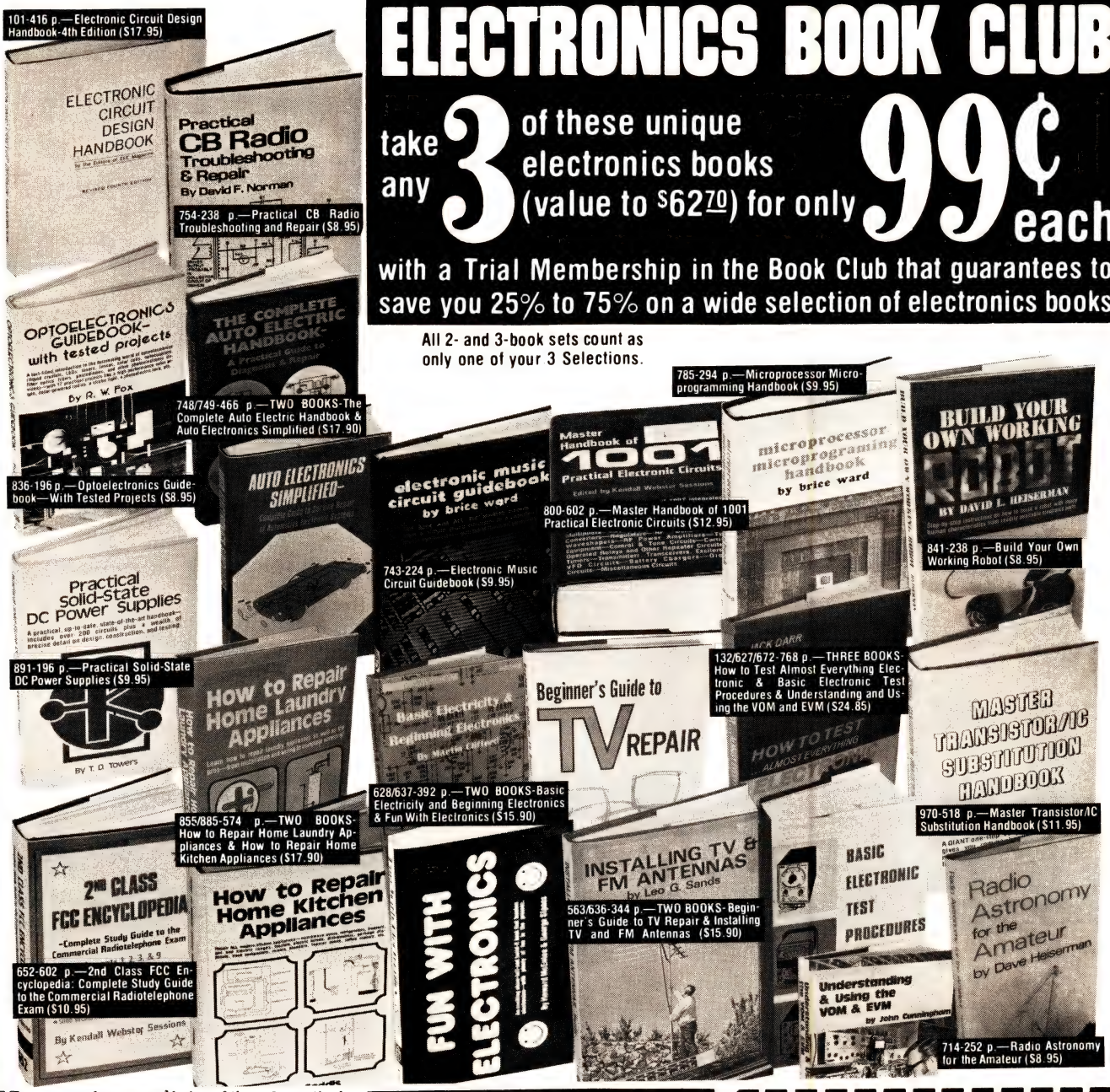

May we send you your choice of these 3 practical, time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club?.

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics. Whatever your interest in electronics, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours...that it *is* possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway...without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 3 books of your choice for 10-day inspection. YOU NEED SEND NO MONEY! If you are not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, P.O. Box 10, Blue Ridge Summit, Pa. 17214

Facts About Club Membership

- The 3 introductory books of your choice carry publishers' retail prices of up to $62.70. They are yours for only 99¢ each (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selection, Alternates and other offerings, every 4 weeks (13 times a year).
- If you want the Selection, do nothing: it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- Personal service for your account—no computers used!
- To complete your Trial Membership, you need buy only four additional monthly selections or alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices, plus a small postage and handling charge.
- **Continuing Bonus**: If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of $1.99, will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

P.O. Box 10
Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send me the 3 books circled below. I understand the cost of the books I have selected is only 99¢ each, plus a small shipping charge. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my membership at any time.

101	652	754	785	800	836	841	855/885	891	970
132/627/672		714				743		748/749	
563/636									
628/637									

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(This offer valid for new Members only. Foreign and Canada add 10%) RE-57

equipment report

VIZ WR-549A Pulse Generator

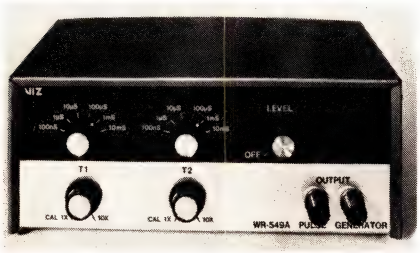

CIRCLE 88 ON FREE INFORMATION CARD

EVERYTHING IS GOING DIGITAL LATELY. SO, for design work or servicing of digital equipment, a reliable source of controllable pulses is needed. All digital circuitry works on pulses of varying shapes, widths and frequencies. Test equipment must be capable of developing the exact one needed for, a given circuit. VIZ Manufacturing Co., 335 E. Price St., Philadelphia, PA 19144, has introduced their *WR-549A* pulse generator that meets all of these requirements.

It's a tiny thing, but versatile. It can develop pulses that are continuously variable over a range from 5 Hz to 5 MHz. Pulse width and repetition rate are independently adjustable. The output is TTL compatible and also suitable for CMOS. The output has a range up to 15 volts P-P, and an impedance of 100 ohms. The risetime of the pulses is held to 20 nanoseconds on all ranges. Frequency can be set to within ± 5% of the dial setting with the two front-panel controls set to their CAL (counter clockwise) positions.

A novel method of pulse generation is used in the *WR-549A*. It uses two separate one-shots. Each of these is timed independently of the other by a selector switch and a set of precision capacitors. Each one-shot triggers the other. So, both pulse-widths may be adjusted independently from 100 nanoseconds to 0.1 second. To achieve maximum sharpness of the pulse (minimum risetime), edge-triggering is used. The trailing edge of the pulse from the first pulse-generator fires the second one. In turn, the trailing edge from the second generator is coupled back to the first, which sets this one off again, completing a cycle.

The outputs of the two generators are combined in a buffer amplifier. The front-panel LEVEL control sets the P-P voltage of the pulses, having no effect on their frequency or duty-cycle.

The first pulse-generator one-shot determines the duration of the positive-going pulse, and the second determines the duration of the off-time between two successive positive going pulses.

Precision timing capacitors are used for each generator, Two 6-position rotary switches select the capacitors. These go from 100 nanoseconds to 10 milliseconds. A continuously-variable control can be used to set the pulse-width exactly.

The *WR-549A* is AC powered with a tightly regulated DC power supply, and complete isolation from the line. Standard IC's and transistors are used. The instruction manual gives full and simple directions for checking the calibration, and adjustment if necessary. A troubleshooting chart is also provided.

This can be a very handy instrument, not

continued on page 32

TIGER .01

Introduced three years ago, our "Tiger .01" is still one of the finest amplifiers available in its power class. This amplifier introduced our 100% complementary circuit which has become a standard feature in many of the better amplifiers. This combined with an output triple produces a circuit that can honestly be rated as having less than .01% IM distortion at any level up to 60 Watts. Relatively low open loop gain and a conservative amount of negative feedback results in clean overload characteristics and good TIM characteristics.

Other features are volt-amp output limiting, plus three fuses and an overheat thermostat. Despite the "budget" price an output meter is standard equipment. Each channel measures 4¼ x 5 x 14. Four will mount in a standard width relay rack for four channel systems.

SPECIFICATIONS

60 Watts—4.0 or 8.0 Ohm load Minimum RMS from 20 Hz to 20 KHz with less than .05% Total Harmonic Distortion.

IM Distortion ..... less than .01%
Damping Factor ..... 50 or greater 20 Hz to 20,000 Hz.
Hum and Noise ..... -90 dB

207/B Amplifier (single channel) ..... $110.00 PPd
207/B Amplifier — Kit ..... $ 77.50 PPd

SWTPC

Southwest Technical Products Corp.
219 W. Rhapsody, Dept. FM
San Antonio, Texas 78216

CIRCLE 69 ON FREE INFORMATION CARD

Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes—take your jacket off, and you're lost!

But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it *is* a kit, supplied *direct* from the manufacturer, it costs only a very reasonable $19.95. And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.

How to make 10 keys do the work of 27

The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions $\sqrt{x}$, $1/x$, x^2; plus a full *5-function memory*.

All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.

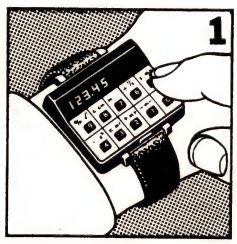

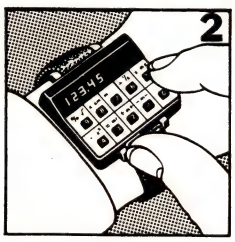

1. The switch in its normal, central position. With the switch centered, numbers—which make up the vast majority of key-strokes—are tapped in the normal way.

2. Hold the switch to the left to use the functions to the left above the keys...

3. and hold it to the right to use the functions to the right above the keys.

The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.

Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron. It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components *free*: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.

Contents

Case and display window.
Strap.
Printed circuit board.
Switches.
Special direct-drive chip (no interface chip needed).
Display.
Batteries.

Everything is packaged in a neat plastic box, and accompanied by full instructions. The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available only direct from Sinclair Instrument. Take advantage of this 10 day money-back offer.

Send the coupon today.

Sinclair Instruments Inc.
6 Commercial Street
Hicksville, N.Y. 11801

To: Sinclair Instruments Inc. RE-5
6 Commercial Street
Hicksville, NY 11801

Please send me

_____ Sinclair wrist calculator kit(s) at $19.95 $_____

Sales tax (NY residents) _____

Shipping & handling ($2.50 per unit) _____

Enclosed is check/MO (payable to Sinclair Instruments Inc.) TOTAL $_____

Name _____

Address _____

City _____

State _____ Zip _____

I understand that you will refund the purchase price of the kit in full if I return it in saleable conditiion within 10 days of receipt.

only for digital work but for general servicing as well. It is an excellent source of very accurate squarewaves for audio test work and can be used for ringing tests of coils, transformers, and so on. It can also be used as a source of a clock signal for digital circuitry. As I discovered, it is also nice for checking other things. After connecting it to a scope getting a set of L-shaped things for a trace, I found out that someone had been dinkering with the frequency compensation of my scope-probes! Quite a lot of useful things in a compact package. **R-E**

Thanks to you it works...
FOR ALL OF US
Ad Council advertising contributed for the public good
United Way

Lightguide telephone system evaluated

A cable of hair-thin glass fiber lightguides is being run under Chicago streets to test the transmission of telephone-customers' voice, data and video signals under actual working conditions. In 1976 a similar system was checked out in Atlanta, GA, under simulated field conditions. The present test, evaluating more accurately the potentialities of the new technology, will help determine how near it is to being economically and technically practical.

A lightguide cable will carry voice, video and data signals about 0.8 kilometers (one-half mile) from the Brunswick Building in Chicago's Loop to the Franklin central office of Illinois Bell, and from there 1.4 kilometers (about nine-tenths of a mile) to the Wabash central office.

The fiber lightguides, approximately 0.005 centimeters (about 2 mils) in diameter, are made of extremely pure silica-glass coated to protect them from mechanical injury and combined into flat ribbons of 12 fibers. Two of these ribbons are enclosed in the cable that protects them in under-street installations. Each pair of fibers can carry 576 simultaneous telephone conversations or their equivalent in video or data channels.

TWENTY-FOUR SLIM LIGHTGUIDES arranged in two ribbons of twelve each in a specially designed cable, will be used as the understreet lightguide conduit in the 1977 tests in Chicago.

The signals are fed into the cables by gallium-aluminum-arsenide lasers made by Bell Labs. Light-emitting diodes will also be used. Though not as powerful sources as lasers, they are expected to be adequate over the short distances involved in the Chicago tests.

Reception is with a special silicon "avalanche" photodetector that is part of a

continued on page 34

CIRCLE 2 ON FREE INFORMATION CARD

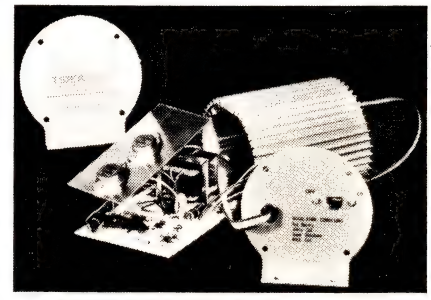

FROM KIT TO CAR
IN 80 MINUTES!

Electronic ignition is "in." Update your car with the TOPS in power, efficiency and reliability — the TIGER SST capacitive discharge ignition (CD).

The TIGER delivers everything other CD's promise — and more: quicker starting, more power, more gas mileage, tune-ups eliminated, lifetime plugs and points, reduced repairs and pollution.

The TIGER can be built and installed in your car in 80 minutes. The TIGER is unique!

The TIGER comes with a switch for TIGER or standard ignition for 12V negative ground only.

Simpli-Kit $21.95
POST PAID U.S.A.

WE ACCEPT:
Mastercharge or BankAmericard.
Send check or money order with order to:

Tri-Star Corporation
DEPT. FF, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 20 ON FREE INFORMATION CARD

Performance features at a price you can afford- and fully backed by Tektronix

Only Telequipment offers you:

TEKTRONIX GUARANTEE

The Telequipment family of oscilloscopes is fully guaranteed by Tektronix, the world's leading oscilloscope manufacturer. This guarantee means that during your first year of ownership, if there are any defects in Telequipment parts or workmanship, you can bring your oscilloscope to any of 35 Tektronix Service Centers across the United States for fast repair by experts—free of charge.

PERFORMANCE FEATURES YOU NEED AT A PRICE YOU CAN AFFORD

Model D61a Designed for portability and easy operation, the D61a is a dual trace 10 MHz 'scope for only $595. For easy, accurate viewing, the D61a features automatic triggering and bright, stable waveforms on an 8 x 10 cm display.

Model S61 NEW from Telequipment, the S61 is a 5 MHz single trace oscilloscope featuring automatic triggering and 8 x 10 cm display for $375. This lightweight (14 lb.) instrument has a straightforward, easy to read front control panel—well suited for education applications.

Model D32 When you demand an extremely portable 'scope, the D32 is ideal. Battery or ac line operated, this 10 MHz dual trace 'scope weighs only 10 lbs. An optional shoulder strap or attaché carrying case can be used to take your 'scope into the field. The $750 price includes batteries and probes.

IDEAL FOR MANY APPLICATIONS

If you're servicing pocket calculators, TV, radio, microwave ovens, alarm systems or dozens of other consumer products, Telequipment 'scopes can do the job for you. Easy viewing and operating make Telequipment ideal for classroom use too.

TELEQUIPMENT... THE CHOICE FOR YOU

Performance features at a price you can afford, plus full backing by Tektronix make Telequipment a wise choice when you're looking for low-cost oscilloscopes.

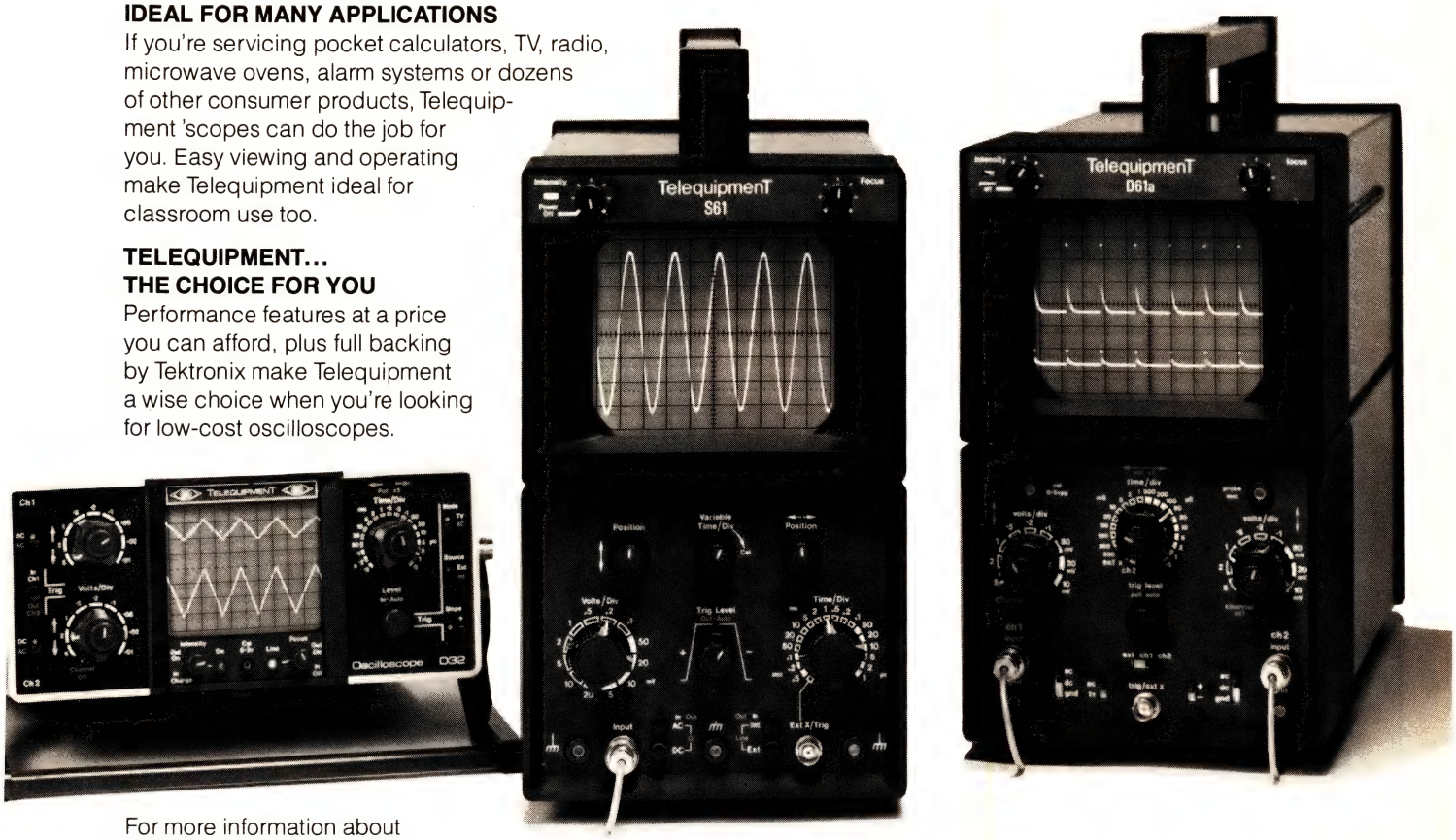

For more information about Telequipment oscilloscopes, contact your nearest Tektronix Field Sales Office, or write Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077. For immediate information, call Bill Glaze at Tektronix: (503) 644-0161, extension 7163.

TELEQUIPMENT ®

Telequipment is a division of Tektronix U.K. Ltd., a wholly owned subsidiary of Tektronix, Inc.
U.S. Sales Price F.O.B. Beaverton, Oregon.

CIRCLE 39 ON FREE INFORMATION CARD

Don't struggle with tools not meant for electronics! **Design-a-kit®** helps you get exactly what you need. Look to Techni-Tool for the best in quality and variety. Delivery of 1 or 1000. Our "Good Buddies" get service first!

- Free Catalog
- Kits
- Tools
- Meters
- Accessories

TECHNI-TOOL INC.
Apollo Road, Plymouth Mtg., Pa.19462
(215)825-4990 Telex 83-4763
Order Dept. 800-523-7798

CIRCLE 24 ON FREE INFORMATION CARD

receiver module with circuitry to process the signals for transmission through the regular telephone network. Transmission is in the infrared, at 0.82 micron, and losses through the lightguide are about 6 dB-per-kilometer, or about 10 dB-per-mile. The modulator circuit can turn the laser transmitters completely on and off 44.7 million times a second, giving a 44.7-megabit digital information rate.

More shows and conferences for computer hobbyists

The magazine *Personal Computing* is sponsoring three computer conference-shows this Spring, and is planning more shows for later in the season.

The Western Personal Computer Show was held on March 19 and 20, in Los Angeles. The Eastern show is May 7 and 8 in Philadelphia, and the New England show is June 18 and 19 in Boston. Exhibitions, seminars, special presentations and tutorial workshops will be featured at all the conferences.

Later shows are being planned for the South, Southwest, Canada and Europe.

Special areas of the exhibition halls are being set aside for personal computing in education, in the home, in ham radio and in small businesses.

Court upholds Magnavox video games patents

The United States District Court for the Northern District of Illinois has ruled that the Magnavox patent on coin-operated video games is valid and that the rights of Magnavox, a subsidiary of North American Philips, have been infringed. The ruling was against the Chicago Dynamics Industries and Seeburg Corp.

In previous suits against Atari, Inc., and Midway Mfg. Co., consent judgments were entered and the two companies entered into licensing agreements with Magnavox. Further suits are pending against Allied Leisure Industries, Inc., for both its coin-operated and home video game units; and against the Radio Shack division of Tandy Corporation that sells home video game units to consumers.

CB COMES TO TOWN IN TEXAS

"WE MONITOR CHANNEL 19," announces a motor inn in Fort Worth. The insert shows a desk clerk acknowledging a room reservation request from a motorist. The CB radio is a wall-mounted *Realistic* TRC-30A.

ok®

WIRE WRAPPING TOOL
For AWG 30, .025" (0,63mm) sq. post, "MODIFIED" wrap, positive indexing, anti-overwrapping device

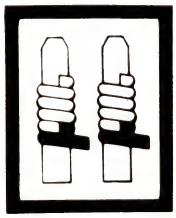

OK MACHINE & TOOL CORPORATION
3455 Conner St., Bronx, N.Y.10475 / (212) 994-6600 / Telex 125091

NEW
HOBBY-WRAP
Model BW-630

Battery **wire wrapping** tool
ONLY $34.95 (batteries not included)
COMPLETE WITH BIT AND SLEEVE

CIRCLE 17 ON FREE INFORMATION CARD

Introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

any one of these great professional books for only $1.89

values up to $42.50

Special $1.89 bonus book comes to you with your first club selection

767/556
RAPID PRACTICAL DESIGNS OF ACTIVE FILTERS
by D. E. Johnson & J. L. Hilburn
Pub. price, $15.00
Club price, $11.50

771/480
MANUAL FOR MOS USERS
by J. D. Lenk
Pub. price, $16.95
Club price, $12.95

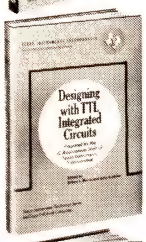

637/458
DESIGNING WITH TTL INTEGRATED CIRCUITS
by Texas Instruments, Inc.
Pub. price, $26.00
Club price, $17.50

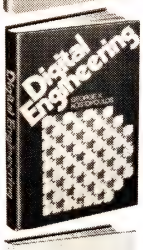

771/456
DIGITAL ENGINEERING, 2/e
by G. K. Kostopoulos
Pub. price, $24.95
Club price, $18.95

238/901
APPLICATIONS OF OPERATIONAL AMPLIFIERS: Third-Generation Techniques
by J. G. Graeme
Pub. price, $18.65
Club price, $11.95

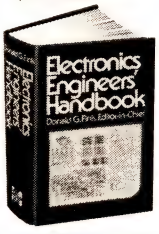

209/804
ELECTRONICS ENGINEERS' HANDBOOK
by D. G. Fink
Pub. price, $42.50
Club price, $32.50

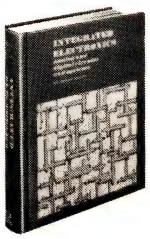

423/156
INTEGRATED ELECTRONICS: Analog Digital Circuits & Systems
by J. Millman & C. Halkias
Pub. price, $21.00
Club price, $15.95

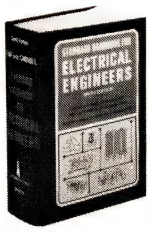

209/731
STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 10/e
by D. J. Fink & J. M. Carroll
Pub. price, $41.50
Club price, $28.50

353/387
MINICOMPUTERS FOR ENGINEERS AND SCIENTISTS
by G. A. Korn
Pub. price, $23.45
Club price, $15.50

287/341
STANDARD HANDBOOK OF ENGINEERING CALCULATIONS
by T. G. Hicks
Pub. price, $19.50
Club price, $15.25

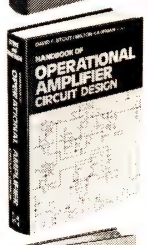

617/97X
HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN
by D. E. Stout & M. Kaufman
Pub. price, $24.50
Club price, $17.50

771/189
ELECTRONIC TROUBLE-SHOOTING
by C. N. Herrick
Pub. price, $13.95
Club price, $10.95

124/485
ELECTRICAL ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS, 3/e
by J. D. Constance
Pub. price, $17.00
Club price, $12.50

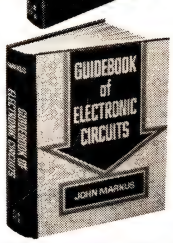

404/453
GUIDEBOOK OF ELECTRONIC CIRCUITS
by J. Markus
Pub. price, $26.95
Club price, $21.50

save time and money by joining the

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

McGraw-Hill

Here is a professional book club designed to meet your on-the-job engineering needs by providing practical books in your field on a regular basis at *below publisher prices.* If you're missing out on important technical literature—if today's high cost of reading curbs the growth of your library—here's the solution to your problem.

The Electronics and Control Engineers' Book Club was organized for you, to provide an economical reading program that cannot fail to be of value. Administered by the McGraw-Hill Book Company, all books are chosen by qualified editors and consultants. Their understanding of the standards and values of the literature in your field guarantees the appropriateness of the selections.

How the club operates: Every month you receive free of charge *The Electronics and Control Engineers' Book Club Bulletin.* This announces and describes the Club's featured book of the month as well as alternate selections available at special members' prices. If you want to examine the Club's feature of the month, you do nothing. If you prefer one of the alternate selections—or if you want no book at all—you notify the Club by returning the card enclosed with each Bulletin.

As a Club member, you agree only to the purchase of four books (including your first selection) over a two-year period. Considering the many books published annually, there will surely be at least four you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB
P.O. Box 582, Princeton Road, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated. I am to receive the bonus book at the introductory price of $1.89 plus my first selection, plus tax, postage and handling. If not completely satisfied, I may return the books within 10 days and request that my membership be cancelled. If I keep the books, I agree to take a minimum of three additional books during the next two years at special Club prices (guaranteed 15% discount, often more). I will receive the Club Bulletin 12 times a year. If I want to examine the featured selection, I need take no action. It will be shipped automatically. If, however, I want an alternate selection—or no book at all—I simply notify the Club by returning the convenient card always enclosed. I will always have a minimum of ten days in which to return the card and you will credit my account fully, including postage, if this is not the case. Membership in the Club is continuous but cancellable by me at any time after the four-book purchase requirement has been filled. *This order subject to acceptance by McGraw-Hill. Orders from outside the continental U.S. must be prepaid. All prices subject to change without notice. Offer good for new members only.*

Write Code # of $1.89 bonus book selection here

Write Code # of first selection here

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

EXTRA SAVINGS: Remit in full with your order, plus any local and state tax, and McGraw-Hill will pay all postage and handling charges. **E33324**

CIRCLE 74 ON FREE INFORMATION CARD

GTE Sylvania, Electronic Components Group, 100 First Ave., Waltham, MA. 02154.

We've got the longest running feature on TV.

Our Color Bright 85® picture tube warranty is the longest in the industry. We can offer it because we're confident that a Color Bright 85 picture tube will probably last longer than five years.

The warranty is a great selling tool that builds customer confidence in your quality work. Plus, it lets you form a long-term customer relationship with each picture tube you replace.

*Limited warranty, naturally. It does not cover labor for replacing a tube.

The Color Bright 85 picture tube offers economy with the high quality standards you expect from Sylvania. Couple that with the new 5-year warranty* and you'll find the Color Bright 85 is an easy sale.

And it can be better for you in the long run.

GTE SYLVANIA

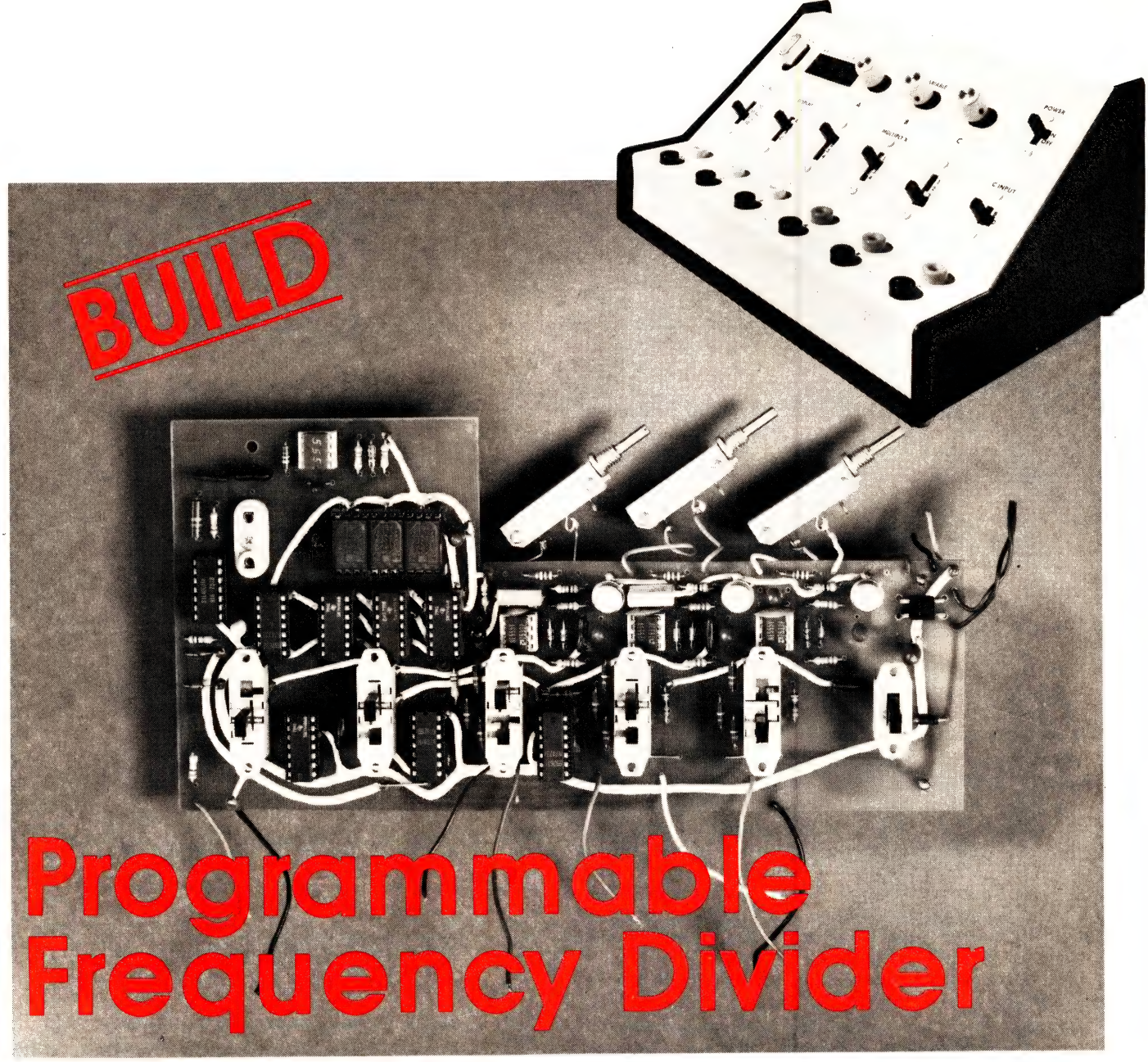

Wide range of frequency division is made possible by three cascaded 555-timer IC stages. The divisor is selected by three 10-turn pots and indicated on an LED display

GEORGE BAUMGRAS

FREQUENCY DIVIDING CIRCUITS ARE WIDELY USED FOR TIMEBASES, test equipment functions, music synthesizers and digital applications to name but a few. If we want a specific output, a crystal oscillator/digital counter combination affords the best accuracy, usually at the price of high package count and limited choice. The programmable version offers considerable improvement in choices available, but the price goes up—many switches and a long list of codes are necessary. A properly calibrated wave generator is an alternative, except that accuracies better than ±3% usually cannot be expected unless monitored by an expensive digital counter. The circuits described here do nothing new; rather, they perform this common task at a fraction of the usual complexity without sacrificing accuracy. A few design applications and the construction of a multi-purpose test instrument will be described—many other unique applications in your field of interest should become obvious.

The basic circuit (Fig. 1-a) is a very simple, stable and reliable means of dividing fixed frequencies with absolute accuracy, using the versatile 555 timer IC. Depending on the R1 and C1 values selected, the input will be divided by some whole number from 2 to at least 500 with off-the-shelf components. With selected parts, careful layout and a well-regulated power supply, much higher divisors are practical. Figure 1-b is a flexible 1-second timebase which demonstrates package count reduction to an absolute minimum. The line frequency can be any commonly available, and by adjusting the value of the 50K potentiometer, the output can be adjusted to 0.5 Hz, 2 Hz or any of several other choices.

By comparison, the conventional TTL timebase requires at least one transistor and two IC's to accomplish the same purpose. You can try out this circuit very quickly on a prototype breadboard, or even on a TTL IC tester if you can isolate pins 2, 6 and 7 from the LED logic-state indicators. Figure 1-c shows the input and output waveforms for a ÷4 using a 555 timer. The values of R and C can drift slightly due to temperature and aging without affecting operation; also long-term supply-voltage variations have no effect.

How the basic circuit works

A 555 timer IC connected in the familiar monostable configuration (Fig. 1-a) will output a positive voltage at pin 3 for a selectable time period, if pin 2 is briefly triggered below ⅓ of the supply potential. The duration of this pulse is approximately equal to R1 × C1 × 1.1, provided pin 2 remains high. Adding C2, R2, R3, D1 and D2 changes this circuit to an efficient divider. When a negative-going pulse through C2 drops the voltage across R2, pin 2 goes low because of the decreased current through R3 and triggers the internal comparator. Pin 3 now flips to near the power-supply level and most of this voltage is fed back to pin 2 through D2 and across R3 which prevents triggering during the time T.

When C1 discharges enough, pin 3 drops to the low level, pin 2 is clamped at about half the supply due to the voltage divider R2, D1 and R3, and cannot be triggered until the next pulse comes along. During time T, the IC will not respond to an input pulse and thus divides by responding to only 1-of-N trigger commands. The rate of division (N) can be calculated by: f_{in} (Hz) × T (secs).

The value of R1 can be varied by means of a potentiometer and a few switched resistors so that a wide range of divisors may be continuously selected, using one capacitor. If a multi-turn potentiometer is used for R1, resolution is excellent and the output pulse width can be varied considerably. If various values of C1 are also switchable, one divider can be set up to handle any input up to at least 1 MHz. If a single output is wanted, however, cascaded variable-R1 dividers are more useful. If three are cascaded, the output is determined by: $f_{in} \div (N \times N \times N) = f_{out}$.

The variable modulo test unit

The schematic in Fig. 2 uses the basic principle of Fig. 1-a for each of its three cascaded sections. The divisor for each is selected by a 10-turn panel-mounted potentiometer, a four-position range switch and a single capacitor. The internal frequency is generated by IC1-b and IC1-c, controlled by a plug-in crystal which can be any conceivable value to 1 MHz. This is fed to the NAND Schmitt triggers IC2-a and IC2-d. The external input goes to the high impedance input of IC1-a and to IC1-d, limited to TTL levels. This source is also conditioned by IC2-b and IC2-c.

Both sources are selected with S1, and either one may be prescaled by IC3, a divide-by-10 counter, if desired. The output pins of S1 go to S2 and the first variable modulo divider, IC4. The output of IC4 carries to IC5 and from there to IC6—all three outputs are also routed to panel output jacks.

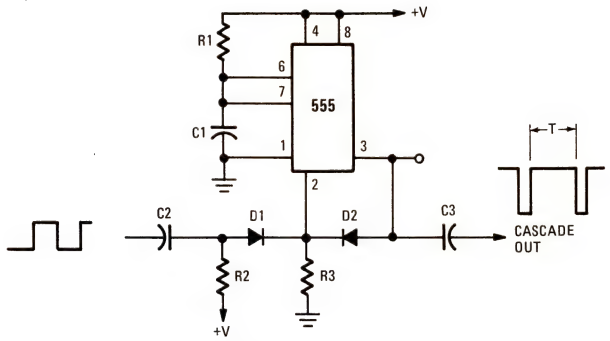

THE BASIC DIVIDING CIRCUIT. ÷ N = f_{IN} × T, T = R1 × C1 × 1.1. C1 SHOULD BE AS SMALL AS PRACTICAL, BUT NOT LESS THAN 500pF.

a

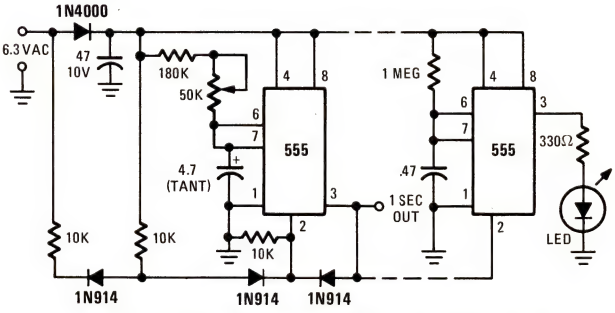

A LINE FREQUENCY TIME BASE USING ONE IC. OUTPUT MAY BE CALIBRATED WITH A PERIOD METER, OR BLINKER LED IN OPTIONAL ADD-ON CIRCUIT MAY BE COMPARED WITH THE SECONDS READOUT OF A DIGITAL CLOCK.

b

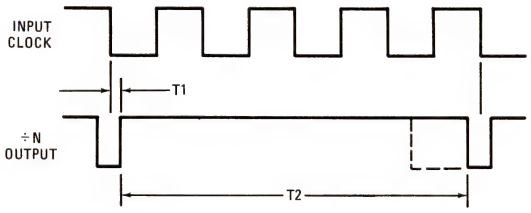

SYNCHRONIZED TRIGGERING. TIMING FOR ÷4 IS SHOWN. T1 IS THE TRIGGER TIME FOR THE 555, LESS THAN 1 μSEC. T2 IS THE PIN 3 "ON" TIME ESTABLISHED BY R AND C, WHICH CAN VARY AT LEAST 1/2 CLOCK CYCLE WITHOUT AFFECTING THE OUTPUT RATE.

c

FIG. 1—FREQUENCY DIVIDER circuits using the 555-timer IC. The basic frequency divider is shown in *a*. A 1-second timebase circuit that divides the line frequency is shown in *b*. Input and output waveforms for a ÷ 4 circuit using a 555 is shown in *c*.

PARTS LIST

Resistors all 5% ¼-watt unless noted
R1—22 megohms, ½ watt, 10%
R2, R3, R4—10,000 ohms
R5 thru R13—220,000 ohms
R14 thru R21—22,000 ohms
R22, R23, R24—330,000 ohms
R25, R26, R27—1200 ohms
R28—180,000 ohms
R29, R30, R31—68 ohms
R32—5100 ohms
R33—22,000 ohms (see text)
R34—180 ohms
R35 thru R39—not used
R40, R41, R42—1 megohm variable (Beckman Helipot model 57 with shaft attached or equal)
CI—20-pF disc
C2—30-pF disc (or optional 4-40 variable)
C3—500-pF mica, 5%
C4—0.047-μF disc
C5—0.001-μF disc
C6, C7, C8—0.05-μF disc
C9, C10, C11, C12—100-pF disc
C13 thru C18—22-μF, 10V, tantalum
C19—2.2-μF, 10V, tantalum
C20—1-μF, 10V, tantalum
C21—4000-μF, 15V, electrolytic (0.9" diameter x 2" maximum)
D1 thru D9—1N914 or 1N4148
D10—HEP177 or HEPR0804
D11—LED, 0.18" diameter
IC1—CD4001BE quad 2-input NOR gate
IC2—74132 quad NAND Schmitt trigger
IC3, IC10, IC11, IC12—7490 decade counter
IC4, IC5, IC6, IC9—555 timer
IC7—7473 dual JK flip-flop
IC8—7402 quad 2-input NOR gate
IC13, IC14, IC15—5082-7300 (or -7302) decoder/latch/display (Hewlett-Packard)
IC16, IC17, IC18—LM309H 5V regulator
IC19—LM340-5T 5V regulator
Q1—HEP50 or equal
S1, S2, S3, S4, S5—double pole, 4-position slide (Continental Wirt or equal) PC type
S6, S7—SPDT slide (Continental Wirt or equal) PC type
T1—power transformer: primary 117 VAC; secondard 8V, 0.7A
XTAL1—1 MHz, plug-in type (see text)
One IC socket, 24-pin Wire-Wrap type
Eight IC sockets, 14-pin Wire-Wrap type
Four IC sockets, 8-pin Wire-Wrap type
Crystal socket type HC6U (.05" pins spaced .487")
Eight Banana sockets, black
Eight Banana sockets, colored
Cabinet, LMB 007-946 or equal
Circuit board
AC line cord
Three Knobs for ⅛-in. shaft
Plastic window, 1 x 2 x 0.05"
No. 22 stranded insulated wire
Grommet for line cord
Assorted hardware
Solder

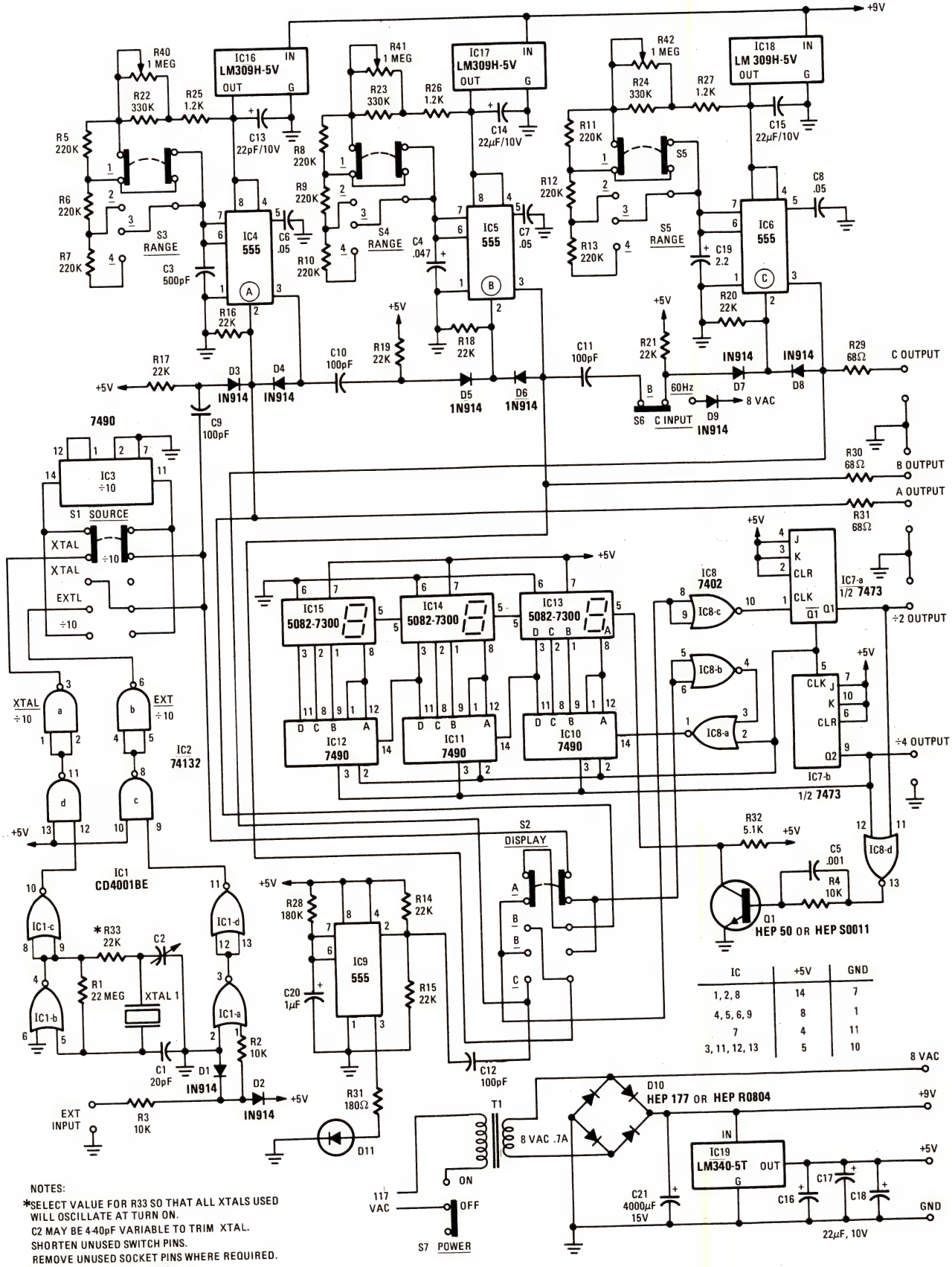

IC	+5V	GND
1, 2, 8	14	7
4, 5, 6, 9	8	1
7	4	11
3, 11, 12, 13	5	10

NOTES:
*SELECT VALUE FOR R33 SO THAT ALL XTALS USED WILL OSCILLATE AT TURN ON.
C2 MAY BE 4-40pF VARIABLE TO TRIM XTAL.
SHORTEN UNUSED SWITCH PINS.
REMOVE UNUSED SOCKET PINS WHERE REQUIRED.
HEAT SINK REQUIRED FOR IC19

FIG. 2—PROGRAMMABLE FREQUENCY DIVIDER has 3-digit LED display to indicate the divisor of the three 555 divider stages.

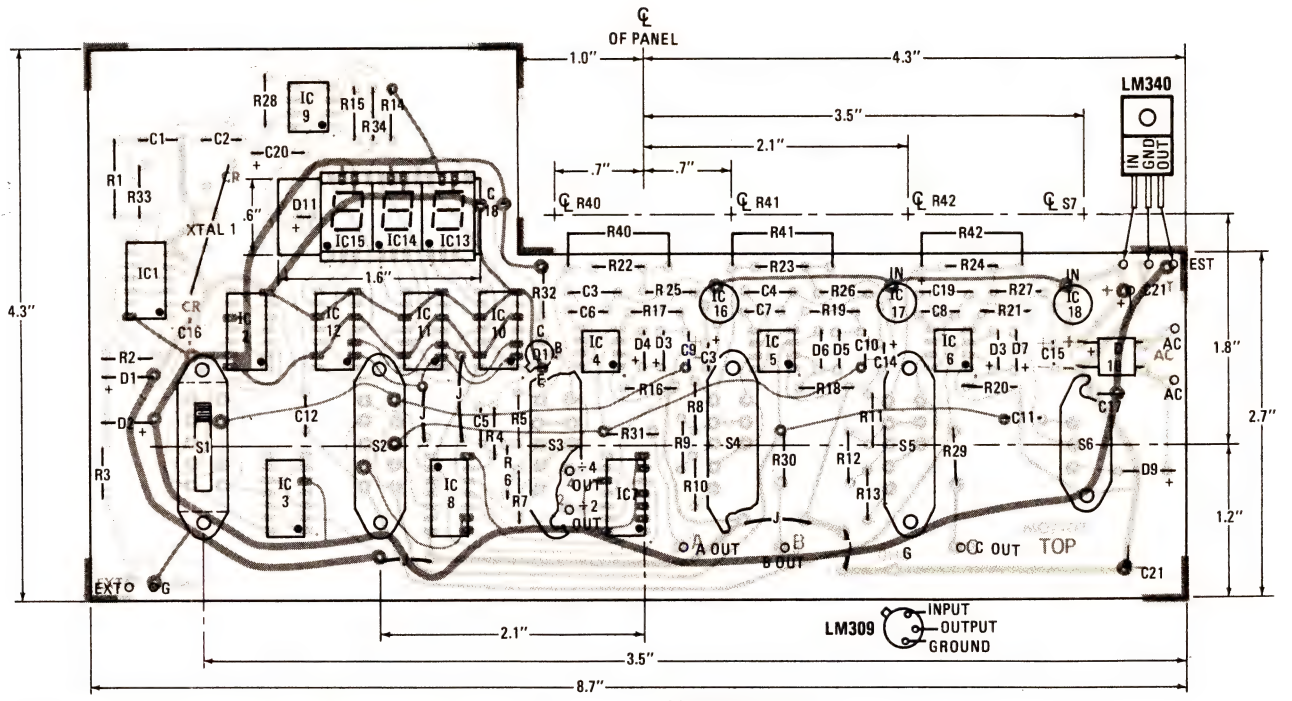

NOTE: DIMENSIONS ARE FOR CIRCUIT BOARD SIZE AND PANEL LAYOUT

C21 MOUNTED ON UNDERSIDE OF BOARD

COMPONENT PLACEMENT diagram showing PC board dimensions.

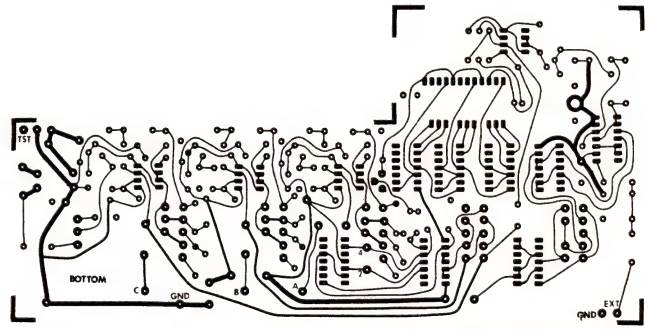

BOTTOM-SIDE foil pattern.

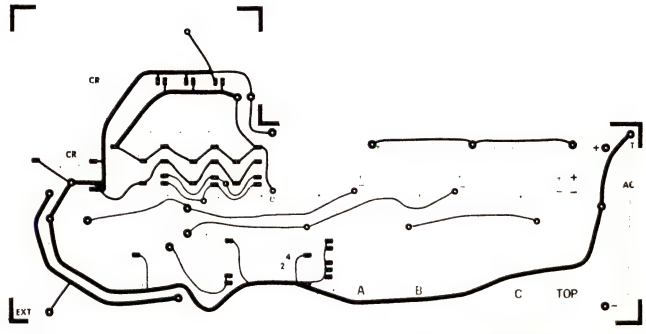

TOP-SIDE foil pattern.

Divider C can be switched by S6 to either the carry output of B or to a 60-Hz half-wave source, but in the latter mode, divider C will not show its divisor in the display. To use this option, divide 1 MHz by (100 × 100 × 100) for a 1-Hz output at C. Change the C input switch to the 60-Hz position and the output will remain 1 Hz. Similarly, for a 2-Hz output, divide by 100 × 100 × 50, or for a 0.5-Hz output divide by 100 × 100 × 200 and so on. This arrangement provides a separate selectable timebase which remains constant while A and B are varied.

The display will directly read the divisor for each section, except as noted above, which makes a frequency counter unnecessary. However, a pocket calculator will be helpful. Since the readout is a ratio rather than a frequency, display updating, for simplicity, must occur at a rate proportional to the output of the section being read. For this reason a dual flip-flop, IC7, is used to sequence the count, latch and reset functions in order to provide the minimum time slot for each.

The divide-by type of readout is preferred since it is much simpler to build-in than a counter capable of reading from 500 kHz to 0.1 Hz and requires only three digits without decimal points. Also, the time between pulses out may be read directly, because the readout is reciprocal. If, for example, the input is 1 MHz and the display reads 100, then the output is 10 kHz and the pulses are 100 μs apart. An LED blinker next to the display is actuated by the C output and IC9 and conveniently indicates visually the slower rates only. When setting the larger divisors for C it may take around 20 seconds for the display to update, which occurs after every fourth blink, and this indicator can be very helpful.

The symmetrical squarewave ÷ 2 and ÷ 4 outputs from IC7 are connected to panel jacks and subdivide the output of the section being read; the divisor for these outputs is determined by mentally doubling or quadrupling the readout. This arrangement makes possible nine related output frequencies at any setting of the variable controls by selecting display switch positions, or five frequencies output simultaneously without switching.

The input and output lines for either A, B or C are selected by S2. The selected output is buffered and inverted by IC8-c and drives the clock input of IC7-a which in turn causes $\overline{Q}1$ to go low, toggle IC7-b and enable IC8-a (Table 1). The selected input is buffered and inverted by IC8-b and IC's 10, 11 and 12 start to accumulate the count from IC8-a. Another output pulse from IC8-c again clocks IC7-a, disabling IC8-a and stopping the count. The Q outputs of IC7-a and IC7-b are now at logical 0 and IC8-d applies a positive voltage to the base of the transistor through R4 and C5, where it is inverted to a logical 0 at the latch inputs of the display IC's, and update occurs.

The next output pulse causes IC7 to go into a holding mode and the latch enable goes high. The final output pulse of this sequence again clocks IC7-a, causing the Q1 output of IC7-a and the Q2 output of IC7-b to go to a logical 1 and reset the decade counters. Each set of four pulses repeats the process to keep the display updated as the divisor is varied by the control knob.

The power supply uses a full-wave rectifier to improve filtering by capacitor C21. IC19 supplies regulated voltage to

all IC's except IC4, IC5 and IC6. These are individually regulated by IC16, IC17 and IC18 to avoid voltage variations originating elsewhere in the circuit that can cause poor resolution and instability. Capacitors C16, C17 and C18 are located on the board for a similar purpose.

Construction details

The three variable potentiometers should each be checked for smooth and gradual resistance change as the shaft is rotated the final two turns on each end. Select the best one, marking the "good" end, and use it for divider A. The other two are not as critical, but do use the same end when wiring them for B and C. It makes no difference which way the knobs turn to set the divisor, but they should all be the same.

The single circuit board mounts nearly all the components on its top surface, capacitor C21 mounts on the bottom side and IC19 is bolted to the cabinet rear panel. Brass nuts (No. 3-56) soldered to the six switch mounting plates attach the assembled board to the panel rear surface and spaces it ⅝-inch away. The enclosure can be a cabinet 9 × 6 × 3-inches minimum, or the type noted in the parts list. Raise the display IC's (and the LED) from the board surface just enough to contact the back side of the plastic window by means of a 24-pin wire-wrap socket, which also permits soldering on both sides of the board.

All of the 14-pin sockets are also the wire-wrap type. Raise them just enough to allow soldering, then clip off the excess pin length. Insert the switches in the board and screw them to the front panel to insure proper alignment and height before soldering them in place. Once the fit is established, assemble the remaining sockets and parts, then solder capacitor C21 to the bottom of the board.

Wire leads for the input, 5 outputs, 2 grounds, 3 potentiometers and IC19 should be installed next (a total of 17 wires), leaving them long enough for connection later on. After installing the IC's, test the circuit in case there is an accidental short somewhere, using a variable regulated power supply. Attach the positive lead to IC19's regulator output connection (marked TEST) and the negative lead to one of the ground wires, then gradually apply a maximum of +5 volts. The display should light at least partially, and current drain should be about 350 mA. If a crystal is plugged in, IC1 should oscillate and the waveform at pin 10 can be observed on an oscilloscope. At this time it is also advisable to test the other crystals to be used. If any of them do not work, try a smaller value for R33, or replace IC1. One of the crystals can be trimmed by the optional capacitor C2 at a later time.

The assembly can now be mounted to the machined, painted and lettered cabinet. Install the 3 potentiometers and 12 banana jack sockets and wire them to the board, keeping the leads as short as practical. The regulator, IC19, is attached to the rear panel for grounding and heat-sinking and connections completed. Splice extra wire to the transformer leads if necessary and assemble it. Connect the power switch and line cord to the primary and the secondary leads to the board. If all has gone well, the Variable Modulo Frequency Divider is now ready for use.

Using the dividers

Each divider section should be considered as a separate unit that performs best at the frequency for which it was designed. Although the total package can, for example, divide 1 MHz by many whole numbers from 2 to more than 10,000,000, not all the divisors in between can be obtained.

The reason for this is simple: specific values of R and C establish a time period which remains constant regardless of the input, while the ratio of input to output varies with frequency. The method of determining any output is: $f_{in} \div N = f_{out}$, as demonstrated by the following example: 1 MHz ÷ (100 × 100 × 100) = 1 Hz. If we change the divisor of A (or B) then the divisor of B (or C) will also change because of the fixed time period as in the next examples: 1 MHz ÷ (200 × 50 × 100) = 1 Hz, or 1 MHz ÷ (100 × 200 × 50) = 1 Hz.

It is nearly impossible to state how many different outputs can be obtained from the cascaded dividers because of the many factors and options involved—only guidelines may be given. To begin with, the basic plan is to extract 1 Hz from 1 MHz, or divide by 1,000,000 as in the above examples. If each section divides by 100, then A input is 1 MHz, B input is 10 kHz and C input is 100 Hz. But also any section will divide its stated input by anything from 2 to 500.

Accordingly there must be initially 4500 choices available, some of which are duplicates. Several thousand more may be added by varying the original ÷ 100 to some odd higher or lower value for A (or B) to result in a new input to B (or C). We can again add many thousands of choices to the list by changing crystals, best done by using odd values. A 971.52 kHz crystal is a good choice for one of these, as explained further on. The prescaler can be easily reconnected as a ÷ 9 or ÷ 7 to add still another option.

Instead of the crystal oscillator, we can use an existing TTL source, or a wave generator, prescaled if necessary, but regardless of the source, accuracy will be the same as the input. Based on these calculations, the availability of something close to what we want becomes dependent on the number of odd-ball crystals on hand plus a little ingenuity in setting the divisors—perhaps 100,000 choices might be a reasonable estimate.

Applications

One interesting use for this project, and the basic circuit, is in the field of music synthesis. Using the 971.52-kHz crystal mentioned earlier, set the dividers at A= ÷ 232, B= ÷ 8 and C= ÷ 8, which will result in nine octaves of note C present or selectable at the five outputs, as shown in Table 1. The outputs must of course be further processed to become usable. The frequencies given do not necessarily hold true for all scales and instruments, and are stated only as typical.

TABLE I

OCTAVE #	OUTPUT AT	f_{out}	f_{true}*
8	A	4187.5	4186.0
7	A ÷ 2	2093.7	2093.0
6	A ÷ 4	1046.8	1046.5
5	B	523.44	523.25
4	B ÷ 2	261.72	261.63
3	B ÷ 4	130.86	130.81
2	C	65.43	65.40
1	C ÷ 2	32.71	32.70
0	C ÷ 4	16.35	16.35

*For note C. Equally tempered music scale

The wide range of available outputs is very useful for calibrating tone generators and other frequency sources, as well as for tuning tank circuits, notch filters and the like. Assembly manuals for kits usually specify the use of an accurate frequency source for calibrating (oscilloscopes, counters, etc.). If one output is made to gate a strobe lamp, very accurate RPM measurements can be simplified. Motor speeds (where RPM depends on frequency) can be continuously varied over a wide range. **R-E**

SPECIAL CONSTRUCTION ISSUE

The June issue of Radio-Electronics will feature five construction projects. These will include a music synthesizer that generates music from pink-noise sources, a pushbutton telephone dialler with expandable memory, an LED wall-clock, a quadriphonic oscilloscope adapter for your hi-fi system and an IC Identifier/Tester for your workbench.

HI-FI

New Way To

Graphic equalizers are commonly used to tailor
from Shure Brothers permits rapid

NOW THAT AUDIO AMPLIFIERS, PREAMPLIfiers, FM tuners and even phono pickups have been refined to the point that they deliver ruler-flat frequency response at barely measurable distortion levels, the audio industry has turned its attention to the final pair of culprits in the quest for uniform frequency response—the loudspeaker and your own listening room. By far the worst offender of the two is the listening room itself, although there are still plenty of "hi-fi" speakers around that have dips and bumps in their response curves even when measured in an anechoic chamber (which is, admittedly, not the way most of us listen to music).

To solve the problem of speaker response and room acoustics, the audio industry has suddenly discovered a device that professional sound contractors have been using for many years—the graphic equalizer. The reasoning goes something like this: if we acknowledge the fact that no speaker actually delivers "flat response" from 20 Hz to 20,000 Hz and, if we also admit that our listening rooms emphasize certain frequency bands while attenuating others (depending upon their dimensions, furnishings, surface absorption coefficients and a host of other variables), why not introduce the inverse of the "actual" net response curve into the electronics of the system and thereby create a total system (room included) that will "sound" absolutely flat?

Equalizers

It was clear at the outset that the conventional bass and treble controls, long a fixture on hi-fi amplifiers and receivers, were not up to the job. These controls operate over nearly one-half of the audio spectrum each. The bass control alters response from around 500-Hz downward, while the conventional treble control boost or cuts all frequencies above around 1,000 Hz. It is fairly obvious that this kind of tonal adjustment cannot possibly eliminate the narrow-band bumps and valleys that often exist in a high fidelity system.

Having tested and measured a number of graphic equalizers on the test bench, I have long been convinced that using this type of product in a home hi-fi system can result in audibly improved musical reproduction in just about any listening room. Unfortunately, having visited a number of dealers and friends who own octave and third-octave equalizers, I must confess that in most cases the devices are not achieving their desired results. The problem seems to be that most users of graphic equalizers are tuning them by ear. Some graphic equalizers are supplied with special test records that are supposed to help you to set up the device for the flattest overall response. But again, unless you have a perfectly "calibrated ear", the final settings of those slide levers or knobs becomes largely a hit-and-miss proposition. Of course, professional sound installers often use real-time analyzers and calibrated microphones to "tune" a room and a system to within a few decibels of "flat", but such equipment, until recently, has cost several thousand dollars.

I recently became aware of a product developed by Shure Brothers, Inc. that, from its description, seemed able to do a good job of "room tuning" and costs under $500.00. Since I had always been somewhat in doubt about the response of my own reference listening set-up, I decided to attempt to equalize it. Some of the things I learned are worth repeating.

Actual response

Just to prove a point that has been made many times before, I decided to examine the response of my total system (including the room) by sweeping single-tone frequencies, from 20 Hz to 20 kHz, through my system and picking up the results by means of a calibrated microphone positioned where I normally sit when listening to music. The "sad" results are shown in the spectrum analyzer photo of Fig. 1. Hardly anything to be proud of. Besides the obvious and severe roll-off beginning just above 5 kHz or so, the series of "holes" at the low end of the response curve (some of which were greater than 20 dB in amplitude) seemed incurable. And even in the region above 500 Hz, where the "average" response settles down to a reasonable degree of flatness, there are multiple narrow-bandwidth peaks and valleys that ride up and down over a range of more than 10 dB. So much for single-tone testing of room acoustics!

Happily, our own human hearing comes to the rescue here. It has been proven that when we hear a very narrow

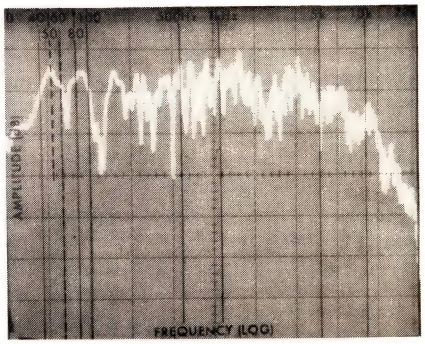

FIG. 1—TOTAL FREQUENCY RESPONSE of hi-fi system, including listening room.

"peak" or "valley" in the response curve (some say that one third of an octave is the limit), we do not aurally perceive it as an abberation in frequency response flatness. For this reason, such frequency response tests are best performed using "pink noise" instead of sweeping, single tones.

So, with that in mind, I borrowed a pair of Shure *SR-107* octave-band equalizers (see Fig. 2), and the same company's newly developed *model M615* equalization analyzer, shown in Fig. 3.

The analyzer kit includes a calibrated microphone, *model ES 615* and the analyzer itself. The analyzer contains a internal source of pink noise, whose

Room Equalization

ne response of the hi-fi/listening room combination. A recent introduction djustment of the graphic equalizer to obtain an overall flat response

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

level can be adjusted, a microphone amplifier and a series of octave-wide amplifiers that are used to activate two rows of LED indicators, one above the octave notations and one below. The pink noise source is fed to the system under test. Pink noise, when listened to over loudspeakers, sounds a bit like the rushing noise you hear when you tune between FM stations, except that it is carefully tailored to contain equal energy in each octave of the audio spectrum. The microphone is positioned where you would normally listen to your hi-fi equipment. An additional control, known as a HI-LO ENVELOPE control on the analyzer determines the amplitude "window" of the system.

If the energy of a given octave is louder than the nominal average level, the LED above that octave number will

FIG. 2—SHURE MODEL SR107 octave equalizer.

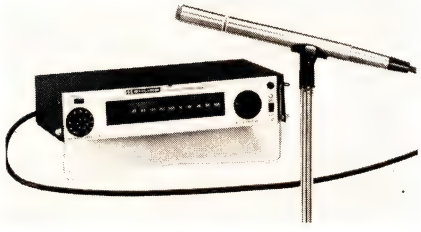

FIG. 3—SHURE MODEL M615 equalization analyzer.

light, while octaves of energy that are lower than average will cause an LED below the octave numbers to light. When the envelope control is rotated fully clockwise, the spread between lower LED illumination and upper LED illumination is ±6 dB. Thus, even with no equalizer in your system, if its response was within ±6 dB from 32 Hz to 16 kHz, all the lights would be off. The procedure involved in proper equalization involves reducing the setting of the envelope control and, as various lights come on (either on the "high" or "low" side), appropriate controls on your equalizer are tweaked until the lights go off. If you are able to gradually rotate the HI-LO ENVELOPE control fully counterclockwise and succeed in getting all the lights to extinguish, the response of your system (on an octave by octave basis) as heard at the microphone's position, would be flat within ±1 dB.

Just for fun, I rotated the envelope control fully counterclockwise before inserting the equalizers into the system. Sure enough, the light indicators gave me a good clue as to how far things were off. In Fig. 4, the 32-Hz octave shows up

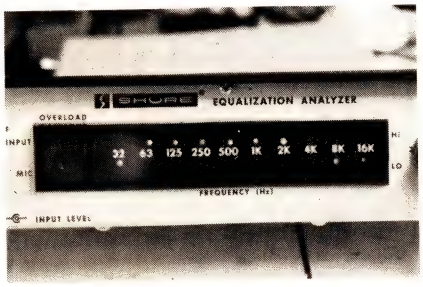

FIG. 4—EQUALIZATION ANALYZER shows the total frequency response of hi-fi system prior to equalization.

as being deficient in energy content, the 63, 125, 250, 500, 1K and 2K lights show too much energy in those bands, while the 4-kHz light is off (showing correct "average" level) and the 8-kHz and 16-kHz lights show that energy in those octaves is too low. Before even attempting to add correct amounts of equalization, I carefully rotated the envelope control clockwise, to determine approximately how much equalization would be needed for each octave. Since the envelope control is roughly calibrated in dB, I was able to plot the approximate octave response of my system prior to equalization, as shown in Fig. 5.

Equalizer set-up

Next came the job of actual equalization. It came as no surprise to me that the equalization settings required for the

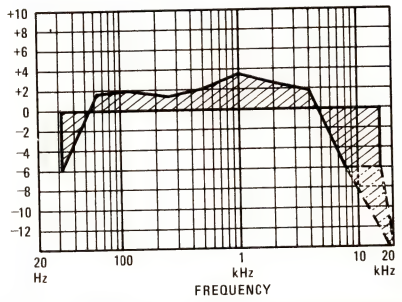

FIG. 5—APPROXIMATE OCTAVE RESPONSE of hi-fi system prior to equalization.

left channel differed in several respects from those required for the right channel. This also suggested the importance of having a graphic equalizer with separate levers or controls for each channel (not all equalizers are so built). The best I was able to do resulted in the individual octave settings shown graphically in Fig. 6. Figure 6-a shows the plotted

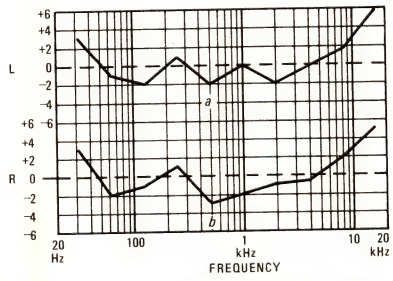

FIG. 6—CONTROL SETTINGS of equalizer. The front-panel control settings for the left channel is shown in *a* and the right channel in *b*.

settings applicable to the left channel and Fig. 6-b shows the settings for the right channel.

At this point, I decided to find out what the actual response of the two graphic equalizers were. So I connected

them to the spectrum analyzer which was swept from 20 Hz to 20 kHz in the usual log-sweep mode. The resultant response curve of the left-channel equalizer is shown in Fig. 7, and it

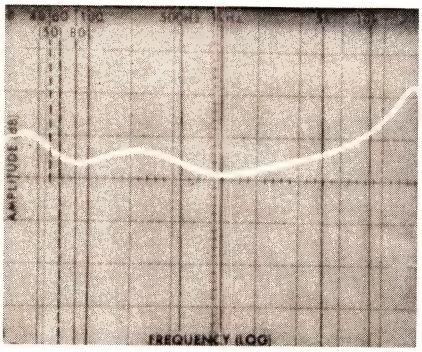

FIG. 7—ACTUAL EQUALIZER RESPONSE with the control settings shown in Fig. 6-b.

corresponds quite closely to the point-by-point or octave-by-octave settings shown of Fig. 6-a.

Connecting the equalizers into the audio chain and, again using pink noise, I observed the face of the Shure analyzer and noted that all lights were extinguished with the exception of the 32 Hz and 16 kHz indicators. (The 63 Hz indicator blinked every now and again, briefly, as I moved about the room, but was off when I returned to my "listening" chair.) The indicator lights are shown in the photo of Fig. 8.

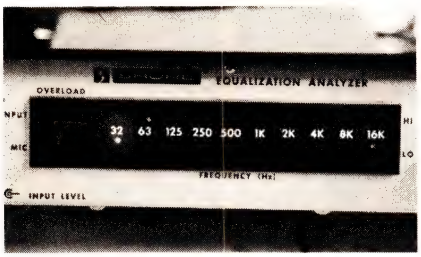

FIG. 8—EQUALIZATION ANALYZER shows total frequency response of hi-fi system after equalization.

Having a good source of pink noise at my command, I decided to measure overall response using this form of wide-band noise and the sweep filters of the spectrum analyzer (which were set to their narrowest bandwidth). First, I measured overall response with the equalizers bypassed. The results are shown in the upper trace of Fig. 9. Then the sensitivity of the analyzer was lowered (but with levels unchanged) so that a second trace could be displayed without superimposing it on the first sweep, and both left- and right-channel equalizers (preset as outlined before) were switched into the system and the sweep was repeated. The much improved results are shown in the lower trace of Fig. 9.

Still aware that single-tone sweeps have their problems, I nevertheless

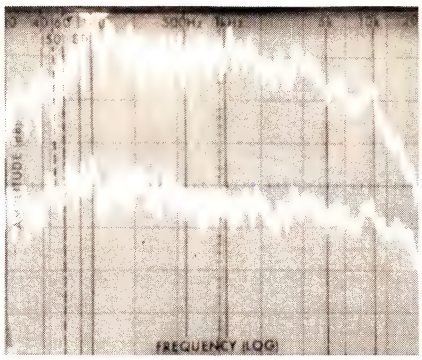

FIG. 9—TOTAL FREQUENCY RESPONSE of hi-fi system without equalization is shown in upper trace. Lower trace shows response after equalization.

decided to have another go using this method and, while those narrow-band bumps and valleys still showed up in Fig. 10, a comparison between Fig. 10 and Fig. 1 shows that even using this crude measurement approach, a great amount of improvement is evident.

You may recall that I never did

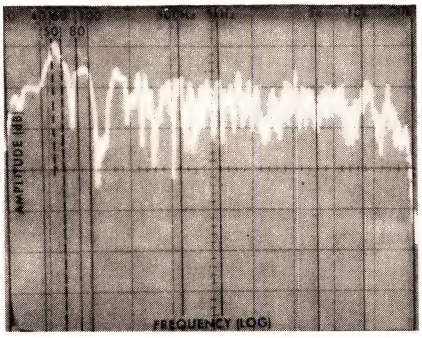

FIG. 10—SINGLE-TONE FREQUENCY RESPONSE of hi-fi system after equalization.

succeed in bringing the 32 Hz and 16 kHz octaves to a "flat" response. Referring to Fig. 6 once more, you will also note that I settled for only +6 dB at the highest octave and less than +4 dB at the lowest octave. Perhaps you are wondering why I didn't crank these end-octave controls up to their full +12-dB capability. This brings us to a possible trouble area caused by equalization.

Moderate amounts of equalization can do wonders for the sound of your hi-fi system and, indeed, having now heard the difference between a *properly* equalized system and one which is not, I would not be without an equalizer from this point onward. But improper use of an equalizer can cause real havoc with your system. Suppose, for example, that my system had been perfect even without equalization except for those end upper and lower octaves. I might have pushed the 32 Hz and 16 kHz levers up to their extremes, but if I had done so, my amplifier would probably clip and distort at those extreme frequencies.

If I was lucky enough to hear the distortion before my tweeter burned out (or my woofer-cone ruptured), I would have had to "back off" on my volume control or lowered the effective power output *average* of my entire system by an enormous factor. Table I shows the *effective* available amplifier power of different amplifiers having different nominal power ratings when one or more equalization levers are set to different degrees of boost in an attempt to flatten the response of a system. Note that if a mid-frequency lever is boosted only 3 dB for example, the effective power available from the system (without clipping) becomes half of the amplifier's actual power rating. And, in an extreme case where 10 dB of boost at some specific frequency is required, a 200-watt amplifier becomes, effectively, no more powerful than a 20-watt amplifier with a flat response.

So, while we are convinced that system equalization can do wonders for a hi-fi system when used in moderation, over equalization to compensate for system deficiencies that are beyond helping can cause more damage and grief than no equalization at all.

The experience gained with the Shure equalization analyzer also convinced us that despite our long years of listening to hi-fi systems, attempting to equalize a system "by ear" can be a hopeless task. We hope that now that correct procedures are available as inexpensively as they are, that more and more audio dealers will offer in-home equalization service to serious audiophiles when they buy a graphic equalizer. Once we became familiar with the analyzer, actual correct setting of our equalizer controls took no more than about five minutes, and, despite the fact that none of the controls for either channel was set more than 6-dB away from "flat" (and most were displaced considerably less than that), we could not help marvelling at the improvement we heard. **R-E**

TABLE 1—EFFECTIVE AMPLIFIER POWER (watts) based upon various amounts of boost (dB).

AMPLIFIER RATING (WATTS)	+1 dB	+2 dB	+3 dB	+4 dB	+6 dB	+8 dB	+10 dB
20	15.8	12.6	10.0	7.96	5.0	3.16	2.0
30	23.7	18.9	15.0	11.94	7.5	4.74	3.0
50	39.5	31.5	25.0	19.90	12.5	7.90	5.0
100	79.0	63.0	50.0	39.80	25.0	15.80	10.0
150	118.5	94.5	75.0	59.70	37.5	23.70	15.0
200	158.0	126.0	100.0	79.60	50.0	31.60	20.0

Build 2650-Based Microcomputer System

Part II. Built on a single printed-circuit board, this 2650 microcomputer contains a video and cassette tape interface and resident supervisor program. Add a keyboard, video monitor, cassette tape recorder and power supply for a complete working system

JEFF ROLOFF

LAST MONTH, A DESCRIPTION INCLUDING specifications and schematic appeared.

This month, an in-depth look at the troubleshooting procedures plus the component placement diagram is given.

Troubleshooting

After applying power to the PC board, the first thing to check is the power-supply voltage. If the output of an adequate (5 volts, 3 amperes) power supply is pulled down by connecting it to the board, there is either an IC put in backwards (if the supply is not pulled completely to ground) or else the power-supply lines are shorted somewhere on the board. If an IC is plugged in backwards, it will become very warm immediately after the power is applied. If the supply is actually shorted to ground, the process is much more tedious since you must inspect both supply lines to discover the point of the short. If quality IC's were purchased, the majority of problems are caused by solder or etch shorts. For this reason, it is a good idea to check the whole board for little solder spatters.

Logic and display circuits

The logic section of the board is the next part of the board to test. You need a scope for this part, and its bandwidth should be above 10 MHz. (You can also send the board into Central Data to have a trained technician test it for $15.00 an hour.) Connect the scope to the composite video signal that appears on plug 5, pin 5, of the board. Observe the sync pulses that appear at the zero-volt level. There should be one short sync pulse (down from 0.5 volt) every 63.5 μs, and one long pulse every 16.667 ms. If either of these two trains of pulses are not there, or have the wrong frequency, you must check the Timing Chain and Sync Generator section of the circuitry.

The Timing Chain and Sync Generator circuit contains a crystal-oscillator as the basic timing source. (A complete schematic appears in last month's issue of **Radio-Electronics.**) This is a standard oscillator with the 14.192640-MHz crystal used as the main feedback element. The signal from this oscillator is buffered using three other inverters from IC53. The first divider network that this signal goes to is formed by IC50, IC51 and IC52. These three IC's are used to divide the master clock down to a signal that has a period of 63.5 μs. The three counters are all fed by the same clock, so that all of the outputs change state at the same instant. The enable pins of the two low-order counters are fed from the previous counter stage(s) in an arrangement that forms a 10-bit syncronous binary counter. Pins 1, 2 and 13 of IC54 monitor the states of this counter. When all three of the monitored lines are high, the clear line is activated which resets all of the counters.

The D1, D2 and D4 outputs of IC52 provide the first three binary divisions of the master clock. Since the characters are eight-dots wide, output D4 has the width of one character (it is the divide-by-eight output). The last output of this counter, along with all of the outputs of IC50 and IC51 (designated the 'C' outputs) provide a count of the current character position on the display. While it is counting from 0 to 79, the characters are actually appearing on the screen. While counting from 80 to 112 (during which the counters are reset), the display is in the process of horizontal blanking.

The horizontal sync signal is generated by IC62-a. The sync signal is eight character-spaces wide, which is about 4.5 μs. Also, the three dot signals that come from IC52 (D1-D4) are all OR'ed together to form the $\overline{\text{LOR}}$ signal that is used in the Display Generator circuit to load the data from the character generator into the shift register once for every character. The $\overline{\text{LOR}}$ signal has a duty cycle of ⅛ (negative duty cycle, that is), and it goes low for this one dot period at the very beginning of each character.

Now that the signals are defined for all of the areas of each scan line, the up and down position on the screen must be defined. The three other counters

(IC55-IC57) serve this function, IC55 is used to count down by 12 and the other two are connected to count down by 21. The input that enables the first counter is the $\overline{\text{EOL}}$ signal that reset the previous counters at the end of a scan line. The output of this counter is monitored at pins 3 and 4 of IC54, to determine when 12 scan lines have been counted. When this event has occurred, its output at pin 6 drops and resets the counter. The reason that it counts to 12 is that there are 12 scan lines for each character line on the screen (i.e., vertically there are 12 dots for each character). The L1, L2, L4 and L8 outputs of this counter are used to determine which scan line of a character line is currently being displayed. From lines 0 to 7, the display section is actually displaying a character (since the actual character size is eight-dots tall), while from lines 8 to 11, the display is blanking between lines.

The reset line for IC55 is used to clock the next two counters that determine the character line being displayed. The counters (IC56 and IC57) are both reset by IC54-b when a count of 21 character lines is reached. From character lines 0 to 15, the display is actually showing characters on the screen (or at least it can be), while from character lines 16 to 21, the vertical blanking is in effect. Vertical sync is generated in this time period by IC62-b. Pins 4 and 5 of IC64-a are inputs to the gate that mixes the vertical and horizontal sync signals to form the composite sync signal.

The video-blanking signal is composed of a horizontal blanking and vertical blanking signal. The horizontal blanking signal is generated by IC64-b and IC66-b. The output of IC66-b is high when C64 and C16 are both high (at character position 80) and later changes back to low when $\overline{\text{EOL}}$ is present. Any of the four inputs to NOR gate IC70 indicate that the screen should be blank when they are high. So there are three other signals that indicate that the screen should be blanked and all of them are OR'ed together to form the master blanking signal. The vertical-blanking area is indicated by LN16. Any one of the four scan lines between character lines is indicated by L8. The DISPMEM line is high whenever the processor is accessing the display RAM. Wrong character patterns would appear when the display RAM is accessed, so we just blank the screen during this small interval to cover up the few out of place dots. The DISPLAY ACCESS signal is low whenever the screen is to be blanked. This signal is delayed one more character time (to make up for the delay in accessing the RAM and character generator in the Display Generator circuit) by IC65, using pins 2 and 5. If the processor is accessing display memory, pin 8 of IC65 is low and is a one character-time delayed version of the DISPLAY ACCESS signal. This in turn keeps $\overline{\text{BLANK VIDEO}}$ (pin 5 of IC65) low a little after DISPLAY ACCESS disappears to make up for the recovery time required by the RAM. The $\overline{\text{BLANK VIDEO}}$ signal goes to the output shift register and keeps the output data low by clearing the register.

If these circuits are operating correctly, a good video signal should be present that can be connected to a video monitor. Figure 1 shows the composite-video

FIG. 1—COMPOSITE VIDEO SIGNAL supplied to video monitor.

signal. If the sync signal is correct, the monitor should immediately lock onto the video signal and display a stable picture. If the picture does not lock-in, try lowering the value of the 330-ohm resistor (R9) in the video output stage (such as 220 ohms) and lower the value of the 100-ohm resistor hooked to the base of the two transistors. This will adjust the sync level and the total video-output level to suit your monitor. If you have a standard monitor, you will not have to do this since the output signal is standard.

If the characters on the screen waver, there is still a problem with the Timing Chain and Sync Generator circuit. Check this circuit out again, looking for any imperfections in the signals that indicate a bad IC or a shorted line. This probably won't happen, since a fault in the circuit usually causes major problems and not just a little wavering on the screen.

Now that a pattern appears on the screen, it must be identified. If it is a prompting character (a period) and the cursor appears in the upper left corner of the screen, the whole system is probably working. All that is needed is to hook up an ASCII keyboard and tape recorder to the correct plugs and see if commands can be entered into the monitor. (The procedure for testing the cassette interface is given later.) If you have either random characters on the screen or just 16 solid horizontal bars, the processor section of the board is probably not working. This prevents the supervisor program from being read in and thus the screen is not cleared.

Processor

The Processor and Bus Driver circuit divides the master clock by 12 to obtain the CPU clock. The divide-by-6 counter IC58 starts its count at 10 and counts up to 15. After the count of 15, inverter IC53-a connected to the carryout line and load input is used to load the 10 and start the division again. Flip-flop IC66 divides this carry signal by 2 to obtain the square CPU clock. The

PARTS LIST

All resistors ¼ watt, 5%.
R1-R6, R14, R18—10,000 ohms
R7, R8, R16, R17—1000 ohms
R9—330 ohms
R10—150 ohms
R11—82 ohms
R12—100 ohms
R13—620 ohms
R15—470 ohms
R19—20,000 ohms
R20—68,000 ohms
R21, R22—20,000-ohm trimmer potentiometer
C1, C2, C11—100 pF, disc
C3, C14—100 μF, 16 volt, electrolytic
C4, C8—0.01 μF, disc
C5, C6, C7, C9, C15-C29—0.1 μF, disc
C10—0.0022 μF
C12, C13—0.056 μF, ±10% polyester film
D1, D2—1N914 diode
D3—1N4729 Zener
D4, D5—1N4148 diode
Q1, Q2—2N5139 transistor

IC1—2650 microprocessor (Signetics)
IC2-IC10, IC21, IC22, IC78, IC79—74126
IC11, IC64, IC69—7408
IC12—7414
IC13, IC17—3624, pre-programmed PROM containing supervisor program
IC14-IC16, IC18-IC20, IC48—3624, PROM (see text)
IC23, IC24, IC65, IC75, IC77—7474
IC25, IC71, IC76—7400
IC26—9344, 4-bit by 2-bit multiplier (Fairchild)
IC27-IC29—74157
IC30-IC45—2102-1, RAM (Signetics)
IC46, IC47—74125
IC49—3624, pre-programmed PROM character generator, upper case
IC50-IC52, IC55-IC58—74163
IC53—74S04
IC54—7410
IC59—7432
IC60—74166
IC61, IC68—7411
IC62—7420
IC63, IC67—7404
IC66—74109
IC70—7425
IC72—555, timer
IC73—74123
IC74—CA3130
XTAL1—14.192640 MHz series-resonant crystal
MISC.—One 40-pin DIP socket for IC1, six 16-pin DIP sockets and printed-circuit board.

The following parts may be ordered from: Central Data Company, P.O. Box 2484, Station A, Champaign, IL 61820.

IC49—3624, pre-programmed PROM character generator, upper case, $27.

IC13, IC17—3624, pre-programmed PROM containing supervisor program, $27 each.

PC board, predrilled and etched, $30.

An assembled and tested microcomputer board, $325.

frequency of this clock is about 1.183 MHz, and if the faster version of the 2650 is put into the board, the counter's inputs can be changed to increase this frequency. The CPU clock signal is gated through IC11-a with the $\overline{\text{STOP CLOCK}}$ signal that allows you to externally stop the clock by bringing the line low. The timing relationships of the microprocessor is shown in Fig. 2.

Pin 16 of the 2650 is the reset input, and the RESET signal is generated using a Schmitt trigger and an R–C time constant. Capacitor C3 is initially discharged and the RESET line is therefore high. As the capacitor charges through resistor R6, the output of the inverter will change to a low level allowing the processor to operate—starting at address zero in memory. All of the outputs of the processor, except for RUN/WAIT, are buffered with tri-state drivers or an inverter in the case of the serial output line.

The tri-state drivers have their enable pins available for data bus override operations. For instance, bringing the $\overline{\text{ADDR DISABLE}}$ line low causes all of the address buffers to be disabled. This allows another device to take control of the address bus. The same is true for the data and control buses. So, by bringing these three enable lines low, you can effectively disconnect the 2650 from any external memory.

The SERIAL INPUT and SERIAL OUTPUT lines come directly from pins on the processor that can be inspected or set by special processor instructions. This allows the system to get by without a UART and also allows high flexibility as far as output rates and formats.

The data bus buffers are tri-state buffers, with either the in or the out buffers being enabled at one time. If the $\overline{\text{R}}$/W line is low, the processor is reading data, so the input buffers are enabled. If this line indicates that the processor is outputting data to the data bus, then the output buffers are enabled. Although buffers are not needed, they were put in so that any memory added to the system would not need to have its own set of buffers.

In the area of expansion, Central Data offers a S100 compatable bus board. It generates signals derived from

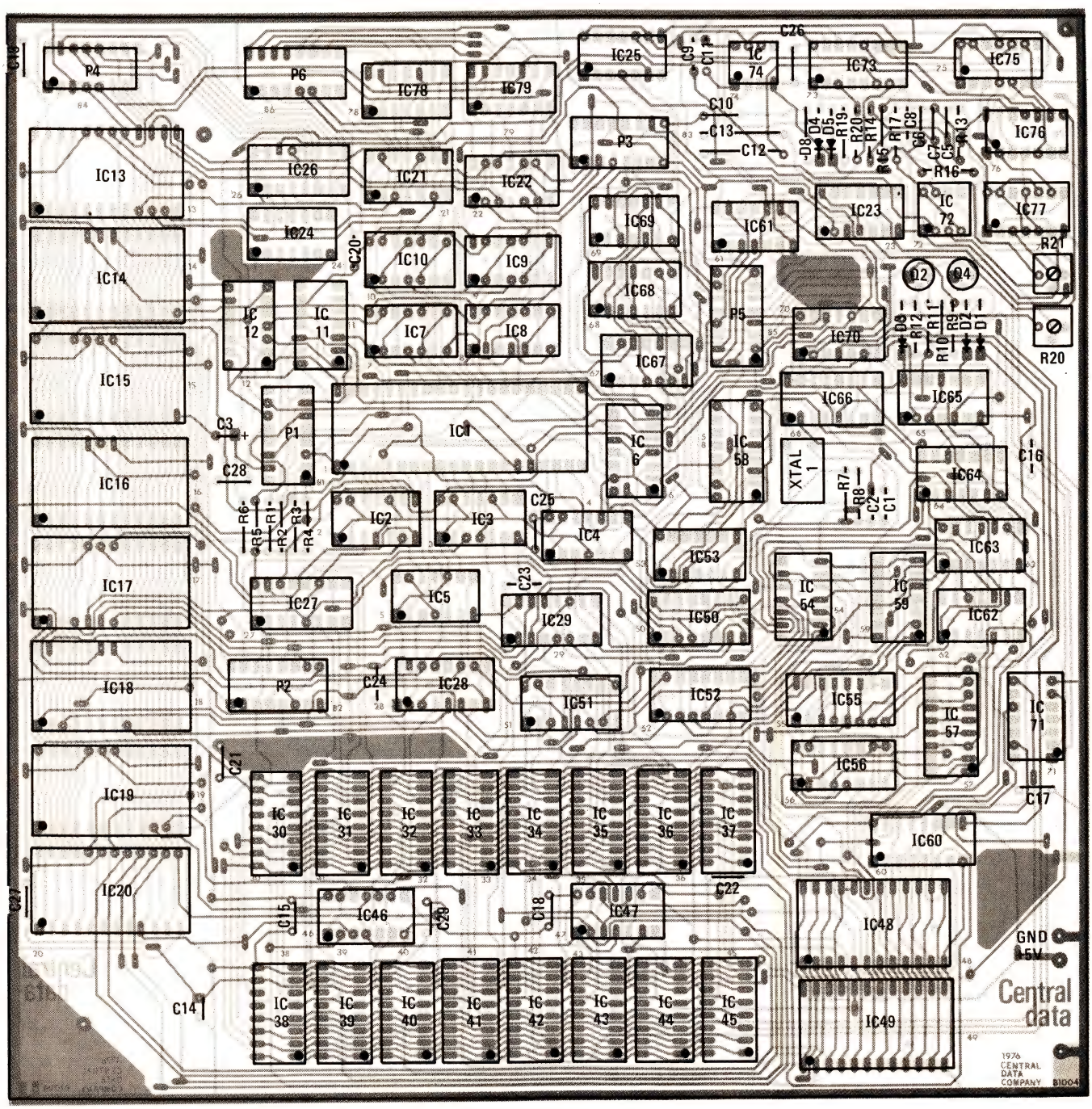

COMPONENT PLACEMENT diagram

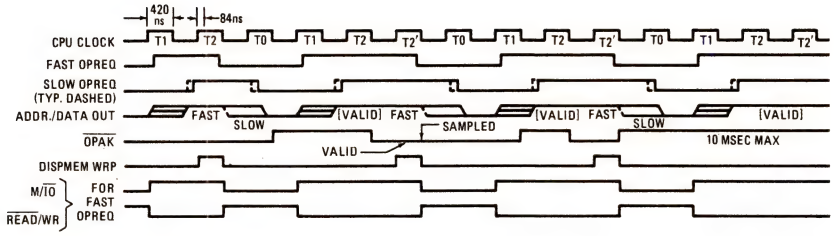

FIG. 2—2650 MICROPROCESSOR timing relationships.

the 2650 board that will interface directly with any standard 8080 static RAM board or I/O board. The board has room for five edge connectors, and is plug expandable with extender boards.

Locating a problem in the Processor and Bus Driver circuit requires inspection all of the address and data-bus lines to be sure that all of the signals are at standard TTL levels. If one line is stuck either high or low, carefully clip the pins of the IC's that this line runs to until the problem clears. The last pin that was clipped is the one holding the line, so replace the IC. Before cutting the IC pins, check the power supply on all of the IC's that the line runs to. Also, if any of the IC's are tri-state buffers, check to be sure that they are not gating data onto the line at the wrong time (an enable pin may be stuck in the enable state.)

If the processor's bus checks out, then you check to be sure that the RAM interface to the processor is working since that would also cause the random characters to appear on the screen. Initially, when the supervisor program is executed (right after reset), it clears the screen by sending the ASCII code for a blank (H20) on the data bus to the RAM, and then sequentially accessing all of the display positions and writing the data. Therefore, right after a reset, the DISPMEM line should undergo many transitions. If it doesn't, check out gates IC61-a and IC69-a that are used to generate this signal from the address lines. Note that the DISPMEM line indicates what page the processor is accessing—if it is the 4K page where the display RAM resides, this line is high.

If the DISPMEM line checks out, then look at the write-pulse generating circuitry. IC61-a (pins 1,2,12 and 13), along with flip-flop IC23-a, is used to generate a signal that is high at pin 5 of IC23-a for the first CPU clock cycle following the low to high transition of the OPREQ-signal. This is gated with $\overline{R}$/w line and the CPU clock by IC61-b. This signal finally goes through one last gate that turns on the write line of the RAM's if the processor is accessing the display memory page. This write line should have high activity right after the power is tuned on.

If these signals check out, then check the data-bus drivers IC46 and IC47. They are used to gate data from the display memory onto the data bus so that the processor can read the contents of the RAM. It is helpful to have a dual-trace scope for this, so that the input to the buffers and the output can be observed at the same time. Then check to see that the input and output of the buffers are the same when the enable is high.

There is almost nothing that can go wrong with the character generators, their operation is simple. IC49 is the one that is used for the normal operation of the board, with IC48 being an optional character generator for lower case, graphics, or other characters. Therefore, when supervisor program is the only thing that is running, it only selects character generator IC49. For this reason, the chip enable on IC49 (pin 20) should be low whenever the video is not blanked. This is easily checked with a dual-trace scope. If the other character generator is selected, and it is absent, a block of all on dots will appear on the screen. So, if you have several of these selections in a line, you will have a big horizontal bar on the screen rather than characters. Two of the output lines of the RAM may also be shorted, which would cause some characters not to be displayed. Again, a dual-trace scope is needed to check the data-out lines against one another to see if any look shorted.

The output shift register is IC60. It is loaded with the character generator's outputs at the first horizontal-dot position of each character, and then sends the eight-bit word out serially at the master-clock rate. Note that the clear line on IC49 is driven by the $\overline{\text{BLANK}}$ $\overline{\text{VIDEO}}$ line from the Timing Chain and Sync Generator circuitry.

The addresses for the display RAM are multiplexed by the Display Memory Address Switch. If the DISPLAY ACCESS line is low, the processor's address lines are selected to address the display RAM. This is the case when the display is being blanked (and thus the processor tries to access the display memory, raising the DISPMEM line and dropping the DISPLAY ACCESS line). The other case is when the display RAM is addressed by the Timing Chain. The signals C1 to C64 are gated in, along with LN1 to LN8, to select the correct address.

If the gating circuit for the ROM is not working properly, the supervisor program will not run. The output at pin 12 of IC-67 goes low whenever the ROM is selected. When using the supervisor program, this line will always be low when the DISPMEM line is also low. In other words, the supervisor only has two places to operate from, it will always be selecting one of these places.

The I/O ports 8 are also enabled using a good deal of gating circuitry. If the data bus doesn't have the right signal levels, check the two groups of data-bus buffers to be sure that they are not gating data onto the bus. This could happen if the enable pins are locked in a high state. Either a write data or a write control instruction will access the output port.

If the circuitry checks out, the supervisor program must be working for all of the operations except the tape routines. It is a simple matter to set up the cassette-tape interface and once it is set, it will stay perfectly aligned until it is changed. The potentiometer for the 555-timer should be adjusted so that the output of the 555 is a 4800-Hz square-wave. This is divided by two by the first flip-flop (pins 3 and 5 of IC77), and again by the second half of this same IC. The serial output line is clocked through part of IC75, and then this output is used to gate on one of the two frequencies. The R—C network at the output of IC76 (pin 11) is used to decrease the output-voltage level and change it into a more rounded signal. The demodulator section is just a monostable and operational amplifier.

continued next month

NOAA updates list

The National Oceanic and Atmospheric Administration (NOAA) National Weather Service has updated its list of stations to about the end of last year. The network is the sole government operated system for communicating weather, disaster or other warnings direct to the public. Weather receivers are available at most electronic stores.

The broadcasts are at 162.40, 162.475, or 162.55 MHz. A listing (by state, call letter and frequency) of the stations in service available free by writing to the National Weather Service, Silver Spring, MD 20910.

Zenith gets a patent for improved electron gun

Zenith's EFL (*E*lectrostatic *F*ocus *L*ens) has received Patent No. 3,995,194, granted to Zenith research and development engineers Allen Blacker and James W. Schwartz.

The EFL gun extends the focusing action over a longer distance by using four electron lens elements, instead of only two as in most electron guns. This concentrates the beam to produce a spot size as much as 60 percent smaller than in conventional gun systems. The new in-line gun is housed in the narrow neck of the company's 19-inch 100-degree picture tube. **R-E**

HEATHKIT GR - 2001

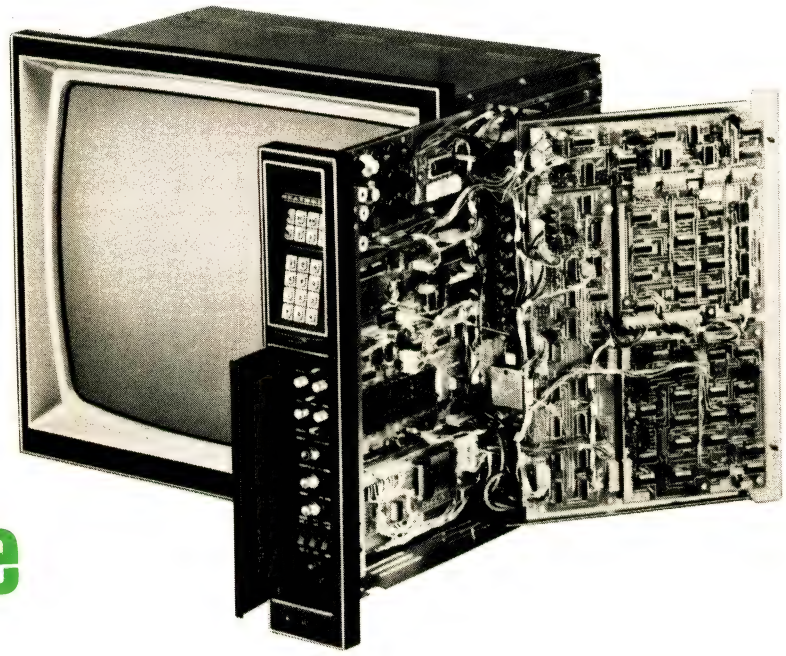

Programmable Color TV

It's the first set on the market with programmable automatic channel selection. Enter a series of time/channel combinations on the keyboard, and the set automatically switches to the channel at the programmed time

ART KLEIMAN
MANAGING EDITOR

BACK IN 1974, THE HEATH COMPANY SHOOK the foundations of the TV industry with the introduction of the GR-2000 color TV receiver. That set contained unique features found in no other set at the time, including silent all-electronic varactor tuning, touch-to-tune channel selection, touch volume control, on-screen digital channel readout, on-screen digital clock readout and a fixed L-C IF bandpass filter. (See the February 1974 issue of **Radio-Electronics** for a full report on the GR-2000.)

Heath's latest introduction—the GR-2001—contains features that set it apart from the rest of today's industry. This is the first TV set to feature programmable automatic channel selection and automatic antenna rotator control. With the programmable channel selection feature (offered as an optional accessory, the GD-1185), the user programs a time/channel combination and the TV set automatically switches to that channel at the programmed time. Two blocks of 16 (for a total of 32) time/channel combinations can be programmed at any one time. The automatic antenna rotator control, also offered as an option, automatically orients the antenna to a programmed direction when a channel is selected. It replaces the control portion of a standard antenna rotator system.

The GR-2001 includes all the features that made the GR-2000 unique. In fact, the two receivers are basically the same. One difference that is immediately apparent is the method of channel selection. On the GR-2000, two pushbuttons scan the channels up and down until the desired channel is reached. The new GR-2001 has a 3 × 4 calculator-type keyboard containing the numerals 0–9. Channel selection is accomplished by entering two digits on the keyboard. The remaining two keys function the same as on the GR-2000—they scan the channels.

As far as the chassis is concerned, it remains basically the same as the GR-2000. Some modifications have been made for improved performance. Heath redesigned the audio circuitry for better sound and included phase-locked-loop circuitry to eliminate the vertical and horizontal hold controls.

The programmable automatic channel selection feature really caught our attention. This one feature sets this set aside from all others on the market. The circuitry for this optional accessory is complex, containing 60 IC's mounted on four printed-circuit boards, not counting the on-screen digital clock option that must be included for this accessory to function. Since the feature is unique, let's take a look at how the channels are programmed.

Channel programming

In addition to the 3 × 4 keyboard used for channel selection, there are 8 pushbuttons and a rocker switch used for operating the programmer. Three of these pushbuttons are used for mode selection and the other five are used for entering data into the programmer.

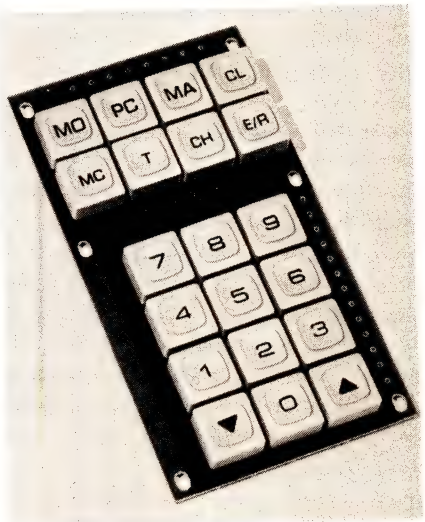

FIG. 1—NUMERICAL KEYBOARD is used for channel selection. The eight keys located above the numerical keyboard are used to control the automatic channel selection feature. Channels can also be scanned using the two keys with the arrowhead designations.

Figure 1 shows the layout of the keyboard and eight pushbuttons. The rocker switch selects between two memory banks and is located behind a door on the front panel.

Programming the time/channel data is a matter of manipulating the mode,

data entry and channel selection keys. First, the programmer must be switched to the memory-access mode by depressing the MA key. A front-panel MA indicator light verifies this. To program the time, the T key is depressed. The on-screen display now reads "00:00:" and the numerical keys on the keyboard are used for entering the desired time. As the time is entered, the on-screen display simultaneously shows it. If a mistake is made in entering the time, it can be corrected by simply re-entering the correct time. The channel information is entered next by depressing the CH key and entering the channel on the numerical keys. When the CH key is depressed, the on-screen display converts to six digits for simultaneous display of the programmed time and channel. If the time/channel combination entered is correct, it is transferred to memory by depressing the E/R key. The on-screen display is blanked except for the two colons to verify storage of the data in memory. Depressing the E/R key a second time displays the stored time/channel combination.

To program another time/channel combination, the MC key is depressed. This steps the memory through the 16 locations. The on-screen display shows the data in each location as the memory is stepped. When an appropriate memory location is found (one not containing a desired time/channel combination), a new time/channel combination can be programmed as previously described.

The data in a memory location can be changed by accessing that location using the MC key and entering a new time/channel combination. If no new data is to be entered, that memory location can be cleared by depressing the CL key. The on-screen display is blanked and the TV set will not respond to this memory location.

The memory is divided into two sections, each has a capacity of storing 16 time/channel combinations. A front-panel rocker switch is used to select between the two memory banks. When all the desired time/channel combinations have been programmed, the PC mode key is depressed. This turns control of the TV set over to the programmer and channel changes are made according to the programmed data. A front-panel PC indicator light verifies that the TV set is under the control of the programmer.

It is not necessary to program the time/channel combinations in sequential order. When the PC mode key is depressed, a memory-access cycle is initiated. All 16 memory locations are scanned and a channel change corresponding to the programmed time that is previous to and closest to the actual time is made. The memory is again accessed for the channel corresponding to the next latest time. When the actual time equals the programmed time, the channel change occurs.

The TV set can be returned to manual operation by depressing the MO mode key. A front-panel indicator light verifies that the TV is in the manual mode. The channels can now be selected by using the numerical keys or the up- and down-scan keys. The on-screen display shows the selected channel and time. The TV set can also be returned to manual operation automatically by the programmer. This is accomplished by

TABLE I—PROGRAMMING SEQUENCE for automatic channel selection feature.

PRESS KEY	ON-SCREEN DISPLAY	REMARKS
MA	Shows last instruction executed.	MA lamp lights.
MC	Changes as memory is cycled.	Will continue to cycle memory until a location is reached which is empty or which contains an instruction that is no longer needed.
CL	All six digits blank.	This operation is optional.
T	00:00:	Time shift register is now cleared.
7	00:07:	
0	00:70:	
0	07:00:	This time is now in the time shift register.
CH	07:00:00	Channel shift register is now cleared.
1	07:00:01	
6	07:00:16	Channel 16 is now in the channel shift register.
E/R	: :	Instruction is entered into memory.
E/R	07:00:16	Instruction is read out of the memory. This operation is optional.
MC	Changes as memory is cycled.	Cycles memory until a suitable location is found.
CL	: :	This operation is optional.
T	00:00:	
8	00:08:	
1	00:81:	
4	08:14:	
CH	08:14:00	
9	08:14:09	
9	08:14:99	
E/R	: :	
E/R	08:14:99	
MC	Changes as memory is cycled.	
CL	: :	This operation is optional.
CH	: :00	The channel may be entered before the time, if desired.
1	: :01	
1	: :11	
T	00:00:11	
1	00:01:11	
2	00:12:11	
3	01:23:11	
0	12:30:11	
E/R	: :	
E/R	12:30:11	This operation is optional.
PC	Shows actual time from Clock Accessory	Channel changes are made according to stored instructions. PC lamp lights.

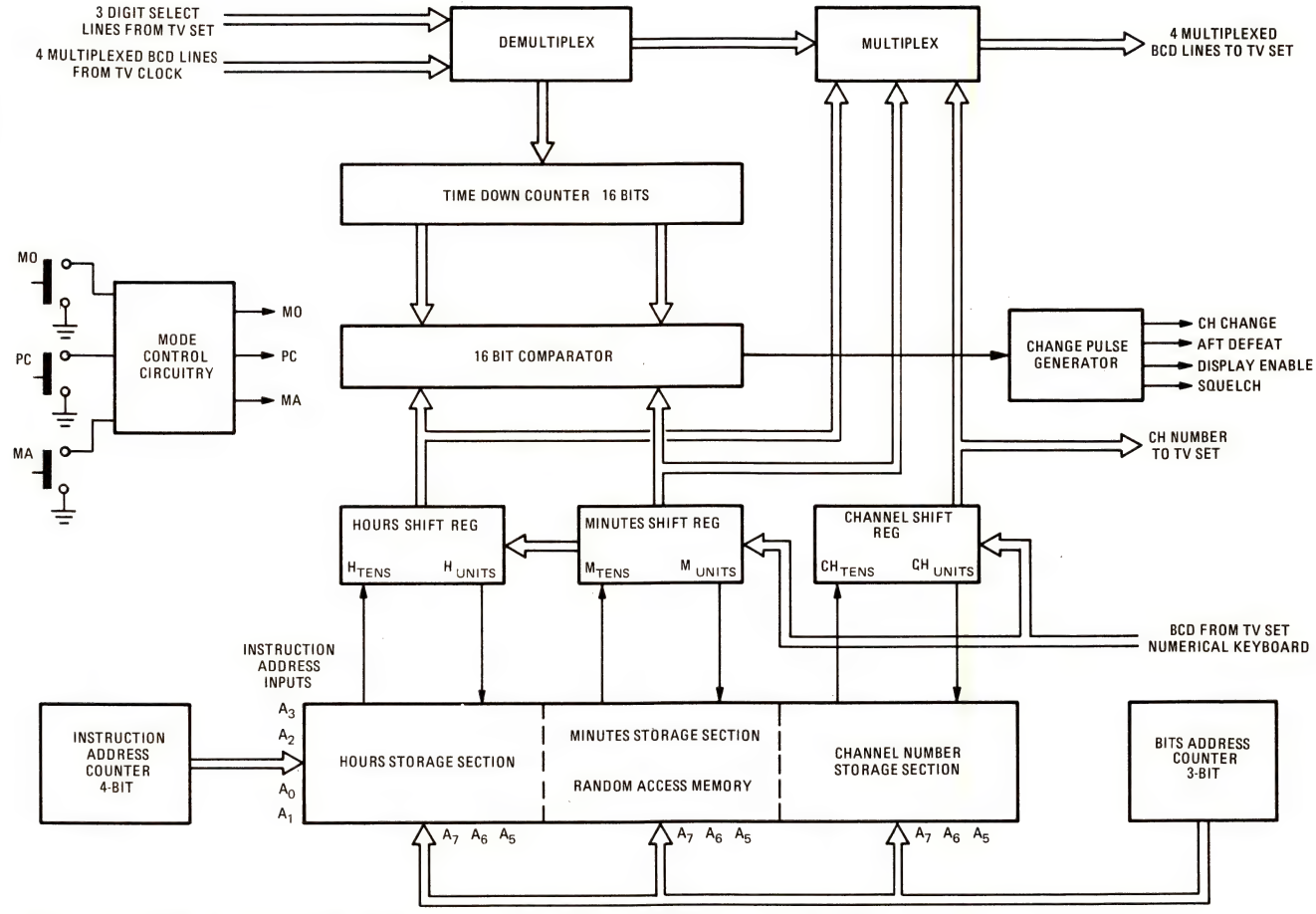

FIG. 2—PROGRAMMER changes channels automatically in accordance with programmed time/channel combination stored in random access memory.

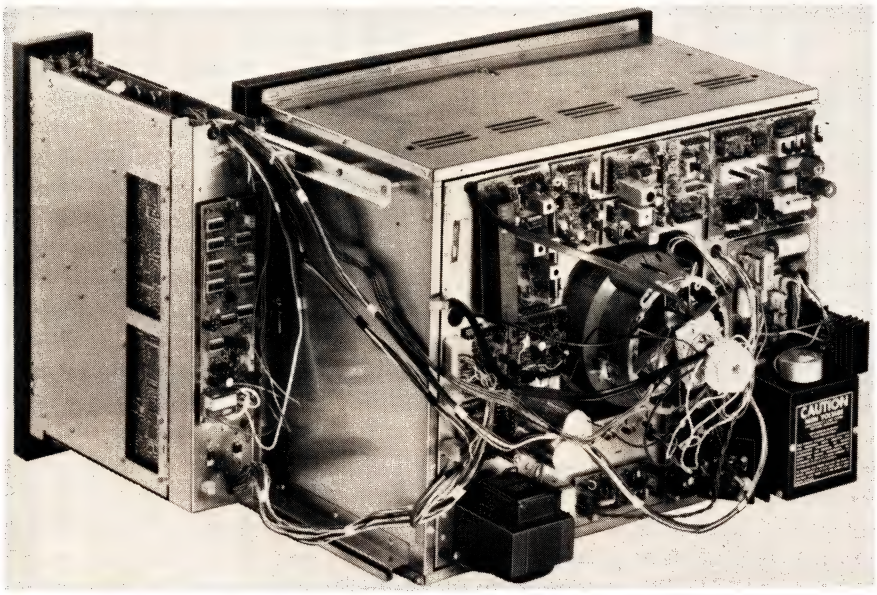

HEATHKIT MODEL GR-2001 color TV set.

programming in the desired time and the code "99" as the channel. The TV set will return to manual operation at the programmed time and remain in the manual mode until a programmed channel change occurs. Table 1 lists a typical programming sequence.

How it works

Figure 2 shows a block diagram of the programmer. To program a time/channel combination, the programmer is set to the memory access mode by depressing the MA key. The programmed time in the form of BCD data from the numerical keyboard is temporarily stored in the hours and minutes shift-registers after the T key is depressed. Channel information is stored in the channel shift-register after the CH key is depressed. The outputs of the shift registers are connected to a multiplexer circuit for on-screen display of the programmed time and channel.

If the programmed time/channel combination is correct, it is stored in the random-access memory by depressing the E/R key. The memory location is determined by the front-panel selector switch and the 4-bit number in the instruction address counter. Any memory location can be selected by depressing the MC key, which increments the instruction address counter. Depressing the E/R key a second time retrieves the contents of the memory location and stores it in the shift registers. The data is now displayed on the TV screen and can either be updated by programming a new time/channel combination or cleared by depressing the CL key. The CL key clears both the shift registers and the memory location.

Automatic channel selection takes place when the PC mode switch is depressed. The BCD data representing the actual time is demultiplexed and each time a change in the minute digit is detected, the data is stored in the time-down counter. Also, the time/channel combination in the first memory location is transferred to the respective shift registers. The actual time and the programmed time are compared by the 16-bit comparator. If the actual time and programmed time are equal, the

continued on page 93

The better the training the better you'l

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath GR-2001 computerized color TV (25" diagonal)** with varactor diode tuning and digital read-out channel selection; (optional programming capability and digital clock avail.).

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

ınd the equipment
ɔe equipped.

COMPARE OUR KITS AND LESSONS. COMPARE OUR TUITION.

tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING
Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-0-57
4000 South Figueroa St., Los Angeles, Calif. 90037
Please send FREE Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

- ☐ Color TV Servicing
- ☐ B & W TV and Radio Servicing
- ☐ Electronic Communications
- ☐ FCC License Course
- ☐ Electronics Technology
- ☐ Computer Electronics
- ☐ Basic Electronics
- ☐ Audio Electronics Servicing

NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service _____

- ☐ Check if interested in G.I. Bill information.
- ☐ Check if interested ONLY in classroom training in Los Angeles.

Radio-Electronics Tests Nikko TRM-750 Integrated Amplifier

1

CIRCLE 99 ON FREE INFORMATION CARD

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

THE NIKKO *MODEL TRM-750* INTEGRATED AMplifier, shown in Fig. 1, is a medium powered combination preamplifier, control center and power amplifier that could well serve as the central electronic component in a moderately priced high-fidelity system. Its front panel simplicity belies the fact that the unit has a great deal of control flexibility. Starting at the upper left, a rotary switch selects main or remote speakers and includes an OFF position for headphone-only listening. A series of four pushbuttons follow, including HIGH- and LOW-cut filter switches, a MONO/STEREO switch and an audio MUTING switch that reduces output levels by a fixed 20 dB for listening interruptions such as phone or doorbell answering without having to alter preferred settings of the huge step-type VOLUME control just to the right of it. Notations around the perimeter of this knob indicate dB's of attenuation, relative to the maximum clockwise setting.

A pair of three-position lever-type switches, located to the right of the volume control, handle selection of the two available tape monitor circuits and tape dubbing from either of two connected tape decks to the other. This dual-switch arrangement for tape monitoring and tape dubbing is by far the easiest for a user to understand. In our opinion, this arrangement is superior to those multi-position rotary switches that are sometimes used for these functions and can be quite confusing. A program SELECTOR switch with settings for two phono and auxiliary inputs plus a tuner input is located at the upper right of the panel. Controls along the panel's lower section include a toggle switch for power ON/OFF, BASS and TREBLE rotary controls, a LOUDNESS switch, rotary BALANCE control and a MIXING-LEVEL control that adds selectable amounts of microphone signal to other program sources. The microphone jack associated with this control is located at the lower-right corner of the panel, while the usual PHONE jack is over at the left, near the POWER switch.

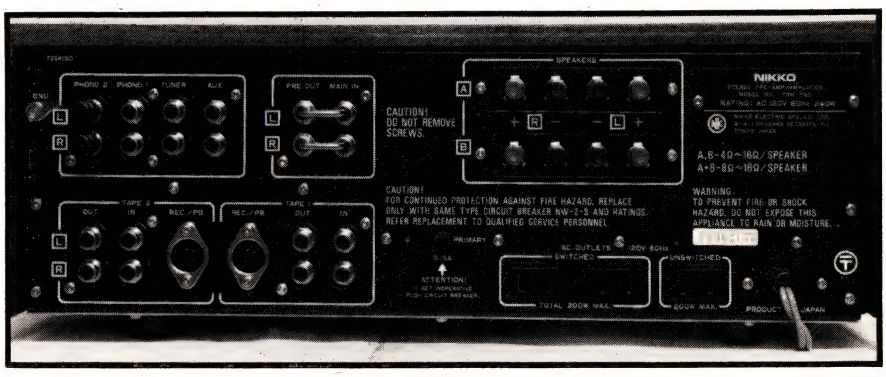

2

The rear panel of the *TRM-750* (see Fig. 2) contains the appropriate input jacks for PHONO, TUNER, AUX and TAPE, corresponding sets of tape-out jacks (as well as paralleled DIN sockets), a ground (GND) terminal, three convenience AC outlets (two switched, one unswitched) and conventional knurl-screw terminals for speaker wire connections. In addition, there are preamplifier-output and main-amplifier input jacks that are interconnected by stiff-wire jumpers which can be removed when separate use of the two major portions of the unit is desired. Instead of a fuseholder, there is a tiny circuit-breaker reset button to restore amplifier operation in the event of an overload condition.

Figure 3 shows the variety of components (including two turntable systems) that may be interconnected with the *TRM-750* amplifier. While no schematic diagram of this amplifier was supplied with the owner's manual, some idea of layout and internal construction may be obtained by referring to the photo in Fig. 4. Since readers may mistakenly conclude that the speaker outputs are capacitively coupled (since only one large filter-capacitor can is visible in the photo), we should clarify that the single capacitor-can actually houses two separate capacitors, each of which filters one polarity of the dual-polarity output supply required for direct speaker coupling at the output stages.

Most of the circuit components are mounted on a single major circuit board that is screened with component designations for ease of identification and servicing. What appears to be an ample heat-sink structure is vertically mounted and separated from the main circuit board. Wiring is carefully harnessed and dressed, and low-level preamplifier circuitry is as far removed from the power-supply transformer area as is physically possible within the dimensional limitations of the amplifier.

Laboratory measurements

The amplifier was able to produce 60 watts of continuous sinewave power per channel, driving 8-ohm loads with a 1 kHz test signal. Considering the fact that the FTC rating for this product is only 45 watts-per-channel, that constitutes a very considerable extra margin of power. Even at the frequency extremes of 20 Hz and 20 kHz, power output was 55 watts for the rated harmonic distortion figure of 0.15%. These and other measured results are summarized in Table I. Actual frequency limits at which rated power could be attained at rated distortion were 11 Hz and 47 kHz—far beyond the 20 Hz to 20 kHz power bandwidth specified by Nikko in their owner's manual.

RIAA phono equalization was within 1 dB of the specified curve from 30 Hz to 15 kHz. Maximum voltage to the phono input before overload distortion was observed measured an adequate 150 mV, while the signal-to-

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Rated Power Output: 45-watts per channel into 8-ohm loads. **Power Bandwidth:** 20 Hz to 20 kHz. **Rated Harmonic Distortion:** 0.15%; less than 0.1% at 1-watt output level. **Rated IM Distortion:** Less than 0.2%; less than 0.1% at 1-watt output level. **Damping Factor:** 50 at 1 kHz into 8-ohm load. **Input Sensitivity:** Phono 1 & 2, 2.5 mV; Aux, Tuner and Tape, 180 mV; Mike, 2.5 mV; Main Amplifier, 1.3 volts. **S/N Ratio:** Phono, 72 dB (IHF A-weighted); Aux, Tuner and Tape, 95 dB (IHF A-weighted). **Bass Control Range:** ±12 dB at 70 Hz. **Treble Control Range:** ±10 dB at 10 kHz. **Filter Response:** low, −8 dB at 70 Hz; high, −7 dB at 10 kHz. **Audio Muting:** −20 dB. **Maximum Power Consumption:** 240 watts. **Dimensions:** 15-3/4 W × 5-5/8 H × 12-3/16-inches D. **Net Weight:** 23.1 lbs. **Suggested Retail Price:** $249.95.

4

noise ratio was 71 dB referenced to an input sensitivity of 2.5 mV. Using an A-weighting filter for the signal-to-noise measurement, we obtained a better reading of 77 dB.

Tone-control range of the BASS and TREBLE controls is shown in the scope photo of Fig. 5, in which a frequency plot was made from 20 Hz to 20 kHz for flat and extreme settings (boost and cut) of the two tone controls.

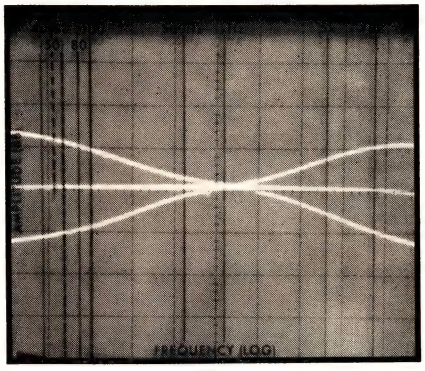

5

High- and low-cut filters are of the 6 dB-per-octave type and, while they provide very little noise reduction at the frequency extremes, their −3 dB points are sufficiently removed from critical center frequencies so that their use does not materially affect much of the musical program content (see Fig. 6).

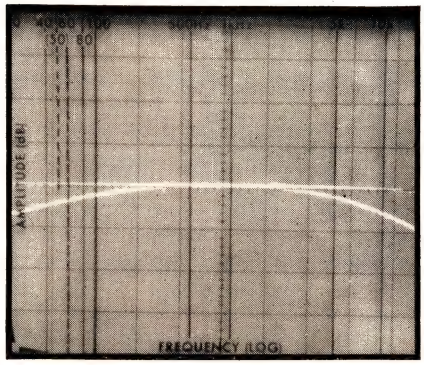

6

In measuring the action of the LOUDNESS control (see Fig. 7), we were impressed with the fact that the dB notations around the VOLUME control were quite accurate, so that we had only to set the control for 0 dB, −10 dB, −20 dB, etc., to obtain the traces shown in Fig. 7, which are 10 dB apart. Significant bass- and treble-loudness compensation does not begin until the VOLUME control is some 20-dB below its maximum setting, and then remains fairly constant at all lower volume

TABLE I

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Nikko** Model: **TRM-750**

AMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	60	**Excellent**
RMS power/channel, 8-ohms, 20 Hz (watts)	55	**Excellent**
RMS power/channel, 8-ohms, 20 kHz (watts)	56	**Excellent**
Frequency limits for rated output (Hz-kHz)	11-47	**Superb**
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.022	**Excellent**
Intermodulation distortion, rated output (%)	0.055	**Excellent**
Harmonic distortion at 1-watt output, 1 kHz (%)	0.043	**Very good**
Intermodulation distortion at 1-watt output (%)	0.028	**Excellent**
DAMPING FACTOR, AT 8 OHMS	53	**Excellent**
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA ± ___dB)	1:0	**Good**
Maximum input before overload (mV)	150.0	**Very good**
Hum/noise referred to full output (dB) (at rated input sensitivity)	71	**Very good**
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ± ___dB)	7–40, 3	**Excellent**
Hum/noise referred to full output (dB)	80	**Very good**
Residual hum/noise (min. volume) (dB)	90	**Very good**
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 5	**Very good**
Action of low frequency filter(s)	See Fig. 6	**Poor**
Action of high frequency filter(s)	See Fig. 6	**Poor**
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.5/2.5	
Input sensitivity, auxiliary input(s) (mV)	200	
Input sensitivity, tape input(s) (mV)	200	
Output level, tape output(s) (mV)	200	
Output level, headphone jack(s) (V or mW)	0.467/8 ohms	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		**Excellent**
Adequacy of input facilities		**Excellent**
Arrangement of controls (panel layout)		**Very good**
Action of controls and switches		**Excellent**
Design and construction		**Very good**
Ease of servicing		**Very good**
OVERALL AMPLIFIER PERFORMANCE RATING		**Excellent**

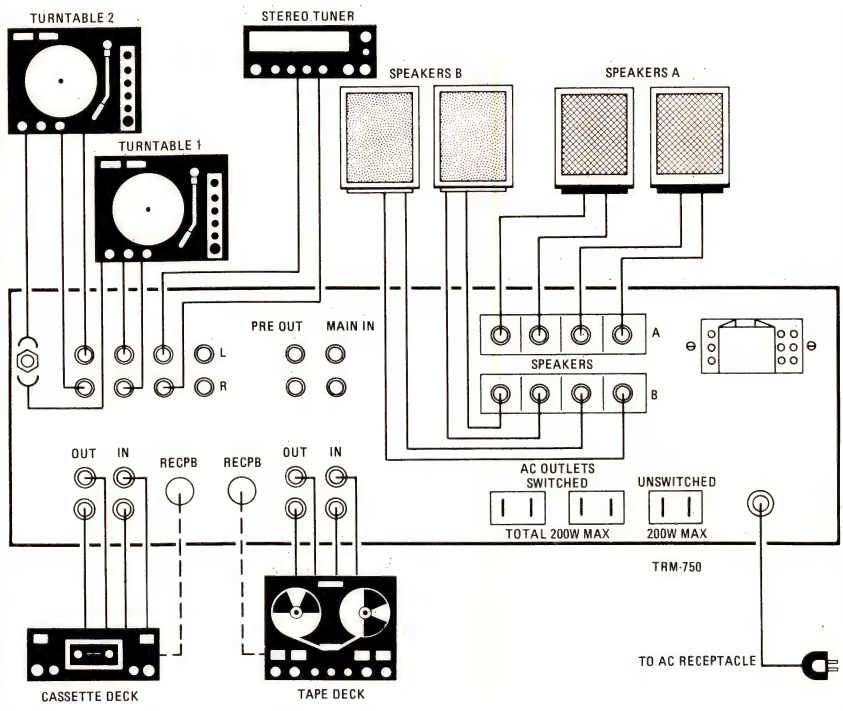

3

TABLE II

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Nikko** Model: **TRM-750**

OVERALL PRODUCT ANALYSIS

Retail price	**$249.95**
Price category	**Low**
Price/performance ratio	**Excellent**
Styling and appearance	**Very good**
Sound quality	**Excellent**
Mechanical performance	**Very Good**

Comments: The Nikko *model TRM-750* belongs to that special group of separate components which disproves the theory that it is necessary to expend an enormous amount of cash to put together a system consisting of a separate tuner and amplifier. If you were to add a tuner in the $150.00 to $200.00 price range to this amplifier, you would come up with a system having a suggested retail price of between $400.00 and $450.00—not very much more than you might expect to pay for an all-in-one receiver in the same power category. Nor are you likely to find such a receiver with all the control features and flexibility (microphone input-mixing, tape dubbing and monitoring in either direction and dual phono inputs), since receiver manufacturers tend to down-grade control features as power ratings are lowered. We were impressed with the quality of construction of this unit, and with its very conservatively rated specifications, all of which were met or exceeded. Ability to separate the preamplifier and main-amplifier sections makes this an ideal unit for driving speakers in a multi-amplifier (electronic crossover) system. In such systems, the included main-amplifier section would be perfect for driving midrange or tweeter elements, where a larger power amplifier is used for woofer powering. Used as the sole amplifier in a stereo system, driving medium efficiency speakers, the *TRM-750* provided clean tight sound with no trace of clipping distortion or overload even at 110-dB sound-pressure levels in our 20 × 14-ft listening room. On the test bench, after having been subjected to high-powered tests and FTC preconditioning tests, thermal conditions were stable and there was no overheating of the output circuitry or power transformer. All in all, a neatly executed amplifier design.

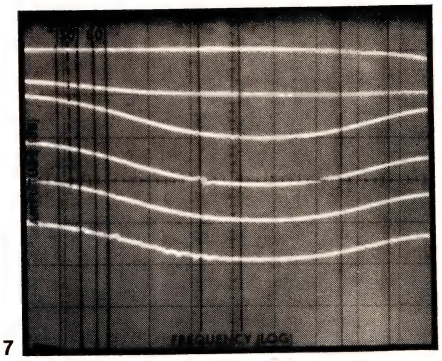

7

settings. Additional flexibility is provided by the −20 dB MUTING switch. If a user finds that the program-source signals are so great that too much loudness compensation is present, he or she can turn the MUTING switch ON. This will require a higher setting of the master VOLUME control, but less loudness compensation will result. It's somewhat like having two input sensitivities for all the program sources connected to the amplifier—each 20-dB apart.

Summary and listening tests

Comments regarding the overall performance of the Nikko *model TRM-750* will be found in Table II along with our brief overall product analysis and evaluation. In our view, the Nikko *model TRM-750* offers good value for its price and includes control features equal to those found on many higher-powered integrated amplifiers selling for considerably more money. Especially for the audiophile who has no desire to use FM as a program source (at least initially), the *TRM-750* offers a good alternative to an integrated receiver of similar power rating at considerably less cost. **R-E**

Heath AP-1615 Preamplifier

WHILE MORE AND MORE MANUFACTURERS seem intent upon designing and manufacturing so-called "high end" separate components at escalating prices, the Heath Company of Benton Harbor, Michigan, goes about its merry way introducing product after product that offer amazingly good performance quality at a price that amazes even the experts. The latest of these to pass through our test laboratory is the simple looking, straightforward preamplifier shown in Fig. 1. At first glance, you might guess that some knobs and switches are missing. The fact is that the *model AP-1615*, like many other new control centers, is devoid of frills and even lacks bass and treble controls. A growing group of audio buffs believes that in a properly matched component system there should be no need for bass and treble controls at all and, as Heath suggests in their advertising copy, if you do require tonal compensation you can do a much better job of tonal tailoring with their matching *model AD-1305* five-band, two-channel graphic equalizer (tested for **Radio-Electronics** in the December 1976 issue) or with any other of the many equalizers which have been appearing on the market lately.

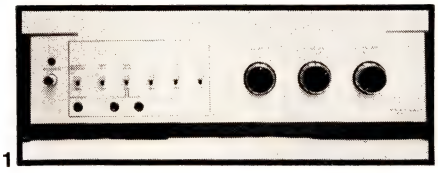
1

CIRCLE 50 ON FREE INFORMATION CARD

MANUFACTURER'S PUBLISHED SPECIFICATIONS:
Rated Output: 1.5 V. **Input Sensitivity:** Phono, 2.0 mV; High Level, 180 mV. **Input Overload:** Phono, 100 mV; High Level, over 10 volts. **Hum and Noise:** Phono, 65 dB; High Level, 85 dB. **Frequency Response:** Phono (RIAA), ±0.5 dB; High Level, ±0.2 dB, 20 Hz to 20 kHz. **Harmonic and IM Distortion:** Less than 0.05% from 20 Hz to 20 kHz. **Channel Separation:** 50 dB at 1 kHz. **Filter Cutoff Points:** Low, –3 dB at 15 Hz; High, –3 dB at 7 kHz, both 12 dB-per-octave. **Power Requirements:** 120/240 VAC, 50/60 Hz. **Dimensions:** 17½ W × 4-9/16 H × 8-⅛-inches D. **Shipping Weight:** 12 lbs. **Price:** Kit only, $129.95.

The major rotary controls seen at the right of the front panel of the *model AP-1615* are the BALANCE control, the SELECTOR switch (with provision for two sets of PHONO inputs, TUNER, AUX and TAPE inputs) and the master VOLUME control. A series of six two-position toggle switches at the left of the panel handle HIGH- and LOW-cut FILTERS, mono L+R reproduction, TAPE DUBBING (accompanied by front panel TAPE-OUT and TAPE-IN jacks), TAPE MONITORING and output cut-off or DEFEAT. A phone jack is included below the OUTPUT DEFEAT switch that permits headphone listening while input to the power amplifier and speakers is shut off. The POWER on-off pushbutton and the POWER indicator light are located at the extreme left of the panel.

The rear panel of this preamplifier (see Fig. 2) is equipped with two unswitched convenience AC receptacles, one switched receptacle, a line fuse, a chassis-ground terminal and the necessary input and output jacks associated with the selector and tape-monitoring positions on the front panel. Since only one set of tape-monitor jacks is

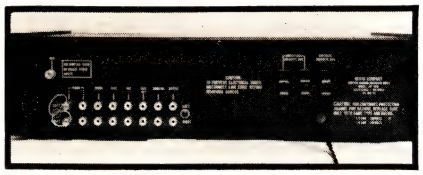

2

provided, if a graphic equalizer is used, it must be connected between the main outputs of the preamplifier and the inputs to an associated power amplifier.

Figure 3 shows the internal layout of the *AP-1516.* All power-supply parts, including the power transformer, are well shielded in a separate housing seen

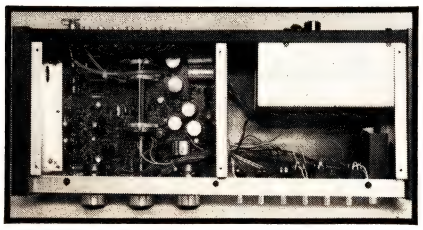

3

at the upper right corner of the chassis. Virtually all other electrical components are mounted on a large printed-circuit board that occupies the entire right section of the chassis. The two rotary potentiometers associated with the BALANCE and master VOLUME controls are mounted directly to the PC board while the SELECTOR switch has its wafers positioned so that they are closest to the circuit points on the main PC board with which they are involved electrically. Visible just behind the BALANCE control is a relay unit for turn-on delay of the audio signals after the POWER switch is depressed to prevent thumps from reaching (and possibly damaging) loudspeakers.

We were supplied with a wired unit for test purposes, but the *model AP-1615* is available only in kit form to the general public. While our sample unit was not accompanied by Heath's construction and owner's manual, we can attest to the fact that layout of the unit makes assembly and wiring extremely simple. Components used are of the highest grade and a minimum of point-to-point wiring is involved in the construction of this product. We would estimate that an experienced kit-builder might be able to complete the construction of this control center in two evenings or so, while the novice might require a third session.

Laboratory measurements

Table I summarizes measured results obtained with the *model AP-1615.* Although phono overload capability was better than claimed, with readings of 120 mV (as against 100 mV claimed), it was not considered to be outstanding compared with some of the overload figures we have been obtaining lately on the current crop of preamplifiers and amplifiers. Still, it is unlikely that

continued on page 95

TABLE I

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Heath** Model: **AP-1615**

PREAMPLIFIER PERFORMANCE MEASUREMENTS

RATED OUTPUT LEVEL REFERENCE: 1.5 volts	**R-E Measurements**	**R-E Evaluation**
DISTORTION MEASUREMENTS		
Rated output, 20 Hz (%)	0.008	**Excellent**
Rated output, 1 kHz (%)	0.006	**Excellent**
Rated output, 20 kHz (%)	0.015	**Very good**
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA ± _ dB)	0.2	**Excellent**
Maximum input before overload (mV)	120	**Good**
Hum/noise referred to full output (dB) (at rated input sensitivity)	70	**Very good**
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ± _ dB)	20-20, 0.2	**Excellent**
Hum/noise referred to full output (dB)	85	**Very good**
Residual hum/noise (minimum volume) (dB)	87	**Good**
TONAL COMPENSATION MEASUREMENTS		
Action of low frequency filter(s)	See Fig. 5	**Excellent**
Action of high frequency filter(s)	See Fig. 5	**Very good**
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1 (mV)	2.0	
Input sensitivity, auxiliary input(s) (mV)	185	
Input sensitivity, tape input(s) (mV)	185	
Output level, tape output(s) (mV)	185	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		**Fair**
Adequacy of input facilities		**Good**
Arrangement of controls (panel layout)		**Very Good**
Action of controls and switches		**Very good**
Design and construction		**Excellent**
Ease of servicing		**Excellent**
OVERALL PREAMPLIFIER PERFORMANCE RATING		**Very good**

TABLE II

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Heath** Model: **AP-1615**

OVERALL PRODUCT ANALYSIS

Retail price	**$129.95**
Price category	**Low**
Price/performance ratio	**Very Good**
Styling and appearance	**Excellent**
Sound quality	**Excellent**
Mechanical performance	**Very good**

Comments: Whenever a new trend becomes apparent in the world of audio, the Heath Company seems able to come up with a product to further that trend along almost as quickly as anyone else, and that's no small feat when one considers that besides coming up with a new design, the company has to translate that design into a unit that can be successfully built even by a novice kit-builder. There have been several examples of "straight-line" preamplifier-control units recently, in which all frills are eliminated and emphasis is placed upon pure performance and ultra-low distortion. The model AP-1615 preamplifeir is just such a unit and, as such, it will appeal to the purists among audiophiles who would rather not have built-in tone controls and a profusion of other knobs or controls. Compared with other examples of such preamplifiers, the pricing of the model AP-1615 is extremely attractive, even when one considers that it is supplied only in kit form. As has been our experience with Heath products in the past, all specifications were either met or exceeded by some margin. As for the sound reproduced by the model AP-1615, we could detect no audible distortion under all listening conditions, nor was there any coloration caused by abberations in the frequency response, which is extremely wideband. As usual, construction is straightforward and should pose no problems for kit-builders. The front-panel dubbing jacks will be appreciated by tape recording enthusiasts who are in the habit of copying tapes from a friend's machine. Such extras as are provided are not apparent from the front panel but manifest themselves in the actual performance of the preamplifier unit itself (e.g., the delayed turn on which prevents "pops" and "thumps" from reaching your speakers before supplies have stabilized). The Heath model AP-1615 certainly provides the means whereby serious audio enthusiasts can create a true system of separates with barely a dent in their pocketbooks.

BUILD

Amplifier For Hands-Off Telephone

Simple add-on accessory allows you to converse
Acoustic coupling eliminates direct

JULES GILDER

NO DOUBT YOU'VE HAD OCCASIONS WHEN YOU PLACED A CALL to, or received a call from, someone you haven't spoken to for a long time, and other members of the family want to speak also. Or you were busy doing something and got annoyed because you had to drop everything and talk to someone on the phone for half an hour.

A speaker phone telephone amplifier can be useful in both these situations. No longer need members of your family argue to talk first on the phone. Now everyone can sit around the telephone and talk together with whomever is on the other end. The speaker phone will also allow you to carry on a conversation while you're still busy moving furniture or painting the walls.

And like most of the other projects in this series of articles, the speaker phone requires no direct electrical connection to the telephone line. All coupling is made either by acoustic or magnetic means.

How it works

The heart of the speaker phone is a three-transistor amplifier that takes the millivolt level signals produced by the telephone pickup coil and amplifies them to room-filling volume. The schematic is shown in Fig. 1. The power supply is shown in Fig. 2.

Just about any telephone pickup coil can be used for the speaker phone, but one of the newer ring-shaped devices is recommended because this particular coil gives a stronger signal. The coil is designed so that it will fit snugly over the receiver portion of the telephone handset, where it will pick up the audio signals to be amplified by induction.

The induced signals are applied to the volume control and then to the voltage amplifier made up of transistors Q1 and Q2. The amplified signal is applied to Q3 where the current, and hence the total power level of the signal, is increased. Power transistor Q3 is capable of handling large currents. The need for an output transformer is eliminated by Q3 because its large current-handling capability means that it can interface directly with a speaker.

So far we have talked about picking up a signal and amplifying it so that everyone in the room can hear it. That constitutes only half of the speaker phone. The other half of the speaker phone requires that people be able to talk into the phone from a remote location. This can be done in two ways. The first is by using another amplifier to pick up the sound generated in a room via a microphone. The second is to acoustically design the speaker phone so that sound focused in the direction of the device will be concentrated and fed into the mouthpiece of the telephone.

The first approach is most desirable but leads to many problems, the biggest of which is feedback oscillation. This of course could be eliminated by using voice-controlled switches, but that would mean conversations would have to be carried on in an artificial manner where one person would have to wait until the other stopped talking before he could be heard.

Simultaneous conversation with an amplified input is possible, but it requires complex circuit design and would considerably raise the cost and difficulty of construction.

To keep things simple, we'll do what most of the manufacturers of speaker phones do, and design the unit so that sound focused in the direction of the speaker phone is concentrated and directed towards the microphone of the telephone. This is not as difficult as it may sound. It is simple and involves constructing the enclosure so sound is deflected upwards.

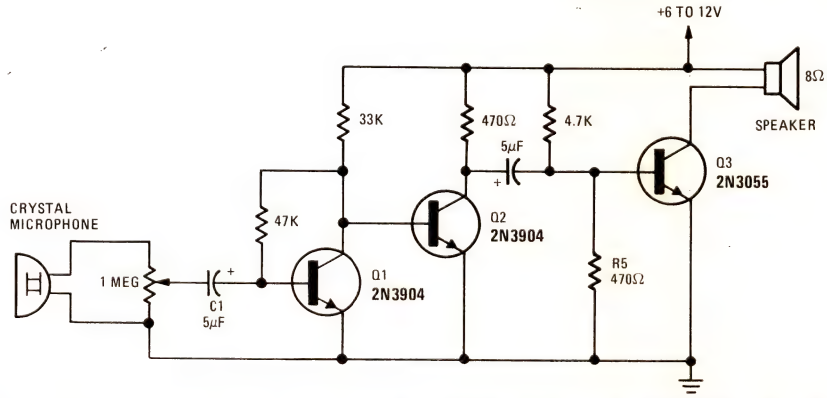

FIG. 1—THREE-STAGE AMPLIFIER raises the level of signals picked up by an induction coil—not a microphone, the mike symbol is an error—to room-filling level.

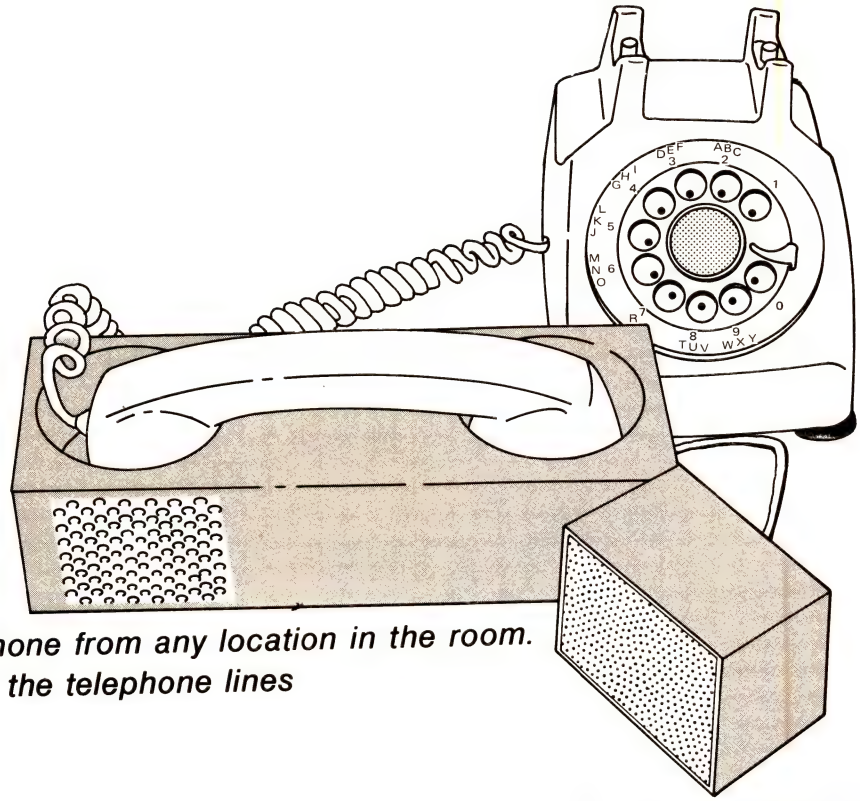

on your telephone from any location in the room. connection to the telephone lines

Construction

The enclosure for the speaker phone is very important, for it is more than a case to hold the electronic circuit. It is a functional part of the design of the device.

To start with, build a thin, plywood box 10 inches wide, 4 inches deep, and 2½ inches high. Cut two holes in the top 3¼ inches in diameter and made on center lines that are located 2 inches from each end.

These holes will be used to allow the handset to drop into the speaker phone and properly position it. With the box assembled and these two holes cut, mark one hole, either one, "microphone" and the other one "receiver." This can be done lightly in pencil and is only necessary to make instructions easier. On the front vertical wall of the box on the microphone side, draw a rectangle that measures 3¼″ × 2″ and place the rectangle so that it is ¼ inch from each of the three edges. Once marked, use a saber saw to cut out that rectangle.

This is the opening that will be used to direct sound into the microphone of the telephone. If you want, you can put a piece of grille cloth over the opening to improve its appearance, but make sure it is thin so that it will not severely attenuate the voice signals entering.

Next, 3½ inches from the inside of the microphone end of the box, place a barrier made from a piece of wood 4″ × 2½″. This will prevent sound entering the microphone opening from being dispersed throughout the box. To further concentrate the sound, take a thin piece of flexible plastic and cut it into a rectangle 3¼″ × 5″. This is the deflecting plate and should be inserted in the microphone compartment on a diagonal whose bottom is in the front of the box (where the rectangular opening is) and whose top is at the back of the box. The deflecting plate will need to be bent to be inserted. Bend it so the curvature of the plate is toward the bottom of the box.

Now, any sound entering the microphone compartment will be deflected upward toward the mouthpiece of the telephone. If done properly, you'll be surprised at just how effective this acoustic coupling can really be.

Proceed to the receiver end of the box. Here work is less critical. Mount a piece of thin plywood, cut into a 3¼-inch square, directly underneath the receiver hole so that when the receiver is placed in it, the surface of the wood is parallel to the receiver of the handset. The square can be held in position by fastening it to spacers, dowels, or wooden blocks. Next, mount the pickup coil on the top of the wooden square so that when the receiver is placed in the box, it will come into contact with the coil.

That's the hard part. The easy part is to fabricate the printed circuit—or use perfboard if you wish—and construct the three-transistor amplifier. Mount the volume control at a convenient spot on the front panel along with an on/off switch. Mount the circuit board, on spacers, at another convenient location. At a third convenient location mount a battery holder for the six penlight batteries.

The output of the amplifier should be fed to a miniature jack located on the side of the case. The speaker is in a little enclosure of its own and connected to the amplifier via a shielded cable and a miniature plug.

Installation and operation

To install the speaker phone, it is simply necessary to place the handset of the telephone into the device, making sure that the microphone and receiver portions are inserted into the proper holes. Turn the unit on. You should immediately hear the dial tone coming through the speaker. If you don't, check the volume control and the coupling between the induction coil and the receiver.

Phone a friend and talk to him using the speaker phone. Try standing at various distances and at various angles from the microphone opening. Ask him to tell you which positions are best. **R-E**

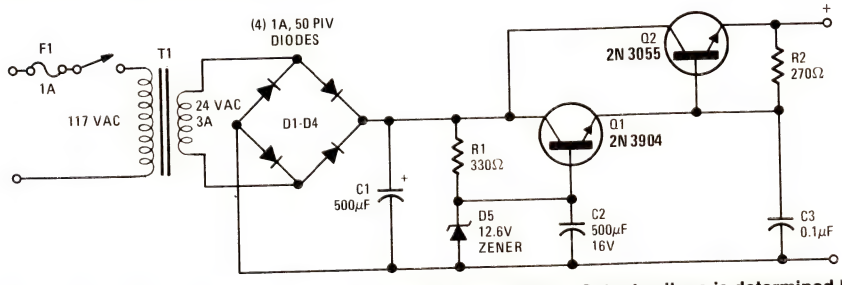

FIG. 2—OPTIONAL POWER SUPPLY FOR TELEPHONE AMPLIFIER. Output voltage is determined by Zener diode. Power is taken from 117 VAC line.

Be the "New Professional" in electronics

CREI trains you at home for one of the most important career levels in electronics—plus offers you special arrangements for engineering degrees

Most people think there are only two levels of careers in electronics: the technician level and that of the degree engineer.

There is, however, a third and very important level. It is that of the engineering technician or *practical* engineer. The growing importance of this career level has created what might well be called the "New Professional" in electronics.

If you look at the various levels of employment in electronics, you will understand why this "New Professional" is so important.

The average technician is a person who has had vocational training in electronics. He understands the basic principles of electronics so he can troubleshoot, repair and maintain equipment. He usually works under close supervision in performing his duties.

The engineer has college training in electronics. He usually supervises technician personnel and is responsible for planning and developing of electronic equipment and systems. Frequently, however, engineers are more heavily trained in the scientific principles of electronics and less in their practical application.

The engineering technician, by contrast, is a specialist in the practical application of electronics. His training usually consists of a two-year college program in electronic engineering technology. In many organizations, the engineering technician handles several of the responsibilities of the degree engineer. He often has the title of engineer.

CREI programs are designed to give you at home the same level and depth of training you receive in a two-year college program in electronic engineering technology. CREI programs are, in fact, more extensive than you will find in many colleges. And CREI gives you the opportunity to specialize in your choice of the major fields of electronics.

Unique Design Lab

CREI gives you both theory and practical experience in circuit design with its Electronic Design Laboratory Program. The professional equipment included in this program allows you to construct, test out and correct the circuits you design until you have an effective circuit.

This Lab Program helps you understand advanced electronics. It also gives you practical experience in many other important areas of electronics, as in pro-

totype construction, breadboarding, test and measurement procedures, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Only CREI offers the unique Lab Program. It is a complete college Lab and, we believe better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

Engineering Degree

CREI offers you special arrangements for earning credit for engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

Free Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Mail card or write describing qualifications to

CREI CAPITOL RADIO ENGINEERING INSTITUTE

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.

XR-2206 IC Function Generator Circuits

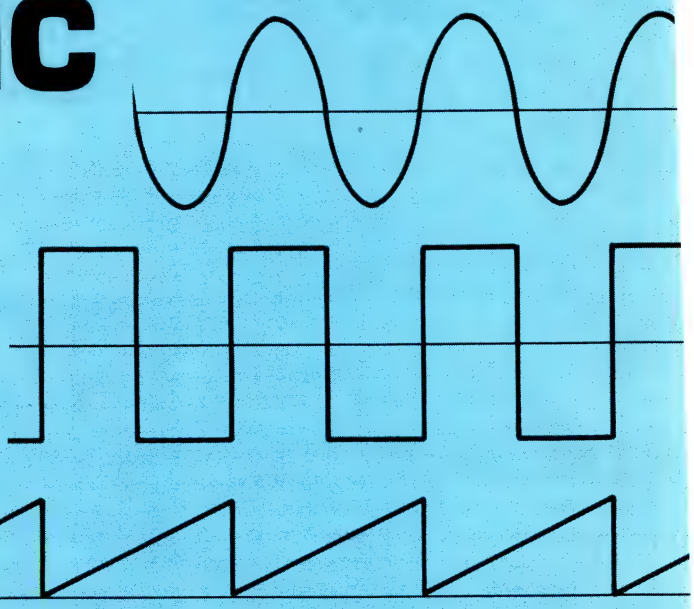

Part II. The XR-2206, IC is a versatile function-generator with many applications. Here are some of the more interesting circuits you can try.

R. M. MARSTON

LAST MONTH, WE LOOKED AT THE PERFORMance characteristics of the XR-2206 IC and its application in sine, triangle and squarewave applications.

This month, we'll look at pulse, ramp, AM and FM applications.

Function generators

The circuits shown in Figs. 2 thru 8 can be combined in a variety of ways to make different types of waveform generators. Figure 9, for example, shows how some of the circuits can be combined to make a simple fixed-amplitude function generator that provides sine, triangular and square waveforms. Here, the squarewave output is taken directly from pin 11 of the IC, and is produced simultaneously with the sine or triangular waveform at pin 2, which are selected by switch S1.

Alternatively, Fig. 10 shows how some of the circuits can be put together to help make a low-cost high-performance function generator that covers 1 Hz to 200 kHz in five switched ranges. Frequencies are selected by RANGE switch S1 and FREQUENCY control R1. Each range of S1 covers a full decade plus 100% overrange at its upper frequency. The circuit has THD adjustment of the sinewave, and produces a typical distortion of 0.5%.

The sine/triangular output of the IC is taken from pin 2, and all outputs are fed to a simple variable attenuator network via the Q1–Q2–Q3 buffer stage. The sine/triangular output can be centered on precisely zero volts using OFFSET control R8, and R3 sets the maximum sinewave output level, which should be set at 2 volts RMS.

The procedure for initially setting up the circuit when it is first built is as follows. First, set the attenuator controls to give maximum output, set the circuit to the sinewave mode at about 1 kHz, and then adjust R8 to give zero offset of the output signal. To do this, connect a 0–2.5 volt DC meter to the output of the circuit, and then adjust R8 for zero reading. Next, connect a 0–2.5 volt AC meter to the output of the circuit, and adjust R3 to give a sinewave output of approximately 2 volts RMS. Finally, adjust R4 and R6 to give minimum distortion of the sinewave, as previously described, and then recheck the DC offset and output amplitude. The setting up procedure is then complete and the circuit is ready for use.

Pulse and ramp waveforms

Figure 11 shows the practical connections for using the XR-2206 as a variable-slope ramp generator circuit. Here, the squarewave output (pin-11) is connected to the FSK input (pin 9) of the IC. The circuit action is such that, when pin 11 is high, timing capacitor C1 charges via R1 until a threshold voltage is reached, at which point pins 11 and 9 switch abruptly to the low state. When this happens, the timing capacitor recharges in the reverse direction via R2 until pins 11 and 9 go high again. The process then repeats. The circuit, therefore, automatically switches between timing resistors on alternate half cycles, and produces a linear ramp output waveform at pin 2. The risetime and falltime are independently controlled by R1 and R2. The operating frequency of the circuit is given as:

$$f = \frac{2}{C1\ (R1+R2)}$$

The circuit shown in Fig. 11 develops a variable duty-cycle squarewave at pin

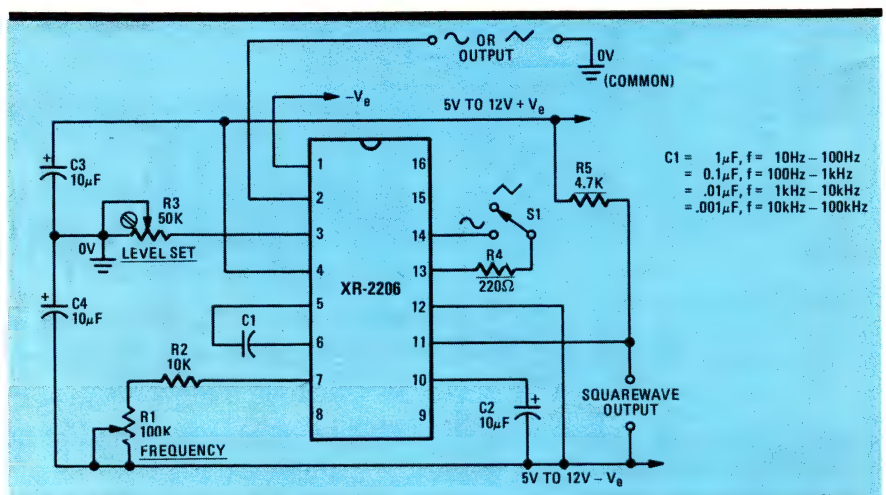

FIG. 9—SIMPLE FUNCTION GENERATOR provides sinusoidal, triangular and square waveforms.

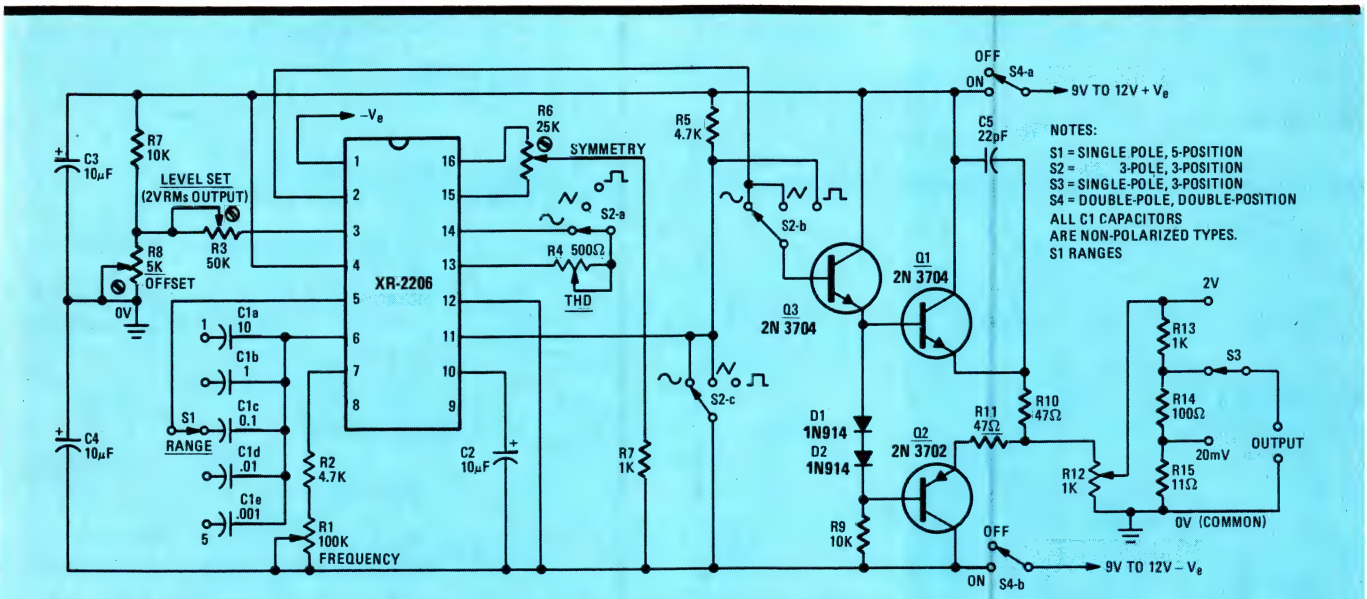

FIG. 10—HIGH-PERFORMANCE FUNCTION GENERATOR has a frequency range of 1 Hz to 200 kHz. The sinewave output has a distortion of 0.5 percent and an amplitude of 5.6-volts P-P maximum. The triangular waveform has a linearity of 1 percent and a maximum peak-to-peak amplitude of 12 volts. The squarewave output has a risetime of 200 ns, a falltime of 100 ns, and a maximum output of 16 volts P-P.

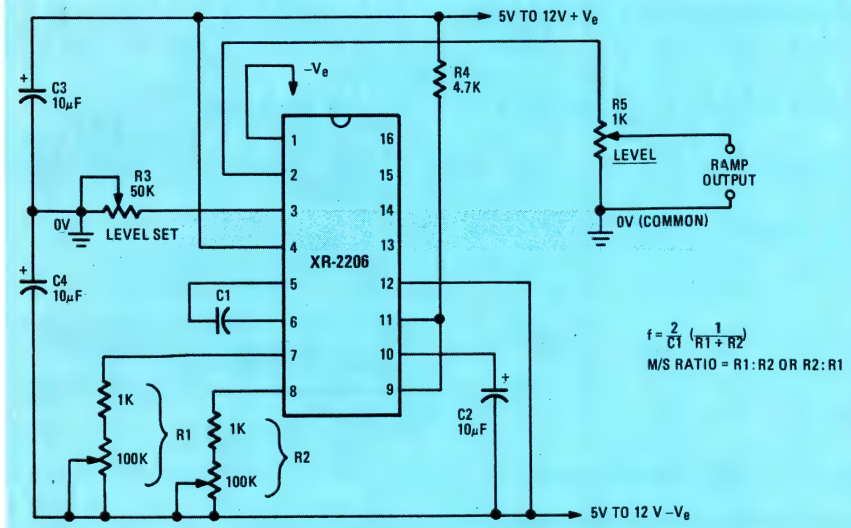

FIG. 11—RAMP GENERATOR provides variable-slope output signal.

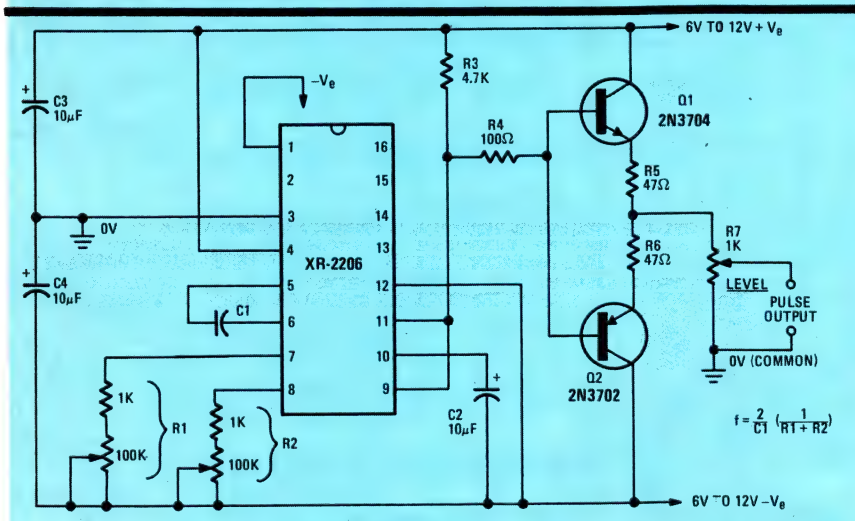

FIG. 12—PULSE GENERATOR provides variable duty-cycle output signal and has an output buffer.

11 simultaneously with the ramp waveform. The squarewave, however, is of fixed amplitude and is not suitable for directly driving low-impedance external loads. If required, the XR-2206 can be used specifically as a pulse or variable duty-cycle squarewave generator as shown in Fig. 12. Here, the SET-LEVEL control is eliminated from the pin–3 terminal of the IC, and the pulse signal at pin 11 is made available to external loads by the Q1—Q2 emitter-follower stage and LEVEL control R7.

Alternatively, the circuits shown in Figs. 11 and 12 can be combined to form a practical variable pulse or ramp generator by using the connections shown in Fig. 13. Here, the desired waveform can be selected by S1, the waveform shapes are varied by R1 and R2, and the waveform amplitudes are controlled by R8.

The versatility of the Fig. 13 circuit can be increased, if desired, by replacing the existing pulse output stage with the one shown in Fig. 14. This circuit enables either positive, negative or symmetrical output pulses to be selected by S2, a 2-pole 3-position switch. Here, load resistor R4 is replaced by a pair of 2.7K, 5%, resistors. With switch S2 in position 1, the pulse output of the circuit is effectively taken from the junction of these two resistors, so the output switches between the fully positive and the half-supply or zero voltage levels. The circuit, therefore, provides positive output pulses. In position 2 of S2, the output is effectively taken from pin 11 of the IC and symmetrical output pulses are available. In position 3, the output is again taken from pin 11 of the IC but the top end of R4 is connected to the zero-voltage line. The output switches

between the zero and negative supply voltage, and negative output pulses are available from the circuit.

FSK modulation

When the FSK input terminal of the XR-2206 IC (pin 9) is open circuit or externally biased above 2 volts with respect to the negative supply voltage, the pin-7 timing resistor is automatically selected and the circuit operates at a frequency determined by the timing capacitor and the pin-7 timing resistor. When pin 9 is connected to the negative supply voltage or is biased 1-volt below the negative supply voltage rail, the pin-8 timing resistor is automatically selected and the circuit operates at a frequency determined by the timing capacitor and the pin-8 timing resistor. The XR-2206 IC can thus be frequency-shift keyed (FSK) by simply applying a suitable keying or pulsing signal between pin 9 and the negative supply. Figure 15 shows the practical connections for making a simple FSK modulated sinewave generator or 'warble-tone' generator.

If required, the keying signal can be referenced to the ground or zero-volt line by using the 3-transistor add-on circuit shown in Fig. 16. Here, with the keying signal at the zero-volt level, all three transistors are cut off. When this occurs, pin 9 of the IC is effectively open circuit, and the output frequency is controlled by timing resistor R1. When the FSK input keying signal is high, transistors Q1 and Q2 conduct, causing Q3 to saturate. When Q3 saturates, pin 9 shorts to the negative supply and the output frequency is controlled by R2. The FSK facility controls both signals appearing at the pin 2 and pin 11 output terminals.

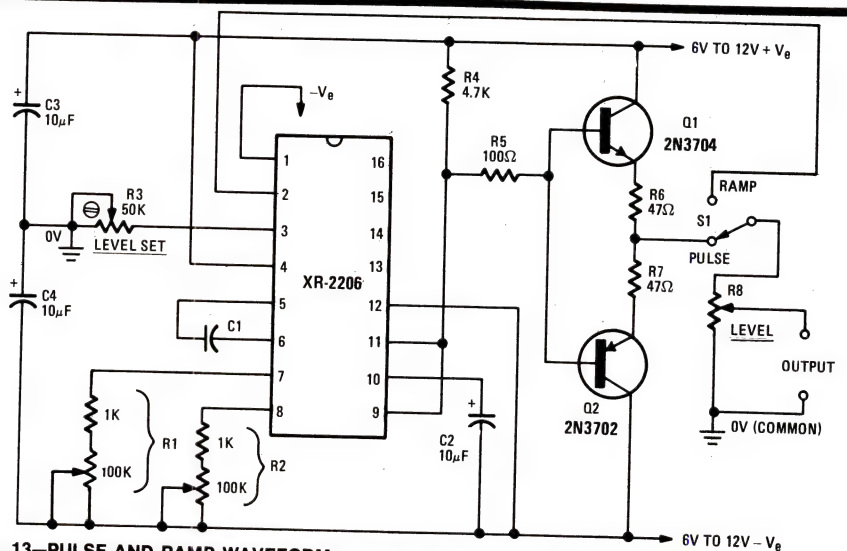

FIG. 13—PULSE AND RAMP WAVEFORM generator provides variable output signals.

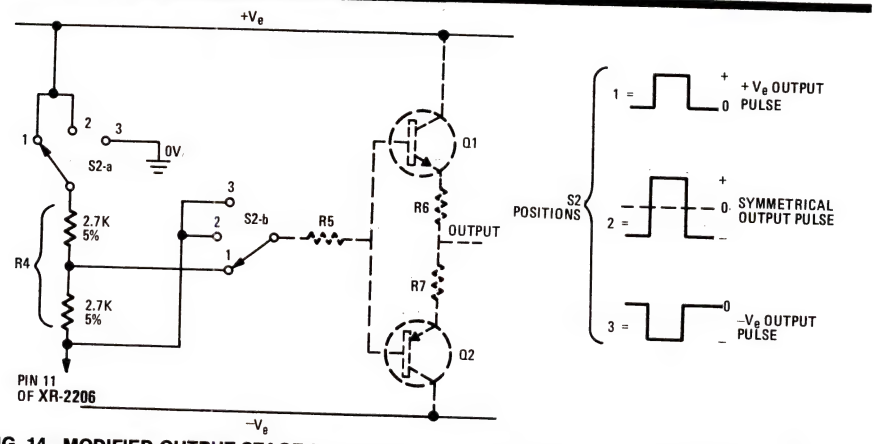

FIG. 14—MODIFIED OUTPUT STAGE for circuit shown in Fig. 13 provides either positive, negative or symmetrical output pulses.

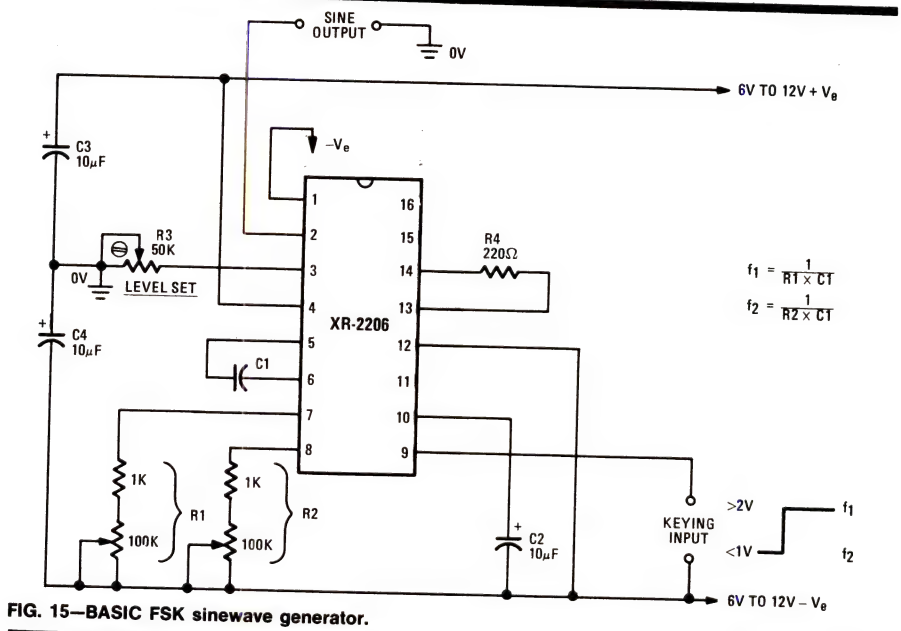

FIG. 15—BASIC FSK sinewave generator.

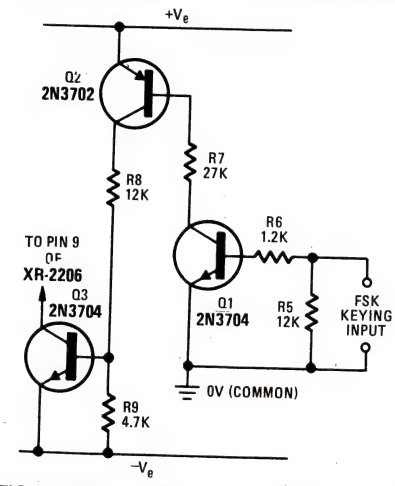

FIG. 16—FSK MODIFICATION to the circuit shown in Fig. 15 references the FSK input to the common or ground line.

Amplitude modulation

The output-signal amplitude at pin 2 of the XR-2206 can be modulated by applying a DC bias and a modulating signal to pin 1, as shown in Fig. 17. The internal impedance at pin 1 is approximately 200K ohms, so this pin should be connected to the negative supply to prevent unwanted pick-up when the AM facility is not in use.

The signal amplitude varies linearly with the applied voltage at pin 1 when this voltage is within 4 volts of the half-supply value. In split-supply circuits, of course, the half-supply value equals

zero volts. When pin 1 is at the half-supply value, the amplitude of the signal at pin 2 is approximately zero. When the pin-1 voltage is increased above the half-supply value, the signal at pin 2 rises in direct proportion. When the pin–1 voltage is reduced below the half-supply value, the pin–2 signal again rises in direct proportion, but the phase of the output signal is reversed. This last-mentioned feature can be used for phase-shift keyed (PSK) and suppressed-carrier AM generation.

The pin-1 terminal can also be used to facilitate gate-keying or pulsing of the output signal at pin 2. This can be achieved by biasing pin 1 at approximately half-supply voltage to give zero output at pin 2, and then imposing the gate or pulse signal on pin 1 to raise the pin 2–signal to the required turn-on amplitude. The total dynamic range of amplitude modulation is approximately 55 dB.

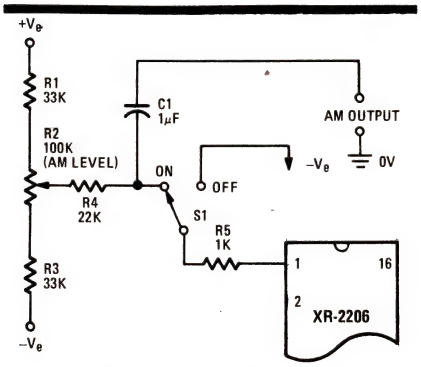

FIG. 17—AMPLITUDE MODULATION is accomplished with this add-on circuit.

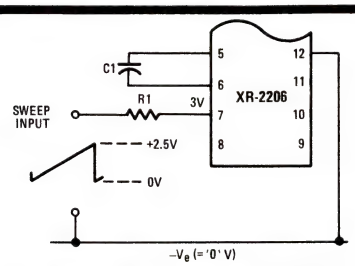

FIG. 18—FREQUENCY-SWEEP CONNECTION provides a 6:1 frequency range.

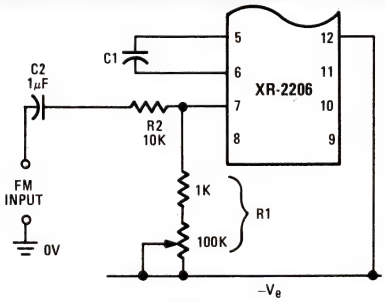

FIG. 19—FREQUENCY MODULATION connection for the XR-2206.

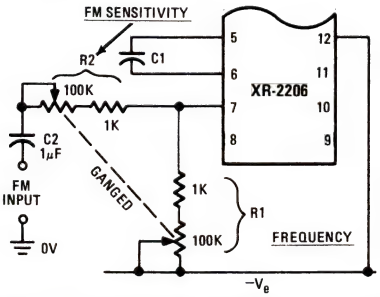

FIG. 20—CONSTANT-SENSITIVITY FM connection.

Frequency modulation

The output frequency of the XR-2206 is proportional to the total timing current (I_T) drawn from pin 7 or 8, and is given by:

$$f = \frac{320 \times I_T}{C} \text{ Hz}$$

where I_T is in milliamperes and C, the timing capacitor, is in microfarads. Pins 7 and 8 are low–impedance terminals and are internally biased at +3 volts with respect to pin 12. The frequency varies linearly with I_T over the range of 1 μA to 3 mA. The frequency can be varied either by wiring a variable current-determining resistor between pin 12 and the timing terminal, or by applying a variable voltage in the range 0 to +3 volts between pin 12 and the timing terminal using a current-limiting resistor, or by a combination of these two techniques.

Figure 18 shows the basic connections of a simple frequency-sweep circuit with a 6:1 frequency range. Here, a sawtooth frequency-sweep signal that has a peak amplitude of 2.5 volts is applied between pin–12 and pin–7 timing terminal. When the instantaneous peak value of the sawtooth voltage is zero, 3 volts is developed across R1, and the frequency is the same as in the case of a simple resistance-controlled XR-2206 oscillator. When, on the other hand, the instantaneous peak value of the sawtooth voltage is 2.5 volts, only 0.5 volt is developed across R1, and the R1 current and, therefore, the frequency is reduced to only 1/6th of that of the case we have just looked at.

Figure 19 shows the essential connections of a simple FM generator. Here, in the absence of a modulating signal, the output frequency is determined by R1 and C1, as in the case of a conventional XR-2206 oscillator. When the modulating signal is connected to the FM input, the timing currents and, therefore, the output frequency of the circuit are modulated.

A weakness of the simple circuit shown in Fig. 19 is that, for a given amplitude of the modulating signal, the percentage of frequency deviation varies with the setting of the R1 FREQUENCY control. This snag is overcome in the constant-sensitivity circuit of Fig. 20. A dual-ganged potentiometer is used with one arm used as the R1 frequency-determining control and the other arm as the R2 FM-SENSITIVITY control, so that the sensitivity is automatically adjusted to track with the frequency setting.

It should be noted that the frequency-sweep and frequency-modulated signals appear at both pins 2 and 11.

Power supplies

Finally, a few notes on choosing power supplies for the XR-2206 IC. It should be noted that the XR-2206 has built-in voltage regulation circuitry controlling the VCO, and that the amplitude of the output signal at pin 2 is not significantly influenced by variations in circuit supply voltage. Consequently, there is little advantage in using higher supply-voltages than are absolutely necessary for correct operation. In most cases, single-ended or split 12-volt supplies are adequate.

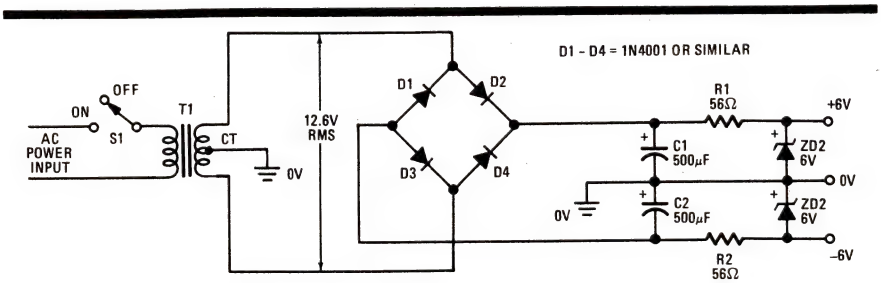

FIG. 21—REGULATED SPLIT-VOLTAGE power supply provides a 6V-0-6V output.

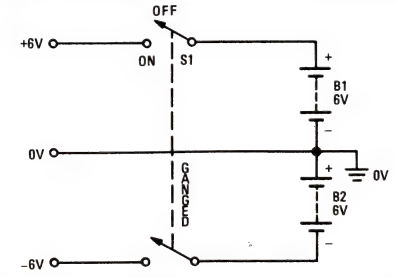

FIG. 22—BATTERY SUPPLY with split 6V-0-6V output.

Figure 21 shows the practical circuit of a line powered Zener-regulated 12-volt split-supply (6V–0–6V) circuit. Figure 22 shows the alternative connections for using a battery power supply. The XR-2206 draws a typical current of about 15 mA when used with these supplies. **R-E**

CB PROJECT

Preamplifier For Long Distance Reception

Pull in those weak signals with this add-on device for your CB transceiver

GEORGE SANTE

A CB TRANSCEIVER IS A COMBINATION OF A receiver and a transmitter. The transmitter power output is limited to 4 watts, so the only thing you can legally do to improve the transmitted signal is to improve the antenna system.

The receiver portion is a horse of another stripe. Chances are that when you originally shopped for a transceiver, you learned that it was in the receive functions that the money-making differences occurred. A straight receiver with only a volume control and squelch costs a lot less to produce than one with noise limiting, noise blanking, and an RF amplifier. These additional circuits, while they improve the reception con-

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise noted.
R1—1200 ohms
R2—5100 ohms
R3—8200 ohms
R4—1500 ohms
R5—100 ohms
R6—560 ohms
R7—27 ohms
R8—270 ohms
R9—150 ohms
R10—1 megohm
R11—1000 ohms
C1, C2, C5, C6—.001 μF disc
C3—25 μF, 12 volt, electrolytic
C4—.01 disc
C7—100 μF, 3 volt, electrolytic
D1, D4—1N4001
D2, D3—1N914
Q1, Q2—2N3563
Q3—2N4123
RY1—DPDT relay, 320 ohm, 12 volt DC

The following parts are available from Guardsman Electronics, Box 215, Brooklyn, NY 11207.

Etched and pre-drilled printed circuit board, $4.00 postage prepaid.

Complete parts kit, including PC board, all components, and case, $14.95 postage prepaid.

New York State residents add state and local sales tax as applicable.

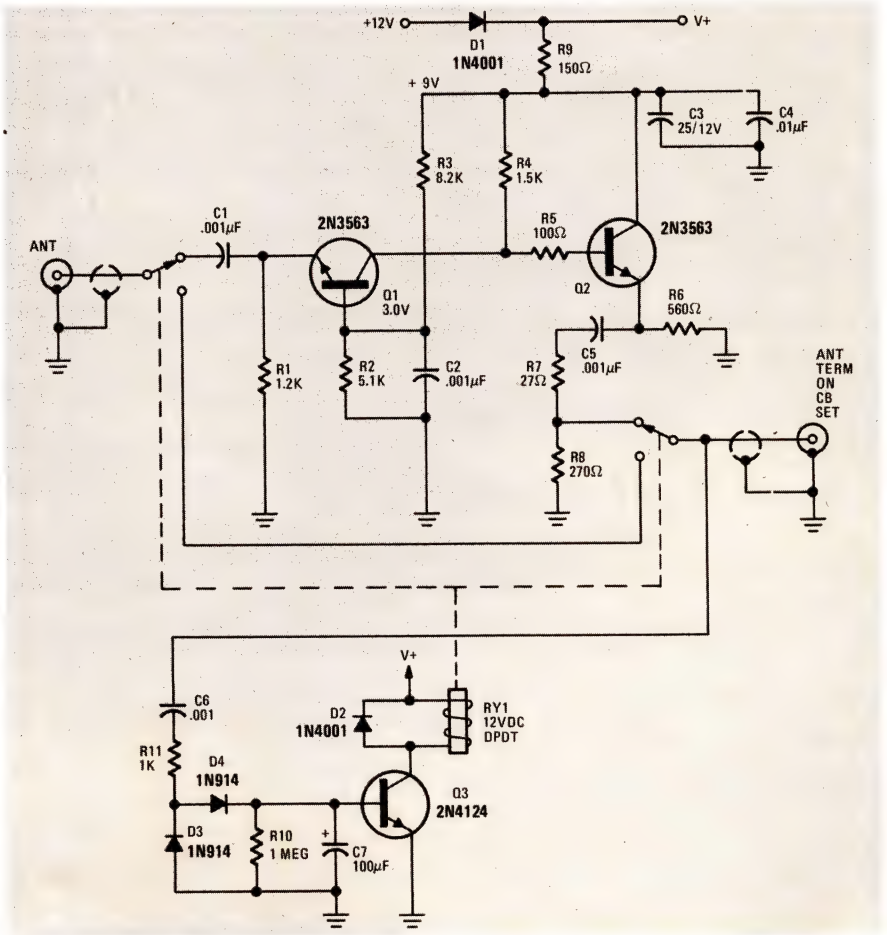

FIG. 1—CB RF PREAMPLIFIER connects between antenna and antenna terminal on CB transceiver.

siderably, can add appreciably to the cost. However, here's one way that the receiver portion of your transceiver can be upgraded so that the down-in-the-mud signals come through loud and clear, crisp and healthy. This add-on RF preamplifier makes any receiver really pull in the signals.

The RF preamplifier connects between the antenna and the antenna terminal on the transceiver. It has no switches or controls, so it can be mounted out of the way. The unit is powered by the 12-volt electrical system in your car.

Figure 1 shows a schematic diagram of the preamplifier. Circuit operation is as simple as it looks. Transistor Q1 is the preamplifier stage. Emitter-follower Q2 is used for impedance matching purposes. When the transmitter is switched on, the preamplifier is bypassed so that the output signal is connected directly to the antenna. Diodes D3 and D4, and associated components monitor the signal level from the antenna terminal of the transceiver. When a high-level signal is detected, Q3 is driven into saturation which energizes relay RY1 to bypass the preamplifier.

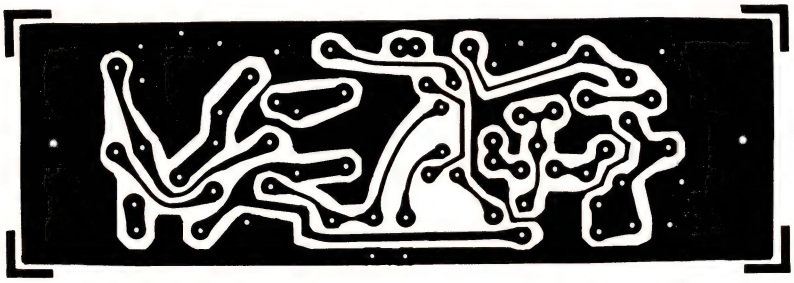

FIG. 2—FOIL PATTERN, shown full-size.

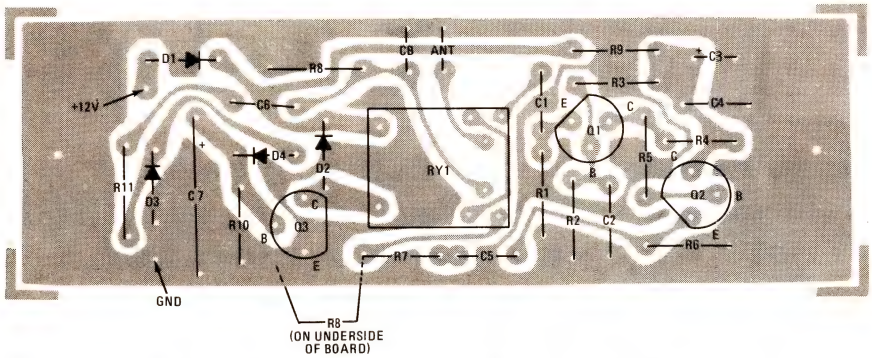

FIG. 3—COMPONENT PLACEMENT diagram. Resistor R8 mounts on foil side of PC board.

Construction

Building the preamplifer is easy as all the components are mounted on a PC board. For those who like to roll their own, the foil pattern is shown in Fig. 2. If you prefer, you can purchase a ready-to-use PC board for $4.00 (see parts list) and save yourself the work.

Begin the assembly by mounting all of the components to the PC board and soldering them in place, removing excess leads. The component placement diagram is shown in Fig. 3. The pre-drilled pre-etched PC board is treated with solder resist where solder is not to be used, however, caution must be taken to avoid solder bridges from the foil paths to other paths. A good way to work is to put a component in place, solder the leads carefully, then check to see that no unintended shorts occur and remove all solder splashes. Clip the lead wires close to the board surface, then install the next component.

Now there's been one design change in this unit, and correcting for it is no problem at all. However, it's a change that you should make for better operation.

Resistor R8 should *not* be connected to its indicated position on the circuit board. Leave it till last, then bend the wire leads at right angles to the resistor body, and connect this resistor on the foil side of the board to ground near the emitter lead of transistor Q3 and the

Go after the best of everything.

Don't settle for less. Especially when it comes to electronics training . . . because everything else in your life may depend on it. That's why you ought to pick CIE!

You've probably seen advertisements from other electronics schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

. . .

Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one . . . with the specialists . . . with CIE!

There's no such thing as bargain education.

If you talked with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

Because we're specialists, we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it . . .

Our step-by-step learning includes "hands-on" training.

At CIE, we believe theory is important. And our famous Auto-Programmed® Lessons teach you the principles in logical steps.

But professionals need more than theory. That's why some of our courses train you to use tools of the trade like a 5 MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a beauty of a 19-inch diagonal Zenith solid-state color TV you use to perform actual service operations.

Our specialists offer you personal attention.

Sometimes, you may even have a question about a specific lesson. Fine. Write it down and mail it in. Our experts will answer you promptly in writing. You may even get the specialized knowledge of all the CIE specialists. And the answer you get becomes a part of your permanent reference file. You may find this even better than having a classroom teacher.

Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up . . . no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.

Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back—the same day. You find out quickly how well you're doing!

CIE can prepare you for your FCC License.

For some electronics jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of your specific knowledge and skills!

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

For professionals only.

CIE training is not for the hobbyist. It's for people who are willing to roll up their sleeves and go to work . . . to build a career. The work can be hard, sure. But the benefits are worth it.

Send for more details and a FREE school catalog.

Mail the card today. If it's gone, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.

Patterns shown on TV and oscilloscope screens are simulated.

CIE **Cleveland Institute of Electronics, Inc.**
1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

☐ **YES . . .** I want the best of everything! Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information. RE-09

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill information: ☐ Veteran ☐ Active Duty

MAIL TODAY!

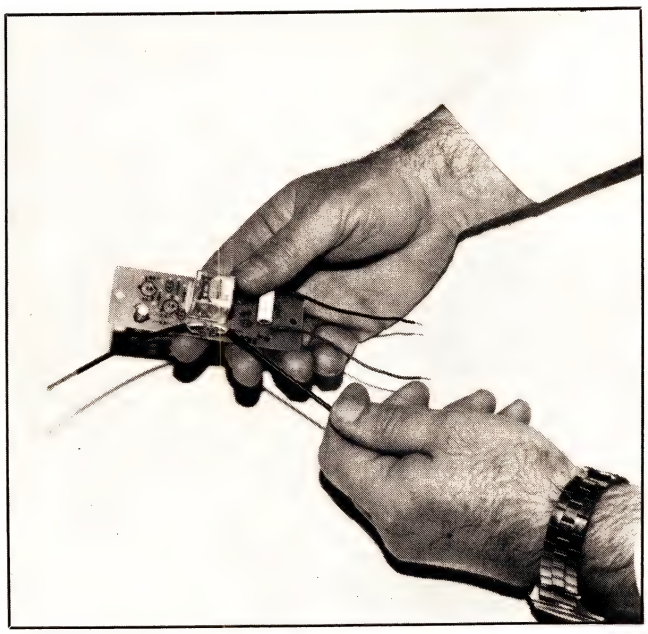

CB PREAMPLIFIER assembles on a single PC board. Coaxial cable is used to connect the PC board to the antenna input and output jacks.

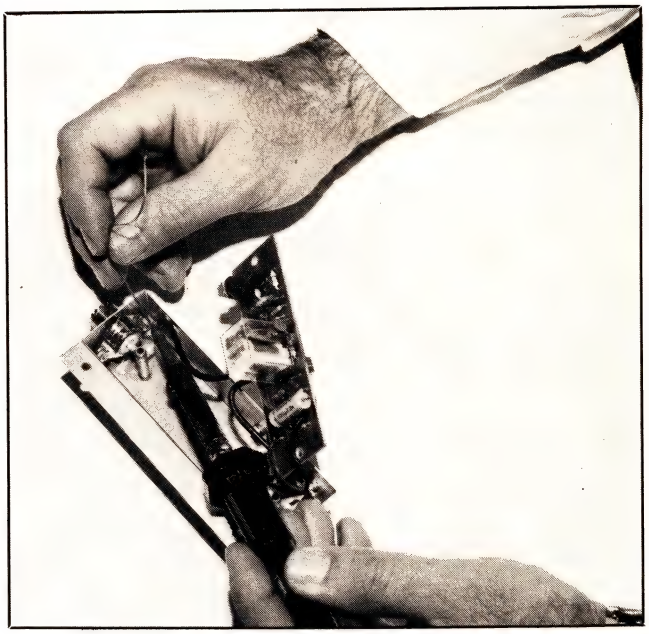

CIRCUITRY AND COAXIAL CONNECTORS are neatly installed in a 5 × 1½ × 1½-inch sheet metal case.

nearest terminal of resistor R7, as shown in Fig. 3. The correct connection for this resistor is also shown on the schematic.

When you've got the board fully wired, mount the power input terminal-strip and the two coaxial connectors to the chassis. Before putting the board in place, wire the leads to the proper terminals as this will be easier to accomplish before the board is put in place.

Now check the board once again, then set it, component side down, foil side up, on the stand-offs and fix it in place with the two screws. Place the cover in position and fasten it with sheet metal screws.

To install the unit, connect a short length of coaxial cable from the transceiver to the preamplifier, then connect the transceiver's antenna to the other end. The unit requires a switched source of 12-volts DC. The best place to pick this up in a mobile rig is to connect the red, or positive lead, to the hot side of the switch on your transceiver's volume control. In this way, the preamplifier will be on only when the transceiver is turned on. The black lead can be connected to any convenient ground.

There are several means for mounting that are available for consideration. If your transceiver has its antenna connector on one side, a right-angle coaxial connector can be used to connect the preamplifier and support it at the same time, concealing it behind the transceiver. If you prefer, or if this is not available to you, try to locate a couple of sheet metal screws on the back of your transceiver and use these to mount the preamplifier.

Remember too, that you are effectively adding length to your transmission line, and it's a good idea to check the VSWR after installation. **R-E**

Police to get radios, funding for highway safety program

A new program, National Emergency Aid Radio (NEAR), will make Federal Highway Safety funds available for the purchase of radios for installation in state police base stations, highway patrol cars and other state agency vehicles. Volunteer CB emergency groups are to be included in the program if federal funding is to be made available. However, no funding is to be made to volunteer groups.

Besides the purchase of equipment, existing Highway Safety funds may be applied, under the program, for planning and organizing, training and training material, public information and education, and statistical data gathering and evaluation, including operating costs, expenses and staff.

This new program of the U.S. Department of Transportation has been warmly welcomed by the organized CB'ers. REACT (*R*adio *E*mergency *A*ssociated *C*itizens *T*eams), possibly the largest of the emergency-oriented CB associations with over 1,500 affiliated local volunteer emergency teams, states: "We foresee this cooperation as strengthening the role of local REACT teams."

Since the states will be required to include public service groups in the planning of the program and its implementation, and REACT is a national volunteer organization closely meeting the requirements of the NEAR program, organization spokesmen feel that cooperation between the two will ease and accelerate the process of setting up an efficient system. "The development of State councils of REACT teams in over half the states provides a direct representative input to the state NEAR organization," REACT says.

Microprocessor courses offered by National Semiconductor

Courses in Microprocessor Fundamentals will be given at National Semiconductor's Western Microprocessor Training Center, 1333 Lawrence Expressway, Santa Clara, CA, June 6–9. A course in Advanced Programming will be given May 9–12.

Courses in the application of National's PACE microprocessor will be offered at the Center, June 13–16. SC/MP (*S*imple, *C*ost-effective *M*icro*P*rocessor) application courses will be given May 2–5 and June 20–23. Class hours are 10 am to 5 pm.

The fee for the four-day courses is $395. Registration information is obtainable from local National Semiconductor sales offices or from National's Western Microprocessor Training Center in Santa Clara, CA, (408) 247-7924.

TV games *vs* tube damage

A suggestion that some TV games could be harmful to the picture tubes of TV sets was hotly challenged by Gary Blondefield, marketing manager for National Semiconductor's game components, at least insofar as his products are concerned.

National's *Adversary* game, now in volume production, uses the MM57100 video game circuit and the LM1889 TV modulator circuit. Mr. Blondefield stated that these combine to form a sophisticated computer-like system that provides a consistent video presentation when the television set is changed from the broadcast TV signal to the signal generated by the game. The presentation is so consistent, Mr. Blondefield stated, that none of the controls on the set need to be changed when switching from one signal to the other. "If the set is adjusted to receive a good-quality broadcast signal, the game colors and intensities will also be very good," he said. **R-E**

1979 WORLD RADIO CONFERENCE

How It Will Affect You

The World Administrative Radio Conference will convene in Geneva in 1979 to discuss possible changes in the allocation of the entire radio spectrum—including the hobby services. Any action taken could directly affect hams, CB'ers and broadcasters.

STANLEY LEINWOLL

ON SEPTEMBER 24, 1979, WHAT MAY BE THE most important radio conference ever held is scheduled to begin in Geneva, Switzerland. The World Administrative Radio Conference (WARC-79) will be convened by the International Telecommunication Union (ITU) and will meet for ten weeks to review and revise the provisions of the Radio Regulations dealing with the allocation of frequency bands for the entire radio spectrum, from 10 kHz to 40,000 MHz, and beyond.

The last international conference to deal with the electromagnetic spectrum on so broad a scope took place in 1947, and it is likely that WARC-79 will be the last conference of the twentieth century with the authority to change frequency allocations so extensively.

During those momentous ten weeks every service using radio waves will come under scrutiny by the conference delegates, who will represent some 150 countries. Although more than two years remain before WARC-79, extensive preparations for this vital conference have been under way in many countries. Here in the United States, preparatory work began in late 1975, and will continue into 1979.

It now appears that WARC-79 will make extensive revisions affecting all or most services using the electromagnetic spectrum, including the hobby services, international broadcasting, amateur radio, and possibly Citizens Band (CB) radio. Since the changes involving these services could be significant, the remainder of this article will attempt to assess the nature of possible WARC-79 action, and the impact it could have on these services.

Current allocations

Table I shows how short-wave frequencies in the 3 to 30 MHz range are allocated under current regulations. Twelve different services are assigned groups of frequencies in various regions of the short-wave spectrum to permit selection of optimum frequencies for different propagation conditions. (For example, during periods of darkness, lower frequencies are more commonly used than during daylight hours; frequency requirements also change from season to season, as well as over an 11-year sunspot cycle.)

It can be seen from Table I that in the Western Hemisphere, a total bandwidth of 2150 kHz is allocated solely to international broadcasting. Radio amateurs have been assigned a bandwidth of 2800 kHz exclusively, and another 500 kHz on a shared basis. Some of the shared bands are allocated to two or more services simultaneously. One notable example of such sharing involves the 7-MHz (41-meter) band, which is used by broadcasters in Europe, Africa and Asia, and amateurs in North and South America. The 400 kHz used by CB'ers is

TABLE I—ALLOCATIONS of the high-frequency spectrum. Radio Regulations, Geneva, 1959.

Radio Service	Total Bandwidth Allocated Exclusively (kHz)*	Total Bandwidth Allocated on a Shared Basis (kHz)*
1. Fixed	10,173	6147†
2. Maritime Mobile	3850	
3. Aeronautical Mobile (R)	1105	150
4. Aeronautical Mobile (OR)	695	150
5. Land Mobile		1985
6a. Mobile (except aeronautical mobile)		2907
6b. Mobile (including aeronautical mobile)		800
7. Broadcasting	2150	
8. Tropical Broadcasting		500
9. Amateur	2800	500
10. Standard Frequency	50	30
11. Meteorological Aids		500
12. Space and Earth-Space		30

* Allocations are for Region 2 (Western Hemisphere). Allocations for Region 1 (Europe, Asiatic U.S.S.R., the Near East, Africa) and Region 3 (Central and South Asia, Australia) are slightly but not significantly different.

† Aeronautical fixed circuits can be assigned within the fixed bands. In addition, 300 kHz has been specifically allocated to aeronautical fixed circuits on a shared basis with other services.

actually part of the spectrum allocated to the fixed and mobile services, and assigned by the FCC to CB radio.

International broadcasting

Of all the services using the short-wave spectrum, international broadcasting is in the most difficulty at present. Over 80 countries operate more than 1,500 transmitters carrying broadcasts to an estimated quarter of a billion listeners. Currently, more than 22,000 frequency-hours are scheduled daily in the seven bands allocated between 5950 and 26,100 kHz.

The amount of spectrum allocated to broadcasting can handle about half the assignments on the air today. The situation is even worse than that because during prime-time listening hours, the spectrum is even more severely overloaded.

This situation has resulted in very serious interference. This can be seen from Fig. 1 which is a spectrum usage chart for the 6-MHz band prepared by technical monitors operating at various locations in central Europe. The frequency in 5 kHz increments is shown on the left and time is shown across the top. Broadcasters using frequencies in the 6-MHz band are indicated by the heavy horizontal lines and are identified in accordance with standard abbreviations.

Inspection of the chart indicates that during peak listening hours in the European area, the 6-MHz band is vastly overloaded. Two broadcasters operating simultaneously on some frequency is commonplace, and the broadcasts are spaced only a few kHz apart. All of these broadcasts reach European receivers, resulting in extensive mutual interference.

Figure 1 is indicative of conditions that exist today throughout much of the world in most of the bands allocated to international short-wave broadcasting. Because the bands are overcrowded, interference levels are intolerably high, and near-chaos exists in many areas of the world. In some parts of the spectrum, there are times when reception comes through as a barrage of meaningless jibberish.

The growth of broadcasting

With the advent of the cold war, many countries recognized that short-wave radio represented the most economical means of reaching great masses of people in most of the world. As the struggle for governmental power increased, even greater emphasis was placed on radio as a means of providing free access to information in totalitarian societies. The Soviet Union, on the other hand, expanded its propaganda efforts and rapidly increased the number of transmitters it had on the air.

As the number of transmitters in use grew and interference levels mushroomed, broadcasters began seeking means of strengthening their services. The most obvious remedy was to use more powerful transmitters and higher-gain antennas. Fifteen years ago there were approximately twenty 250-kW transmitters in operation. Today there are over three-hundred transmitters with power ranging from 250 to 1000 kW.

In many cases, interference levels were so great that even high power was ineffective, and broadcasters, attempting to capitalize on whatever good frequencies they had, began to synchronize transmitters. Some broadcasters presently use as many as three transmitters simultaneously on a single frequency, each beamed in a different direction. Such techniques were made possible through the use of high-gain narrow-beam antenna systems developed after World War II.

These techniques did not help, and in desperation, another solution was found by a number of broadcasters—they moved out-of-band. As indicated previously, the services using the short-wave spectrum are allocated discrete bands of frequencies. Table II shows the bands currently allocated exclusively to international broadcasting.

TABLE II—INTERNATIONAL BROADCASTING frequencies in kHz.

5950—6200
9500—9770
11700—11975
15100—15450
17700—17900
21450—21750
25600—26100

Frequencies outside these bands are not assigned to broadcasting, and any country adhering strictly to the Radio Regulations would not consider use of such frequencies for broadcasting. However, there is a section of the Radio Regulations, Paragraph 115, that allows for the possibility of such use, as follows:

> "Administrations of the Members and Associate Members of the Union shall not assign to a station any frequency in derogation of either the Table of Frequency Allocations given in this Chapter or the other provisions of these Regulations, except on the express condition that harmful interference shall not be caused to services carried on by stations operating in accordance with the provisions of the Convention and of these Regulations."

Paragraph 115 gives countries the right to use *any* frequency in the spectrum for *any* service, provided it does not cause harmful interference to the service operating in accordance with the regulations.

Fortunately, there has been a sharp reduction in the use of frequencies in the fixed services—that is, point-to-point communication via teletype, facsimile, telephone, data, etc. This has come about because of the advent of satellite communications as well as the expanded use of cable facilities to carry traffic generated by the fixed services. RCA Global Communications, Inc., for example, has shut down virtually all of its domestic short-wave plants and has discontinued its high-frequency operations. So, the combination of decreased

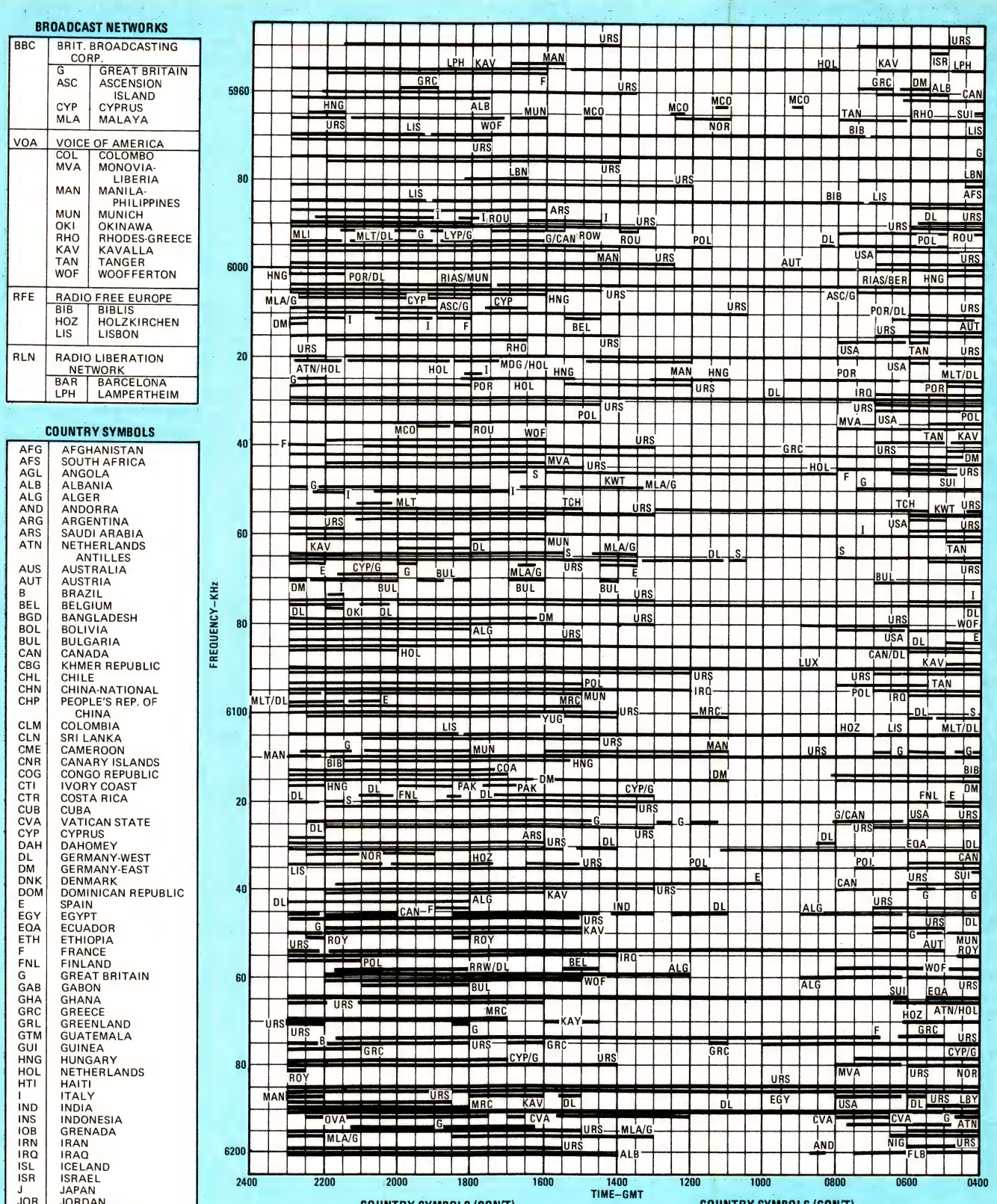

BROADCAST NETWORKS

BBC	BRIT. BROADCASTING CORP.	
	G	GREAT BRITAIN
	ASC	ASCENSION ISLAND
	CYP	CYPRUS
	MLA	MALAYA
VOA	VOICE OF AMERICA	
	COL	COLOMBO
	MVA	MONOVIA-LIBERIA
	MAN	MANILA-PHILIPPINES
	MUN	MUNICH
	OKI	OKINAWA
	RHO	RHODES-GREECE
	KAV	KAVALLA
	TAN	TANGER
	WOF	WOOFFERTON
RFE	RADIO FREE EUROPE	
	BIB	BIBLIS
	HOZ	HOLZKIRCHEN
	LIS	LISBON
RLN	RADIO LIBERATION NETWORK	
	BAR	BARCELONA
	LPH	LAMPERTHEIM

COUNTRY SYMBOLS

AFG	AFGHANISTAN
AFS	SOUTH AFRICA
AGL	ANGOLA
ALB	ALBANIA
ALG	ALGER
AND	ANDORRA
ARG	ARGENTINA
ARS	SAUDI ARABIA
ATN	NETHERLANDS ANTILLES
AUS	AUSTRALIA
AUT	AUSTRIA
B	BRAZIL
BEL	BELGIUM
BGD	BANGLADESH
BOL	BOLIVIA
BUL	BULGARIA
CAN	CANADA
CBG	KHMER REPUBLIC
CHL	CHILE
CHN	CHINA-NATIONAL
CHP	PEOPLE'S REP. OF CHINA
CLM	COLOMBIA
CLN	SRI LANKA
CME	CAMEROON
CNR	CANARY ISLANDS
COG	CONGO REPUBLIC
CTI	IVORY COAST
CTR	COSTA RICA
CUB	CUBA
CVA	VATICAN STATE
CYP	CYPRUS
DAH	DAHOMEY
DL	GERMANY-WEST
DM	GERMANY-EAST
DNK	DENMARK
DOM	DOMINICAN REPUBLIC
E	SPAIN
EGY	EGYPT
EQA	ECUADOR
ETH	ETHIOPIA
F	FRANCE
FNL	FINLAND
G	GREAT BRITAIN
GAB	GABON
GHA	GHANA
GRC	GREECE
GRL	GREENLAND
GTM	GUATEMALA
GUI	GUINEA
HNG	HUNGARY
HOL	NETHERLANDS
HTI	HAITI
I	ITALY
IND	INDIA
INS	INDONESIA
IOB	GRENADA
IRN	IRAN
IRQ	IRAQ
ISL	ICELAND
ISR	ISRAEL
J	JAPAN
JOR	JORDAN
KOR	KOREA-SOUTH
KRE	KOREA-NORTH
KWT	KUWAIT
LBN	LEBANON
LBR	LIBERIA
LBY	LIBYA
LUX	LUXEMBOURG
MCO	MONACO
MDG	MALAGASY REPUBLIC
MEX	MEXICO
MLA	MALAYSIA
MLI	MALI
MLT	MALTA
MNG	MONGOLIAN PEOPLE'S REPUBLIC
MOZ	MOZAMBIQUE
MRC	MOROCCO
NCG	NICARAGUA
NIG	NIGERIA
NOR	NORWAY
NZL	NEW ZEALAND
OCE	TAHITI

COUNTRY SYMBOLS (CON'T)

PAK	PAKISTAN
PHL	PHILIPPINES
POL	POLAND
POR	PORTUGAL
PRG	PARAGUAY
PRU	PERU
QAT	QATAR
ROU	RUMANIA
RRW	RWANDA
S	SWEDEN
SDN	SUDAN
SEN	SENEGAL
SEY	SEYCHELLES
SLV	EL SALVADOR
SNG	SINGAPORE
SOM	SOMALIA
SUI	SWITZERLAND
SWN	SWAN ISLAND
SYR	SYRIA
TCH	CZECHOSLOVAKIA
TGK	TANZANIA

COUNTRY SYMBOLS (CON'T)

TGO	TOGO
THA	THAILAND
TUN	TUNISIA
TUR	TURKEY
URG	URUGUAY
UAE	UNITED ARAB EMIRATES
URS	USSR
USA	UNITED STATES OF AMERICA
VEN	VENEZUELA
VTN	VIETNAM
YEM	YEMEN
YMS	PEOPLE'S REPUBLIC OF SOUTH YEMEN
YUG	YUGOSLAVIA
ZAI	ZAIRE
ZMB	ZAMBIA
AOE	SAHARA (SPANISH)
SRL	SIERRA LEONE
SWZ	SWAZILAND

FIG. 1—SPECTRUM USAGE CHART for 6-MHz international broadcasting band for the winter 1976 period.

use of the fixed bands, and Paragraph 115, gave broadcasters entrance into what would have been forbidden territory.

Broadcasters have been quick to fill the spectrum void as other services vacated it. At present, the number of broadcasters moving into bands allocated to other services is increasing rapidly, although many countries such as the Federal Republic of Germany and Portugal, for example, have interpreted the Radio Regulations more rigidly, and have refused to permit operation in bands other than those specifically allocated to broadcasting. At present, the United States operates only in-band.

For these countries, in-band interference continues to be severe, and the only hope for improving their services is for a formal expansion of the bands allocated to international broadcasting by WARC-79. What are the prospects for such an expansion? They appear to be good.

TABLE III—CURRENT ALLOCATIONS, needed allocations and a prediction of what is to come out of WARC-79.

Present (kHz)	Needed (kHz)	WARC-79 Projection (kHz)
5950—6200	5750—6200	5750—6200
	7300—7700	7100—7500
9500—9770	9400—9900	9400—9800
11,700—11,975	11,500—12,000	11,600—12,000
	13,600—14,000	
15,100—15,450	15,050—15,700	15,050—15,600
17,700—17,900	17,500—18,000	17,600—18,000
21,450—21,750	21,450—21,850	21,450—21,850
25,600—26,100	25,600—26,100	25,600—26,100

TABLE IV—AMATEUR RADIO ALLOCATIONS requested by ARRL and current allocations.

Worldwide Allocations Requested by ARRL for WARC-79 (in kHZ)	Actual Allocations to Amateur Radio, U.S. (in kHz)
3500—4000	3500—4000
7000—7500	7000—7300
10,100—10,600	
14,000—14,500	14,000—14,350
18,100—18,600	
21,000—21,500	21,000—21,450
24,000—24,500	
28,000—29,700	28,000—29,700

The outlook

There appears to be universal acceptance of the fact that the short-wave broadcasting bands are severely congested, and that at the same time point-to-point use of the fixed bands is decreasing. The principal resistance to this concept comes from military representatives, who claim that even though satellite and other modern methods of long-range communication have largely replaced the need for high-frequency circuits, the frequencies are nevertheless required for use in emergency situations. Defending this position will be difficult. Extensive monitoring operations in the fixed bands to determine usage is now under way. It is showing that large portions of these vitally needed bands are either now in use by broadcasters, or lying dormant, unused by anyone. In light of this, many broadcasters have begun to contact, educate, and work for support among other non-committed countries for expansion of the bands at WARC-79.

It is reasonable to expect that WARC-79 will expand the bands by approximately 50%. This will *not solve* the problem, but it will *remedy* it. Hopefully, WARC-79 will also provide for the broadcasters to continue to move into the spectrum allocated to the fixed services, as the role of satellites continues to increase in the future. This could be done by continuing Paragraph 115 and by allocating the space immediately adjacent to the broadcast bands to services that are most likely to benefit from expanded availability of satellites and cables.

Table III repeats what is currently allocated, and indicates what is needed to improve the broadcasters situation, as well as a prediction of what is apt to come out of WARC-79 for international broadcasting. The table lists only the bands that are shared, such as 80 and 41 meters. A new broadcasting band in the region between 13,600 and 14,000 kHz is proposed because the spread between the 11- and 15-MHz bands is too great to permit smooth operational transition during sunrise and sunset periods.

Amateur radio

Amateur radio has its own severe congestion problems. The number of amateurs now operating in the United States is close to 300,000, and growing. In the short-wave portion of the spectrum, the amateurs have only five bands (80, 40, 20, 15, and 10 meters), and during certain periods interference levels are extremely high. It is obvious that relief would be most welcome.

The American Radio Relay League, the official amateur organization in this country, has requested new allocations at WARC-79. These requests as well as the present amateur allocations in the U.S. are listed in Table IV.

If the allocations requested by the ARRL are approved, the total bandwidth for the amateur service will be over 5 MHz, or approximately 19% of the entire short-wave spectrum. Although this appears high, it must be remembered that the requested space will have to serve the group for the remainder of the 20th century. Many people believe that as more sophisticated methods of communication become available (including higher capacity satellites), decreasing use of the short-wave spectrum will occur by all services other than broadcasting—amateurs and CB'ers. In light of this, the request for over 5 MHz of spectrum does not appear unreasonable.

Current sentiment appears to be running against the amateurs. This is unfortunate, because the list of accomplishments to the radio art by this group can fill a book, and its contributions include pioneering discoveries, training much needed technical manpower, and untiring and dedicated service to humanity during times of great disasters.

There are two serious problems, however, that the amateurs must overcome to protect their interests. First, the number of amateurs varies significantly from country to country. The bulk of the world's amateurs are in only two countries, the United States and Japan. In many countries the number of amateurs is in the tens or hundreds, and many foreigners have called amateur radio an American hobby. Consequently, considerable anti-amateur sentiment has been developing, particularly among Third-World countries.

The United States, long a staunch supporter of amateur radio, will have only one vote at WARC-79. Although it will have the right to reserve—that is, refuse any part of the new regulations that are unacceptable—its influence will be limited. As a result, amateur radio could be dealt a severe blow if WARC-79 sentiment runs against it.

The second problem facing the amateurs is more restricted, dealing with the 41-meter band. The band is shared, as we have indicated before, being allocated to amateur radio in this hemi-

continued on page 86

R-E's Service Clinic

Your service shop

How does it rate?

JACK DARR
SERVICE EDITOR

This column is for the service technician's problems—TV, radio, audio or industrial electronics. We answer all questions submitted by service technicians on their letterheads individually, by mail, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Avenue South, New York, NY 10003

HERE'S A DO-IT-YOURSELF TEST FOR FINDing out just how smart you really are (without letting anyone else know, even your wife). It has nothing to do with your competence as an electronics technician; that is taken for granted. The test tells you how *efficient* you are—how much you get out of each hour in your working day. If you're a one-man-gang, like so many of us, you're the only producer on the force. So, if you want to get the best results, your efficiency rating must be high. Anything that reduces your efficiency reduces your output and your income.

Efficiency involves nothing but good common sense. Like all other successful processes, it was worked out over a period of a good many years by trial and error. In other words, I learned all about this by first doing it wrong and then finding out how to do it right. In many cases, I had to try quite a few wrong ways before I found one that worked much better. As far as I know, I have made all of the possible mistakes. If I left out any, let me know and I'll try them too. This evaluation will work with electronics shops from the one-man shop on up. I can guarantee one thing from several years of experience in finally doing it right: it *will* work and it will make life easier.

To begin take a close look at the working area—the bench. Are all of the necessary and frequently-used test instruments set up so that you can reach them easily, read them and use them? If the answer is yes, add 10 points. If the answer is no—if you have to get up and move to reach an instrument used often—take off 10 points.

Now how about your most frequently used hand-tools? Are they placed on the bench where you can get them quickly when needed? Yes? Add another 10 points. If you have to move to get them, or dig them up where you dropped them after the last job, deduct 10 points. In the same category, how about the special tools? For one very good example, where's that extra long Spintite wrench you need to get the tuner out of certain TV sets very quickly? There are several of these. If you don't have any of them, take off another 10; if you do, and have them where they can be gotten quickly, add 10.

How about service data? Check the bench and the rest of the shop. Are your Sams *Photofact* folders all over the place? If you find them lying on the bench and the set for which they were pulled has been delivered some time ago, take off 10 points for each one. This applies to factory and all other data. If all data folders are properly filed except those on sets currently being worked on, add 10.

Still on the bench: Are there any repair parts *stored* on the bench, where access to them can be blocked by sets being repaired? If so, take off 10 points. If the parts are neatly stored on the side of the shop opposite the bench, where you can get them by just turning around, add 10.

Staying with the parts stock for a while, do you have a full stock (say at least two each) of all stock EIA values of resistors and capacitors filed by size and working voltage, wattage, and so on in cabinets so that you can find the size you need in the least possible time? This applies to resistors and capacitors, but could be used for tubes and transistors as well. If you do, add 10 points. If your stock is incomplete, so that you have to stop work and run all over town to find a 0.0039 μF capacitor, take off 25 points. (That'll teach you to keep up a good working stock.)

Now back to the bench itself. If this is at least 20-feet long, how many sets (radio or TV, etc.) are on it at the present? If the bench is at least 20-feet long, and it is set up so that all the test equipment used for TV is at one work-position, and the test equipment used for radio, audio, etc., is at another, add 25 points. Now comes a stinger.

How many of the sets on the bench are being worked on? If there are only two, add another 25 points. If there are *any* sets on the working surface that are waiting for parts, take off 50 points. Check to see how long each one has been there; take off 10 points for each day. All units waiting for parts should be taken out of the work area, plainly tagged, and stored in a special place. While you're at it, check the tags. If all sets in the shop have plainly written tags, with all the necessary information, add 25 points. If there are any sets without tags of any kind, take off 25 for each one.

Now let's check the overall layout of

MATHEMATICS
ELECTRONICS
ENGINEERING MATHEMATICS
ADVANCED MATHEMATICS

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay,* and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA
HOME STUDY INSTITUTE
P.O. BOX 1189
PANAMA CITY, FLA 32401

CIRCLE 34 ON FREE INFORMATION CARD

the shop. If you have a work area that includes the bench, parts and service-data storage; plus two storage areas (one for incoming sets and the other for finished jobs waiting for delivery) and a smaller area for sets awaiting parts, add 100 points.

Check the "in-shop mobility" of the work. If each set is on a wheeled cart of the same height as the bench so that one man can move it easily from storage area to work area, add another 50 points. If sets are stacked on top of each other, or chassis laid out on the floor, take off 25 points. (That should be a −50 pointer, but I'm beginning to feel sorry for you.)

One more little but handy one. If each set being worked on or awaiting parts has all of the knobs, bolts, loose parts and defective parts removed and neatly stored in a small box with the set, add 20 points. If parts are scattered on the bench, take off 20; and if parts are on the floor, take off 30.

Finally, check the record-keeping system. If your shop tags are designed so that you can get all of the data you need from them instantly, without a lot of scratch-paper bits and pieces, add another 50 points. Finished jobs awaiting pickup or delivery should have the job ticket filled out with the price, labor done, parts replaced and everything else pertaining to that job.

continued on page 84

SUPER SIGNAL SOURCE!

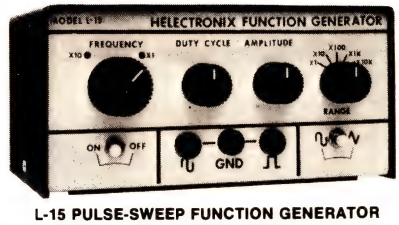

L-15 PULSE-SWEEP FUNCTION GENERATOR

\$55 KIT \$75 ASSEMBLED (+\$2.00 P&H)

FOR: Designers, Service Techs, anyone working with electronics!

FEATURES: 1Hz to 100KHz in 5 ranges, at constant amplitude • Sine and triangle adjustable to 20vp-p into 600 ohms • Sine distortion is .5% typical • Voltage controlled sweep of sine and triangle waves • TTL square wave has a fully adjustable pulse and drives 600 ohms • Frequencies of lower than 1Hz and greater than 100KHz are obtainable • short proof and guaranteed for 1 full year • Small, only 3″ H x 6¼″ W x 4″ D • State-of-the-art design!

DEALER INQUIRIES INVITED

HELECTRONIX
8100 St. Clair Ave.
N. Hollywood, CA 91605
(213) 767-5624

CIRCLE 61 ON FREE INFORMATION CARD

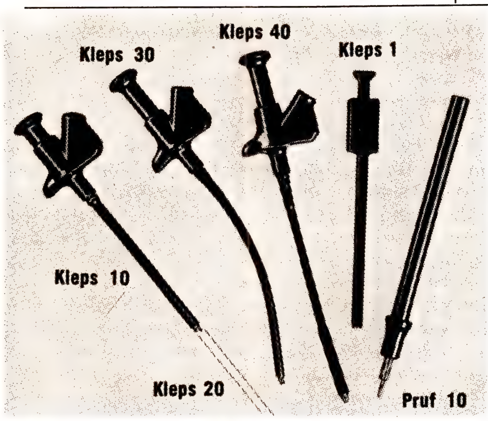

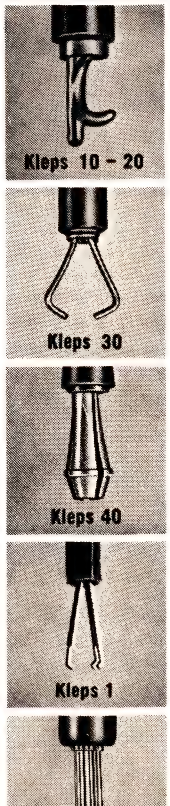

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾″ long. **\$1.39**

Kleps 20. Same, but 7″ long. **\$1.49**

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6″ long. **\$1.79**

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼″ long. **\$2.59**

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4½″ long. **\$ .99**

Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½″ long. **\$ .89**

All in red or black - specify. (Add 50¢ postage and handling).
Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.
131 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 35 ON FREE INFORMATION CARD

SYSTEM 5000

The New Programmable Clock Kit from Digital Concepts. \$29.95

SYSTEM 5000 is the programmable clock kit that makes kit-building a new experience. The system has been designed to meet a variety of particular requirements and tastes, and programming techniques are used to create a truly individualized timepiece. Numerous functions and features are provided for maximum flexibility and adaptability, and any or all can be used to construct many different types of time-keeping and timing devices.

SYSTEM 5000 is not a simple LED time of day clock, but a full feature digital timing system. Programming is accomplished by connecting the appropriate jumpers and switches to produce the desired system configuration. Complete assembly and programming manuals are included.

SYSTEM 5000 has a fluorescent readout panel with four 0.5″ numerals that brighten and dim automatically according to the ambient light. This unique digital display provides optimum readability at all times from almost any viewing angle.

SYSTEM 5000 can be built as a desk clock, alarm clock, calendar clock, or all of these in one full-feature timepiece. The Duplicate Time Register can monitor elapsed time or another Time Zone such as GMT. A ten minute "ID" reminder capability is included for Radio Station use. A quartz time base is available for high precision, stability and uninterrupted operation if the AC line should fail.

SYSTEM 5000 can automatically control AC or DC accessories up to 700 Watts by adding the optional relay. Plug in your radio or stereo to construct a full-function clock radio that puts you to sleep with gentle music and wakes you to music, a tone, or both. The system will also control TV's, small appliances, or other accessories.

SYSTEM 5000 can be used to construct timers for a variety of applications. It is ideal for automatic process timers and controllers in laboratories, workshops, and engineering facilities.

SYSTEM 5000 includes all components, speaker, two time setting switches, and comprehensive instruction and programming manuals. Case & switches for programming additional functions are not included but available as options. **\$29.95**

FEATURES AND SPECIFICATIONS

Timekeeping Functions	Display	General
• Time of Day Register	• Bright 4-Digit Fluorescent Panel	• Forward or Reverse Time Setting
• Duplicate Time Register	• Automatic Brightness Circuit	• Reset and Count Inhibit Controls
• True 24 Hour Alarm	• 12 or 24 Hour Display Format	• Seconds Display
• Duplicate 24 Hour Alarm	• PM and Power Failure Indication	• Single 9 Volt Battery Backup
• 10 Minute Snooze on Alarms	• 1 Hz Activity Indicator	• 700 Watt Relay Optional
• True Four Year Calendar	• Power-On Clear	• 50 or 60 Hz, 117Vac, 3 Watts
• One Hour Down Counter	• Direct Drive Eliminates all RFI	• 1.5″H. x 4″W. x 4″D.

RELAY OPTION – \$4.00
Includes 700 watt relay and all interface components. Will control AC or DC accessories such as appliances, stereos, etc.

QUARTZ TIME BASE OPTION – \$6.95
Generates precise 60 Hz. buffered output with exceptional stability, reliability, and accuracy. Direct interface to System 5000 and most other clocks. Includes Quartz Crystal, IC Divider, trimmer, compact G-10 board, all necessary components, instructions, and installation directions.

SWITCH OPTION – \$3.75
Contains 4 black SPST pushbuttons, 2 black DPDT pushbuttons, and 2 black SPST slide switches. Programs all major features.

CASE OPTION – \$11.00
This deluxe, hand finished solid walnut (3/8″) cabinet forms an ideal housing for the completed system. Includes rear panel and standard blue faceplate; extra faceplates (blue or green) are \$1.00 ea. Cabinet dimensions – 5¾″ x 5¾″ x 3″.

ORDER THIS EXCITING KIT TODAY AND PUT ELECTRONIC TIMEKEEPING TO WORK FOR YOU!

Send your check or money order today for fast delivery. Add 5% to total order to cover shipping and insurance. N.J. residents must also add 5% sales tax.

master charge — BANKAMERICARD

digital concepts
Digital Concepts Corporation • 247 Route 46
Saddle Brook, New Jersey 07662 • (201) 845 7101

CIRCLE 51 ON FREE INFORMATION CARD

EVERY PROJECT IN THIS BOOK IS ANOTHER REASON TO OWN CSC'S QT SOCKETS AND BUS STRIPS.

With QT solderless breadboarding sockets and bus strips, you can build twice the projects in half the time. Because making connections or circuit changes is as fast as pushing in—or pulling out—component leads. No special clips or jumpers required, either.

When you're building circuits just for the fun of it, you can take them apart in minutes—not hours. So you save money by re-using parts, while eliminating heat damage to expensive components. Interlocking QT Sockets and Bus Strips are infinitely expandable, too: start small and "grow" breadboards as large as you wish.

For as little as $3.00, you can get a lot more out of your time in electronics—so why not treat yourself to a QT Socket today?

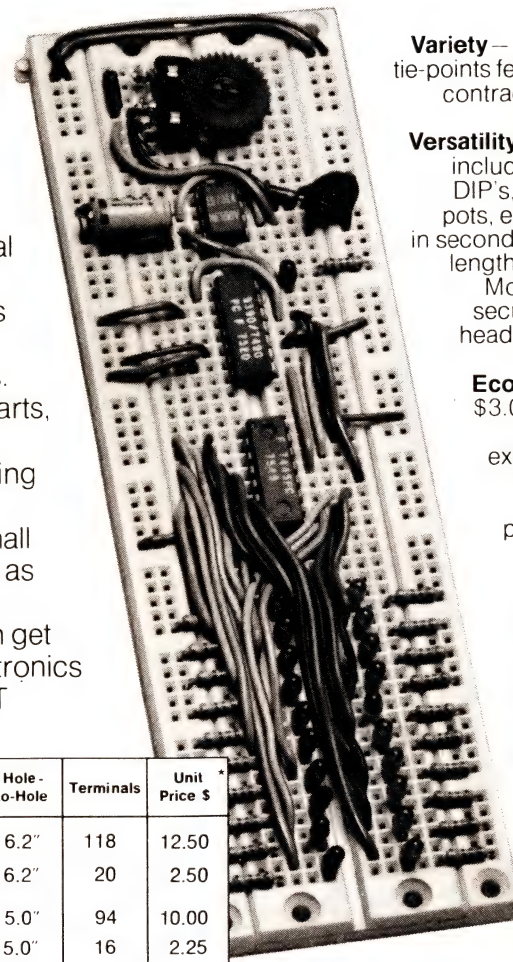

Variety—10 models from 70 to 590 solderless tie-points feature snap/lock design to expand or contract your breadboard to fit every circuit and budget requirement.

Versatility—Use with virtually all types of parts, including resistors, capacitors, transistors, DIP's, TO-5's, LED's, transformers, relays, pots, etc. Most plug-in directly and instantly, in seconds. No special jumpers required—just lengths of #22-30 AWG solid hookup wire. Molded-in holes let you mount QT units securely on any flat surface with 4-40 flat head screws, or 6-32 self-tapping screws, from behind panel.

Economy—Sockets are priced as low as $3.00.* Save more money by eliminating heat and mechanical damage to expensive parts, re-using components.

Speed—For fast circuit layouts, QT Sockets have 5 interconnecting tie-points per terminal; Bus Strips feature 2 separate rows of interconnecting terminals. Both connect and disconnect easily, without damage to socket or parts.

Visibility—All parts are instantly and easily visible and accessible, for quick signal tracing, circuit analysis and diagramming.

Durability—Higher-temperature sockets with abrasion-resistant, glass-filled plastic, rated better than 100°C. Screw-down-and-interlocked design provides high mechanical strength.

Reliability—Ruggedly designed to professional engineering standards, for heavy day-in, day-out use. Non-corrosive prestressed nickel-silver contacts insure more secure mechanical and electrical connections. Vinyl backing prevents shorting when mounted on conductive surfaces.

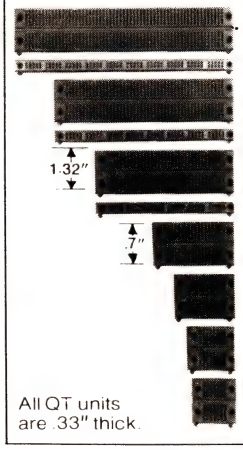

	Length	Hole-to-Hole	Terminals	Unit Price $*
QT-59S	6.5"	6.2"	118	12.50
QT-59B	6.5"	6.2"	20	2.50
QT-47S	5.3"	5.0"	94	10.00
QT-47B	5.3"	5.0"	16	2.25
QT-35S	4.1"	3.8"	70	8.50
QT-35B	4.1"	3.8"	12	2.00
QT-18S	2.4"	2.1"	36	4.75
QT-12S	1.8"	1.5"	24	3.75
QT-8S	1.4"	1.1"	16	3.25
QT-7S	1.3"	1.0"	14	3.00

CONTINENTAL SPECIALTIES CORPORATION

See your CSC dealer or call 203-624-3103 (East Coast) or 415-421-8872 (West Coast) major credit cards accepted.

44 Kendall Street, Box 1942
New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227
West Coast office: Box 7809, San Francisco, CA 94119 • 415-421-8872
TWX: 910-372-7992 • Mexico: Elpro, S.A., Mexico City 5-23-30-04
Canada: Len Finkler Ltd., Ontario

*Manufacturer's suggested list • Prices and specifications subject to change without notice.

© 1976, Continental Specialties Corporation

CIRCLE 36 ON FREE INFORMATION CARD

SERVICE CLINIC
continued from page 82

Here's one more. If you have a habit of getting into long discussions with customers (or friends or passers-by, etc.) and spending half an hour or more telling jokes, discussing competitors, tough-dog service jobs, the state of the economy, etc., etc., take off 100 points! Save this for service meetings and coffee-breaks.

These are simple things. It does not take up much time to set up your shop so that you get the maximum return from the time you spend in it. It does take quite a lot of will-power. I can vouch for this personally. It's so easy to be sloppy. However, an efficient shop is a heck of a lot easier to work in, and you'll get a much greater return for the *time* you spend on each job. When you find an area where efficiency can be improved, do it; stop and fix it just as if it was a flat tire (which it is, when you think of it).

The plus and minus "points" are more of a gag than anything else. However, if you will give your shop this test and keep a scratch pad score, it can help. If you come out with a pretty good score on the plus side, good for you. If you come out with a score that is all on the minus side, boy are you sloppy!

Be just as honest in evaluating yourself as you are in analyzing a case of TV trouble. It'll pay off in increased income, reputation and customer satisfaction. (They get their sets back faster.) **R-E**

reader questions

TRANSISTOR VOLTAGES

After an arc in the focus circuit of this solid-state set, I'm having a lot of other problems. There is a raster, but it's blank. The collector voltage on the first video amplifier is zero and the DC voltages on the AGC transistors are all the same. My ohmmeter shows a good junction on all of them. The DC voltage on both sides of the video detector are also the same.—B.C., Thurmont, MD.

After an arc, you can have all kinds of problems in solid-state circuitry, often in places far from the location of the arc. Here are some hints: A transistor, like your first video transistor, with the collector going to ground through a resistor, should have some DC voltage if it is conducting. No voltage and the transistor is cut off or open.

DC voltages the same on all three elements of a transistor usually means

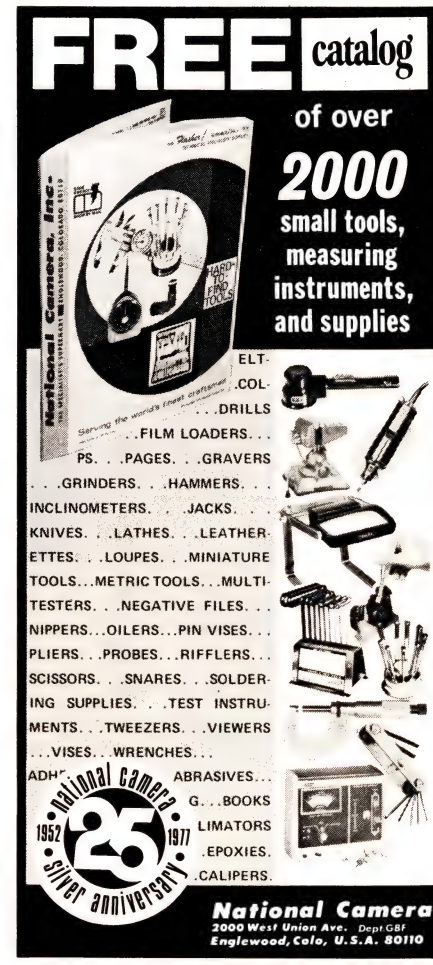

CIRCLE 6 ON FREE INFORMATION CARD

that it is shorted; you may be reading the junction of the gate diode that is shunted across it—same for the video detector diode. The cure is the same for all; take them OUT of the circuit and repeat the checks.

12AX7 TUBES BLOW OUT

The owner brought this Pilot 610 amplifier in saying that he'd replaced both 12AX7 driver tubes. Within a few minutes, the new tubes flashed up and went out. These tubes use a DC heater voltage. I checked the circuitry; it didn't seem that the voltage went up, it actually dropped a little. This problem is in both the left- and right-channel driver tubes. I don't understand it. Any advice would be appreciated.—R.Z., Glenside, PA.

To put it mildly, this is an odd circuit. The use of DC heater voltages on preamp and driver tubes to avoid hum isn't uncommon, but this is the first time I've ever seen them get this DC voltage from the cathode circuit of the output tubes. (See diagram.) Never afraid to make obvious statements, I'd say that the reason for the burnout was that too much current was being drawn through the tubes. Since the source of this current is the (common) cathodes of the ECL86 tubes, I would check the bias voltages on them as well as checking all four of the output tubes for possible internal shorts.

There are two 1800-ohm resistors shunted across the 12AX7 heaters. Be sure that these are OK. It would be a very good idea to break this circuit and hook in a DC milliammeter (on the 0–1000 mA scale). Now plug the amplifier into a variable-voltage transformer and bring the line voltage up slowly. Normal

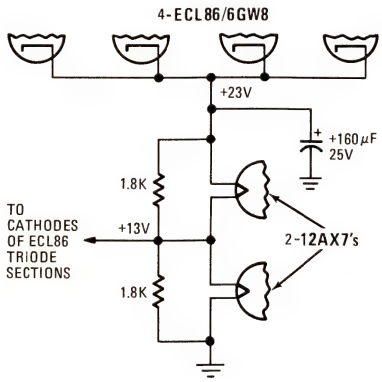

current for the 12AX7 heaters is 150 mA. Since they are in series, the current would be the same in each. Watch the current; if it goes above 150 mA with the line voltage well below normal, the fault is still there.

Incidentally, the Mullard data sheet shows the ECL86 as a 9-watt output type. Maximum plate currents for both sections is only 42.7 mA. They are being pushed pretty hard with +320 volts on the plate and screen; this might have caused an internal short. **R-E**

✱ SAVE GAS! SAVE on TUNE-UPS!
MODERNIZE and Bring Your Car "UP-TO-DATE" with the MOST EFFICIENT Ignition ever invented!

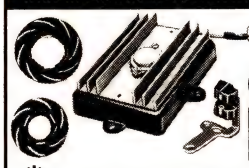

ALLISON XR-700

✱ The "XR-700" is a COMPLETELY NEW Ignition System that replaces the inefficient Breaker-Points and Condensor with a highly RELIABLE, Invisible "Infra-red" Light-Beam which CONTROLS the Latest design Solid-State POWER MODULE. This new "Patented" Invention produces the HIGHEST ENERGY, Longest Duration Spark of ANY Ignition System manufactured TODAY!

✱ CUSTOMERS REPORT: "THE XR-700 MORE THAN PAYS FOR ITSELF ...and KEEPS ON SAVING MONEY with...
★ INCREASED "GAS-MILEAGE" up to 30%!
★ ELIMINATING COSTLY "TUNE-UPS!"
★ IMPROVED ENGINE PERFORMANCE!
★ QUICKER STARTING IN ANY WEATHER!
★ FASTER ACCELERATION...SMOOTHER RUNNING!
★ PLUGS LAST UP TO 4-TIMES and LONGER!"

✱ THE XR-700 has NO moving parts to wear out...never needs adjustment! Engineered to OUTLAST Your Car...So RELIABLE... So PERFECTED...that we give you a LIFETIME WARRANTY... "FREE Repair or Replacement" for as long as you OWN the Unit... even if you change Cars, we will supply the necessary Parts FREE.

✱ FITS ALL ENGINES...Domestic or Foreign...4, 6 or 8-Cylinder
✱ EASY INSTALLATION...Completely Factory ASSEMBLED!

Thousands sold at $59.95
✱ NOW...ONLY.. $39.95 (Cal. Res. add Tax)
THAT'S EVERYTHING..INCLUDING POSTAGE & INSURANCE

✱ SAVE! ORDER FACTORY DIRECT!
Send Check or M/O, State Car Make, Year and No. of Cylinders.
✱ MASTERCHARGE or BANKAMERICARD Cardholders
Order by TOLL FREE PHONE (800) 423-6525 Ext. 3

CALL or WRITE for FREE BROCHURE
✱ America's Oldest and Largest Manufacturer of Opto-Electronic Ignition Systems. ©
ALLISON AUTOMOTIVE CO.
1267– RL, East EDNA PL., COVINA, CAL. 91722

CIRCLE 1 ON FREE INFORMATION CARD

Use this versatile frequency counter when accuracy counts.

WD-752A
$255.00

Exceptional accuracy and sensible features make our new wide-range frequency counter the ideal choice for checking out audio, video, CB, ham radio and other communications equipment.

- Wide range—10Hz to 60MHz
- Precise 10.000MHz crystal-controlled time base for ±0.1ppm stability
- 1KHz audible tone for SSB carrier frequency measurement
- Selectable input sensitivity (for noise rejection)—10 or 100mV
- 6-digit bright LED readout
- Indicators for signal, overflow, and range
- Small and compact; ac operated

See it at your VIZ distributor

VIZ Test Instruments Group
of VIZ Mfg. Co.
335 E. Price St., Philadelphia, Pa. 19144

Formerly EICO Instruments

© VIZ 6644

CIRCLE 41 ON FREE INFORMATION CARD

CONFUSED BY ELECTRONIC IGNITION CLAIMS ?

The PROOF is in PERFORMANCE!

Amazing MEGASPARK, the advanced-design Opto-Electronic Breakerless Ignition System, FITS ANY CAR! Replaces points and condenser — gives longer spark plug life. Increases performance, mileage and driving satisfaction while cutting fuel and maintenance costs dramatically. Learn the facts and don't settle for less than the best.
Models from $29.50 to $64.50

The only unit that gives you all these features:

- LIFETIME WARRANTY
- DIFFERENTIAL AMPLIFIER CIRCUITRY
- FULL INTERNAL VOLTAGE REGULATION
- AUTOMATIC OVERCURRENT PROTECTION

Rush name and address for FREE information package including catalog and discount offer. Or call toll-free 24-hours 800-648-4711, Ext. 22.

MEGASPARK™
by Ignition Systems Inc.
2547 8th Street
Berkeley, CA 94710
(415) 845-3584

CIRCLE 18 ON FREE INFORMATION CARD

sphere, and to broadcasting in Europe, Asia, and Africa. Many European communicators with whom I have spoken feel that 41 meters should be allocated exclusively to broadcasting on a worldwide basis, and they can be expected to fight to accomplish this at WARC-79. As previously indicated, the United States could reserve on such an act, but the best that could be hoped for would be continued amateur use in this country but with increasing levels of interference as Europeans use 41-meter frequencies to transmit to the Americas. Hopefully, a compromise solution can be found, in which both the broadcasters and amateurs are assigned 41-meter channels exclusively, at the expense of the fixed services. Such an arrangement could result in the assignment of 6800–7300 kHz to the broadcasters, as an example.

In addition to expanded and exclusive use of 41 meters, the amateurs are asking for three new bands—10, 18, and 24 MHz—to accommodate their growing needs. This request is certain to bring the requirements of the broadcasters, with an estimated quarter of a billion listeners worldwide, into conflict with those of the less than one million

Our whole family helped assemble this wonderful Schober Organ... and now we all play it!

Talk about real *family* fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son—he's only 12—installed the transistors. Me? I was the quality control inspector—they let me do the final wiring.

Our completed Schober Organ compares favorably with a "ready-made" one costing twice as much! (The five models range from $650 to $2850.)

Just send the coupon for the fascinating Schober color catalog (or enclose $1 for a 12-inch LP record that lets you hear as well as see Schober quality).

The *Schober* Organ Corp., Dept. RE-162
43 West 61st Street, New York, N.Y. 10023
☐ Please send me Schober Organ Catalog.
☐ Enclosed please find $1.00 for 12-inch L.P. record of Schober Organ music.

NAME
ADDRESS
CITY STATE ZIP

CIRCLE 48 ON FREE INFORMATION CARD

PROFESSIONAL AIDS
SHELF FILES
KEEP MAGAZINES, CATALOGS, MANUALS, JOURNALS, DIRECTORIES AND REPORTS NEAT, ORGANIZED

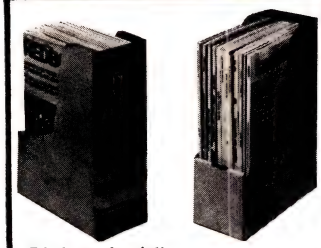

Eliminate the clutter of loose magazines, catalogs, etc. Find what you want, when you want it by utilizing these handy shelf or desk top files. Available in 6 sizes from Reader's Digest to newspaper size. Constructed of heavy duty fibreboard. Attractive blue front panel. Adhesive identification labels included.

STORE ON SHELVES

ORGANIZE YOUR DESK

Popular letter size: 11½x9x3¾
10 for $15.89
25 for $28.97 Other sizes available
Shipped pre-paid Canada, add $1.00 Request Catalog

PROFESSIONAL AIDS CO.
1 S. WACKER DR., SUITE 477R
CHICAGO, ILL. 60606

CIRCLE 65 ON FREE INFORMATION CARD

DESK TOP INSTANT DATA SYSTEM
FIND THOUSANDS OF FACTS AT COMPUTER SPEED

NO FILING OR REFILING EVER! | COMPACT. EASY-TO-DO

The modern rapid way to locate countless facts at your desk without thumbing thru files. Specially coded cards are used to record any information you want close at hand — technical data, formulas, abstracts, case hist., bibliographies. Obtain just what you need in seconds—any group separates automatically simply by inserting a rod. No slow inefficient cross filing . . . no mechanical parts . . . no special training . . . minimum set up time.

30 DAY MONEY BACK GUARANTEE

ONLY
Basic package $38.00 POSTPAID
(200 cards, hand notcher, sorting rods, instructions).
Additional cards: 1000 for $57.00 postpaid. Sample Card Available

FREE LITERATURE ON REQUEST

Information Retrieval System, Div. of
PROFESSIONAL AIDS CO.
1 S. WACKER DR., SUITE 577R
CHICAGO, ILL. 60606

CIRCLE 66 ON FREE INFORMATION CARD

Convert DC battery to AC
...power TV, CB, PA, tools, etc.
from car, boat, trailer, plane

Low cost Transistorized Inverter TI-250B

Convert 12 VDC to 117 VAC 250 watt output

Protects battery and unit – relay insures 100% reverse polarity.
Protects appliance and unit against overloads if output is shorted or overloaded.
Inverter automatically turns off and turns back on when short is removed.
Warns of low battery charge – indicator light signals low battery charge, shorted output or overload.
Instant starting of motor, lights, equipment with "Start" switch.
Less battery drain – even at high output loads.
Includes leads for battery hook-up.
Stocked at your distributor.
Request FREE Bulletin TI-B and Prices

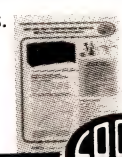

EPSCO

EPSCO, Inc., 920-R Westwood, Addison, IL 60101

CIRCLE 42 ON FREE INFORMATION CARD

amateurs in the world.

Amateurs and CB'ers

The United States will strongly support amateur radio at WARC-79. In addition to the great contributions made by the group, economic and political considerations are also a factor. The electronics industry provides equipment and supplies for some 300,000 American hams, giving this industry a substantial boost. The amateurs in this country are well organized and represent a significant voting bloc–factors that assure continued U.S. support of the group.

Although the survival of amateur radio is not at stake, there appears to be little likelihood that the amateurs will obtain any additional spectrum space. Furthermore, the loss of the 41-meter band is a possibility, and this is a contingency the amateurs will have to be prepared to cope with in Geneva.

On the other hand, Citizens-band radio is safe and will not be affected by WARC-79, unless the portion of the band (26 and 27 MHz) currently allocated to the fixed and mobile services are unexpectedly reassigned. This is highly improbable. Furthermore, the manner in which CB radio has mushroomed has made it a major economic and political factor, even more so than amateur radio. It seems inconceivable, therefore, that the frequencies currently allocated by the FCC to CB radio will be affected by WARC-79. **R-E**

R-E TESTS HEATH

continued from page 59

medium output cartridges would ever deliver greater transient peaks than 100 mV even when playing highly modulated discs and so this does not constitute a limitation in performance. On the other hand, it was virtually impossible to overload the high-level input stages of the unit as we ran out of voltage from our signal source at an input level of 10 volts with still no evidence of first-stage

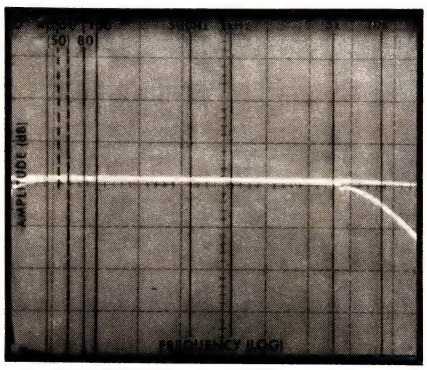

4

distortion. The subsonic filter action is barely visible in our spectrum analyzer scope photo of Fig. 4 (sweep extends from 20 Hz to 20 kHz whereas the subsonic filter has a –3-dB point of 15 Hz). However, the action of the high-cut filter is clearly visible and is seen to have the 12 dB-per-octave slope and the 7-kHz rolloff or –3-dB point, as claimed. The –70-dB signal-to-noise ratio in phono is referred to the actual input sensitivity of 2.0 mV and is an unweighted measurement–not as high as measured for some of the new superpriced preamplifiers but high enough so that record listening is not marred by audible noise, or hum.

Our overall product analysis and summary comments for the Heath *model AP-1615* are contained in Table II. Whether you choose to build a matching power amplifier from Heath (they suggest their *model AA-1640,* a powerful 200 watt-per-channel unit that sells in kit form for $449.95 less meters, $499.95 with power meters) or plan to use any other high-quality ready-made power amplifier, the Heath *model AP-1615* is certainly worth its modest price–even if you figure in your own labor rate. **R-E**

Red Cross.
The Good Neighbor.

sound power

You can improve the sound of any CB transceiver—23 or 40 channel—with a "KRIKET®" external speaker. AFS' acoustic design provides greater voice intelligibility, overcomes transceiver and road noise.

Lets you hear what's on the air more clearly than you believed possible.

Available at CB dealers everywhere.

afs®/Kriket® Speakers

World Wide Headquarters
Acoustic Fiber Sound Systems, Inc.
7999 Knue Road Suite 116
Indianapolis, IN 46250
(317) 842-0620

Exclusive Canadian Distributor
Persona Communications L.T.D.
1149 Pioneer Road
Burlington Ontario, Canada
(416) 629-5373

All AFS®/KRIKET® speakers are manufactured in the U.S.A. using American materials and craftsmen.

Copyright 1976 Acoustic Fiber Sound Systems, Inc.

new products

More information on new products is available from the manufacturers of items identified by a Free Information number. Free Information Card follows page 98.

DIGITAL MULTIMETER, *model LM-40,* is a full 4-digit DMM. Sensitivity for DC and AC volts is as great as 100 mV, and for resistance, sensitivity is 100 milliohms. DC voltage accuracy is 0.1%. AC and DC voltage ranges of 1, 10, 100 and 1000 volts are provided. Resistance ranges include 1, 10, 100, 1000 and 10,000 kilohms. Fuseless protection on ohms and optional current shunts are available for AC and DC current measurements providing ranges of 0.1, 1, 10, 100, 1000 and 2000 milliamperes. The instrument comes complete with test leads, rechargeable batteries and a charger, and features automatic zeroing. The unit measures 1.9 × 2.7 × 4 inches. Power consumption is less than 3 watts. Priced at $190.00.—**Non-Linear Systems, Inc.,** P.O. Box N, Del Mar, CA 92014.

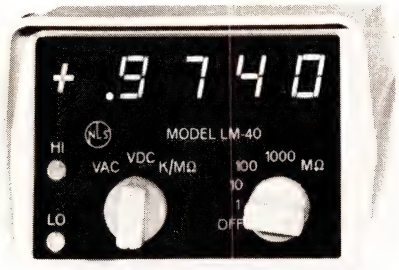

CIRCLE 76 ON FREE INFORMATION CARD

SERVICE KIT, *model 99SMW,* is a 26-piece tool kit for electronics technicians, featuring a wire stripper/cutter and 25-watt soldering iron. The tool set fits into a roll-up, plastic-coated canvas case and also includes long nose and diagonal cutting pliers, adjustable wrench, and an assortment of the *Series 99* quick-change regular and stubby blade screw and nut drivers, plus both regular and stubby handles, extension blade and reamer.—**Weller-Xcelite Electronics Div.,** The Cooper Group, Apex, NC 27502.

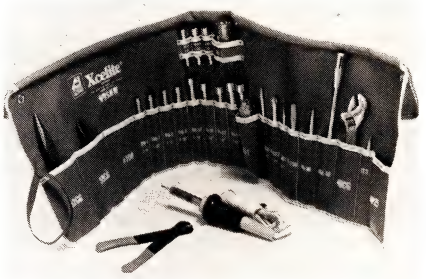

CIRCLE 77 ON FREE INFORMATION CARD

8K STATIC MEMORY BOARD. Altair and Imsai compatable. Access time of 500 ns maximum. Current required, less than 200 mA/1024 words maximum. Memory chip is AMD 91L02 APC or equivalent. Voltage supply: +5 volts to +10 volts. Address select: DIP switch accessable from top of board—no need to remove board to

EIGHT INSTRUMENTS IN ONE

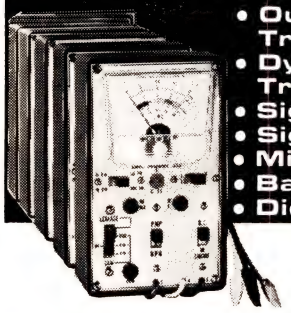

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested—**$28.84**
Easy-to-Assemble Kit—**$19.21**

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N.Y.

Send me **FREE catalog of the complete** value-packed **EMC line, and name of** local distributor.

NAME_____ RE-5

ADDRESS_____

CITY_____ ZONE____ STATE____

EMC
ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012

Interested in HAM Radio?

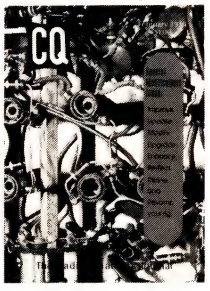

Then your magazine should be CQ, the country's oldest and largest independent ham monthly. **CQ** is aimed at the operator; it has all the latest info on DXing, contests, propagation, and much more. You'll find Bill Orr on antennas, Irwin Math on gadgets and Herb Brier on dope for the novice.

CQ is where it's at in ham radio today. And we'll even make it easy for you to save extra bucks by using the handy coupon below. Regularly $1.25 a copy or $7.50 for a year, it will cost **just $5.95 for a full twelve issues** with the discount coupon.

COWAN PUBLISHING CORP.
14 Vanderventer Ave.
Port Washington, N.Y. 11050

SPECIAL DISCOUNT COUPON

Start my subscription with the _____ issue.

☐ CQ 12 issues $5.95

Name_____

Address_____

City_____

State _____ Zip _____

(Allow 6 to 8 weeks for delivery of first issue)

relocate. Power regulators: 4 each 7805. Wait states: none. CPU runs at maximum speed.

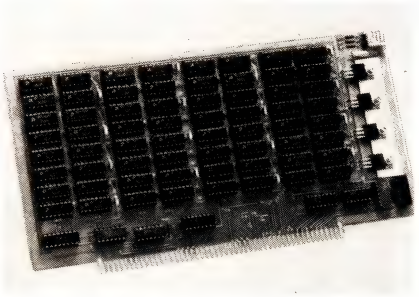

Buffered address and data out lines buffer disable line for transparent loader. Priced at $239.00 for kit; $335.00 assembled.—**Vector Graphic Inc.,** P.O. Box 4785, Thousand Oaks, CA 91359.

CIRCLE 78 ON FREE INFORMATION CARD

FUNCTION GENERATOR, *model 12,* has external frequency control VCO, DC to 1 MHz.

Remote frequency-shift keying, frequency modulation, remote tone bursts, simultaneous sine, triangle and squarewaves. Has a selectable function output—continuously adjustable amplitude and DC offset. 1 Hz to 1 MHz. Priced at $79.95 for the kit and $124.95 for wired.—**A E Corp.,** 65 Wellesley Ave., Needham, MA 02194.

CIRCLE 91 ON FREE INFORMATION CARD

ELECTRICAL OUTLET STRIP, *SGL Power Master,* instantly multiplies the number of available electrical outlets at any given location. Handy

and ready to use; just plug in. Saves hours and effort of wiring a work area. Especially designed for the handyman's workshop, it can be used in any part of the home, apartment or garage.

Put Professional Knowledge and a

COLLEGE DEGREE

in your Electronics Career through

HOME STUDY

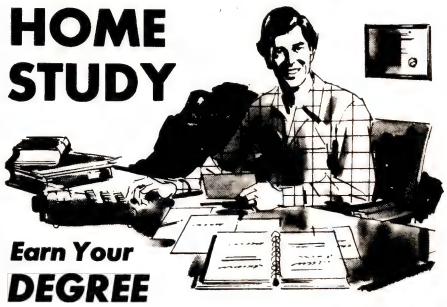

Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our *free* bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin R-77.*

Grantham College of Engineering
2000 Stoner Avenue
P. O. Box 25992
Los Angeles, CA 90025

Worldwide Career Training thru Home Study

CIRCLE 13 ON FREE INFORMATION CARD

ONE RIG DOES IT ALL!

Tube and Solid State

33KV

THE UNIVERSAL
PJS-298

33KV LEADED GLASS 19" CRT
EIA recommended to protect against dangerous X-radiation

BUILT-IN SPEAKERS
Easy audio checking

40 KV METER
50aU sensitivity monitoring

FRONT CONNECTORS
Convenient cable plug-in

OBSOLETE PROOF
Plug in modules for up-dating

A MUST FOR TODAY'S SERVICING

ACCESSORIES INCLUDE:

- CRT 90° Extension
- Yoke Extension
- Transverter
- Convergence Load
- Universal Yoke
- Convergence Assembly
- Blue Lateral Assembly
- Anode Extension

SOLD THROUGH DISTRIBUTORS ONLY

~~$298.98 VALUE~~

SPECIAL INTRODUCTORY OFFER

$229.95

COMPLETE WITH CRT

TeleMatic
2849 FULTON ST., BROOKLYN, NY 11207
PHONE: (212) 827-1500

PLEASE SEND ME MORE INFORMATION 5-77

NAME_____

ADDRESS_____

CITY_____ STATE_____ ZIP_____

CIRCLE 44 ON FREE INFORMATION CARD

VIBRA-JET®

TURNS TUN-O-WASH INTO A

PULSATING...VIBRATING... "CLEANING MACHINE"

You have never seen anything like Vibra-Jet, our new patent pending aerosol pulsating device. Just plug it into a can of Tun-O-Wash and you get strong vibrational solvent impacts that instantly penetrate heavy grease, gunk and baked-on contaminants. Vibra-Jet action even washes away dirt on horizontal surfaces . . . makes Tun-O-Wash more effective, leaving tuner parts and controls "vibrantly clean."

Vibra-Jet is made of strong durable polyurethane construction. Works in all positions and comes complete with 26 in. hose and 12 in. probe for hard-to-reach parts.

FREE! FREE! FREE!

FOR A LIMITED TIME ONLY, Vibra-Jet will be offered free with the purchase of 2 cans of Tun-O-Wash or Super Tun-O-Wash.

Pick up our "Cleaning Machine" . . . it will be the best time saving investment you've ever made.

Available at participating Chemtronics distributors.

CHEMTRONICS INCORPORATED
45 HOFFMAN AVE., HAUPPAUGE, N.Y. 11787 • (516) 582-3322

Our business is improving yours!

CIRCLE 30 ON FREE INFORMATION CARD

For faster service

USE ZIP CODE on all mail

1 out of 2 who have it don't know it...

Do you?

21 million Americans have high blood pressure. But 50 percent of those who have it, don't know it.

When blood pressure goes higher than it should, and stays high, it sets the stage for heart attack or stroke.

Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association

Available in two lengths and from three to eight outlets, the strip features a 15-ampere circuit breaker that shuts off power on overloads or short circuits. All models include both mechanical and electrical grounding, "U"-grounded outlets, 6-ft 3-wire jacketed power cord and a 15-amp, 125-volt rating. Most models available with master switch and pilot light.—**SGL Waber Electric,** 330 Harvard Ave., Westville, NJ 08093.

CIRCLE 80 ON FREE INFORMATION CARD

MAGNETIC CB RADIO MOUNT is especially designed for two-way communications equipment. The *"Easy Mount"* uses three permanent magnets to make positive contact, assuring maximum signal transfer with perfect VSWR match. The unit can be installed under the dash or on the transmission hump. All necessary hardware and instructions are included. Additional optional top sections permit the user to transfer the transceiver from vehicle to vehicle or to a boat, trailer, office, or home. Weight, 1.25 pounds; Profile, $1\frac{1}{8}$ inch; Mounting Area, $4\frac{3}{8}$

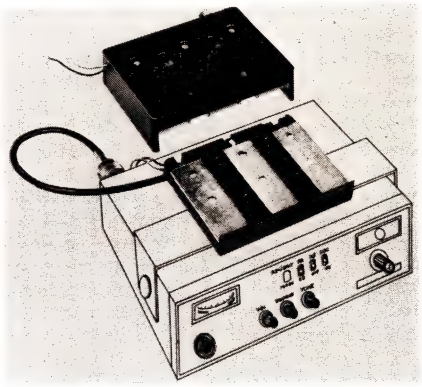

Use Quick-Wedge to install a bus, connect a motor, mount a p.c. board, cinch up a connector

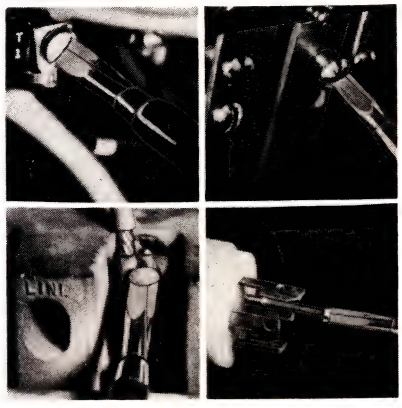

They do all that ordinary screwdrivers do, PLUS they hold and start the screw

QUICK-WEDGE 17 sizes

Screw-holding screwdrivers

Unconditionally guaranteed.

BUY A SET TODAY

See your dealer or write to:

Kedman Company, P.O. Box 25667, Salt Lake City, Utah 84125

© Copyright 1977

CIRCLE 16 ON FREE INFORMATION CARD

inches wide by 3¼ inches deep.—**Cornell-Dubilier Electronics,** 150 Avenue L, Newark, NJ 07101.

CIRCLE 79 ON FREE INFORMATION CARD

WIRE-WRAPPING KIT, *model WK-2-B,* includes wire-wrapping tool *WSU-30* that wraps and unwraps 30 AWG wire on .025-inch square pins,

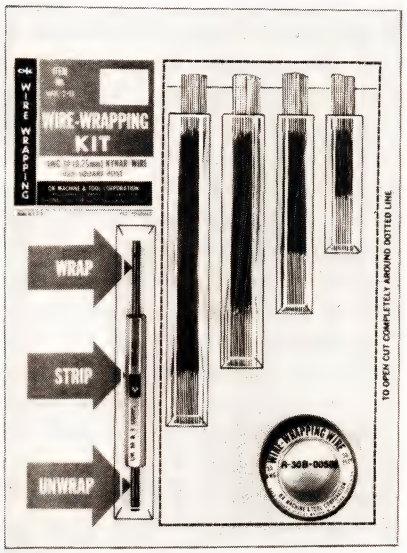

it also strips AWG wire, using handy built-in stripper. The wire is insulated silver-plated copper. Supplied in the kit are a 50-foot roll plus precut and stripped wire in insulated lengths from 1 to 4 inches, stripped 1 inch on each end. Available with blue wire as *model WK-2B,* white wire as *WK-2W,* yellow wire as *WK-2Y,* and red wire as *WK-2R.*—**OK Machine and Tool Corp.,** 3455 Conner Street, Bronx, NY 10475.

CIRCLE 82 ON FREE INFORMATION CARD

CB/RF GENERATOR, *model 256,* is designed for 40-channel transceivers. Five-band frequency tuning covers Channels 1 through 40 on an expanded tuning range for easy, precise channel selection. Frequencies of 100 kHz through 16 MHz are covered on the other four bands to provide all IF requirements including: 455 kHz, 10.7 MHz, and any other, current or future. A calibrated/attenuated output control provides RF signal output of 100,000 μV down to less than 1 μV for receiver sensitivity checks. The attenuated output is variable in 20-dB steps and by a 20-dB continuously-variable control calibrated in microvolts. Internal modulation at a

frequency of 1 kHz is variable from 0 to 100%, calibrated at 30%. Priced at $199.00—**Hickok Electrical Instrument Co.,** 10514 Dupont Ave., Cleveland, OH 44108.

CIRCLE 83 ON FREE INFORMATION CARD

DVM KIT
CONVERTIBLE INTO MULTIMETER

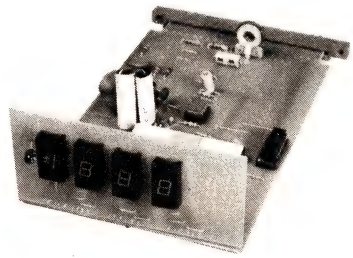

FEATURES • BASIC 2 RANGE DVM ACCURATE TO 1%. CIRCUITS FOR ADDITIONAL VOLTAGE RANGES, OHMS, D.C. CURRENT, AND A.C. VOLTS CAN BE ADDED. PARTS MOUNT ON EDGE CARD CONNECTOR P.C. BOARD. DISPLAY BOARD HAS EASY TO READ ⅓" LED'S AND CAN BE REMOTE MOUNTED.

BASIC D.V.M. KIT $39.90

Send Check Or Money Order. Add $1 for Postage and Handling in U.S. N.J. Residents Add 5% Tax.

J. B. Electronics Inc.
Box 321
Short Hills, N.J. 07078

A "bestseller" you'll never put down.

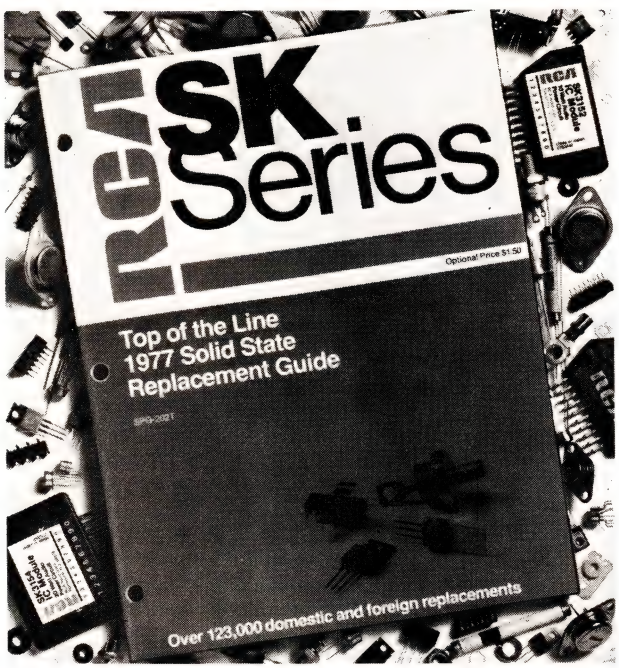

It's RCA's all new 1977 "Top of the Line" SK Series Replacement Guide. The most comprehensive list to date of transistors, rectifiers, thyristors and integrated circuits — 381 RCA types, including 68 brand new, that will replace 123,000 domestic or foreign semiconductors in entertainment and industrial equipment. The 68 new types have enabled us to increase our replacement capability by over 11,000 additional industry devices.

You can't afford to be without it. The 1977 Replacement Guide is a complete, accurate information source for your Solid State replacement needs. The book represents thousands of hours of engineering know-how. Keep in mind, too, that RCA SK replacement semiconductors measure up to strict AQL standards.

Get yours now. RCA's SK Replacement Guide. Contact your RCA Distributor. Or send $1.50 (check or money order) to RCA Distributor and Special Products Division, PO Box 85, Runnemede, NJ 08078.

RCA SK Replacement Semiconductors

THE GENERAL TELEVISION SERVICER

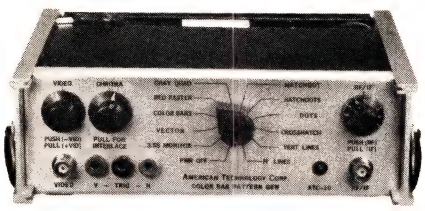

Patents Pending
covering 13 unique features.

YOUR PORTABLE, COST EFFECTIVE SOURCE OF A CONVENTIONAL COLOR BAR PATTERN GENERATOR, A SUBSTITUTE TUNER AND MOST USED FUNCTIONS OF AN ANALYST, PLUS:

- Extra wide range **RF/IF** attenuator for testing receiver sensitivity.
- **GRAY QUAD** pattern for gray scale tracking checks/adjustments.
- **COLOR BARS** pattern with 6th bar marked to make your job easier.
- **3.58 MONITOR** pattern for oscillator frequency checks with no need to short the AFPC test point.
- **RED RASTER** pattern for checking and adjusting purity at the flip of a switch.
- **HATCHDOTS** - versatile composite pattern for dynamic & static convergence plus other checks.
- High level, 75 ohm video output.

ALL THIS FOR ONLY $299.95!

Write for more information on the ATC-10 General Television Servicer, or try it at our risk.
— 30 DAY SHOP TRIAL —
(If not 100% satisfied in every way, return for instant refund in full.)

American Technology Corporation

225 Main Street, Dept. 5C
Canon City, CO 81212

For your convenience, we accept Master Charge, BankAmericard and COD phone orders.
Same day shipment!
(303) 275-8991

FOR LITERATURE ONLY CIRCLE 40 ON FREE INFORMATION CARD
FOR IMMEDIATE SALE CONTACT CIRCLE 90 ON FREE INFORMATION CARD

new lit

More information on new lit is available from the manufacturers of items identified by a Reader Service number. Use the Free Information Card following page 98

ELECTRONICS CATALOG, 148-page illustrated catalog is specially tailored for the radio/TV service technician, electronic technician, CB user and hobbyist. Included are test equipment, CB equipment, tools, service and repair kits, tubes, phono cartridges and needles, speakers and microphones, antennas, components and many other servicing aids. Free copies of the catalog are available on request.—**Fordham Radio Supply Co.,** 855R Conklin St., Farmingdale, NY 11735

CIRCLE 85 ON FREE INFORMATION CARD

AR GUIDE TO LOUDSPEAKERS, 36-page book describing manufacturer's line of speakers, including the *AR-10π, AR-11, AR-12, AR-14,* and *AR-16.* In addition, the booklet describes AR's philosophy of music reproduction and explains what goes into the design, production and testing of these features. It is available for $1.00 from the manufacturer, or free from AR dealers. The dealers' list will be sent free on request.—**Acoustic Research,** 10 American Dr., Norwood, MA 02062

CIRCLE 86 ON FREE INFORMATION CARD

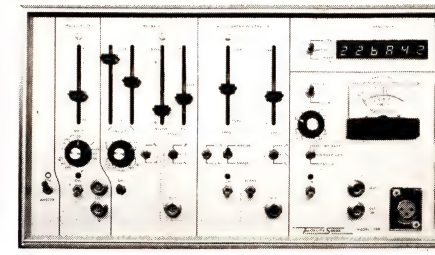

MODEL 100A AUDIO RESPONSE PLOTTING SYSTEM and general purpose sweep/tone burst/pulse generator consists of two sine /square/triangle function generators, pulse generator, frequency counter and peak amplitude measurement sections. It is primarily intended to generate a frequency response plot on an X - Y recorder or scope.

Time base generator offers symmetrical or independent control of the positive and negative sides of the ramp providing a duty cycle of .7% to 99.3%. Frequency range is .0035Hz to 100kHz. Amplitude is 15Vpp into 500 Ω with ±5VDC offset. The time base output drives the X axis of an X - Y recorder. Manual mode provided for setup.

Audio sweep generator provides manual frequency adjustment or log/linear sweep of 20Hz to 20kHz. Blanking mode produces zero reference line onn X - Y recorder or tone burst. Amplitude is 15 Vpp into 500 Ω or 10 Vpp into 8 Ω.

Pulse generator frequency range is .0035Hz to 525kHz. Pulse wideth is adjusted independent of frequency from 4 seconds to 40 nanoseconds. Outputs are complimentary TTL.

Peak amplitude measurement section measures internal or external signals from mike to power amp level. Amplitude output drives Y axis of X - Y recorder.

Frequency counter is 6 digit, line triggered, and reads either internal or external. Sensitivity is 50 mv peak at 20kHz.

Dimensions: 8 x 14 x 3. Shipping Weight 9 lbs.
$550, stock to 30 days. Warranty: 1 year.

FIDELITY SOUND
1894 Commercenter W. #105
San Bernardino, Ca 92408
(714) 889-7623

CIRCLE 5 ON FREE INFORMATION CARD

QUICK CHARGE IRON-QUICK CHANGE TIPS

ISO-TIP® Quick Charge Cordless Soldering Iron recharges in 3-4½ hours. Uses any of Wahl's 16 snap-in tips.

Low voltage, battery powered, ground free isolated tip design.

WAHL CLIPPER CORPORATION
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
Sterling, Illinois 61081 (815) 625-6525
"Manufacturing Excellence Since 1919"

CIRCLE 43 ON FREE INFORMATION CARD

FREE burglar — fire alarm catalog

over 900 systems, detectors, controls, sounders, tools, locks, supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 64 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today. (Outside U.S., send $1.00.)

mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

CIRCLE 3 ON FREE INFORMATION CARD

HEATH COLOR TV

continued from page 51

generator to issue signals to change the channel, defeat the automatic fine tuning, activate the squelch circuitry and activate the on-screen display for displaying the new channel and time.

If the programmed time and actual time are not equal, then the instruction address counter is incremented to the next memory location. The programmed time/channel combination in the second memory location is stored and compared to the actual time.

After the programmed time in all 16 memory locations is compared to the actual time, the time-down counter is decremented so that the BCD data in it represents a time that is one minute earlier than the actual time. The programmed time in all 16 memory locations is compared to the new time in the time-down counter. If equality is detected, the process stops.

The process of decrementing the time-down counter and comparing it to the programmed time continues until equality is detected. When the process stops, the BCD data in the shift registers represent the time that the TV set made the last channel change and the channel to which the change was made. This data is displayed on the TV screen when the MA key is depressed. R-E

COMPUTER MUSIC?

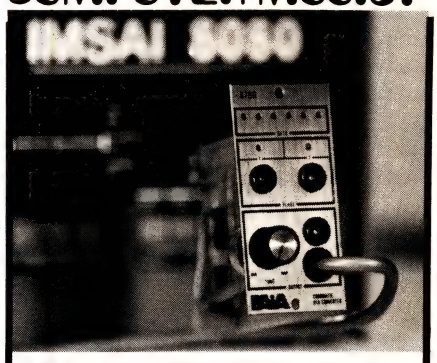

OUR EQUALLY TEMPERED D/A CONVERTER MAKES IT EASY!

- : 5+ octaves of control voltage from 6 bits of data.
- : hand-shaking logic.
- : use with any processor.
- : drives even the simplest linear oscillators & filters.

8780 D/A CONVERTER KIT $34.95
(plus $1.00 postage for mail orders)

8782 ENCODED KEYBOARD . . . . . $109.95 . . wt. 20lbs.*
COMPLETE SYNTHESIZER PACKAGES AS LOW AS $239
MODULES; VCO's, VCF's, NOISE SOURCES, & MORE
* keyboards shipped freight collect

DETAILS IN OUR **FREE CATALOG**

PAIA ELECTRONICS
DEPT 5-R
1020 W. WILSHIRE BLVD.
OKLAHOMA CITY, OK 73116

CIRCLE 7 ON FREE INFORMATION CARD

Circuits happen Faster and Easier with Super-Strip.™

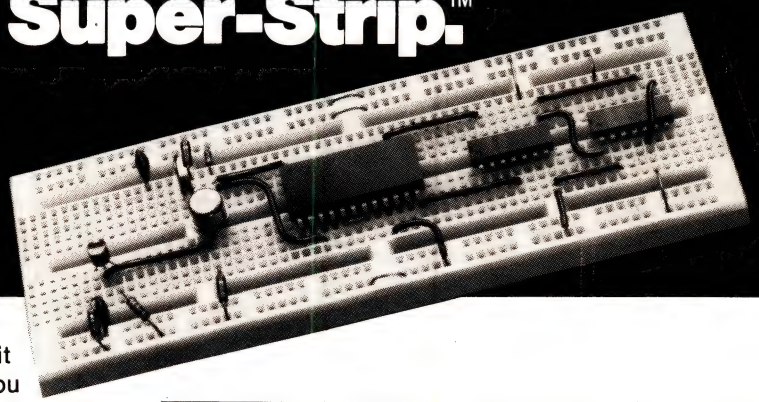

As little as $17

Now, whenever you'd like to give a circuit a try, you can build it up nearly as fast as you can dream it up with Super-Strips™, the faster, easier and less expensive solderless breadboards from A P Products. When you build your circuit on a Super-Strip, everything stays as good as new. Once you're through, you can use everything again and again. Instantly. Put a Super-Strip to work for you. Eight distribution lines handle signal and power, and 128 five-tie-point terminals can handle 9 ICs and then some. It's a whole lot easier than printing a circuit and a whole lot handier than haywire.

Part Number	Model Number	Terminal Type	Price Each
923252	SS-2	nickel-silver	$17.00
923748	SS-1	gold-plated	$18.90

Order from your A P distributor today. Our distributor list is growing daily. For the name of the distributor nearest you call Toll-Free 800-321-9668.

Send for our complete A P catalog, the Faster and Easier Book.

A P PRODUCTS INCORPORATED
Box 110 Painesville, OH 44077 (216) 354-2101 TWX: 810-425-2250

CIRCLE 4 ON FREE INFORMATION CARD

INTERNATIONAL FM 2400CH

FREQUENCY METER for testing mobile transmitters and receivers

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: ±.0005% from +50° to +104°F.

Frequency stability with built-in thermometer and temperature corrected charts: ± .00025% from +25° to +125° (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only) **$595.00**
RF crystals (with temperature correction) ... **24.00** ea.
RF crystals (less temperature correction) .... **18.00** ea.
IF crystals ..... catalog price

ICM

International Crystal Manufacturing Company, Inc.
10 North Lee, Oklahoma City, Oklahoma 73102

CIRCLE 70 ON FREE INFORMATION CARD

LOOKING AHEAD

continued from page 4

(1) Sony formally unveiled its new two-hour Betamax (you read about it in last December's **Radio-Electronics),** which gets double the playing time from a standard Betamax cassette (492 feet of half-inch tape). (2) Zenith announced it would put its own-brand home VTR on the market this year, using the new Sony format and, at least initially, buying decks from Sony. (3) The two developers of the V-Cord II format, Sanyo and Toshiba, announced they would switch over to the new Betamax, and both plan to market decks here this year. (4) RCA said it would also offer a home VTR this year, but was silent as to which format it would use.

The new Betamax deck resembles the current one. A one- and two-hour switch permits it to play back tapes recorded in the current one-hour mode, or to record in the one-hour mode if desired. For two-hour recording, tape speed has been cut in half to 0.785 IPS, track width has been halved to 29.2 micrometers and new noise-reduction circuitry has been added that is claimed to make possible the same 250-line color resolution and 45-dB color signal-to-noise ratio as the current model. The net result is a machine that overcomes the earlier model's deficiency of short playing time, and which, in effect, cuts tape costs in half—since a $16 cassette will now record and play for two hours instead of one. **R-E**

Revolutionary New Wiring "Pencil" Makes

Interconnections in 1/3 the Time!

- **Create Finished Wired Circuits In Hours, Not Days**
- **For Breadboarding, Prototypes and Production**
- **Interconnects Circuit Elements in Digital and Analog Circuits**

Easy for anyone — just hook up your components using the insulated "solder thru" wire (your choice of blue, red, green or clear). Wire feeds off a replaceable spool thru the P173 tool body and out of a steel tip so fine it easily routes wire around even the smallest I.C. lead. A touch of the iron, with solder, completes the joint.

Available accessory items include P179WS Wire Spacers for neat routing, tenth-tenth Micro-Vectorboards®, circuit Padbords and frames, like the 3677-6 and 51X-1. Order a P173 Now! Supplied with two 200' spools of AWG solder thru wire (1 red, 1 green), complete instructions. At your Vector distributor **$9.50**

Mail orders, add $2 shipping and handling charge. California residents add 6% sales tax.

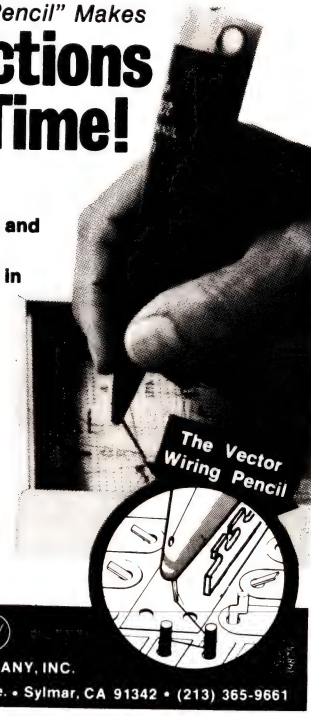

Vector W P DIVISION
ELECTRONIC COMPANY, INC.
12460 Gladstone Ave. • Sylmar, CA 91342 • (213) 365-9661

See Us at Electro'77: Booth 2405

CIRCLE 59 ON FREE INFORMATION CARD

SHOP YOUR NEARBY RADIO SHACK FOR QUALITY PARTS AT LOW PRICES!

Top quality devices, fully functional and carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Count on Radio Shack for the finest quality parts.

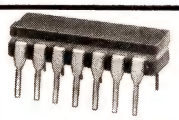

TTL Digital ICs

First Quality Devices Made by National Semiconductor and Motorola

Type	Cat. No.	Reg.	SALE
7400	276-1801	$ .49	29¢
7402	276-1811	$ .49	29¢
7404	276-1802	$ .59	29¢
7406	276-1821	$ .69	39¢
7408	276-1822	$ .49	29¢
7410	276-1807	$ .49	29¢
7413	276-1815	$1.19	69¢
7420	276-1809	$ .49	29¢
7427	276-1823	$ .69	39¢
7432	276-1824	$ .69	39¢
7441	276-1804	$1.59	89¢
7447	276-1805	$1.99	89¢
7448	276-1816	$1.99	89¢
7451	276-1825	$ .49	29¢
7473	276-1803	$ .79	39¢
7474	276-1818	$ .79	39¢
7475	276-1806	$1.19	69¢
7476	276-1813	$ .79	49¢
7485	276-1826	$1.59	99¢
7486	276-1827	$ .69	49¢
7490	276-1808	$1.19	69¢
7492	276-1819	$1.19	69¢
74123	276-1817	$1.69	89¢
74145	276-1828	$1.49	1.19
74150	276-1829	$1.79	1.39
74154	276-1834	$1.79	1.19
74192	276-1831	$1.69	99¢
74193	276-1820	$1.69	99¢
74194	276-1832	$1.69	1.19
74196	276-1833	$1.69	1.19
74C and 4000 Series CMOS ICs			
74C00	276-2301	$ .69	39¢
74C02	276-2302	$ .69	39¢
74C04	276-2303	$ .69	39¢
74C08	276-2305	$ .69	39¢
74C74	276-2310	$1.29	59¢
74C76	276-2312	$1.59	69¢
74C90	276-2315	$2.29	99¢
74C192	276-2321	$2.49	1.29
74C193	276-2322	$2.49	1.29
4001	276-2401	$ .69	39¢
4011	276-2411	$ .69	39¢
4013	276-2413	$1.29	89¢
4017	276-2417	$2.49	1.49
4020	276-2420	$2.49	1.49
4027	276-2427	$1.29	89¢
4049	276-2449	$ .99	69¢
4050	276-2450	$ .99	69¢
4511	276-2447	$2.69	1.69
4518	276-2490	$2.49	1.49

Linear ICs

First Quality Devices by National Semiconductor and Motorola

Type	Cat. No.	Reg.	SALE
301AH	276-017	$ .69	29¢
324N	276-1711	$1.99	1.49
339N	276-1712	$1.99	1.49
386CN	276-1731	$1.99	99¢
555CN	276-1723	$1.49	89¢
556CN	276-1728	$2.99	1.29
566CN	276-1724	$2.99	1.29
567CN	276-1721	$2.99	1.99
723CN	276-1740	$ .99	59¢
723H	276-009	$ .99	59¢
741CN	276-007	$ .69	35¢
741H	276-010	$ .69	35¢
3900N	276-1713	$1.99	59¢
3909N	276-1705	$1.29	99¢
3911N	276-1706	$2.19	1.99
4250CN	276-1732	$1.99	1.19
4558CN	276-038	$ .99	69¢
13741H	276-1733	$2.59	1.49
75491	276-1701	$1.49	69¢
75492	276-1702	$1.49	69¢

8080A Microcomputer Chip

Direct Plug-In Replacement for Intel 8080A

17.95

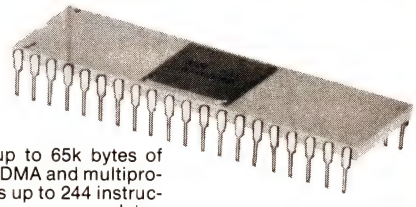

A CPU with a 16-bit address bus capable of addressing up to 65k bytes of memory and up to 256 I/O ports. "TRI-State" data bus gives it DMA and multiprocessing capability, and all buses are TTL compatible. Handles up to 244 instructions of variable length, with 6 general purpose registers plus an accumulator. 40-pin DIP. *100% Prime.* **276-2510** **17.95**

LEDs/Optoelectronics

Item	Cat. No.	Reg.	SALE
L Red LED	276-041	2/99¢	2/69¢
L Clr LED	276-047	2/99¢	2/69¢
M Red LED	276-026	2/99¢	2/69¢
M Clr LED	276-040	2/99¢	2/69¢
S Red LED	276-042	2/99¢	2/69¢
Infrared Det.	276-140	$1.19	
Infrared Em.	276-141	$1.19	
Solar Cell	276-115	$1.49	
Photocell	276-116	$ .99	
FPT 100	276-130	$ .79	

Digital Displays

276-056

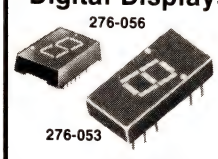

276-053

276-059

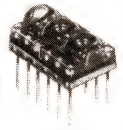

276-055

276-1201

276-060

Digits	Size	Drive	Cat. No.	Reg.	SALE
1	0.3"	Anod.	276-053	$2.99	1.99
1	0.3"	Cath.	276-062	$2.99	1.99
1	0.3"	Anod.	276-1210	4/$8.97	4/6.95
1	0.3"	Cath.	276-1211	4/$8.97	4/6.95
1	0.6"	Anod.	276-056	$3.99	2.99
1	0.6"	Cath.	276-066	$3.99	2.99

Digits	Size	Drive	Cat. No.	Reg.	SALE
3	0.120"	Cath.	276-055	$1.49	99¢
5	0.110"	Cath.	276-059	$1.99	1.49
9	0.150"	Cath.	276-060	$2.99	1.99
4	0.5"	Anod.	276-1201	$9.95	7.95
4	0.5"	Cath.	276-1202	$9.95	7.95

Project Accessories

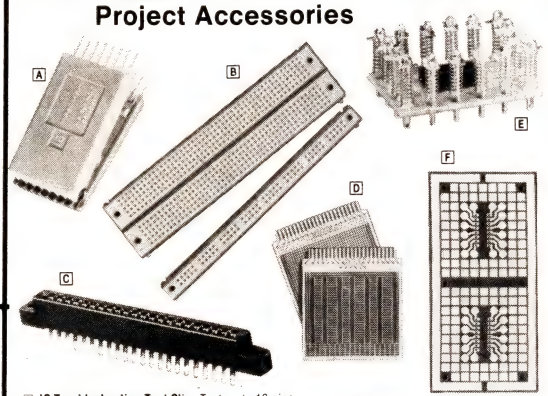

Ⓐ **IC Troubleshooting Test Clip.** Test up to 16 pins with probes or clips. **276-1951** **4.99**

Ⓑ **Experimenter Socket.** 2x47 rows of 5 connected tie points. **276-172** **9.95**

Ⓑ **Bus Strip.** 2x40 connected tie points. Clips to socket above. **276-173** **1.99**

Ⓒ **22-Pin Edge-Card Board Connector.** 44-terminals. **276-1551** **2.99**

Ⓓ **Standard Edge-Card Board.** 22-pin, 1295 mounting holes. **276-152** **2.99**

Ⓓ **2-Voltage Source Edge-Card Board.** 1368 mounting holes. **276-154** **2.99**

Ⓓ **3-Voltage Source Edge-Card Board.** 1368 mounting holes. **276-153** **2.99**

Ⓔ **Solderless IC Experimenter Kit.** For 8, 14 or 16-pin IC's. **277-101** **2.99**

Ⓕ **Experimenter's PC Board.** Mount 2 IC's, 8, 14 or 16-pin. **276-151** **2.49**

Ⓖ **Plastic Face Plates.** 2x6x⅛.
Brown Tint. 270-298 ..... **99¢**
Red Tint. 270-299 ..... **99¢**
Photographic PC Board Processing Kit. Complete negative process. 8 pieces.
276-1560. Reg. $12.95 ..... **Sale 9.95**

Transformers

Heavy-duty filament transformers with primaries designed to operate from 120 VAC at 60 Hz. Long, color-coded leads. All U.S. made.

25.2 Volts (Center Terminal), 2 Amps. 2¾x2¼x2". **273-1512** **4.99**

12 Volts, 5 Amps. 4x2x2½". **273-1513** **8.95**

18 Volts (Center Terminal), 4 Amps. Ideal for 5V (using CT), or 12V solid-state regulators. 4x2x2½". **273-1514** **8.95**

Selected Diodes

Type	Cat. No.	Reg.	SALE
1N4001	276-1101	2/$.39	2/29¢
1N4003	276-1102	2/$.59	2/39¢
1N4004	276-1103	2/$.69	2/49¢
1N4005	276-1104	2/$.79	2/59¢
1N4735	276-561	2/$.89	2/69¢
1N4739	276-562	2/$.89	2/69¢
1N4742	276-563	2/$.89	2/69¢
1N4744	276-564	2/$ .89	2/69¢
1N5401	276-1141	2/$.69	2/59¢
1N5402	276-1142	2/$.89	2/69¢
1N5403	276-1143	2/$.99	2/79¢
1N5404	276-1144	2/$1.19	2/89¢
1N914/4148	276-1122		10/99¢

276-1101

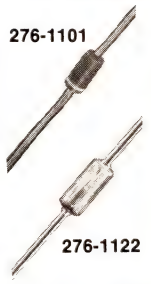

276-1122

SCRs and Triacs

Device	Rating	Cat. No.	Reg.	SALE
SCR	50V, 6A	276-1089	$ .99	69¢
SCR	100V, 6A	276-1090	$1.29	79¢
SCR	200V, 6A	276-1067	$1.39	89¢
SCR	400V, 6A	276-1020	$1.49	99¢
Triac	50V, 6A	276-1003	$ .99	69¢
Triac	100V, 6A	276-1002	$1.29	79¢
Triac	200V, 6A	276-1001	$1.39	89¢
Triac	400V, 6A	276-1000	$1.49	99¢

Reference Books

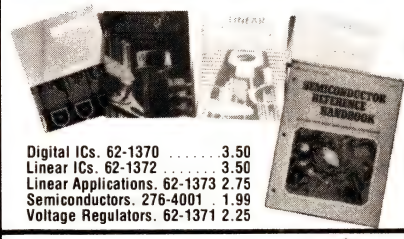

Digital ICs. 62-1370 ..... **3.50**
Linear ICs. 62-1372 ..... **3.50**
Linear Applications. 62-1373 2.75
Semiconductors. 276-4001 . **1.99**
Voltage Regulators. 62-1371 2.25

ASCII Encoded Computer Keyboard

Style May Vary from Photo

Reg. ~~67.95~~ 49.95 Pkg.

Operates on the scan principle utilizing TTL logic. With repeat key, negative/positive going data valid strobe, latch outputs, shift and shift-lock capability. True/false ASCII outputs, 6 extra control keys. With all necessary parts, including TTL components. Does not include test jigs, optional features or case and hardware. See store sales persons for parts list.

277-117. Complete Pkg. ..... **Sale 49.95**

Low-Profile DIP Sockets

8-Pin. 276-1995. Reg. 2 for $.69 ..... **Sale 2/59¢**
14-Pin. 276-1999. Reg. 2 for $1.19 ..... **Sale 2/99¢**
16-Pin. 276-1998. Reg. 2 for $1.19 ..... **Sale 2/99¢**
28-Pin. 276-1997. Reg. $1.19 Each ..... **Sale 99¢**
40-Pin. 276-1996. Reg. $1.39 Each ..... **Sale 1.19**

WHY WAIT FOR MAIL DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

OVER 5000 LOCATIONS IN NINE COUNTRIES

Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76107

SEND FOR

FREE CATALOG WITH ALMOST 3000 ITEMS

INCLUDING B&K, EICO, RCA, FLUKE, SENCORE, SIMPSON, HICKOK and LEADER

plus a complete line of tubes, tools and electronic supplies at prices you won't believe.

FORDHAM

RADIO SUPPLY CO., INC.
855R Conklin St., Farmingdale, N.Y. 11735
Tel: (516) 752-0050

CIRCLE 46 ON FREE INFORMATION CARD

Olson® ELECTRONIC PARTS AND ACCESSORIES

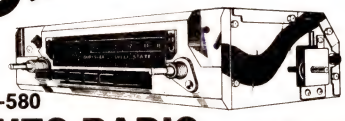

AU-580
AUTO RADIO Pushbutton AM 10.99

	REG.	SALE
60 Min. Cassette, Pkg. of 3, TA-879	1.49	.87
2V. RED L.E.D., Pkg. of 5, PL-233	1.99	.59
40 Min. 8-Track Tape, TA-907	.69	.39
Elect. Cap. Kit, 50 Asst., CD-407	5.00	1.70
Black Light Bulb, XM-291	1.00	.49
CB Converter for Car, CB-417	14.99	9.99
Resistors ½-1 watt, Pkg. 100, RR-077	1.79	.79
Volume Controls, 12 Asstd. VC-274	1.00	.49
Empire 999 Mag. Phono Cart. PC-188	9.99	6.99
3-6V DC Hobby Motors, 5 Asstd. MO-333	2.00	.59
Solder Terminal Strips, 40 Asstd. XM-501	1.30	.50
Double Face Foam Tape ¾"x52", TA-903	1.00	.80
¼ RPM Timing Motor, 117 VAC, MO-277	.49	.30
8 RPM Revers. Motor 117 VAC, MO-393	2.50	.99
Ceramic Disc Cap., 100 Asstd. CC-210	1.29	.80
3½ Digit Liquid Crystal Display, XM-371	10.00	3.00
Knob Kit, 25 Pcs. Asstd., KN-030	1.00	.69

Send to: Olson Electronics, Dept. LX 260 S. Forge St. Akron, Ohio 44327. Allow for Postage, C.O.D. 20% Deposit. Ohio Residents Add 4½% Sales Tax.

FREE Ask for our Catalog when you Order

CIRCLE 68 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **$1.40 per word (no charge for zip code) . . .** minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word . . .** no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

BUSINESS OPPORTUNITIES

RECTILINEAR Research Corp. would appreciate comments from interested parties on the feasibility of offering our highly rated models 5a and 7a fully assembled, wired and tested, **less cabinet,** at very substantial savings. Freight prepaid within UPS zone. Detailed drawings for enclosure included. Franchised and non-franchised dealers can participate. To assist in this survey, write: Kit Division/RE, **RECTILINEAR,** 107 Bruckner Boulevard, Bronx, NY 10454—212/585-9400

HIGHLY PROFITABLE **ONE-MAN ELECTRONIC FACTORY**

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-BQ, Box 248, Walnut Creek, CA 94507.**

$500/1000 immediately, stuffing envelopes, free supplies, rush stamped self-addressed envelope. **D. CONRAD COMPANY,** 206 Cedar, Rosemere, Quebec, Canada, J7A-2W4. U.S. inquiries invited

WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! **BARRY,** 512 Broadway, New York, NY 10012, 212 WAlker 5-7000

EDUCATION & INSTRUCTION

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure $1.00. **NEGEYE LABORATORIES,** Box 547-RE, Pennsboro, WV 26415

Breaker 10-33

Violation of Federal regulations can cost your license, and more, ol' buddy. Know the law. Keep our booklet on Federal rules in your car. Send $2 to: **CB & UNCLE SAM**
Box 2847 Longview, Tex. 75601

CB'ers—Be a "Ham"—We'll teach you! Life membership: $4.00—**AMERICAN RADIO COUNCIL;** Box #1171-F; Garland, TX 75040

HIGHLY effective degree program in electronics engineering. Advance rapidly! Our 31st year. Free literature. **COOK'S INSTITUTE,** Box 20345, Jackson, MS 39209

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests-Answers for FCC 1st and 2nd class Radiotelephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. $9.95 postpaid. Money-back guarantee.

COMMAND PRODUCTIONS
RADIO ENGINEERING DIV.
P.O. BOX 26348 E
SAN FRANCISCO, CAL. 94126

GRANTHAM's FCC License Study Guide—377 pages, 1465 questions with answers/discussions—covering third, second, first radiotelephone examinations. $13.45 postpaid. **GSE PUBLICATIONS,** 2000 Stoner, Los Angeles, CA 90025

ELECTRONICS courses, radio-television, FCC licenses. Home study. **GENN TECHNICAL INSTITUTE,** 5540 Hollywood Blvd., Los Angeles, CA, 90028, or **RA-TEL ELECTRONICS,** Post Box 167-P, Toronto, Ontario, Canada. U.S. inquiries invited.

BURGLAR/fire alarm experts needed for cars, homes, industry. Learn high-profit systems installation at home spare time. Simple, quick, complete. Free information by mail. No salesmen. **SECURITY SYSTEMS MANAGEMENT SCHOOL** (homestudy), Dept. 7339-057, Little Falls, NJ 07424

PLANS & KITS

ARTISAN organ kits feature all new modular construction with logic-controlled stops and **RAM** Preset Memory System. Write for brochure to **A O K MANUFACTURING INC.,** P. O. Box 445B, Kenmore, WA 98028

WERSI KITS

Organs, Pianos, Strings
Rhythms, PA Systems
104-page catalog $2
WERSI electronics, Inc.
Dept.A4, Box 5318,
Lancaster, PA 17601

5TH anniversary package deal: TVT-III system (4 page capability); includes basic kit, screen read, manual cursor, U.A.R.T., plus power supply $160. One per customer. Offer expires June 30, 1977. Postage free shipping (US only) starting with catalog #9 or this ad. SASE for inquiries. Free catalog. **ELECTRONIC DISCOUNT SALES,** 138 N. 81st Street, Mesa, AZ 85207

BI-LINEAR amplifier, 3-30MHz, 100 watt mobile. Construction plans, $3.00. **IGOR,** Box 5516-FE Walnut Creek, CA 94596

6-DIGIT LED CLOCK CALENDAR KIT

DATE-TIME-SNOOZE ALARM & MORE... KIT 7001

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME — 29-30-31 DAY CALENDAR. ALARM, SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

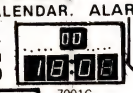

7001C DISPLAY

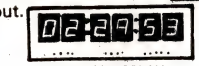

7001 X DISPLAY

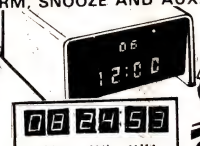

CHOICE OF DIGITAL DISPLAYS — 7001 B DISPLAY

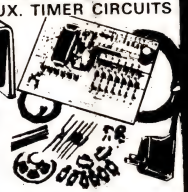

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout. Specify for 7001 **B, C or X - $7.95**

KIT - 7001B WITH 6 - .5" DIGITS $39.95
KIT - 7001C WITH 4 - .6" DIGITS & 2 - .3" DIGITS FOR SECONDS $42.95
KIT - 7001X WITH 6 - .6" DIGITS $45.95

KITS ARE COMPLETE (**LESS CABINET**) WITH PC BOARDS, POWER SUPPLY, IC & SOCKET, 16 TRANSISTORS, 9 SWITCHES AND ALL REQUIRED PARTS. ALL 7001 KITS FIT CABINET I AND ACCEPT (OPTIONAL) QUARTZ CRYSTAL TIME BASE KIT # TB-1

6 DIGIT LED CLOCK KIT #850-4

12/24 HR. OPERATION BIG .4" DIGITS - 50/60 HZ OPERATION.

KIT INCLUDES
- INSTRUCTIONS
- QUALITY COMPONENTS
- 50 or 60 Hz OPERATION
- 12 or 24 HR OPERATION

6-LED Readouts (FND-359 Red, com. cathode)
1-MM5314 Clock Chip (24 pin)
13-Transistors
3-Switches
6-Capacitors
5-Diodes
9-Resistors
24-Molex pins

Kit #850-4 will fit Plexiglas Cabinet II

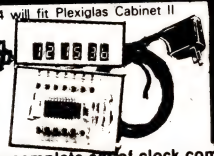

$11.95 ea. QTY. 1-5
$10.95 ea. QTY. 6-11
$9.95 ea QTY. 12 OR MORE

"Kit #850-4 will furnish a complete set of clock components as listed. The only additional items required are a 7-12 VAC transformer, a circuit board and a cabinet, if desired."

PRINTED CIRCUIT BOARD FOR KIT # 850-4, SCREEN PRINTED DRILLED AND SOLDER PLATED FIBERGLASS $2.95
MINI-BRITE RED LED'S (FOR COLON IN CLOCK DISPLAY) ... Pkg. of 5-$1.00
MOLDED PLUG TRANSFORMER 115/10 VAC (WITH CORD) $2.50

NOTE: Entire Clock may be assembled on one PC Board or Board may be cut to remote display.

MOBILE LED CLOCK

12/24 HR .4" DIGITS!

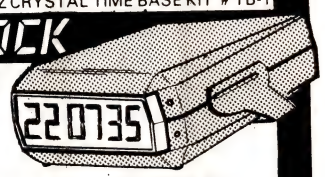

MODEL #2001 — 12 VOLT AC or DC POWERED

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY — TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
- TOP QUALITY PC BOARDS & COMPONENTS - EXCELLENT INSTRUCTIONS
- MOUNTING BRACKET INCLUDED

KIT #2001 COMPLETE KIT (Less 9V. Battery) $29.95 EA. 3 OR MORE $27.95 EA.
115 VAC Power Pack #AC-1 $2.50 EA.

ASSEMBLED UNITS WIRED & TESTED ORDER #2001 WT (LESS 9V. BATTERY) $39.95 EA. 3 OR MORE $37.95 EA.
WIRED FOR 12 HR. OP. IF NOT SPECIFIED OTHERWISE

60 HZ. XTAL TIME BASE

Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC.
1"x2" PC Board
Power Req: 5-15V (2.5 MA. TYP.)
Easy 3 wire hookup
Accuracy: ± 2PPM
#TB-1 (Adjustable)
Complete Kit $4.95 ea.
Wir & Cal $9.95

PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

CABINET I 3"H,6¼"W,5½"D — **Black, White or Clear Cover**
CABINET II 2½"H,5"W,4"D — $6.50 ea.

RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS 3"x6"x1/8" 95¢ ea. 4/$3

SEE THE WORKS Clock Kit Clear Plexiglas Stand

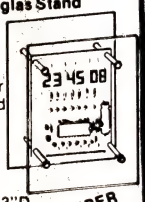

- 6 Big .4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included

Plexiglas is Pre-cut & drilled
Kit #850-4 CP
Size: 6"H, 4½"W, 3"D
$23.50 ea. 2/$45.
A SUPER CLOCK!

JUMBO DIGIT CLOCK

A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC, 12/24 Hr. time, 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts. (Ideal Fit in Cabinet II) Kit # 5314-5 ... $19.95 2/$38.
WITH PC Board s

JUMBO DIGIT CONVERSION KIT $9.95 ea.
Convert small digit LED clock to large .5" displays. Kit includes 6 - LED's; Multiplex PC Board & easy hook-up info.
Kit # JD-1CC For common Cathode
Kit # JD-1CA For common Anode

TELEPHONE FORMAT KEYBOARD
BY Chomerics
EF-21360
2-1/4"x3"

5/32" thick
$4.95
6/$28.

25 AMP BRIDGE

$1.95 ea.
3/$5.00

NEW LSI TECHNOLOGY

FREQUENCY COUNTER KIT

8 LARGE .4" RED LED DIGITS

• ONLY 8 IC's! • XTAL TIME BASE

A truly "State of the Art" counter using quality components throughout.

KIT INCLUDES: DETAILED INSTRUCTIONS, XTAL, TOP QUALITY FIBERGLASS DOUBLE SIDED PC BOARD, IC'S WITH SOCKETS AND ALL PARTS LESS POWER SUPPLY AND CABINET.

50 MHZ COUNTER KIT	#FC-50	$69.95
5 VOLT REGULATED 1 AMP POWER SUPPLY KIT	#PS-02	$9.95
350 MHZ PRESCALER KIT	#PSL-350	23.95
650 MHZ PRESCALER KIT	#PSL-650	$29.95
CABINET [& MTG HARDWARE]	#CAB III	$19.95

[CABINET WILL HOUSE #FC-50, #PS-02, AND A PRESCALER]

DELIVERIES TO START IN MAY, 1977

Fairchild Super Digit FND-359

.4" Char. Ht. 7 segment LED RED Com. Cath. Direct pin replacement for popular FND-70.
95¢ ea, 10/$8.50 100/$79.00

SET OF 6 FND-359 WITH MULTIPLEX PC BOARD $6.95

NYLON WIRE TIES

8" TIE-WRAP 100/$1.95
4" TIE-WRAP 100/$1.75

PLUG TRANSFORMERS

12 VAC at 150 MA $2.50
12 VAC at 500 MA 3.50
7VAC at 1.75 VA $3.50

SCHOTTKY TTL

74S00	$ .35
74S01	.40
74S04	.55
74S05	.60
74S09	.55
74S10	.40
74S20	.50
74S22	.45
74S40	.45
74S50	.45
74S51	.55
74S60	.85
74S64	.55
74S74	.85
74S75	1.75
74S78	1.50
74S86	.95
74S107	.95
74S112	.95
74S113	1.40
74S114	.95
74S133	.75
74S134	.75
74S138	1.75
74S139	1.50
74S151	1.95
74S153	1.95
74S155	1.95
74S156	1.95
74S157	1.80
74S158	2.50
74S174	2.50
74S175	2.50
74S181	2.95
74S182	1.95
74S251	2.75

DIGITAL CLOCK IC's

MM5312	$ 4.95
MM 5314	3.95
MM 5375 AB	3.95
CT-7001	7.95
CT-7002	13.95
MM 5369	2.50

LED DRIVERS

7447	$ .95
7448	.95
75491	.65
75492	.65

PRESCALE

11C90DC	$15.95
95H90	9.95

VOLTAGE REGULATORS

LM 309 H	TO-5	$ .95
LM 309 K	TO-3	1.25
7805	TAB	.95
7812	TAB	1.25
7812	TO-3	1.50
7815	TO-3	1.25
7815	TAB	1.25
78L 15	TO-5	.75
7824	TO-3	1.25
723	DIP	.75
723	TO-5	.75

PROM

1702 E Prom $8.95
.5203 E Prom $8.95

SWITCHES

ROCKER SPDT	6/$1.
MINI-SLIDE SPDT	5/$1.
REG. SLIDE DPDT	6/$1.
PUSH BUTTON N.O.	3/$1.
MINI TOGGLE SPDT	$1.30
DPDT	1.50

IC SOCKETS

PINS	1-24	25	100
8	$ .25	$ .22	$ .20
14	.25	.22	.20
16	.28	.25	.23
18	.31	.28	.26
24	.50	.45	.40
28	.60	.55	.50
40	.75	.70	.65

XTAL

3.579545 MHZ. $1.95

21L02

PRIME - 450 NS LOW POWER FAIRCHILD OR SIGNETICS

1-24	$1.95
25-99	1.75
100-199	1.60
200-499	1.45
Over 500	1.40

TRANSISTORS

2N2222 A	TO-18	3/$1.00
2N2712	TO-98	5/$1.00
2N3415	TO-9	5/$1.00
2N3704	TO-92	5/$1.00
2N4400	TO-92	5/$1.00
2N4125	TO-92	5/$1.00
2N4249	TO-92	5/$1.00
2N4437	TO-92	5/$1.00
2N6027	PUT	2/$1.00
2N5457	N J-Fet	2/$1.00

DIODES

IN 4002	1A, 100 PIV	12/$1.00
IN 4005	1A, 600 PIV	11/$1.00
IN 4007	1A, 1000 PIV	10/$1.00
RECTIFIER	2.5A, 1000 PIV	4/$1.00
IN 914	SIL. SIGNAL	20/$1.00
IN 4148	SIL. SIGNAL	20/$1.00
DYAC	28V.	4/$1.00

LINEAR

555	TIMER	2/$1.00
556	DUAL TIMER	.95
565	PLL	.95
566	FUNCTION GEN.	1.75
567	TONE DECODER	1.75

TRANSISTOR SOCKET TO-5/18 GOLD PINS

5/$1.00

7-SEG LED

COMMON CATHODE

COLOR	HT.	DEC PT	PR EA
FND-359 RED	.4"	RHDP	$ .95
FND-503 RED	.5"	RHDP	$1.35
DL-750 RED	.6"	LHDP	$2.95
XAN-654 GREEN	.6"	NDP	$1.95
XAN-664 RED	.6"	NDP	$1.95

COMMON ANODE

DL-747	RED	.6"	LHDP $1.95
XAN-72	RED	.3"	LHDP $1.25
MAN-72	RED	.3"	LHDP $1.25
XAN-81	YELLOW	.3"	RHDP $1.75
XAN-351	GREEN	.3"	RHDP $1.50
XAN-361	RED	.3"	RHDP $1.50
XAN-362	RED	.3"	LHDP $1.50
XAN-662	RED	.6"	NDP $1.95
XAN-692	RED	.6"	NDP $1.95

OP AMPS

3/$1.00
301 TO-5
709 DIP
709 TO 5
741 DIP
741 M-DIP
741 TO-5
747 TO 5

DISCRETE LED's

JUMBO RED

10 FOR $1.00
100 FOR $9.50

PC TRIM POTS

25K 6/$1.00
4.7K 6/$1.00

SPECTROL 10K 10 TURN 95c 4/$3.00

MOLEX PINS

Form Inexpensive Sockets

100 for $1.25
Reel of 1000 $8.50

AUTO BURGLAR ALARM KIT

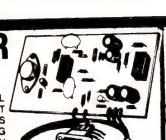

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR POS. & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1HZ RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.

KIT #ALR-1 $9.95
#ALR-1WT WIRED & TESTED $19.95

VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

- VARIABLE FROM 4 to 14V
- SHORT CIRCUIT PROOF
- 723 IC REGULATOR
- 2N3055 PASS TRANSISTOR
- CURRENT LIMITING AT 1 Amp

KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (Less TRANSFORMER) KIT #PS-01 $8.95

TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V with #PS-01. $3.50

STORE: 823 S. 21 AVE.

OPTOELECTRONICS, INC.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056

master charge — BANKAMERICARD

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME
Orders Under $15 Add $1.00 Handling
Fla. Res. Please Add 4% Sales Tax.

WE PAY ALL SHIPPING IN CONTINENTAL USA — OTHERS ADD 5% [10% FOR AIRMAIL]
SEE OUR BOOTHS AT THE ATLANTA HAMFESTIVAL - JUNE 18-19, 1977

CIRCLE 52 ON FREE INFORMATION CARD

GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

TERMS: Add 50¢ orders under $10; add postage when indicated. Cal res add tax. Mastercharge®/BankAmericard® call 415-562-0636.

12V 8A supply
CB, HAM...$39.95

+ POSTAGE. Now you can connect CB and ham transceivers...auto tape players...portable TVs...to your AC house current; also makes a superb lab or bench supply. Crowbar overvoltage protected, short protection, 0.05V regulation, adjustable output 11-14V, and EASY ASSEMBLY---heat sinks, power transistors etc. mount on board. A SUPER SUPPLY!!

500 KHz xtal
$4.95

New-SPDT switch
#SW3 - 95¢

PC mount type (bushing not threaded). Includes mounting frame.

READOUT SPECIAL

.5" BIG
ACTUAL SIZE

FND510 COMMON ANODE
FND503 COMMON CATHODE
95¢ ea. or 10/$8.50

CIRCLE 54 ON FREE INFORMATION CARD

PARTS

NEW AND SURPLUS PARTS
IC's-RES-CAPS-SWITCHES
P.C.BOARDS & CHEMICALS
COMPUTER PARTS
ORGAN/SYNTH. KEYBOARDS
LCD WATCH PARTS

KITS

MUSIC SYNTHESIZER KITS
KITS FOR MUSICIANS
AUDIO KITS AND PARTS
POWER SUPPLIES
WE CAN ASSEMBLE & TEST
COMPUTERS & OTHER KITS

SERVICES

CUSTOM CIRCUIT BOARDS-
DESIGN AND FABRICATION
CIRCUIT BOARD COOKBOOK
METAL FAB. & MATERIALS
CIRCUIT BOARD LAYOUT

SEND 13¢ STAMP

UTEP
DEP. 3-BOX 26231
S.L.C., UT. 84125

CIRCLE 57 ON FREE INFORMATION CARD

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number		Page
	Acoustic Fiber Sound Systems	87
1	Allison	85
40,90	American Technology	92
4	AP Products	93
	Audio-Technica	16
62	B&K-Div. of Dynascan	14
2	Channellock	32
30	Chemtronics	90
	CIE-Cleveland Institute of Electronics	72-75
8	Cobra-Div. of Dynascan	Cover IV
36	Continental Specialties	83
	Cowan Publishing	88
	CREI-Div. of McGraw-Hill Continuing Education	62-65
51	Digital Concepts	82
31	Dynaco	22
87	Eastern Industries (Gem's)	Cover III
26	Edmund Scientific	116
67	EICO	28
	E&L Instruments	84
11	Electronics Book Club	29
	EMC-Electronics Measurements	88
42	EPSCO	86
5	Fidelity Sound	92
	GFN Communications	31
13	Grantham College of Electronics	89
	GTE Sylvania-Consumer Renewal	36
100	Heath	18-21
61	Helectronix	82
12	Hickok Electrical Instruments	24
18	Ignition Systems	86
34	Indiana Home Study Institute	82
70	International Crystal	94
	JB Electronics	91
	JS&A	Cover II, 1, 6, 7
16	Kedman	90
60	Mallory	15
74	McGraw-Hill Books	35
3	Mountain West Alarm Supply	93
6	National Camera Supply	84
	National Radio Institute (NRI)-Div. of McGraw-Hill Continuing Education Center	8-11
	National Technical Schools	52-55
17,22	OK Machine & Tool	34, 17
7	PAIA	93
29	Pearce-Simpson-Div. of Gladding	27
21	PTS	25
65,66	Professional Aids	86
	Radio Shack	2, 95
	RCA Distributor & Special Products	91
35	Rye Industries	82
28	SBE	5
14	Sencore	22
48	Schober Organ	86
69	Southwest Technical Products	30
24	Techni-Tool	34
39	Tektronix	33
45,44	Telematic-Div. of UXL	26, 89
20	Tri-Star	32
25,75	Tuner Service	23
64	Vaco Products	13
41	VIZ Mfg.	85
59	Vector Electronics	94
43	Wahl Clipper	92

MARKET CENTER

33	Active Electronics	104
	AMC Sales	106
	Amateur Radio Supply	110
	American Used Computer	110
	American Surplus Trading	112
53	Babylon Electronics	108
	Karel Barta	96
	Burdex Security	104
	CB & Uncle Sam	96
	CFR Associates	110
	Command Productions	96
	Cornell Electronics	110
	Dage Scientific Instruments	104
27	Delta Electronics	114
	Devtronix Organ Products	106
71	Digi-Key	111
46	Fordham Radio Supply	96
56	Formula International	101
54	Godbout Electronics	98
	Information Unlimited	106
58	International Electronics	105
9,10	James Electronics	102, 103
	Lab Science	110
	Lakeside Industries	106
49	Lin	112
37	Meshna	108
38	New-Tone	112
68	Olson Electronics	96
52	Optoelectronics	97
	Parasitic Engineering	110
	P.P.G.	106
23	Poly Paks	107
55	Quest	110
73	Radio Hut	109
72	SD Sales	115
63	JB Saunders	113
47	Solid State Sales	114
	Speakerlab	104
15	Surplus Center	104
19	Trico Electronics	108
32	TV Tech Aids	106
57	Utep Marketing	98
	Wersi Electronics	96

MOVING?

Don't miss a single copy of **Radio-Electronics.** Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80302

TV Games

FCC Approved

Direct Sales Only

$38.50

MODEL PP460

USES 6 C SIZE BATTERIES (Not Included)

JUST SIMPLY HOOK THE OUTPUT LEAD OF THE UNIT TO THE ANTENNA INPUT OF YOUR TV SET AND YOU'RE READY TO PLAY!

FEATURES:

* 4 Games—Tennis, Hockey, Racquet Handball and Single Handball.
* Adjustable bat size.
* Automatic or manual serve!
* 20° or 40° ball angles.
* Pair of extension control units optional (3.00 each)
* Auto counter display on the screen.
* 3 different beeps: Ball against bat-high beep Ball against boundry-low beep Ball out of play-2 low beeps.

TIMER KIT

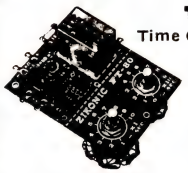

Time Controlled from 1-100sec.

Ideal to be used as time delay unit for burglar alarm, photo service, and other purposes. Max. loading 110V, 2 AMP. Supply voltage 12-18V D.C.

FT-80 ELECTRONIC IC TIMER

$11.50 each

Electronic Police Siren Kit

Ideal for use as an alarm unit. High output up to 5 watt at 12V DC supply. Can be used with horn-type speaker.

AU-999 POLICE ALARM UNIT

$14.00 EACH

COLOR ORGAN KIT

Music on Light in Colour !

Operates in low voltage (9V-24V DC). Can control up to 100 low voltage light bulbs. Light bulbs change colors to the tones of music. Connect to the speaker output of the amplifier.

MC-520 MINI MUSIC COLOR UNIT

$10.50 PER KIT

LIGHT CONTROL SWITCH KIT

Don't move !

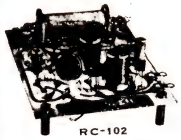

Can control TV, radio, lights or can be used with the Police Siren Kit to form a burglar alarm system.

RC-102

$4.50 EACH

POWER SUPPLY KIT

0-35V D.C. REGULATED

Uses UA723 and ZN3055 Power TR output can be adjusted from 0-35V, 2 AMP. Complete with PC board and all electronic parts.

035 POWER SUPPLY

$9.50 each

SOUND CONTROL SWITCH KIT

Now you can turn your lights, radio, or even TV on with sound. Sensitivity can be adjusted. Operating voltage from 9-18V DC. It is a lot of fun to build one.

RC-103

$5.50 each

4 Digits Alarm Clock

0.7" Led Clock Module

LT701E, 60 Hz 12 hr. display.
LT701G, 60 Hz 24 hr. display.
Power Supply 12V AC
Ideal for panel clock, desk clock, or auto clock with our time base kit.

$13.50 EACH

COMPLETE ALARM CLOCK

* 4 Digits 0.5" LED with brightness control
* 12 Hour display with AM/PM indication
* True 24 hour alarm with repeatable snooze
* Power failure indication for power interrupt

MODEL EC 400

(Not A Kit)

Only ~~$22.50~~

ON SALE **$17.50 ea.**

CLOCK KIT

MOST POPULAR MM5314 KIT

WITH A NEW CASE!!

Features: 12/24 Hour Display 50/60 HZ Input 6 Digits Readout

Kit Includes: Grey Color Plastic Case MM5314 Clock Chip PC Boards and Transformer, 6 Green Color 0.3" Tube Readouts, All other transistor Drivers and other Components.

Special Only $14.95 ea.

MODEL OC

ALARM CLOCK

only $19.50

Kit Includes: TI Alarm clock chip, LD8132 0.5" Green readouts, PC board with all electronic parts, speakers, transformer and specially designed case.

5W AUDIO AMP KIT

USE 2 LM380 with Volume Control POWER SUPPLY 6VDC

only $5.00 ea.

TV GAME MODULATOR UNIT

FCC Approved For channel 3 and 4

With Occ. Coil

ONLY $4.50

NI-CD RECHARGEABLE BATTERIES

AA SIZE, 1.2V . . . . $1.25 each
C SIZE, 1.2V . . . . . $1.50 each

ALL GUARANTEED BRAND NEW

AUTO ALARM KIT

The Crimefighter Auto Alarm is an electronic, self-controlled auto protection system, normally mounted within the glove box of an automobile. Two minutes after turning off the ignition, the alarm automatically turns itself "on." When the auto is re-entered, the horn will sound after a 10-45 second entry delay. The automobile owner, by inserting the ignition key, will activate the alarm. Once activated, the alarm will sound for two minutes before automatically turning off. The alarm then resets and is ready to again protect the vehicle from unwanted entry.

FEATURES: Simple installation: 5 wires, Automatically turns on when auto is parked, Adjustable entry time, Extended exit time to allow for unrushed exit from vehicle, Numerous applications include protection of boats, campers, trailers, motorcycles, trucks, Cannot be deactivated by "hot wiring" an auto, Cannot be turned off without ignition key, Negative ground only.

ONLY $10.00 per kit Completed Unit $16.00

ELECTRONIC SWITCH KIT

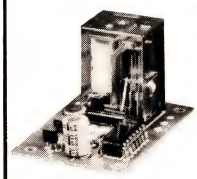

CONDENSER TYPE

Touch on Touch Off uses 7473 I.C. and 12V relay

$5.50 each

FM WIRELESS MIC KIT

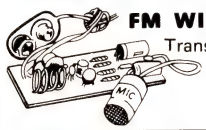

Transmit range up to 500 ft.
Easy to assemble
(Mic included)

$4.50 each

Sub-Mini Size Condenser Microphone

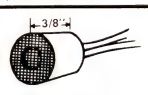

$2.50 each

FET Transistor Built-in

T1-AY3-8500-1

(28 pin Dip)
6 Game, TV Game Chip With Data
Tennis, Squash, hockey, practice and two-shooting.

Special Only $11.00

COMPUTER KEYBOARDS

Standard Teletype Keyboards with gold plated contact switches. All switches are independent and allow you to connect into any form of output.

63 Keys — 19.50
60 Keys — 14.50

NEW !

NATIONAL MM 5369 17 STAGE PROGRAMMABLE OSC/DIVIDER generate A 60 Hz reference Frequency with a 3-58 MHZ Color TV X'TAL in Mini DIP Package

ONLY $2.25 each

19 KEY HEXADECIMAL KEYBOARD

STANDARD SIZE KEY TOPS WITH UNENCODED SPST KEYS

ONLY $9.95 EACH

50 UA PANEL METER

First designed for metal Finder. Scaled from 0-10 but can be erased and your own scale put on top. Brand new in box.

Size 2 ¼" x 2¼"

Only $3.80 ea.

150UA METER

only **$1.50 ea.**

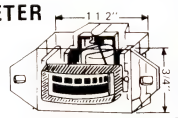

QUAD VOLUME CONTROL

(JOY STICK)

4 100K Volume pot in one unit, vary resistance proportional to the angle of the stick. Perfect for electronic games or model remote control.

only $7.50

Knob for Joystick 50¢ ea.

SOLAR CELL

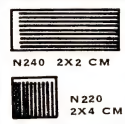

N240 2X2 CM — Large Size $3.00 Each (85MW, 200MA, 430MV)

N220 2X4 CM — Small Size $1.50 Each (43MW, 100MA, 430MV)

SAE DIP SWITCHES

Part No. 1004 692 4XSPST SW
1008 692 8XSPST SW

4 Toggle SPST Switches on a Mini DIP (8 pins) Only $1.50 ea
8 Toggle SPST Switches on a DIP (16 pins) Only $2.60 ea

SUBMINIATURES TOGGLE SWITCHES

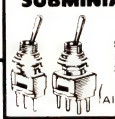

SPDT On-Off $1.30 ea.
DPDT On-Off $1.50 ea.
3PDT On-Off $1.75 ea.

Mini-Size Rocker Type Also Available at the Same Price

COMPUTER GRADE CAPACITOR

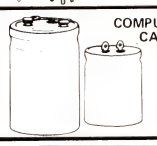

15500 MFD 75V-DC $5.95 ea.
6000 MFD 75V-DC $4.00 ea.

PUSH-BUTTON SWITCH

N/Open Contact. Color: Red, White, Blue, Green, Black.

4/$1.00

LARGE QTY. AVAILABLE

SOLID STATE ELECTRONIC BUZZER

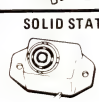

Mini Size 1"x3/4"x3/4"
Supply voltage 1.5V—12V
Ideal for Alarm or Tone Indicator

$1.50 each or 2/$2.50

MINIMUM ORDER $10.00. California residents add 6% sales tax.
All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage.
SEND CHECK OR MONEY ORDER TO:

FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10-7 Monday - Saturday

master charge

your BANKAMERICARD welcome

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case/Style	Price
CY1A	1.000 MHz	HC33/U	$5.95
CY2A	2.000 MHz	HC33/U	$5.95
CY3A	4.000 MHz	HC18/U	$4.95
CY7A	5.000 MHz	HC18/U	$4.95
CY12A	10.000 MHz	HC18/U	$4.95
CY14A	14.31818 MHz	HC18U	$4.95
CY19A	18.000 MHz	HC18/U	$4.95
CY22A	20.000 MHz	HC18/U	$4.95
CY30B	32.000 MHz	HC18/U	$4.95

EXAR

XR-2206KB Kit $27.95 — **XR-2206KA Kit $17.95**

WAVEFORM GENERATORS

XR-205	$8.40
XR-2206CP	4.49
XR-2207CP	3.85

STEREO DECODERS

XR-1310CP	$3.20
XR-1310EP	3.20
XR-1800P	3.20
XR-2567	2.99

MISCELLANEOUS

XR-2211CP	$6.70
XR-4136	.99
XR-1468	3.85
XR-1488	5.80
XR-1489	4.80
XR-2208	5.20

TIMERS

XR-555CP	$ .39
XR-320P	1.55
XR-556CP	1.85
XR-2556CP	3.20
XR-2240CP	3.25

PHASE LOCKED LOOPS

XR-210	5.20
XR-215	6.60
XR-567CP	1.95
XR-567CT	1.70

CONNECTORS

PRINTED CIRCUIT EDGE-CARD

.156 Spacing-Tin-Double Read-Out

Bifurcated Contacts — Fits .054 to .070 P.C. Cards

15/30	PINS (Solder Eyelet)	$1.95
18/36	PINS (Solder Eyelet)	$2.49
22/44	PINS (Solder Eyelet)	$2.95
50/100 (.100 Spacing)	PINS (Solder Eyelet)	$6.95

25 PIN-D SUBMINATURE

DB25P	PLUG	$3.25
DB25S	SOCKET	$4.95

iMC 3½ DIGIT DVM KIT

This 0-2 VDC .05 per cent digital voltmeter features the Motorola 3½ digit DVM chip set. It has a .4" LED display and operates from a single +5V power supply. The unit is provided complete with an injection molded black plastic case complete with Bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

A. 0-2V DVM with Case $49.95

B. 5V Power Supply $14.95

VECTOR WIRING PENCIL

Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) tool which is used to guide and wrap insulated wire, fed off a self-contained replaceable bobbin, onto component leads or terminals installed on pre-punched "P" Pattern Vectorboard™. Connections between the wrapped wire and component leads, pads or terminals are made by soldering. Complete with 250 FT of red wire. **$9.50**

REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3-A-Pkg. 3	250 ft. 36 AWG GREEN	$2.40
W36-3-B-Pkg. 3	250 ft. 36 AWG RED	$2.40
W36-3-C-Pkg. 3	250 ft. 36 AWG CLEAR	$2.40
W36-3-D-Pkg. 3	250 ft. 36 AWG BLUE	$2.40

1/16 VECTOR BOARD

	0.1" Hole Spacing Part No.	P-Pattern L	P-Pattern W	Price 1	Price 2-Up
PHENOLIC	64P44 062XXXP	4.50	6.50	1.72	1.54
	169P44 02XXXP	4.50	17.00	3.69	3.32
EPOXY GLASS	64P44 062	4.50	6.50	2.07	1.86
	64P44 062	4.50	8.50	2.56	2.31
	169P44 062	4.50	17.00	5.04	4.53
	169P84 062	8.50	17.00	9.23	8.26
EPOXY GLASS COPPER CLAD	169P44 062C1	4.50	17.00	6.80	6.12

HEAT SINKS

205-CB	Beryllium Copper Heat Sink with Black Finish for TO-5	$ .25
291-.36H	Aluminum Heat Sink for TO-220 Transistors & Regulators	$ .25
680-.75A	Black Anodized Aluminum	$1.60

HEXADECIMAL ENCODER 19-KEY PAD

- " - 0
- ABCDEF
- Return Key
- Optional Key (Period)
- — Key

$10.95 each

63 KEY KEYBOARD

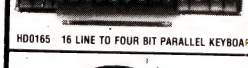

This keyboard features 63 unencoded SPST keys, unattached to any kind of P.C.B. A very solid molded plastic 13" x 4" base suits most applications

$19.95

HD0165 16 LINE TO FOUR BIT PARALLEL KEYBOARD ENCODER $7.95

JOYSTICK

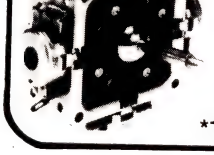

These joysticks feature four * potentiometers, that vary resistance proportional to the angle of the stick. Sturdy metal construction with plastics components only at the movable joint. Perfect for electronic games and instrumentation.

***5K Pots $6.95**

***100K Pots $7.95**

MICROPROCESSOR COMPONENTS

8080A	CPU	$19.95	8228	System Controller - Bus Driver	$10.95
8212	8 Bit Input/Output	4.95	MC6800L	8 Bit MPU	35.00
8214	Priority Interrupt Control	15.95	MC6820L	Periph. Interface Adapter	15.00
8216	Bi-Directional Bus Driver	6.95	MC6810AP1	128 x 8 Static RAM	6.00
8224	Clock Generator/Driver	10.95	MC6830L7	1024 x 8 Bit ROM	18.00
CDP1802	- with user manual	39.95	Z80	CPU	49.95

CPU'S

8080	Super 8008	24.95
8080A	Super 8008	19.95

SR'S

2504	1024 Dynamic	$ 3.95
2518	Hex 32 BIT	7.00
2519	Hex 40 BIT	4.00
2524	512 Dynamic	2.49
2525	1024 Dynamic	6.00
2527	Dual 256 BIT	3.95
2529	Dual 512 BIT	4.00
2532	Quad 80 BIT	3.95
2533	1024 Static	7.95
3341	Fifo	6.95
74LS670	16 x 4 Reg.	3.95

UART'S

AY-5-1013	30K Baud	$5.95

ROM'S

2513	Char. Gen	$ 9.95
2516	Char. Gen	10.95
74S387	1024-Bit Programmable	1.95

RAM'S

1101	256 x 1	Static	$ 1.49
2101	256 x 4	Static	5.95
2102	1024 x 1	Static	1.75
2107/5280	4096 x 1	Dynamic	4.95
2111	256 x 4	Static	6.95
7489	16 x 4	Static	2.49
8101	256 x 4	Static	6.95
8111	256 x 4	Static	6.95
8599	16 x 4	Static	3.49
91L02	1024 x 1	Static	2.25
74200	256 x 1	Static	6.95
93421	256 x 1	Static	2.95
MM5262	2K x 1	Dynamic	2 for 1.00

PROMS

1702A	2048	Famos	$ 9.95
5203	2048	Famos	14.95
82S23	32 x 8	Open C	5.00
82S123	32 x 8	Tristate	5.00
74S287	1024	Static	7.95
3601	256 x 4	Fast	3.95
2708	8K	Eprom	34.95
6301-1	1024	Tri-State Bipolar	3.49
6330-1	256	Open Collector Bipolar	2.95
6331-1	256	Tri-State Bipolar	2.95

SPECIAL REQUESTED ITEMS

MC3061P	3.50	CD4508	6.75	82S115	25.00	3341	6.95
MC4016P (74416)	7.50	CD4515	6.50	5841	9.95	9368	3.95
MC14583	3.50	CD4520	2.70	MK50240	17.50	MC1408L7	9.95
MC14562	14.50	MCM6571	17.50	11C90	19.95	LD110/LD111	25.00/set
CD4059	9.95	MCM6574	17.50	DS0026CH	3.75	AY-5-9100	17.50 ea.
CD4070	.95	MCM6575	17.50	TIL308	10.50	95H90	13.95

ELECTRONIC 'PENDULUM' CLOCK

- Unique Electronic 'Swing' Pendulum
- Real Furniture Quality
- Handicrafted Unfinished Wood Case
- Large .7" Hours, and Minutes LED Display
- Alarm Feature
- 12 or 24 Hour Mode
- Time Set Push Buttons
- Use Module For Easy Assembly
- **Special programed ROM in pendulum for animated effect!**

Dimensions - 10¼" x 10½" x 3¼"

KIT — UNFINISHED* $59.95

*Case Unassembled

ASSEMBLED — STAINED* $69.95

*Case Assembled

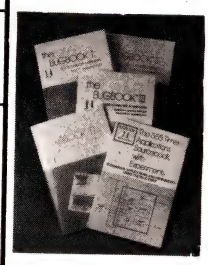

BUGBOOK ®

Continuing Education Series

BUGBOOK I & II - Basic concepts of TTL Logic — over 90 experiments **$17.00/set**

BUGBOOK IIa - Introduces UART — recommended for RTTY enthusiast **$5.00/book**

BUGBOOK III - Explores 8080 chip — introduces Mark 80 Microcomputer **$15.00/book**

555 TIMER APPLICATIONS SOURCEBOOK WITH EXPERIMENTS — over 100 design techniques **$6.95/book**

CMOS-M-DESIGNERS PRIMER AND HANDBOOK a complete CMOS instruction manual **$6.00**

Introductory Offer — all 6 books (worth $49.95) **SPECIAL - $42.95**

CONTINENTAL SPECIALTIES

PROTO BOARD 6

$15.95

(6" long X 4" wide)

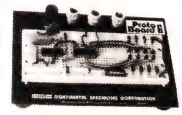

Other CS Proto Boards

PB100 - 4.5" x 6"	$ 19.95
PB101 - 5.8" x 4.5"	29.95
PB102 - 7" x 4.5"	39.95
PB103 - 9" x 6"	59.95
PB104 - 9.5" x 8"	79.95
PB203 - 9.75 x 6½ x 2¾	75.00
PB203A - 9.75 x 6½ x 2¾ (includes power supply)	120.00

Logic Monitor $84.95

for DTL, HTL, TTL or CMOS Devices

PROTO CLIPS

14 PIN	$4.50
16 PIN	4.75
24 PIN	8.50

DESIGN MATES

DM1 - Circuit Designer 54.95

DM2 - Function Generator 69.95

DM3 - RC Bridge 59.95

QT PROTO STRIPS

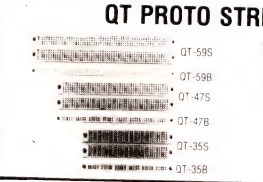

QT type	#holes	price
QT-59S	590	12.50
QT-59B	bus strip	2.50
QT-47S	470	10.00
QT-47B	bus strip	2.25
QT-35S	350	8.50
QT-35B	bus strip	2.00
QT-18S	180	4.75
QT-12S	120	3.75
QT-8S	80	3.25
QT-7S	70	3.00
Experimentor 300		$ 9.95
Experimentor 600		$10.95

$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets - 25¢ — Send 35¢ Stamp for 1977A Catalog
Dealer Discount Available — Request Pricing

NOW OPEN SATURDAYS

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
All Advertised Prices Good Thru May

PARATRONICS

LOGIC ANALYZER KIT

(as shown in Feb. Popular Electronics)

Troubleshoot any type of digital system including Microcomputers.

(includes IC, power supply, PC Board, case and manual)

LA100 KIT $189.00

DIGITAL AUTO INSTRUMENT

SEVEN DIFFERENT INSTRUMENTS!

MEETS OR EXCEEDS ORIGINAL AUTOMOTIVE SPECS.

*Please specify which **one** of the seven models you want when ordering - these **do not** all come in one unit. Each model must be bought separately.*

1 TACHOMETER 0-9900 RPM 4, 6 or 8 Cylinders

2 WATER TEMP 100-250° F

3 FUEL LEVEL Percentage Low Fuel Indicator

4 SPEEDOMETER* 0-99 MPH

5 OIL PRESSURE 0-80 PSI

6 OIL TEMP 200-350° F

7 BATTERY MONITOR ±1 Volts From 11-15 VDC

BRIGHT YELLOW ORANGE .3" LED DISPLAY!

Kit includes case, bracket and all componets — complete. Nothing else to buy! 12 Volt NEG GRD.

DIMENSIONS: 4½ x 4 x 2

KIT: $49.95

* Add $10.00 for required speed transducer **ASSEMBLED: $59.95**

DIGITAL STOPWATCH

- Bright 6 Digit LED Display
- Times to 59 minutes 59.59 seconds
- Crystal Controlled Time Base
- Three Stopwatches in One Times Single Event — Split & Taylor
- Size 4.5" x 2.15" x .90" (4½ ounces)
- Uses 3 Penlite Cells.

Kit — $39.95

Assembled — $49.95

Heavy Duty Carry Case $5.95

Stop Watch Chip Only (7205) $19.95

Timeband™

A Trademark of Fairchild Camera and Instrument Corporation

DIGITAL ALARM CLOCK $16.95

- 24-Hour Alarm
- "DOZE" Button
- 100% Solid State
- Large Red Led Display (.8" high)
- AM/PM Indicator
- Seconds Display at touch of button
- SPECIFY BLACK OR IVORY

QUARTZ DIGITAL AUTO CLOCK OR ELAPSED TIMER!

Elapsed Timer: Hrs, Mins and Secs
12 or 24 Hr Capacity
Simple Reset - Start Pushbutton Control

Complete kit includes mounting bracket, case and all components, nothing else to buy. Features MM5314 chip. Large .4" LED's. Accuracy better than ± min. per mo. internal battery backup. 12 volt non-polar operation.

DIMENSIONS: 4½" x 4" x 2"

12 or 24 HOUR MODE

Kit: $29.95

Assembled: $39.95

CASE ONLY (includes hardware, mounting bracket and bezel) **$6.50**

JE700 CLOCK

The JE700 is a low cost digital clock, but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2½" x 1". It utilizes a MAN72 high brightness readout, and the MM5314 clock chip.

12 or 24 Hour

115 VAC

$17.95

DIGITAL CLOCK KIT — 3½ INCH DIGITS

4 DIGIT KIT $49.95 — **4 DIGIT ASSEMBLED $59.95**

6 DIGIT KIT $69.95 — **6 DIGIT ASSEMBLED $79.95**

This clock features big 3½" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2" LED's. The clock operates from 117 VAC, has either 12 or 24 hr. operation. The 6 digit version is 27" x 3½" x 1½" and the 4 digit is 18" x 3½" x 1½". Kits come complete with all components, case and transformer.

Specify 12 or 24 Hour When Ordering

JE803 PROBE

The Logic Probe is a unit which is for the most part indespensible in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result

$9.95 Per Kit

printed circuit board

T²L 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only.

$9.95 Per Kit

CIRCLE 9 ON FREE INFORMATION CARD

7400N TTL

SN7400N	.16	SN7459A	.25		
SN7401N	.16	SN7460N	.22	SN74154N	1.00
SN7402N	.21	SN7470N	.45	SN74155N	.99
SN7403N	.16	SN7472N	.39	SN74156N	.99
SN7404N	.18	SN7473N	.37	SN74157N	.99
SN7405N	.24	SN7474N	.32	SN74160N	1.25
SN7406N	.20	SN7475N	.50	SN74161N	.99
SN7407N	.29	SN7476N	.32	SN74163N	.99
SN7408N	.25	SN7479N	5.00	SN74164N	1.10
SN7409N	.25	SN7480N	.50	SN74165N	1.10
SN7410N	.18	SN7482N	.98	SN74166N	1.25
SN7411N	.30	SN7483N	.70	SN74167N	5.50
SN7412N	.33	SN7485N	.89	SN74170N	2.10
SN7413N	.45	SN7486N	.39	SN74172N	8.95
SN7414N	.70	SN7488N	3.50	SN74173N	1.50
SN7416N	.35	SN7489N	2.49	SN74174N	1.25
SN7417N	.35	SN7490N	.45	SN74175N	.99
SN7420N	.21	SN7491N	.75	SN74176N	.90
SN7421N	.33	SN7492N	.49	SN74177N	.90
SN7422N	.49	SN7493N	.49	SN74180N	.99
SN7423N	.37	SN7494N	.79	SN74181N	2.49
SN7425N	.29	SN7495N	.79	SN74182N	.95
SN7426N	.29	SN7496N	.89	SN74184N	1.95
SN7427N	.37	SN7497N	4.00	SN74185N	2.20
SN7429N	.42	SN74100N	1.00	SN74186N	15.00
SN7430N	.26	SN74107N	.39	SN74187N	6.00
SN7432N	.31	SN74121N	.39	SN74188N	3.95
SN7437N	.27	SN74122N	.39	SN74190N	1.19
SN7438N	.27	SN74123N	.50	SN74191N	1.25
SN7439N	.25	SN74125N	.60	SN74192N	.89
SN7440N	.15	SN74126N	.60	SN74193N	.89
SN7441N	.89	SN74132N	1.09	SN74194N	1.25
SN7442N	.59	SN74136N	.95	SN74195N	.75
SN7443N	.75	SN74141N	1.15	SN74196N	1.25
SN7444N	.75	SN74142N	4.00	SN74197N	.75
SN7445N	.75	SN74143N	4.50	SN74198N	1.75
SN7446N	.81	SN74144N	4.50	SN74199N	1.75
SN7447N	.69	SN74145N	1.15	SN74200N	5.59
SN7448N	.79	SN74147N	2.35	SN74279N	.90
SN7450N	.26	SN74148N	2.00	SN74251N	1.79
SN7451N	.27	SN74150N	1.00	SN74284N	6.00
SN7453N	.27	SN74151N	.79	SN74285N	6.00
SN7454N	.20	SN74153N	.89	SN74367N	.75

MANY OTHERS AVAILABLE ON REQUEST
20% Discount for 100 Combined 7400's

CMOS

CD4000	.25			74C04N	.75
CD4001	.25			74C10N	.65
CD4002	.25	CD4035	1.85	74C20N	.65
CD4006	2.50	CD4040	2.45	74C30N	.65
CD4007	.25	CD4042	1.90	74C42N	2.15
CD4009	.59	CD4044	1.50	74C73N	1.50
CD4010	.59	CD4046	2.51	74C74	1.15
CD4011	25	CD4047	2.75	74C90N	3.00
CD4012	.25	CD4049	.79	74C95N	2.00
CD4013	.47	CD4050	.79	74C107N	1.25
CD4016	.56	CD4051	2.95	74C151	2.90
CD4017	1.35	CD4053	2.95	74C154	4.00
CD4019	.55	CD4060	3.25	74C157	2.15
CD4020	1.49	CD4066	1.75	74C160	3.25
CD4022	1.25	CD4069	.45	74C161	3.25
CD4023	.25	CD4071	.45	74C163	3.00
CD4024	1.50	CD4081	.45	74C164	3.25
CD4025	.25	CD4511	2.50	74C173	2.60
CD4027	.69	CD4518	2.50	74C193	2.75
CD4028	1.65	MC14566	3.00	74C195	2.75
CD4029	2.90	74C00N	.39	MC4044	4.50
CD4030	.65	74C02N	.55	MC14016	.56

LINEAR

LM300H	.80			LM1351N	1.65
LM301H	.35			LM1414N	1.75
LM301CN	.35			LM1458C	.65
LM302H	.75	LM370N	1.1.5	LM1496N	.95
LM304H	1.00	LM373N	3.25	LM1556V	1.85
LM305H	.95	LM377N	4.00	LM2111N	1.95
LM307CN	.35	LM380N	1.39	LM2901N	2.95
LM308H	1.00	LM380CN	1.05	LM3065N	.69
LM308CN	1.00	LM381N	1.79	LM3900N	.55
LM309H	1.10	LM382N	1.79	LM3905N	.60
LM309K	.99	NE501K	8.00	LM3909	1.25
LM310CN	1.15	NE510A	6.00	LM5556N	1.85
LM311H	.90	NE531H	3.00	MC5558V	1.00
LM311N	.90	NE536T	6.00	LM7525N	.90
LM318CN	1.50	NE540L	6.00	LM7535N	1.25
LM319N	1.30	NE550N	.79	8038B	4.95
LM320K-5	1.35	NE555V	.39	LM75450	.49
LM320K-5.2	1.35	NE560B	5.00	75451CN	.39
LM320K-12	1.35	NE561B	5.00	75452CN	.39
LM320K-15	1.35	NE562B	5.00	75453CN	.39
LM320T-5	1.75	NE565H	1.25	75454CN	.39
LM320T-5.2	1.75	NE565N	1.75	75491CN	.79
LM320T-8	1.75	NE566CN	1.25	75492CN	.89
LM320T-12	1.75	NE567H	1.95	75494CN	.89
LM320T-15	1.75	NE567V	1.50	**RCA LINEAR**	
LM320T-18	1.75	LM703CN	.45	CA3013	2.15
LM320T-24	1.75	LM709H	.29	CA3023	2.56
LM323K-5	9.95	LM709N	.29	CA3035	2.48
LM324N	1.80	LM710N	.79	CA3039	1.35
LM339N	1.70	LM711N	.39	CA3046	1.30
LM340K-5	1.95	LM723H	.55	CA3059	3.25
LM340K-6	1.95	LM723H	.55	CA3060	3.25
LM340K-8	1.95	LM733N	1.00	CA3080	.85
LM340K-12	1.95	LM739N	1.00	CA3081	2.00
LM340K-15	1.95	LM741CH	.35	CA3082	2.00
LM340K-18	1.95	LM741CN	.35	CA3083	1.60
LM340K-24	1.95	LM741-14N	.39	CA3086	.85
LM340T-5	1.75	LM747H	.79	CA3089	3.75
LM340T-6	1.75	LM747N	.79	CA3091	10.20
LM340T-8	1.75	LM748H	.39	CA3102	2.95
LM340T-12	1.75	LM748N	.39	CA3123	2.15
LM340T-15	1.75	LM1303N	.90	CA3130	1.39
LM340T-18	1.75	LM1304N	1.19	CA3140	1.25
LM340T-24	1.75	LM1305N	1.40	CA3600	1.75
LM350N	1.00	LM1307N	.85	RC4194	5.95
LM351CN	.65	LM1310N	2.95	RC4195	3.25

74LS00 TTL

74LS00	29			74LS139	1.95
74LS02	.29			74LS151	1 55
74LS03	29	74LS74	49	74LS153	1 89
74LS04	35	74LS75	69	74LS157	1 55
74LS05	.35	74LS76	49	74LS162	2 25
74LS08	29	74LS83	1.75	74LS163	2 25
74LS10	29	74LS85	2.49	74LS164	1 95
74LS13	69	74LS86	49	74LS175	1.95
74LS14	1 75	74LS90	1.25	74LS181	3 69
74LS20	29	74LS92	1.25	74LS190	2 85
74LS26	39	74LS93	1 25	74LS191	2 85
74LS27	39	74LS95	1 95	74LS192	2 85
74LS28	39	74LS96	1 89	74LS193	2 85
74LS30	29	74LS107	59	74LS194	1 89
74LS32	39	74LS109	59	74LS195	1 89
74LS40	39	74LS112	59	74LS257	1 75
74LS51	29	74LS132	1 25	74LS260	55
74LS55	29	74LS136	59	74LS279	79
74LS73	49	74LS138	1 89	74LS670	3 95

CLOCK CHIPS

MM5309	6 Digit, BCD Outputs, Reset PIN.	$9 95
MM5311	6 Digit, BCD Outputs, 12 or 24 Hour	4.95
MM5312	4 Digit, BCD Outputs, 1 PPS Output	4.95
MM5314	6 Digit, 12 or 24 Hour, 50 or 60 Hz	4.95
MM5316	4 Digit, Alarm, 1 PPS Output	6.95
MM5318	Video Clock Chip, For Use With (MM5841 - $9.95)	9.95
CT7001	6 Digit, Calendar, Alarm, 12 or 24 Hour	5.95

DATA HANDBOOKS

7400	Pin-out & Description of 5400/7400 ICS	$2.95
CMOS	Pin-out & Description of 4000 Series ICS	$2.95
Linear	Pin-out & Functional Description	$2.95

ALL THREE HANDBOOKS $6.95

There is only *one*

James ELECTRONICS

They can try and copy our ad,
BUT
They can't copy our service!

DISCRETE LEDS

.125" dia.			.200" dia			.185" dia.			.200" dia.			.190" dia.		
XC209	Red	10/$1	XC22	Red	10/$1	XC526	Red	10/$1	XC556	Red	10/$1	XC111	Red	10/$1
XC209	Green	4/$1	XC22	Green	4/$1	XC526	Green	4/$1	XC556	Green	4/$1	XC111	Green	4/$1
XC209	Orange	4/$1	XC22	Yellow	4/$1	XC526	Yellow	4/$1	XC556	Yellow	4/$1	XC111	Yellow	4/$1
XC209	Yellow	4/$1	XC22	Orange	4/$1	XC526	Orange	4/$1	XC556	Orange	4/$1	XC111	Orange	4/$1
			SSL-22	RT	4/$1	XC526	Clear	4/$1	XC556	Clear	7/$1			

.085" dia. MV50 - Red - 6/$1

INFRA-RED LED ¼" x ¼" x 1/16" Flat **5/$1.00**

SPECIAL * — XC556 Red 100/$8.00 1000/$60.00 — SPECIAL *

DISPLAY LEDS

DL707 DL33B

TYPE	POLARITY	HT		TYPE	POLARITY	HT	
MAN 1	Common Anode	.270	2.95	MAN 3640	Common Cathode-orange	.300	1.75
MAN 2	5 x 7 Dot Matrix	.300	4.95	MAN 4710	Common Anode-Red	.400	1.95
MAN 3	Common Cathode	.125	3/1.00	DL701	Common Anode-red ±	.300	99
MAN 4	Common Cathode	.187	1.95	DL704	Common Cathode	.300	99
MAN 7	Common Anode	300	1 25	DL707	Common Anode	.300	99
MAN 7G	Common Anode-green	.300	1.95	MAN 4740	Common Anode-Red	.400	.99
MAN 7Y	Common Anode-yellow	.300	1.95	DL741	Common Anode	.600	1.50
MAN 52	Common Anode-green	.300	.99	DL 747	Common Anode	.600	2.25
MAN 64	Common Anode-red	.400	.99	DL 750	Common Cathode	600	2.49
MAN 74	Common Cathode	.300	1.50	DL 33B	Common Cathode	.110	.50
MAN 82	Common Anode-yellow	.300	.99	FND70	Common Cathode	.250	.75
MAN 84	Common Cathode-yellow	.300	.99	FND503	Common Cathode	.500	1.00
MAN 3620	Common Anode -orange	.300	1 75	FND507	Common Anode	500	1.00

FACTORY REJECTS ATARI GAME BOARDS

BOARD A — 8½" x 16" — **$6.95 ea.** ONLY 500 EA AVAILABLE
Over 60 each reusable IC's
Misc. Transistors, Resistors,
Diodes, Caps, Crystals, Switch, etc.

DELUXE BOARD B — 11½" x 18" — **$9.95 ea.** ONLY 500 EA. AVAILABLE
Over 100 each reusable IC's
Misc. Tranistors, Resistors,
Diodes, Caps, Crystals, Switches, LEDS, etc.

NEW AY-3-8500-1 TV GAME CHIP

- Score display
- Selectable angles, speed and bat size
- Auto or manual ball service
- Realism sounds
- 6 Games — tennis, hockey/soccer, squash, pelota/practice and two rifle games

28 Lead Dual In Line

The circuit is intended to be battery powered. Minimum number of external components required for complete system.

$24.95

IC SOLDERTAIL — LOW PROFILE (TIN) SOCKETS

	1-24	25-49	50-100		1-24	25-49	50-100
8 pin	$ 17	16	.15	24 pin	$ 38	37	.36
14 pin	.20	19	18	28 pin	45	.44	43
16 pin	22	.21	.20	36 pin	.60	.59	58
18 pin	.29	28	27	40 pin	63	62	61
22 pin	.37	.36	.35				

SOLDERTAIL STANDARD (TIN)

	1-24	25-49	50-100		1-24	25-49	50-100
14 pin	$ 27	.25	.24	28 pin	$ 99	.90	81
16 pin	30	.27	.25	36 pin	1.39	1.26	1 15
18 pin	.35	32	30	40 pin	1 59	1.45	1.30
24 pin	.49	.45	42				

SOLDERTAIL STANDARD (GOLD)

	1-24	25-49	50-100		1-24	25-49	50-100
8 pin	$.30	.27	.24	24 pin	$. 70	.63	.57
14 pin	.35	.32	.29	28 pin	1.10	1.00	.90
16 pin	.38	.35	.32	36 pin	1.75	1.40	1.26
18 pin	.52	.47	.43	40 pin	1.75	1.59	1 45

WIRE WRAP SOCKETS (GOLD) LEVEL #3

	1-24	25-49	50-100		1-24	25-49	50-100
10 pin	$.45	.41	.37	24 pin	$1 05	.95	.85
14 pin	.39	.38	.37	28 pin	1.40	1.25	1.10
16 pin	.43	.42	.41	36 pin	1.59	1.45	1.30
18 pin	.75	.68	.62	40 pin	1.75	1.55	1.40

Plastic Push Button Switch

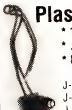

- **18 AWG Solid Wire - 5" Long**
- **.50 (wide) X .60 (high) ⅜-27 Thread**
- **8 AMP @ 14 Volt - 1 AMP @ 10 Volt**

		1-9	10-Up
J-188-1	Push On-Push Off	.59	.49
J-188-2	Normally Open	.59	.49
J-188-3	Normally Closed	.59	.49

MINATURE TOGGLE SWITCH

JMT-221	DPDT	on/off/on	$1.95
JMT-223	DPDT	on/none/on	$1.75
JMT-121	SPDT	on/off/on	$1.50
JMT-123	SPDT	on/none/on	$1.25

CLIPLITE 8/$1.49

LED MOUNTING SYSTEM
use with XC556 LEDS
Specify Colors — Red - Green - Amber - Yellow

DIP SWITCHES

SPST Slide Action

#206-4 (8 pin dip) 4 switch unit **$1.75 ea.**
#206-7 (14 pin dip) 7 switch unit **$1.95 ea.**
#206-8 (16 pin dip) 8 switch unit **$2.25 ea.**

50 PCS. RESISTOR ASSORTMENTS $1.75 PER ASST.

ASST. 1	5 ea.	10 OHM 27 OHM	12 OHM 33 OHM	15 OHM 39 OHM	18 OHM 47 OHM	22 OHM 56 OHM	1/4 WATT 5% = 50 PCS.
ASST. 2	5 ea.	68 OHM 180 OHM	82 OHM 220 OHM	100 OHM 270 OHM	120 OHM 330 OHM	150 OHM 390 OHM	1/4 WATT 5% = 50 PCS.
ASST. 3	5 ea.	470 OHM 1.2K	560 OHM 1.5K	680 OHM 1.8K	820 OHM 2.2K	1K 2.7K	1/4 WATT 5% = 50 PCS.
ASST. 4	5 ea.	3.3K 8.2K	3.9K 10K	4.7K 12K	5.6K 15K	6.8K 18K	1/4 WATT 5% = 50 PCS.
ASST. 5	5 ea.	22K 56K	27K 68K	33K 82K	39K 100K	47K 120K	1/4 WATT 5% = 50 PCS.
ASST. 6	5 ea.	150K 390K	180K 470K	220K 560K	270K 680K	330K 820K	1/4 WATT 5% = 50 PCS.
ASST. 7	5 ea.	1M 2.7M	1.2M 3.3M	1 5M 3.9M	1.8M 4.7M	2.2M 5 6M	1/4 WATT 5% = 50PCS.

ASST. 8R Includes Resistor Assortments 1-7 (350 PCS.) **$10.95 ea.**

$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets - 25¢ — Send 35¢ Stamp for 1977A Catalog
Dealer Discount Available — Request Pricing

NOW OPEN SATURDAYS

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
All Advertised Prices Good Thru May

WIRE WRAP CENTER

HOBBY-WRAP TOOL-BW-630

- Battery Operated (Size C)
- Weighs ONLY 11 Ounces
- Wraps 30 AWG Wire onto Standard DIP Sockets (.025 inch) Complete with built-in bit and sleeve

$34.95
(batteries not included)

WIRE-WRAP KIT — WK-2-W

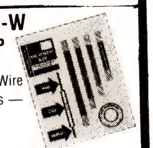

WRAP • STRIP • UNWRAP

- Tool for 30 AWG Wire
- Roll of 50 Ft. White or Blue 30 AWG Wire
- 50 pcs. each 1", 2", 3" & 4" lengths — pre-stripped wire.

$11.95

WIRE WRAP TOOL WSU-30

WRAP • STRIP • UNWRAP - $5.95

WIRE WRAP WIRE — 30 AWG

25 ft. min. $1.25 50 ft. $1.95 100 ft. $2.95 1000 ft. $15.00
SPECIFY COLOR — White - Yellow - Red - Green - Blue - Black

CUTTER CRIMPER TOOL (CS-8)

- Plier Nose (serrated-jaw)
- Scissors Action Cutting
- 6 Bolt Cutters (4-40, 5-40, 6-32, 8-32, 10-32, 10-24)
- Crimp Stations (7mm Auto — 22-20 to 12-X0 elect.)
- "Up-Front" Wire Cutting
- Scissors Action Stripping (No. 22-20 to No. 10)
- Crimp Stations — insulated (2w-20 to 12-10 elect.)

Actual Size - 8¼" length **$8.50**

Permacel Electrical Tape

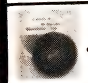

- ¾" (wide) X 66 ft. (long) • All weather • Not import

$1.25 per roll — $9.95 per 10 roll package

ZENERS — DIODES — RECTIFIERS

TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE
1N746	3.3	400mm	4/1.00	1N4005	600 PIV	1 AMP	10/1.00
1N751A	5.1	400m	4/1.00	1N4006	800 PIV	1 AMP	10/1.00
1N752	5.6	400m	4/1.00	1N4007	1000 PIV	1 AMP	10/1.00
1N753	6.2	400m	4/1.00	1N3600	50	200m	6/1.00
1N754	6.8	400m	4/1.00	1N4148	75	10m	15/1.00
1N959	8.2	400m	8/1.00	1N4154	35	10m	12/1.00
1N965B	15	400m	4/1.00	1N4305	75	25m	20/1.00
1N5232	5.6	500m	28	1N4734	5.6	1w	28
1N5234	6.2	500m	28	1N4735	6.2	1w	28
1N5235	6.8	500m	28	1N4736	6.8	1w	28
1N5236	7.5	500m	28	1N4738	8.2	1w	28
1N456	25	40m	6/1.00	1N4742	12	1w	28
1N458	150	7m	6/1.00	1N4744	15	1w	28
1N485A	180	10m	6/1.00	1N1183	50 PIV	35 AMP	1.60
1N4001	50 PIV	1 AMP	12/1.00	1N1184	100 PIV	35 AMP	1.70
1N4002	100 PIV	1 AMP	12/1.00	1N1185	150 PIV	35 AMP	1.50
1N4003	200 PIV	1 AMP	12/1.00	1N1186	200 PIV	35 AMP	1.80
1N4004	400 PIV	1 AMP	12/1.00	1N1188	400 PIV	35 AMP	3.00

SCR AND FW BRIDGE RECTIFIERS

C36D	15A @ 400V	SCR	$1.95
C38M	35A @ 200V	SCR	1.95
2N2328	1.6A @ 200V	SCR	.50
MDA 980-1	12A @ 50V	FW BRIDGE REC.	1.95
MDA 980-3	12A @ 200V	FW BRIDGE REC.	1.95

TRANSISTORS

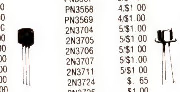

MPS A05	5/$1.00	PN3567	3/$1.00	PN4249	4/$1.00
MPS A06	5/$1.00	PN3568	4/$1 00	PN4250	4/$1.00
2N2219A	3/$1.00	PN3569	4/$1.00	2N4400	4/$1.00
2N2221	4/$1.00	2N3704	5/$1.00	2N4401	4/$1.00
2N2222A	5/$1.00	2N3705	5/$1 00	2N4402	4/$1.00
2N2369	5/$1.00	2N3706	5/$1 00	2N4403	4/$1.00
2N2369A	4/$1.00	2N3707	5/$1.00	2N4409	5/$1 00
2N2484	4/$1.00	2N3711	5/$1 00	2N5086	4/$1 00
2N2906A	4/$1.00	2N3724	$. 65	2N5087	4/$1.00
2N2907A	5/$1.00	2N3725	$1 00	2N5088	4/$1.00
2N2925	5/$1.00	2N3903	5/$1.00	2N5089	4/$1.00
2N3053	2/$1.00	2N3904	4/$1 00	2N5129	5/$1.00
2N3055	$ .89	2N3905	4/$1 00	2N5138	5/$1.00
MJE3055	$1.00	2N3906	4/$1.00	2N5139	5/$1 00
MJE2955	$1.25	2N4013	3/$1 00	2N5209	5/$1.00
2N3392	5/$1.00	2N4014	3/$1.00	2N5951	5/$1 00
2N3398	5/$1.00	2N4123	10/$1.00	C106B1SCR	2/$1 00
				2N5432	$2.00

CAPACITOR CORNER

50 VOLT CERAMIC DISC CAPACITORS

	1-9	10-49	50-100		1-9	10-49	50-100
10 pf	.05	.04	.03	.001μF	.05	.04	.035
22 pf	.05	.04	.03	.0047μF	.05	.04	.035
47 pf	.05	.04	.03	.01μF	.05	.04	.035
100 pf	.05	.04	.03	.022μF	.06	.05	.04
220 pf	.05	.04	.03	.047μF	.06	.05	.04
470 pf	.05	.04	.035	.1μF	.12	.09	.075

100 VOLT MYLAR FILM CAPACITORS

.001mf	.12	.10	.07	.022mf	.13	.11	.08
.0022	.12	.10	.07	.047mf	.21	.17	.13
.0047mf	.12	.10	.07	.1mf	.27	.23	.17
.01mf	.12	.10	.07	.22mf	.33	.27	.22

+20% DIPPED TANTALUMS (SOLID) CAPACITORS

.1/35V	.28	.23	.17	1.5/35V	.30	.26	.21
.15/35V	.28	.23	.17	2.2/25V	.31	.27	.22
.22/35V	.28	.23	.17	3.3/25V	.31	.27	.22
.33/35V	.28	.23	.17	4.7/25V	.32	.28	.23
.47/35V	.28	.23	.17	6.8/25V	.36	.31	.25
.68/35V	.28	.23	.17	10/25V	.40	.35	.29
1.0/35V	.28	.23	.17	15/25V	.63	.50	.40

MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS

Axial Lead				Radial Lead			
.47/50V	.15	.13	.10	.47/25V	.15	.13	.10
1.0/50V	.16	.14	.11	.47/50V	.16	.14	.11
3.3/50V	.15	.13	.10	1.0/16V	.15	.13	.10
4.7/25V	.16	.14	.12	1.0/25V	.16	.14	.11
10/25V	.15	.13	.10	1.0/50V	.16	.14	.11
10/50V	.16	.14	.12	4.7/16V	.15	.13	.10
22/25V	.17	.15	.12	4.7/25V	.15	.13	.10
22/50V	.24	.20	.18	4.7/50V	.16	.14	.11
47/25V	.19	.17	.15	10/16V	.14	.12	.09
47/50V	.25	.21	.19	10/25V	.15	.13	.10
100/25V	.24	.20	.18	10/50V	.16	.14	.12
100/50V	.35	.30	.28	47/50V	.24	.21	.19
220/25V	.32	.28	.25	100/16V	.19	.15	.14
220/50V	.45	.41	.38	100/25V	.24	.20	.18
470/25V	.33	.29	.27	100/50V	.35	.30	.28
1000/16V	.55	.50	.45	220/16V	.23	.17	.16
2200/16V	.70	.62	.55	470/25V	.31	.28	.26

CIRCLE 10 ON FREE INFORMATION CARD

TTL 7400N

SN7400N	.13	SN74125N	.40
SN7401N	.14	SN74126N	.40
SN7402N	.14	SN74128N	.59
SN7403N	.14	SN74132N	.69
SN7404N	.17	SN74136N	.59
SN7405N	.17	SN74141N	.88
SN7406N	.25	SN74142N	3.70
SN7407N	.25	SN74143N	3.98
SN7408N	.17	SN74144N	3.98
SN7409N	.17	SN74145N	.69
SN7410N	.14	SN74147N	1.58
SN7411N	.20	SN74148N	1.19
SN7412N	.21	SN74150N	.95
SN7413N	.39	SN74151N	.61
SN7414N	.64	SN74153N	.61
SN7416N	.24	SN74154N	.95
SN7417N	.29	SN74155N	.70
SN7420N	.14	SN74156N	.64
SN7421N	.20	SN74157N	.59
SN7422N	.20	SN74159N	2.50
SN7423N	.25	SN74160N	.85
SN7425N	.25	SN74161N	.85
SN7426N	.22	SN74162N	.85
SN7427N	.25	SN74163N	.85
SN7428N	.28	SN74164N	.98
SN7430N	.14	SN74165N	.97
SN7432N	.23	SN74166N	1.09
SN7433N	.30	SN74167N	2.75
SN7437N	.21	SN74170N	1.69
SN7438N	.21	SN74172N	8.75
SN7440N	.14	SN74173N	1.24
SN7442N	.37	SN74174N	.94
SN7443N	.68	SN74175N	.84
SN7444N	.85	SN74176N	.77
SN7445N	.65	SN74177N	.76
SN7446AN	.70	SN74178N	1.19
SN7447AN	.67	SN74179N	1.49
SN7448N	.69	SN74180N	.67
SN7450N	.14	SN74181N	1.94
SN7451N	.14	SN74182N	.59
SN7453N	.14	SN74184N	1.75
SN7454N	.14	SN74185AN	1.74
SN7460N	.14	SN74186N	6.95
SN7470N	.26	SN74188N	2.98
SN7472N	.25	SN74190N	1.04
SN7473N	.29	SN74191N	1.04
SN7474N	.29	SN74192N	.84
SN7475N	.46	SN74193N	.84
SN7476N	.30	SN74194N	.89
SN7480N	.35	SN74195N	.54
SN7481AN	.95	SN74196N	.87
SN7482N	.55	SN74197N	.73
SN7483AN	.65	SN74198N	1.64
SN7484AN	1.50	SN74199N	1.64
SN7485N	.84	SN74221N	1.14
SN7486N	.30	SN74246N	1.95
SN7489N	1.85	SN74247N	1.70
SN7490AN	.43	SN74248N	1.75
SN7491AN	.59	SN74249N	1.75
SN7492AN	.44	SN74251N	1.05
SN7493AN	.44	SN74265N	.85
SS7494N	.69	SN74278N	1.99
SN7495AN	.67	SN74279N	.57
SN7496N	.65	SN74283N	1.39
SN7497N	2.50	SN74284N	4.50
SN74100N	.97	SN74285N	4.50
SN74104N	.42	SN74290N	.85
SN74105N	.42	SN74293N	.63
SN74107N	.28	SN74298N	1.64
SN74109N	.47	SN74351N	1.92
SN74110N	.52	SN74365N	.65
SN74111N	.69	SN74366N	.65
SN74116N	1.50	SN74367N	.65
SN74120N	1.40	SN74368N	.65
SN74121N	.34	SN74390N	1.40
SN74122N	.38	SN74393N	1.40
SN74123N	.48	SN74490N	1.90

TTL LOW POWER SCHOTTKY

SN64LS00N	.23	SN74LS174N	1.25
SN74LS01N	.23	SN74LS175N	1.25
SN74LS02N	.23	SN74LS181N	3.30
SN74LS03N	.23	SN74LS190N	1.80
SN74LS04N	.28	SN74LS191N	1.80
SN74LS05N	.28	SN74LS192N	1.80
SN74LS08N	.23	SN74LS193N	1.80
SN74LS09N	.23	SN74LS194AN	1.30
SN74LS10N	.23	SN74LS195AN	1.30
SN74LS11N	.23	SN74LS196N	1.40
SN74LS12N	.25	SN74LS197N	1.40
SN74LS13N	.65	SN74LS221N	1.30
SN74LS14N	1.35	SN74LS240N	2.50
SN74LS15N	.23	SN74LS241N	2.40
SN74LS20N	.23	SN74LS242N	2.40
SN74LS21N	.23	SN74LS243N	2.40
SN74LS22N	.23	SN74LS244N	2.50
SN74LS26N	.37	SN74LS247N	1.30
SN74LS27N	.27	SN74LS248N	1.30
SN74LS28N	.30	SN74LS249N	1.30
SN74LS30N	.23	SN74LS251N	1.50
SN74LS32N	.33	SN74LS253N	1.50
SN74LS33N	.37	SN74LS257N	1.40
SN74LS37N	.37	SN74LS258N	1.40
SN74LS38N	.37	SN74LS261N	2.95
SN74LS40N	.27	SN74LS266N	.55
SN74LS42N	.89	SN74LS279N	.75
SN74LS47N	1.10	SN74LS283N	1.35
SN74LS48N	1.10	SN74LS290N	1.30
SN74LS49N	1.10	SN74LS293N	1.30
SN74LS51N	.23	SN74LS295AN	1.75
SN74LS54N	.23	SN74LS298AN	1.75
SN74LS55N	.23	SN74LS324AN	2.25
SN74LS63N	1.75	SN74LS352AN	1.45
SN74LS73N	.45	SN74LS353AN	1.70
SN74LS74N	.45	SN74LS365AN	.69
SN74LS75N	.65	SN74LS366AN	.69
SN74LS76N	.45	SN74LS367AN	.69
SN74LS78N	.45	SN74LS368AN	.69
SN74LS83AN	1.39	SN74LS375AN	.75
SN74LS85N	1.60	SN74LS386AN	.59
SN74LS86N	.48	SN74LS395AN	1.95
SN74LS90N	.89	SN74LS670AN	2.75
SN74LS91N	1.15		
SN74LS92N	.85		
SN74LS93BN	.85		
SN74LS95AN	1.50		
SN74LS96N	1.65		
SN74LS107N	.45		
SN74LS109	.50		
SN74LS112N	.45		
SN74LS113N	.45		
SN74LS114N	.45		
SN74LS122N	.89		
SN74LS123N	.99		
SN74LS124N	1.95		
SN74LS125N	.75		
SN74LS126N	.75		
SN74LS132N	1.19		
SN74LS136N	.50		
SN74LS138N	1.25		
SN74LS139N	1.35		
SN74LS145N	1.19		
SN74LS151N	.99		
SN74LS153N	.99		
SN74LS155N	1.45		
SN74LS156N	1.45		
SN74LS157N	.99		
SN74LS158N	1.10		
SN74LS160N	1.50		
SN74LS161N	1.50		
SN74LS162N	1.50		
SN74LS163N	1.50		
SN74LS164N	1.60		
SN74LS168N	2.25		
SN74LS169N	2.25		
SN74LS170N	2.70		

CMOS

CD4000BE	.09	CD4024BE	.67
CD4001BE	.18	CD4025BE	.17
CD4002BE	.13	CD4026BE	1.39
CD4006BE	.99	CD4027BE	.39
CD4007BE	.17	CD4028BE	.75
CD4008BE	.80	CD4029BE	.79
CD4009BE	.37	CD4030BE	.37
CD4010BE	.37	CD4033BE	1.60
CD4011BE	.18	CD4034BE	2.95
CD4012BE	.17	CD4035BE	.99
CD4013BE	.37	CD4040BE	.99
CD4014BE	.89	CD4041BE	.67
CD4015BE	.89	CD4042BE	.63
CD4016BE	.37	CD4043BE	.45
CD4017BE	.94	CD4044BE	.45
CD4018BE	.99	CD4046BE	2.45
CD4019BE	.42	CD4047BE	2.45
CD4020BE	1.04	CD4049BE	.37
CD4021BE	.99	CD4050BE	.37
CD4022BE	.89	CD4051BE	1.15
CD4023BE	.18	CD4052BE	1.15
		CD4053BE	1.19
		CD4055BE	1.29
		CD4060BE	1.40
		CD4066BE	.59
		CD4068BE	.24
		CD4069BE	.24
		CD4070BE	.24
		CD4071BE	.24
		CD4072BE	.29
		CD4073BE	.29
		CD4075BE	.29
		CD4076BE	1.05
		CD4078BE	.24
		CD4081BE	.24
		CD4082BE	.29
		CD4085BE	.75
		CD4086BE	.75
		CD4502BE	1.15
		CD4507BE	.52
		CD4510BE	1.05
		CD4511BE	1.25
		CD4512BE	1.15
		CD4514BE	2.50
		CD4515BE	2.50
		CD4516BE	1.10
		CD4518BE	.90
		CD4519BE	.79
		CD4520BE	.79
		CD4522BE	1.98
		CD4526BE	1.50
		CD4527BE	1.50
		CD4528BE	1.20
		CD4531BE	1.25
		CD4539BE	1.20
		CD4555BE	.75
		CD4556BE	.75
		CD4585BE	1.80
		74C85/40085PC	1.20
		74C160/40160PC	1.50
		74C161/40161PC	1.50
		74C162/40162PC	1.50
		74C163/40163PC	1.50
		74C174/40174PC	1.40
		74C175/40175PC	1.40
		74C192/40192PC	1.50
		74C193/40193PC	1.50
		74C195/40195PC	1.40

MOS AND BI-POLAR MEMORIES

C1702A	(1 Microsecond) 256 X 8 EPROM	8.95
C1702A	(1.5 Microsecond) 256 X 8 EPROM	5.95
C2708	1K X 8 EPROM (450 NS)	49.00
8080A	8 Bit MOS Cpu (2 Microseconds)	14.95
2102-1P	1K Static Ram 1024 X 1 (450 NS)	2.50
3342PC	Quad 64 Bit Static Shift Register	4.50
3347PC	Quad 80 Bit Static Shift Register	4.50
3341APC	4 X 64 MOS Fifo 1 Mhz Shift Register	4.50
TMS0117NC	Decimal Arithmetic Processor	10.00
LCM1001	Microprocessor Learning Module	149.95
TMS4024NC	64 X 9 Fifo	8.95
TMS4050NL	4K Dynamic Ram Plastic 300NS (18 Pin)	6.95
TMS4060NL	4K Dynamic Ram Plastic 300NS (22 Pin)	6.95
AY5-1013P	8 Bit Uart	6.95
Semi 4804A	4K Static Ram 1024 X 4 (450 NS) Single 5V Supply	14.95
93415PC	1K Ram 40 NS Open Collector	11.00
93425PC	1K Ram 40 NS Tri-State	11.00
AM2901DC	4 Bit Bi-Polar Microprocessor Slice	31.50
AM2902PC	Carry Look Ahead Circuit	3.18
AM2905PC	Quad 2 Input Bus Transceiver	8.10
AM2907PC	Quad Bus Transceiver with Tri-State Receiver and Parity	7.00
AM2909PC	4 Bit Cascadable Microprogram Sequencer	7.15
AM2918PC	Quad Deregister with Standard and Tri-State Outputs	4.32
F8 Kit	8 Bit Microprocessor Evaluation Kit With Software	185.00

TEXAS INSTRUMENTS DATA BOOKS

STK NO.	DESCRIPTION	PRICE
LCB1011	Understanding Solid State Electronics	2.95
LCB1891	Software Design for Microprocessors	12.95
LCC4041	Power Data Book	3.95
LCC4112	TTL Data Book	4.95
LCC4131	Transistor and Diode Data Book	4.95
LCC4151	Linear and Interface I.C. Data Book	3.95
LCC4200	Semiconductor Memories Data Book	2.95
LCC4230	Optoelectronics Data Book	2.95
LCC4241	Linear Control Circuits Data Book	2.95

FAIRCHILD DATA BOOKS

Power Data Book	3.00
Bi-Polar Memory Data Book	2.50
Linear Integrated Circuit Data Book	2.95
Low Power Schottky and Macrologic TTL Interface Data Book	1.75
	1.00

Raytheon Linear Integrated Circuit Data Book 1.50

Solid State Scientific CMOS 'B' Series Data Book 2.50

Unitrode Semiconductor Data Book 4.95

STANDARD MICROSYSTEMS

COM2502	8 Bit Uart	7.95
COM2601	Universal Synchronous Recevier Transmitter	23.50
COM2017	8 Bit Uart	8.50

"ONLY MAJOR MANUFACTURERS SUPPLIED"

"This is a partial listing. Our complete catalogue lists many more device types & series which are available" "Our quality cannot be surpassed".

Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Telephone Orders & Enquiries (617) 879-0077 New Catalogue available on request

MINIMUM ORDER $10.00 ADD $1.00 TO COVER POSTAGE & HANDLING

NOW IN CANADA 2 Locations

5647 Ferrier st. Montreal, Quebec Tel.(514) 735-6429

44 Fasken Dr-Unit 25 Rexdale, Ontario Tel.(416) 677-4287

Canadian customers add an additional 30% for duty and handling. All federal and provincial sales taxes extra.

U.S. GOV'T ELECTRONIC SURPLUS

• **Nationally Known - World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.**

AUTOMATIC BATT. CHARGER

• (**ITEM #11-018**) - - Charges 12-volt batteries at 2-ampere rate. Turns off when battery reaches full charge, turns on when battery is low, automatically. Can be mounted permanently in engine compartment. 5½" x 3¾" x 2¼".

$12.95 (3½ lbs.)

SNAP-AROUND VOLT-AMMETER

• (**ITEM #21-1028**) - - **"MINIPROBE"** clamp type AC ammeter-voltmeter. Small enough to carry in shirt pocket. Will measure 0 to 50-amperes, 0 to 250-volts. Furnished with test leads. Overall size 4-1/2" x 2-3/4" x 1". (1 lb.) **List $33.00**

$22.95

STANDARD DIAL TELEPHONE

• (**ITEM #715**) - - Same as used on commercial systems in U.S.A. Use as extension to private system. Connect several together for local intercom system. Instructions furnished.

$8.79 **Original Cost $24.50** (9 lbs.)

RUNNING TIME METER

• (**ITEM #2188**) - - Record number of operating hours of electric lights, electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths to 9,999.99 hours. For 115-volts, 60-cycles. 4¼" x 3" x 2½". (2 lbs.)

Cost $29.00

$4.39

SPECIAL SALE
Correspondence Course In ELECTRICAL ENGINEERING

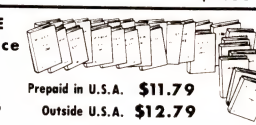

Prepaid in U.S.A. $11.79
Outside U.S.A. $12.79

• (**ITEM #9-181**) - - Technical training at low cost! Lincoln Engineering School suspended Correspondence Course because of rising costs. Limited number of Electrical Engineering Courses are available without exams and grading services. Consists of fifteen lesson books, each with associated exams and standard answers. Book showing how to build prize-winning Home Experimental Laboratory Bench included at no extra cost.

ALL ITEMS SHIPPED F.O.B. LINCOLN, NEBR.
Order Direct From Ad — — Send For FREE Catalog

SURPLUS CENTER

DEPT. RE-057 **LINCOLN, NEBR. 68501**

CIRCLE 15 ON FREE INFORMATION CARD

BUILD YOUR OWN SPEAKERS AND SAVE UP TO 50%.

Send for our free, fact-packed 40-page catalog manual and learn how to assemble your own multi-element stereo speakers from scratch or from kits. Our catalog includes chapters on design, construction, x-overs, enclosures, midranges, woofers, tweeters and horns. Write us today.

SPEAKERLAB
Dept. RE-A 5500 35th N E
Seattle, Washington 98105

COLOR bar generator, 16 different patterns with single MOS IC. Complete, detailed plans $2.00. TV tennis game plans $2.00. **ARS SYSTEMS,** POB 61922, Sunnyvale, CA 94088

FREE KIT Catalog

STOP! Take a minute & let us send our latest kit catalog. If you like, send us the name & address of a friend who may also be interested and we'll include to you our booklet "How to build-electronic thermometer"

contains TEST & EXPERIMENTER'S EQUIP.

DAGE SCIENTIFIC INSTRUMENTS BOX 1054R LIVERMORE CA 94550

Burglar. Smoke Fire Alarm Catalog

• Billions of dollars lost annually due to lack of protective warning alarms.

FREE CATALOG Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.

Burdex Security Co.

Box 82209 Dept. RE Lincoln, Ne. 68501

CIRCLE 33 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

10% OFF WITH $25 ORDER
15% OFF WITH $100 ORDER

THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

TTL

7400	.13	7451	.17	74153	.89
7401	.16	7453	.17	74154	1.20
7402	.15	7454	.17	74155	.97
7403	.15	7460		74156	.97
7404	.16	7464	.35	74157	.99
7405	.19	7465	.35	74158	1.79
7406	.20	7470	.30	74160	1.23
7407	.28	7472	.30	74161	.97
7408	.18	7473	.35	74162	1.39
7409	.19	7474	.28	74163	1.09
7410	.16	7475	.49	74164	.99
7411	.25	7476	.30	74165	.99
7413	.43	7483	.68	74166	1.25
7414	.65	7485	.88	74170	2.10
7416	.35	7486	.40	74173	1.49
7417	.35	7489	2.25	74174	1.23
7420	.16	7490	.43	74175	.97
7422	.30	7491	.75	74176	.89
7423	.29	7492	.48	74171	.84
7425	.27	7493	.48	74180	.90
7426	.26	7494	.78	74181	2.45
7427	.29	7495	.79	74182	.79
7430	.20	7496	.79	74184	1.90
7432	.23	74100	.98	74185	2.20
7437	.25	74105	.44	74187	5.75
7438	.25	74107	.37	74190	1.15
7440	.15	74121	.38	74191	1.25
7441	.89	74122	.38	74192	.95
7442	.59	74123	.65	74193	.85
7443	.73	74125	.54	74194	1.25
7444	.73	74126	.58	74195	.74
7445	.73	74132	.89	74916	1.25
7446	.81	74141	1.04	74197	.73
7447	.79	74145	1.04	74198	1.73
7448	.79	74150	.97	74199	1.69
7450	.17	74151	.79	74200	5.45

LOW POWER

74L00	.29	74L51	.29	74L90	1.40
74L02	.29	74L55	.29	74L91	-1.20
74L03	.23	74L71	.29	74L93	1.50
74L04	.29	74L72	.45	74L95	1.50
74L06	.29	74L73	.56	74L98	2.25
74L10	.29	74L74	.56	74L164	2.25
74L20	.29	74L78	.75	74L165	2.30
74L30	.29	74L85	1.09		
74L42	1.39	74L86	.65		

LOW POWER SCHOTTKY

74LS00	.36	74LS32	.38	74LS95	2.09
74LS02	.36	74LS40	.45	74LS107	.59
74LS04	.36	74LS42	1.40	74LS164	2.20
74LS08	.38	74LS74	.59	74LS193	2.20
74LS10	.36	74LS90	1.30	74LS197	2.20
74LS20	.36	74LS93	1.30		

HIGH SPEED

74H00	.25	74H22	.25	74H61	.25
74H01	.25	74H30	.25	74H62	.25
74H04	.25	74H40	.25	74H74	.39
74H08	.25	74H50	.25	74H101	.58
74H10	.25	74H52	.25	74H102	.58
74H11	.25	74H53	.25	74H103	.60
74H20	.25	74H55	.25	74H106	.72
74H21	.25	74H60	.25	74H108	.72

SCHOTTKY

74S00	.59	74S08	.68	74S22	.65
74S02	.59	74S10	.65	74S32	.68
74S03	.59	74S20	.65	74S74	.68
74S04	.72				

8000 (NATIONAL)

8091	.61	8220	1.49	8811	.65
8092	.61	8230	2.19	8812	1.02
8095	1.25	8288	1.49	8822	2.19
8121	.80	8520	1.16	8830	2.19
8123	1.43	8552	2.19	8831	2.19
8200	2.33	8563	.62	8836	.29
8214	1.49	8810	.70	8880	1.19

8000 (SIGNETICS)

8263	5.79	8267	2.59

9000

9002	.40	9309	.79	9601	.61
9301	1.03	9312	.79	9602	.79

ELECTRONIC GAMES

We have available in kit form **Electronic Roulette** and **Electronic Craps.** Both kits contain P.C. boards, LED's, all necessary components, transformer, case and instructions for easy assembly. Included with each kit is a 55 page booklet explaining the entire game.

Electonic Roulette
Dimensions 6½" x 6½" x 1½" **$23.95**

Electronic Craps
Dimensions 6½" x 3½" x 1½" **$14.95**

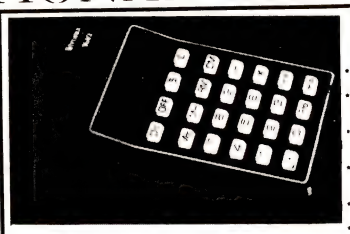

CALC. KIT ONLY **$9.95**

ADAPTER -60Hz **$3.95**

CMOS

4000A	.26	4018A	1.39	4066A	.89
4001A	.25	4020A	1.72	4068A	.44
4002A	.25	4021A	1.18	4069A	.44
4006A	1.35	4022A	.94	4071A	.26
4007A	.26	4023A	.25	4072A	.35
4008A	1.52	4024A	.89	4073A	.39
4009A	.57	4025A	.25	4075A	.39
4010A	.54	4027A	.59	4078A	.39
4011A	.29	4028A	.98	4082A	.35
4012A	.25	4030A	.44	4518A	1.56
4013A	.45	4035A	1.27	4528A	1.56
4014A	1.27	4040A	1.39	4585A	2.10
4015A	1.27	4042A	1.47		
4016A	.48	4049A	.59		
4017A	1.01	4050A	.59		

74C00	.19	74C74	1.04	74C162	2.49
74C02	.26	74C76	1.34	74C163	2.66
74C04	.44	74C107	1.13	74C164	2.66
74C08	.68	74C151	2.62	74C173	2.22
74C10	.35	74C154	3.15	74C195	2.26
74C20	.35	74C157	1.76	80C95	1.15
74C42	1.61	74C160	2.48	80C97	.96
74C73	1.04	74C161	2.49		

MULTIPLE DISPLAYS

NSN33	3 digit .12" red LED	1.79
HP5082-7405	5 digit .11 red LED	3.49
HP5082-7414	4 digit .11 red LED	3.25
SP-425-09	9 digit .25 gas disch.	1.79

LED DISPLAYS

MAN 1	$1.95	DL33B	.45
MAN 2	3.95	DL33-	.35
MAN 5	2.25		
MAN 7	1.49	DISCRETE LED'S	
MAN 8	2.25	ME 4	.29
MAN 66	2.25	MV10B	.25
MAN 72	1.25	MV50	.12
MAN 3620	1.50	NSL100	.12
FND 359	.95		
FND 500	1.89	MV5020	
FND 507	.95	RED	.15
DL10A	2.19	CLEAR	.15

MEMORIES

1101	256 bit RAM MOS 16 pin	1.39
1103	1024 bit RAM MOS dynamic 18 pin	1.95
1702A	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
2102	1024 bit RAM static 16 pin	1.95
5203	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
5260	1024 bit RAM MOS dynamic 16 pin	1.95
5261	1024 bit RAM MOS dynamic 16 pin	1.95
7489	64 bit ROM TTL 16 pin	2.25
82S23	256 PROM-SCHOTTKY 16 pin	3.69
F93410	256 bit RAM bi-polar 16 pin	1.95
74187	1024 bit ROM TTL 16 pin	5.75
74200	256 bit RAM tri-state 16 pin	5.45

CLOCK CHIPS

MM5311	6 digit multiplexed BCD, 7 seg, 12-24 Hr, 50-60 He — 28 pin	4.45
MM5312	4 digit multiplexed BCD, 7 seg, lpps. 12-24 Hr. 50-60 Hz — 24 pin	3.95
MM5314	6 digit multiplexed 12-24 Hr, 50-60 Hz 24 pin	4.45
MM5316	4 digit, 12-24 Hr, 50-60 Hz, alarm 40 pin	4.95
15375AA	4-6 digit, 12 hour, 60 Hz snooze alarm brightness control capability, alarm tone output — 24 pin	4.95
CT7001	6 digit, 12-24 Hr, 50-60 Hz, alarm, timer and date circuits — 28 pin	6.95

CALCULATOR CHIPS

CT5002	12 digit, 4 function fixed decimal battery operation — 40 pin	1.95
CT5005	12 digit, 4 function plus memory, fixed decimal — 20 pin	2.49
MM5725	8 digit, 4 function, floating decimal 18 pin	1.98
MM5736	6 digit, 4 function, 9V battery operation — 18 pin	2.95
MM5738	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation — 24 pin	3.95
MM5739	9 digit, 4 function, 9V battery operation — 22 pin	3.95

OPTO ISOLATORS

MCD2	Opto isolator diode	1.09
MCT2	Opto isolator transistor	.70

CALCULATOR KIT
LITRONIX 1602 MEMORY

- **FULL ACCUMULATING MEMORY —** STORES AND RECALLS SUBTOTALS
- **% KEY —** PERFORMS ALL PERCENT FUNCTIONS INCLUDING ADD-ONS, DISCOUNTS, MARKUPS AND YIELDS.
- **$ KEY —** ALLOWS DOLLAR AND CENTS ENTRIES WITHOUT PRESSING DECIMAL POINT KEY.
- **SQUARE ROOT** PERFORMS SQUARE ROOT BY PRESSING — AND + = SEQUENTIALLY.
- **ARITHMETIC LOGIC —** LETS YOU ENTER PROBLEMS IN ADDING MACHINE MODE.
- **FLOATING DECIMAL SYSTEM —** AUTOMATIC DECIMAL POINT POSITIONING FOR FULL 8-DIGIT ACCURACY.
- **OVERFLOW SAVE —** IN CASE OF OVERFLOW IN DISPLAY, THIS CLEARS THE CONDITION AND ALLOWS CALCULATOR TO CONTINUE USING THE OVERFLOWED RESULTS DIVIDED BY 10^8
- **AUTOMATIC TIMEOUT TO SAVE BATTERIES**

2518 $2.95
HEX 32-bit STATIC SHIFT REGISTER

SHIFT REGISTERS

MM5013	1024 bit accum. dyn. 8 pin	1.75
MM5016	500/512 bit dyn. 8 pin	1.59
SI5-4025	Quad 25 bit	.99
2504	1024 bit multiplexed dyn 8 pin	3.95

ALARM CLOCK CHIP
MM5375AA 4-6 digit, 12 hour, 60Hz snooze alarm, brightness control capability, alarm tone output 24 pin DIP **$3.95**

TANTALUM CAPACITOR KIT **$19.95**
60 solid dipped tantalum capacitors + 20%
1st quality capacitors in a durable styrene utility box — with color code charts

5 each	.1 ufd	35V	.33 ufd	35V	1 ufd	35V	2.2 ufd	35V
	4.7 ufd	16V	6.8 ufd	6V	10 ufd	25V	15 ufd	20V
	22 ufd	16V	33 ufd	10V	47 ufd	6V	56 ufd	6V

MM5369 Divider mDIP $2.35
Crystal 3.58 MHZ color TV $1.50

2102
1024 bit static RAM 16 pin
$1.49

1702A
2048 bit static PROM elect. prog. UV ears. 24 pin
$6.95

IC BREADBOARD
Accommodates 5 16 pin IC's with additional interconnection holes. 1/16" phenolic with silver plated copper circuits. 2 5/16" x 6 9/16" **$1.80 ea.**

CENTRAL PROCESSING UNIT

8008 $19.95
8080A $19.95

IC SOCKETS
Solder Tail - low profile

8 pin	$ .17	24 pin	.42
14 pin	.20	28 pin	.59
16 pin	.22	40 pin	.69
18 pin	.29		

WIRE WRAP - gold plate
14 pin .49

SPECIAL DEVICES

372	AF-IF Strip Detector DIP	2.93
546	AM Radio Receiver Subsystem DIP	.75
1310	FM Stereo Demodulator DIP	2.90
1496	Balanced Modulator-Demodulator	.99
1800	Stereo multiplexer DIP	2.48
ULN2208	FM Gain Block 34db (typ) mDIP	1.18
ULN2209	FM Gain Block 48db (typ) mDIP	1.35
2513	Character Generator 64x8x5 DIP-24	10.20
3046	Transistor Array DIP-14	.73

7489 $1.79
64 bit ROM TTL 16 pin

TV GAME CHIP
AY-3-8500-1
Six games with scoring and sound $24.95

KEYBOARD
20 KEYS
2 SLIDE SW
3" x 3¼"

99 ¢

CALCULATOR DISPLAY
9 MAN 3 M
ON PC BOARD

99 ¢

733
DIFFERENTIAL VIDEO AMPLIFIER **$ .59**

LINEAR CIRCUITS

300	Pos V Reg (super 723) TO-5	$ .71
301	Hi Perf Op Amp mDIP TO-5	.29
302	Volt follower TO-5	.53
304	Neg V Reg TO-5	.80
305	Pos V Reg TO-5	.71
307	Op AMP (super 741) mDIP TO-5	.26
308	Mciro Pwr Op Amp mDIP TO-5	.89
309K	5V 1A regulator TO-3	1.35
310	V Follower Op Amp mDIP	1.07
311	Hi perf V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
320T	Neg Reg 5, 12, TO-220	1.39
320K	Neg Reg 5.2, 12 TO-3	1.39
322	rrecision Timer DIP	1.70
324	Quad Op Amp DIP	1.52
339	Quad Comparator DIP	1.58
340K	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3	1.69
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1.49
372	AF-IF Strip detector DIP	2.93
373	AM/FM/SSB Strip DIP	2.42
376	Pos V Reg mDIP	.68
380	2w Audio Amp DIP	1.30
380-8	.6w Audio Amp mDIP	1.25
381	Lo Noise Dual preamp DIP	1.75
382	Lo Noise Dual preamp DIP	1.75
531	High Slew rate Op Amp	2.95
540	Power driver TO-5	2.95
550	Prec V Reg DIP	.79
555	Timer mDIP	.45
556A	Dual 555 Timer DIP	1.19
560	Phase Locked Loop DIP	3.39
562	Phase Locked Loop DIP	3.39
565	Phase Locked Loop DIP TO-5	1.18
566	Function Gen mDIP TO-5	1.95
567	Tone Decoder mDIP	1.95
709	Operational AMP TO-5 or DIP	.26
710	Hi Speed Volt Comp DIP	.35
711	Dual Difference Compar DIP	.26
723	V Reg DIP	.62
733	Diff. video AMPL TO-5	.89
739	Dual Hi Perf Op Amp DIP	1.07
741	Comp Op Amp mDIP TO-5	.32
747	741 Dual Op Amp DIP or TO-5	.71
748	Freq Adj 741 mDIP	.35
1458	Dual Comp Op Amp mDIP	.62
1800	Stereo multiplexer DIP	2.48
3900	Quad Amplifier DIP	.49
7524	Core Mem Sense AMPL DIP	.71
7525	Core Mem Sense AMPL DIP	.90
8038	Voltage contr. osc. DIP	4.25
8864	9 DIG Led Cath Drvr DIP	2.25
75150	Dual Line Driver DIP	1.75
75451	Dual Perepheral Driver mDIP	.35
75452	Dual Peripheral Driver mDIP	.35
75453	(351) Dual Periph Driver mDIP	.35
75491	Quad Seq Driver for LED DIP	.71
75492	Hex Digit driver DIP	.80

Data included with order on request. Add $.30 ea. if item is priced below $1.00

FREE CATALOG AVAILABLE ON REQUEST

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), or money order. Phone Orders — BofA and M C card or C.O.D

Add $1.00 to cover shipping and handling if order is less than $10.00.
California residents add sales tax. Include shipping expense for orders shipped out of U.S. and Canada approx. 10 % of order.

INTERNATIONAL ELECTRONICS UNLIMITED
VILLAGE SQUARE, P.O. BOX 449
CARMEL VALLEY, CA 93924 USA
PHONE (408) 659-3171

CIRCLE 58 ON FREE INFORMATION CARD

SPRING SALE

GENERAL ELECTRIC TUBES NEW & BOXED 73% OFF LIST

☐ 3A3	5 for $7.63	☐ 6LB6	5 for $15.19
☐ 6BK4	5 for $14.11	☐ 6LQ6	5 for $15.80
☐ 6C13	5 for $7.09	☐ 6LR6	5 for $14.51
☐ 6FQ7	5 for $5.74	☐ 17JZ8	5 for $7.83
☐ 6GH8	5 for $5.94	☐ 23Z9	5 for $9.65
☐ 6HA5	5 for $7.22	☐ 42KN6	5 for $12.96

DIODES—RECTIFIERS

100—2.5 Amp. 1000 PIV	$9.95
10—15 KV FOCUS RECT.	$4.50
4—BOOST RECTIFIERS	$2.00
5—8KV FOCUS RECTIFIERS	$2.00
20—1N60 CRYSTAL DIODES	$2.00

ZENITH IC CHIPS

REPL—221-62	4 for $5.00
REPL. 221-46—221-51	4 for $5.00
REPL. 221-69	4 for $5.00
1 LB SOLDER 60/40	$4.95
PHILCO FOCUS BLOCK 200 MEG-40 MEG.	$2.50
25 ASST'D PHONO NEEDLES (BOXED)	$4.95
WELLER CORD. SOLD IRON	$13.95
WAHL CORD. SOLD IRON	$13.95

COLOR CRT BOOSTERS

70°—COLOR CRT BOOSTER	$4.49 ea.
3—70° COLOR CRT BOOSTER	$12.50
90°—COLOR CRT BOOSTER	$4.95 ea.
3—90° COLOR CRT BOOSTER	$12.95
SONY COLOR CRT BOOSTER	$3.75
100 Asst'd Resistors (Cut Leads)	$1.00
20 Asst'd Wire Wound Resistors	$1.00
20 Assorted Controls	$1.00
20 Asst'd Filter Cond. (Trans. Work)	$1.00
10 HV Anode Leads—Small Cup	$1.00
2-HV Anode Leads Large Cup	$1.00
2—BOOST RECTIFIERS	$1.00
2—8 KV FOCUS RECTIFIERS	$1.00
10—1N34A CRYSTAL DIODES	$1.00
5—UHF LOOP ANT. 18" Lead	$1.00
2—SHUNT REG. HOODS (6BK4, Etc.)	$1.00
3-Audio Output Xfmrs.	$1.00
4 CRT Harness Color 19" 23" 25" CRT	$1.00
1—21" CRT Converg. Assembly	$1.00
1—25" CRT Converg. Assembly	$1.00
25 Asst'd Plate Caps	$1.00
1—BSR 8TCS Cart. With Needles	$1.00
1—75-300 Ant. Match. Xfmr.	$1.00
2—UHF TUNERS DETENT TYPE	$1.00
3—Asst'd UHF TUNERS	$1.00
1—3.58 MHZ COLOR CRYSTAL	$1.00
2—PL 259 CB CONNECTORS	$1.00
3—66 MEG. HV RESISTOR	$1.00
5—ANT. CLOTHESPINS	$1.00
10—RCA PHONO PLUGS	$1.00
20 ASST'D SLIDE SWITCHES	$1.00
1—UNDER PILLOW SPKE. 6 FT. LEAD-PLUG	$1.00

ZENITH

COLOR YOKE—S-89750	$7.95
VIDEO IF STRIP-150-115	$7.95
COLOR FLYBACK S-964530-2	$6.95
ZENITH B/W YOKE-95-2874 (OTHERS)	$6.95
VOLTAGE TRIPLER-212-139	$7.95
VOLTAGE TRIPLER—212-109	$2.95
2—15 MEG FOCUS CONTROL	$1.00
1-CONV. DIODE PAK	$1.00
1—45 KV HV STICK	$3.95

COLOR FLYBACK XFMRS.

MAGNAVOX 361374-1	$5.95
PHILCO 32-10132-1	$2.95 Each
RCA 136640	$2.95
RCA 137545	$2.95
GRAB BAG JAP FLYBACKS	2 for $1.00

COLOR YOKES

REPL. DY 95AC-Y-109-(LESS COVER)	$6.95
GEN. ELECT. 76X8	$1.50
70°—(21" CRT ROUND)	$3.95
SYLVANIA 51-35809-2	$6.95
SYLVANIA 51-29986-2	$6.95
SYLVANIA 51-38553-2	$6.95
SYLVANIA 51-33657-4	$6.95
PACK BELL 290545-2E	$6.95
FLEETWOOD 70F1811	$6.95

ANTENNA EQUIPMENT

1000 FT. 300 Ohm FOAM 7 Str.-100 Mil.	$26.95
1000 Ft. COAX CABLE (BLACK)	$42.95
2—2 SET COUPLERS—300 OHM	$3.00
2—4 Set COUPLERS—300 Ohm	$4.50
2-BEHIND SET ANT (UNIV.)	$5.00
UHF-VHF SPLITTER	$1.49
UHF-VHF-FM-300 OHM SPLITTER	$1.99

B/K 280-3 DIGIT MULTIMETER LIST $99.95-YOUR COST $79.95

VOLTAGE TRIPLERS

ADMIRAL 93D99-3	$6.95
ADMIRAL 93D96-3	$6.95
ZENITH 212-131	$6.95
REPL. ECG 500	$6.95

CONDENSERS AXIAL LEADS

6—33 Mfd. 350 Volts	$2.59
6—40 Mfd. 350 Volts	$2.99
6—100 Mfd. 250 Volts	$2.89
6—500 Mfd. 50 Volts	$2.89
6—1000 Mfd. 35 Volts	$2.98
2—200 Mfd. 175 V. (RAD LEADS)	$1.69
4—1 Mfd. 50 Volts	$1.19
4—25 Mfd. 25 Volts	$1.19
3—1000 Mfd. 15 Volts	$1.19
3—500-1000 Mfd. 15 Volts	$1.59
3—1000 Mfd. 16V-500 Mfd. 12 V.	$1.39
20—.0068 Mfd. 100 Volts	$1.19
10—.0068 Mfd. 600 Volts	$1.19
10—.047 Mfd. 1KV	$1.29

CONDENSERS CANS

3—500 Mfd. 200 Volts	$1.89
3—400-400-40 Mfd. 150V-500 Mfd. 35 V.	$1.98
3—500-500-100 Mf. 50 V.	$1.98
3—300 Mfd. 175V-400-4-20 Mfd. 150 Volts	$1.98
3—200-50 Mfd. 300V-400 Mfd. 150V-2000 Mfd. 25V	$1.98
12 V. REG. POWER SUPPLY 4 AMP.	$17.95

SPEAKERS

5" HORN—5 W INDOOR-OUTDOOR	$5.75
6X9 COAX—10 OZ. MAGNET	$8.95
4X6—(16 OHMS)	$1.19
3" Sq.	$.79
2" TWEETER	$.79
6X9—20 OZ. MAGNET	$10.95

AUDIO-PHONO

3—C-60 IRISH CASSETTE TAPES	$1.29
3—C-90 IRISH CASSETTE TAPES	$1.79
MONO TONEARM	$1.69
25 Asst'd NEEDLES (GRAB BAG BOXED)	$4.95
SHURE N3D	$1.95 (Repl)
SHURE N-44	$2.95 (Repl)
SHURE N-75	$2.95 (Repl)
SHURE N-91	$2.95 (Repl)
PICKERING V-15 Grey	$2.95 (Repl)
PICKERING V-15 Orange	$2.95 (Repl)
12 SPADE NEEDLES CARDED	$2.59
50 Ft. Speaker Wire	$.99
100 Ft. Speaker Wire	$1.89
3 WAY SPEAKER KIT WIRE	$.79
89T CARTRIDGE	$1.39
3—Asst'd B/W FLYBACKS (JAP)	$1.00
6—6 Ft. Cheater Cords	$2.98
6—ROLLS BLACK TAPE PLASTIC 66 Ft.	$2.98
10 TEST LEADS ALLIGATOR CLIPS 15"	$1.79
6—ASST'D ALIGN TOOLS	$1.00

ZENITH IC CHIPS-TRANSISTORS

REPL. 221-62	4 for $5.00
REPL. ZEN. 221-46—221-51	4 for $5.00
REPL. ZENITH 221-69	4 for $5.00
221-39	$2.95 Ea.
Zen. Vert Trans. 121-758	$2.95 Ea.
UNIV. FOCUS COIL REPL.	$1.29
6 ASST'D FOCUS SOCKETS	$1.19
CHEMTRONICS TUN-O-WASH-24 OZ.	$2.99
CHEMTRONICS—TUN-O-FOAM 8 OZ.	$2.19
CHEMTRONICS—TUN-O-POWER 8 OZ.	$2.39
TECH SPRAY BLUE STUFF 8 OZ.	$1.89
TECH SPRAY BLUE SHOWER 24 OZ.	$2.99
TECH SPRAY BLUE FROST 20 OZ.	$2.89
TECH SPRAY MINUS "62" 15 OZ.	$2.39
TV TECH SPEC. FREEZE—6 OX.	$.79
TV TECH SPEC. TUNER CLEANER-6 OZ.	$.89
TV TECH SPEC. TUNER CLEANER 16 OZ.	$1.89
LPS INSTANT CONT. CLEANER-7 OZ.	$1.59
LPS INSTANT CONTACT CLEANER—16 OZ.	$2.98
LPS #1-LUBE-RUST INHIB.—7 OZ.	$1.29
LPS #1-LUBE-RUST INHIB.—16 OZ.	$1.98

DIST. FOR B/K TEST EQUIPMENT
DIST. FOR SBE—CB—RADIOS
SEND FOR FREE CATALOG
MINIMUM ORDER $50.00
Orders under $50.00—$2.00 shipping & handling
SEND CHECK OR M.O.

TV TECH SPECIALS
P.O. BOX 603
KINGS PARK, LI., NEW YORK 11754
PHONE 516-269-0805

Wurlitzer reproductions

ORGAN KITS KEYBOARDS
THE ULTIMATE IN DESIGN AND SOUND
DEMO RECORD AND BROCHURE $1.00
DEVTRONIX ORGAN PRODUCTS, Dept.4B
5872 Amapola Dr. • San Jose, CA 95129

FOR SALE

CANADIAN discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications, telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush $1. **ETCO-RE,** 521 5th Ave., NYC, 10017

FREE catalog. IC's, Semi's. **CORONET ELECTRONICS,** 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US Inquiries.

MICRO MINI MIKE™
WIRELESS MICROPHONE
World's smallest; solid state, self-contained. Picks up and transmits most sounds without wires up to 300 ft. through FM Radio. Use as mike, ampf., alarm & alert sys., hot line, baby sitter, etc. Money back guar. B/A, M/C cds, COD ok. $18.95 plus $1.00 post. & hdlg. Calif. res. add tax. Mail orders only. Qty. Disc. Avail. **AMC SALES, INC.**
SIZE 2¼" x ¾" x ½" Dept. 19, Box 928 • Downey, Calif. 90241

MAY goodies: 555—39¢, 741—49¢, Fairchild jumbo LED's red 12/$1, green 8/$1, 2N3055—88¢, 309K—88¢. Free catalog. **DIAMONDBACK,** Box 194R, Spring Valley, IL 61362

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL,** 4217-E University, San Diego, CA 92105

MANUALS for Govt. surplus radios, test sets, scopes, List 50¢ (coin). **BOOKS,** 7218 Roanne Drive, Washington, DC 20021

PICTURE TUBE MACHINE
We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFGR.
For complete details send name, address, zip to:
LAKESIDE INDUSTRIES
3520 W. Fullerton Ave.
Chicago, Ill. 60647
Phone: 312-342-3399

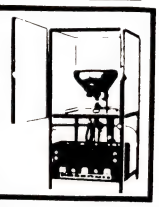

NAME brand digital/analog test equipment. Discount prices. Free catalog. **SALEM ELECTRONICS,** P.O. Box 82, Skokie, IL 60076

POWERFUL, adjustable, regulated, three-output power supply and 900 easily removable parts in complete **Cartrivision** television recorder electronic assembly with documentation. Perfect for **microprocessor, IC,** transistor, television, **CB** radio applications. $21.45. Free brochure. **MADISON ELECTRONICS, INCORPORATED,** 369, D101, Madison, AL 35758. **Satisfaction guaranteed.**

TV JAMMER
Amaze your friends! Makes TV's go into distortion. Max. range 20'. IN EASY KIT FORM...$2.65
* SEND FOR FREE CATALOG *
PRG ELECTRONICS COMPANY
14725 Oxnard St. Van Nuys Ca. 91401

CONNECTORS, audio, and RF and accessories. Low prices. Free catalog. **COAKIT,** Box 101, Dumont, NJ 07628

KITS, semiconductors, components. Free flyer. **CHIPS ELECTRONICS,** Box 1030, Oakville, Ont., Canada L6J5E9 U.S. Inquiries invited.

AMAZING ELECTRONIC PROJECTS and PRODUCTS:
Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog $1. **Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.**

CIRCLE 32 ON FREE INFORMATION CARD

POLY PAK'S IS THE "BARREL KIT KING" OF THE WORLD!

Your choice of any kit $1.98

Poly Pak's EXCLUSIVE

Avg. Ship. Wt. 6 ozs.

BARREL KITS® ARE LIKE FINDING MONEY!!!

Each kit carries a money-back guarantee!
Test 'em yourself 'n save! Includes 100% material, too!

KIT #237 LED DISPLAY MOLEX PINS 200 for $1.98
Pins 3/8" long, 1/10" spacing. For displays, keyboards. Wt. 4 ozs. 5R 3594

BARREL KIT #229 MULTI-DIGIT READOUTS 10 for $1.98
Barrels of 3's, 6's, & 9-digit readouts, some with driver chips. Wut a buy! Untested. No. 5R 3628

BARREL KIT #225 SOUND TRIGGERS 3 for $1.98 6 ozs.
"Hand clap" sensitizes crystal mike amplifier, triggers SCR. Cat. No. 5R 3625

BARREL KIT #221 IC SOCKETS 8 for $1.98
Mfr unloads! Four 14-pin, four 18-pin. Solder tail, lo-profile. No. 5R 3621

MIXED READOUTS KIT #219 15 for $1.98
Barrels of untested .17", .3", .5", 7-segs. Like FND-357, 500, 503, MAN-3's. Wut a buy! No. 5R 3619

BARREL KIT #217 25 for LAMPS! $1.98
Distributor unloads barrels of asstd bulbs, pop'l'r voltages to 24V. Screw & bayonet. Wt. 4 ozs. No 5R 3561

BARREL KIT #211 LO-PROFILE TO-5 50 for $1.98
NPN power transistors, mostly good. Bvceo 40V. Ic 2A, Hfe 30-100. Up to 250 MHZ! Like RCA 2N5189. Wt. 12 oz. No. 5R 3551

BARREL KIT #210 GLOWIN' PANELS 3 for $1.98
4" x 1" panels that glow blue-green with 110VAC. Use for nite lites, indicators, etc. Cat. No. 5R 3550

BARREL KIT #205 MINI BLOCK CAPACITORS 50 for $1.98
Unbelievable! Worth $50. High precision submini caps for all applications. Wt. 3 ozs. Cat. 5R 3528

BARREL KIT #203 CALCULATOR KEYBOARDS 10 for $1.98
It's true! 20-key, 4 function keyboards at ridiculous give-away. Wt. 12 ozs Cat. No. 5R 3524

Buy 10 BARREL KITS AND CHOOSE THE 11TH KIT Free

KIT #202 100 for $1.98 **PLUGS, SOCKETS**
Distributor unloads! Includes AC, DC, RF, audio, 4-9 pin, all kinds. Wt. 1 lb. Cat No. 5R 3527

BARREL KIT #201 6V INDICATORS w/leads 15 for $1.98
Test lamp manufacturer dumps inventory! Worth 69¢ ea. Like grain-o-wheat. Cat. No. 5R 3526

BARREL KIT #200 9 DIGIT READOUT MODULES 5 for $1.98 with calculator driver chips beneath epoxy. Cat. No. 5R 3515

BARREL KIT #198 TRANSISTORS & DARLINGTONS 50 for $1.98
Motorola dumps 1,000,000 TO-220 in barrels. NPNs & PNPs. Cat. No. 5R 3533

BARREL KIT #194 10-AMP INLINE BRIDGE RECTIFIERS 20 for $1.98
Asstd voltage. We can't test 'em. No. 5R 3475

BARREL KIT #192 NYLON GEARS 40 for $1.98
Wide variety of sizes 1" to 3" gears for the mechanical gear train hobbyists. Wt. 10 ozs. No. 5R 3427

BARREL KIT #191 CARBOFILM RESISTORS 800* for $1.98
*1/2 pound, approx. 1/8, 1/4 watters. Asst values. Unmarked, Cat. No. 5R 3445

BARREL KIT #188 400 Parts $1.98
Includes resistors, caps, transformers, rectifiers, diodes, etc. for p.c. work. Preformed, dumped into barrels by factories. 100% Cat. No. 5R 3401

BARREL KIT #186 KEYBOARD CHIPS 10 for $1.98
Truthfully we can't test em, MM5740's, keyboard encoder chips. No. 5R 3414

BARREL KIT #184 1/4-WATT METAL FILM 150 for $1.98
100% metal film resistors. Long leads. 5R 3413

BARREL KIT #182 JUMBO RED LEDS 15 for $1.98
100% material, user cancellation from factory dumps, 3V 10 mils. For 100's of projects, red lens. Cat. No. 5R 3369

BARREL KIT #181 MICRO ZENERS 100 for $1.98
1-Watt, tiny, 100% material, from 2V to 30V. Axial leads. No shorts, no opens. DO-7 & micro epoxy units. Cat. No. 5R 3368

BARREL KIT #163 MINI TRIM POTS 30 for $1.98 1 oz.
Asst. values 100 to 1 meg What a buy. Single turn. 1/4 W. Wt. 6 oz. 5R 3345

BARREL KIT #161 'POP' PLASTIC TRANSISTORS 25 for $1.98
2N3904's with some 2N3906's of 100% material. TO-92. Preformed. Cat. No. 5R 3343 1 oz.

BARREL KIT #160 V. REGULATORS 10 for $1.98
No. 5R 3330
LM309KC TO-3 V.R.'s barreled. Bot by the pound,

BARREL KIT #159 MODULAR SWITCHES 25 for $1.98
Centralab switches. TV-makers excess. Dpdt, 6pdt, etc. Brand new. Cat. No. 5R 3150

BARREL KIT #158 MAGNIFIED MAN-3's 20 for $1.98
MAN-3, 7-seg readout, with built-on magnifier. Factory discontinued line. 100% material. Cat. No. 5R 3325 1 oz.

BARREL KIT #154 CLOCK CHIPS 20 for $1.98
We gathered an assortment of clock chip, alarm, calendar, beepers, who knows, all mixed. Cat. No. 5R 3308

BARREL KIT #149 ROCKER SWITCHES 12 for $1.98
No. 5R 3302

BARREL KIT #145 MINI TRANSFORMER 15 for $1.98
outputs, interstage and audio. Only 1" sq. Wt. 2 lbs. 5R 3294

BARREL KIT #144 RCA PHONO PLUGS 40 for $1.98
1,000,000 RCA phono plugs for this one. You hi-fi-ers know wut they are . . . 100% material. 5R 3293

BARREL KIT #138 PANEL SWITCHES 30 for $1.98
Did you hear of OAK? Another eqpt maker barrelled all types of rotaries, electric, slides, etc. 5R 3268

BARREL KIT #135 MICRO MINI LAMPS 20 for $1.98 1 oz.
Imagine! Micro size (1/4 x 1/4) with wire leads, 3 to 5 VDC, 40 mils. 5R 3259

BARREL KIT #134 CALCULATOR CHIPS 15 for $1.98
National type. Can be MM5736, 38, etc. Untested. Cat. No. 5R 3258

BARREL KIT #131 TANTALUM ELECTROS 30 for $1.98
Mixed, marked prime, top grade asst. values, voltages. Cat. No. 5R 3255

BARREL KIT #128 MINI DIP ICS 100 for $1.98
Large mfgr dumped 100's of lbs into barrels. Includes 741s, LM-380-8, 703, 567, 555, 558—but who knows? Wt 1 lb. 5R 3245

BARREL KIT #127 AXIAL ELECTROS 40 for $1.98
Asst. capacities and voltages. Cat. No. 5R 3227

BARREL KIT #126 UPRIGHT ELECTROS 40 for $1.98
1mf to 300mf in mixture of voltages. 100% marked 'n good. 5R 3226

BARREL KIT #115 MOLEX SOCKETS 200 for $1.98 100% good Cat. No. 5R 3144
Calculator maker dump! We gut a zillion of 'em.

BARREL KIT #112 MICRO MINI LEDS 40 for $1.98
All the tiny leds, axial, upright of Monsanto, Litronix, variety of colors. Yield 50% or better. 5R 3139

BARREL KIT #109 TERMINAL STRIPS 100 for $1.98
Wide asst. of terminal strip connectors, from 1 contact up. Strip manufacturers barrel dump is your gain. Wt. 1 lb. Cat.No 5R 3136

BARREL KIT #108 TO-5 PLASTIC TRANSISTORS Cat.No. 5R 3101 40 for $1.98
Includes PNP, NPN, 2N-3638, 2N3641, 2N5000 series, etc. Untested.

BARREL KIT #104 SLIDE VOLUME CONTROLS 10 for $1.98
Cat.No. 5R 3057

BARREL KIT #101 RESISTOR SPECIAL 200 for $1.98
Includes: 1/8, 1/4, 1/2, 1, 2-watters, carbon. 8 oz. 100% good. 5R 3054

BARREL KIT #99 PHOTO ELECTRIC CELLS 10 for $1.98
Asst. GE types, CDS types. Mixed by factory. Big job for us to separate. 100% good. Cat.No. 5R 3052

BARREL KIT #93 HALF WATTERS 200 for $1.98
Resistor factory tried to fool us by mixing 100% color-coded resistors in barrel. But value is there. 4 oz. 5R 3046 Untested

BARREL KIT #92 3 AMP EPOXY RECTIFIERS Untested 100 for $1.98
Cosmetic rejects, electrically fine business! You check 'em, it's not for us. Asst. voltages. 5R 3204

BARREL #91 SILVER MICAS 100 for $1.98
Axial, red case, variety of physical sizes & values. Cat.No. 5R 3018

BARREL KIT #88 LITRONICS LED READOUTS 10 for $1.98
747's, 727's, singles, triples, etc. .33 to 0.6. Bot from factory, all mixed; have fun! No. 5R 2861

BARREL KIT #87 NATIONAL IC BONANZA 100 for $1.98
Types 8000, 7400 series, DTLs, ROMs, registers, clock & calc. chips, linears, etc. Cat.No. 5R 2860 Untested.

BARREL KIT #86 HOBBY LEDS 40 for $1.98 Untested
747's, 727's, singles, triples, etc. .33 to 0.6. Bot from factory, all mixed; have fun! 5R 2855

BARREL KIT #83 15 for $1.98 **LM-340T VOLT REG**
Factory rejected them for length of leads. May include 5, 6, 8, 12, 15, 18, 24 volts. Power tab Cat. 5R 2635

BARREL KIT #81 SUBMINI RESISTORS 200 for $1.98
PC, upright type, color coded, 1/8 watt. Asst values. Came to us in a barrel. Cat.No 5R 2746 100% good.

BARREL KIT #76 1-WATT ZENERS 100 for $1.98
Factory same as 400-mw's. Never-to-see-again offer. 6, 8, 10, 12, 15V. under glass. Double plug. Cat.No. 5R 2741 Untested.

BARREL KIT #73 TRANSISTOR ELECTROS 50 for $1.98
We don't wish to separate wide asst voltages & values up to 300 mf. Cat. 5R 2747

BARREL KIT #71 CAPACITOR SPECIAL 100 pcs. $1.98
micas, moldeds, plastics, ceramics, discs, etc. Nifty 100% good Cat.No 5R 2738

BARREL KIT #68 2 WATTERS 100 for $1.98 100% good.
Suppliers throw 'em in the barrel. It's a li'l gold mine. All marked. Cat.No. 5R 2735

BARREL KIT #65 MIXED READOUTS 10 for $1.98
Factory returns — such numbers as MAN-4's, MAN-7's, MAN-3's, 11 barrels & no time to separate. Cat.No. 5R 2733 Untested.

BARREL KIT #61 POLYSTYRENE CAPS 100 for $1.98
Finest caps made. As a gamble we bought 10 barrels from factory, mixed values; all good. Cat.No. 5R 2729

BARREL KIT #58 SLIDE SWITCHES 30 for $1.98
All shapes, sizes, spst, dpdt, momentaries, etc. Tremendous shop pak for 100's of switching projects. Cat.No. 5R 2726 100% good

BARREL KIT #56 POWERS! POWERS! $1.98 100 for
Large distributor cleaned house. Barrels of power resistors 3 to 7 watts. Cat. No 5R 2724

BARREL KIT #54 8 DIGIT READOUTS 10 for $1.98
Bargain of a lifetime! All we got was 1 barrel — the "blisdor digit" types. Multiplexed. Cat. No. 5R 2722

BARREL KIT #40 PNP HIGH-POWER TRANSISTORS 20 for $1.98
Popular germanium TO-3 case 5R 2618 100% good

BARREL KIT #39 2N3055 HOBBY TRANSISTORS 15 for $1.98
Fallouts of the famous 2N3055. 5R 2617 100%

BARREL KIT #37 1 AMP "BULLETT" RECTIFIERS Untested 100 for $1.98
Famous style, asstd. voltages, silicon, axial includes all types of voltages to 1KV. Cat.No. 5R 2615

BARREL KIT #36 GERMANIUM DIODES Untested 200 for $1.98
Cat.No. 5R 2614
Famous maker, popular item. Never grows old.

BARREL KIT #35 NEON LAMPS 30 for $1.98 100% good.
Famous NE-2's. All prime, but factory made millions and barrel'ed 'em. Your advantage Cat.No 5R 2613

BARREL KIT #31 METALLIC RESISTORS 100 for $1.98
Made mostly by Corning, the finest resistor made. Mostly 1/2 watters. 1% to 5% tol. & a barrel of values. Cat. No. 5R 2609

BARREL KIT #30 PREFORMED RESISTORS 200 for $1.98
We got barrels of 1/4 and 1/2" watters for pc use., 100: 1/4, 100 1/2" watters. No. 5R 2608 100% good

BARREL KIT #27 PREFORMED DISCS 150 for $1.98
Hi-Fi mfr's shelf inventory but he dumped 'em in barrels. Preformed, for PC use, Mixed values too! 5R 2605

KIT #26 PLASTIC TRANSISTORS 100 for $1.98 Untested.
Type TO-92 (TO-18), all manufacturers, variety of 2N #'s. Cat.No 5R 2604

BARREL KIT #25 METAL CAN TRANSISTORS 100 for $1.98
Includes TO-5, TO-1, TO-18, etc., assorted 2N numbers, unmarked etc. Cat.No 5R 2603 Untested.

BARREL KIT #20 LONG LEAD DISCS 100 for $1.98
"auction sale". Prime, marked only. Long leads Cat.No 5R 2598 100% good

BARREL KIT #19 DIPPED MYLARS 60 for $1.98
Finest capacitors made, shiny finish. Imagine factory dumping 'em in barrels. Cat.No. 5R 2597 100% good

NEW FACTORY ARRANGEMENTS! Why mix 'em? They decided to "bag" same types, then throw bags into barrels. WE DON'T TEST! You test 'em yourself. Buy types of your choice at BARREL PRICES!

U-TEST EM-N-CHOOSE EM IC'S

LINEARS
Order by Cat. No. 5R 3171 and Type No.

☐ LM300H	30 for $1.98	☐ LM1810N	30 for 1.98
☐ LM307V	40 for 1.98	☐ LM1902N	30 for 1.98
☐ LM308V	30 for 1.98	☐ LM2111N	50 for 1.98
☐ LM319V	30 for 1.98	☐ LM2901N	30 for 1.98
☐ LM339N	30 for 1.98	☐ LM3065N	30 for 1.98
☐ LM351V	30 for 1.98	☐ LM7528N	20 for 1.98
☐ LM709H	50 for 1.98	☐ LM75451V	40 for 1.98
☐ LM1303N	30 for 1.98		
☐ LM1304N	30 for 1.98		
☐ LM1310N	30 for 1.98		

Case code: V=Mini dip; H= TO-5; N=DIP.

BARREL KIT #17 LINEAR & 7400 DIPS 100 for $1.98 Untested
Marked and unmarked, internal numbers of raw factory stock. Cat.No 5R 2431

BARREL KIT #15 MOSFET TRANSISTORS 60 for $1.98
All 4 leaders TO-18 case, includes UHF transistors too! Cat.No. 5R 2429

BARREL KIT #14 PRECISION RESISTORS 200 for $1.98
Marked and unmarked 1/4, 1/2, 2 watts. No 5R 2428

BARREL KIT #11 POWER TAB TRANSISTORS 40 for $1.98
NPN, plastic TO220 type. Assorted 2N numbers. No. 5R 2425 Untested.

BARREL KIT #10 ROMS-REGISTERS 75 for $1.98 Untested
28 to 40 pin devices, marked, internal factory numbers, etc Cat.No 5R 2424

BARREL KIT #8 SUBMINIATURE IF TRANSFORMERS 75 for $1.98
Amazing, includes 455kcs, osc, antenna, who knows? Cat.No. 5R2422 100% good

BARREL KIT #7 VOLUME CONTROL 30 for $1.98 100% good
Singles, duals, variety of values, styles, big ones — small ones. Cat.No. 5R 2421

BARREL KIT #5 SCRS, TRIACS, QUADRACS 40 for $1.98
Raw factory stock! All the 10 amp types. Cat.No. 5R 2419 Untested.

BARREL KIT #4 "4000" RECTIFIERS 100 for $1.98 Untested.
1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000 volters, 5R 2417

BARREL KIT #3 1N4148/914 SWITCHING DIODES 100 for $1.98
Imagine famous switching diodes at these prices! Cat.No. 5R 2418 Untested.

BARREL KIT #2 LINEAR OR AMPS, DIPS 75 for $1.98 Untested
May include 709's, 741's, 703's, 560 series. 555 includes. 5R 2416

BARREL KIT #1 SN7400 DIP IC'S. 75 for $1.98
Marked 14 and/or with 16 pin dips, may include gates, registers, flip flops, counters. 5R 2415 Untest

Terms: Add postage Rated: net 30
Phone: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield,

POLY PAKS

P.O. BOX 942 LYNNFIELD, MA. 01940

SALE ☐ *Send for FREE* SPRING CATALOG

C.O.D.'s MAY BE PHONED

©Poly Paks Inc.® Wakefield, Mass., U.S.A. 1977

MINIMUM ORDER — $6.00

CIRCLE 23 ON FREE INFORMATION CARD

CARBON FILM RESISTORS

IN STOCK- A FULL LINE OF QUALITY ¼W 5% RESISTORS
STANDARD VALUES FROM 2.7 ohm to 4.7Mohm

5 for .25 10 for .40 100 for $1.60 1000 for $14.
(no mix of values) 100 per value for 1000 price

Memory
MOS 256 by 1
INTEL 1101A
.59 ea

Photocells
Dual Cadmium Sulfide Photocells, by Clairex.
.25 Each 10 for 2.00

Bipolar Memory
Fairchild 93410
256 by 1 - 40NS
$1.00 ea

NE2 Neon Lamps
W/39K Resistor
10/$1.00

25K Trimmer
Printed Circuit Board Type
Each $.20
10 for $1.50

Zener Diodes
6 V 1 W
6.8 V 1/2 W
5% 6 / $1.00

RESISTORS
Preformed
1/2 W 5 & 10%
Popular Values
100 Asst. $1.00

RESISTORS
Preformed
1/4 W 5 & 10%
Popular Values
100 Asst. $1.00

HP
5082-4557
Bright Yellow
LEDs W/panel
clips 3 / $1.00

150 Mhz PRESCALER

ECL INPUT-TTL COMPATIBLE OUTPUT-- DIVIDE BY 10 AND 100, BOARD, IC'S, COMPONENTS AND COMPLETE INSTRUCTIONS........ $12.95

650MHZ OPTION - DIVIDE BY 100 OR 1000 INCLUDES ABOVE PLUS 11C90 FAIRCHILD ECL CHIP $29.95

MONTHS SPECIALS
747 DUAL 741 OP-AMP .65
REGULATORS
1 AMP TO-220 TAB
+5, +12, +24
-5, -12, -24 EACH .75
1 AMP TO-3
+5, +12, +24 EACH $1.00

free INTEL data book with $25 order

Specials

Diode Array
10-1N914 SILICON SIGNAL DIODES IN ONE PACKAGE. 20 LEADS ALTERNATELY SPACED .1"; NO COMMON CONNECTIONS.
25¢ ea. Ten for $2.25

Transistor Sale!
2N5964 - HEPS0005, NPN, 150V
Each .20 10 for 1.50
2N4248 - HEP715, PNP, 40V.
Each 15¢ 10 for $1.00
2N2222 - NPN, 20¢ 10 for $1.75
2N4400 NPN $ .15 10 $1.35

POWER TRANSISTORS
TIP 31 PWR TAB NPN 50 EA 10 FOR 4.00
D41D1 PWR TAB PNP 50 EA 10 FOR 4.00
2N3773 T03 160 V 15 A. 1.50 EACH

POTTER BRUMFIELD

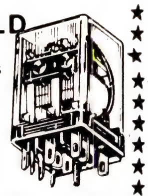

Type KHP Relay
4 PDT 3A Contacts
24V DC . .$1.50
(650 coil)
120V AC. .$1.75
(10.5 MA coil)

BOOKS

Learn Microprocessing!

I An Introduction to Microcomputers
by Adam Osborne $7.50
II An Introduction to Microcomputers Volume II:Some Real Products $12.50
III 8080 Programming for Logic Design
by Adam Osborne $7.50
Complete Set of Three for $25.00

High Quality PCB Mounting IC Sockets

wire wrap sockets
14 PIN WW .35
16 PIN WW .45

8 pin .$ .19
14 pin . .19
16 pin . .21
24 pin . .55
28 pin . .70
40 pin . 1.10

FULL WAVE BRIDGE RECTIFIERS
25 AMP 500 PIV
EACH $2.00 10 FOR $16.50

TRIACs 59¢ each
RCA 8 amp 500+ volt triacs, house numbered

MOLEX
500 . . $ 4.50
1000 . . 8.00
2000 . . 15.00

SPACE AGE CLOCK KIT

Instructions & parts - 12 or 24 hour format.
Four digit clock kit includes all parts for complete clock: 3¼"x 2":
-FND 70 readouts
-MM5314 clock chip & all transistors, etc.
-extruded aluminum case
-cord with transformer plug
$16.95

Diac .25 ea

DIP Trimmer
-12 turn trimpots which plug into a DIP socket
-5K and 200K
-¼" x ¼" x ¼"
-4 leads spaced .3" x .2"
Each $.65 10 for $4.95

1 Amp OP AMP
Sim. National LH0021.
General purpose operational amplifier in an 8-pin TO-3 package. Capable of large output currents. Complete data included.
$4.50 each
5 for $20.00

Send a stamp for our flyer listing more money-saving bargains!

Orders under $7.00 add $1.00 postage and handling. Residents of Cal. add sales tax. Orders shipped promptly. $10 minimum on C.O.D.s.

Money Back Guarantee

Phone (916)334-2161

Mail orders to:
P.O. Box 41778
Sacramento, CA
95841

Your BANKAMERICARD welcome here

BABYLON ELECTRONICS

CIRCLE 53 ON FREE INFORMATION CARD

LAST CHANCE!
Order before May 31, 1977
or you have to pay more!

4 or 6 Digit Alarm Clock Kit
0.5" FND503 Display
Kit includes 2 PC Boards, IC, Transformer, Transistors, Switches, all necessary parts with detailed instructions.
4 Digits $12.50
6 Digits $14.50

4 Digit Jumbo Display Alarm Clock Kit
Using FSC 8000 0.8" display and MM5316. This kit provides all the features of MM5316 such as second display, sleep output, etc.
SPECIAL ONLY $19.50

Inter-Com Board
Fully Assembled
Output Power 1W.
2 small speakers make it work!
$3.00 each or 2 for $5.00

TRANSFORMERS
28V C.T. 0.6A $1.75

Car-Shaped Radio 10"

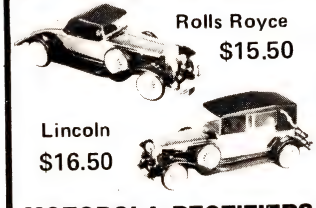

Rolls Royce $15.50
Lincoln $16.50

MOTOROLA RECTIFIERS
MDA962-2
100V 12A Bridge . . $2.00 ea.
IN1202A - Used
200V 12A . . . . . . $0.65 ea.

I.C.S.
MM5375 AA or AB
6 Digit Alarm Clock Chip
$3.00 each
2102A-6 $1.75 2107B-4 $5.95

Fairchild 0.25" LED's
.20 ea., 6/1.00, 100/$13.00

MINIATURE SLIDE SWITCH
DPDT — .20 each
1.75/10 pcs.

EXTENSION SPEAKERS
For CB or CAR RADIO
3W, 4W, or Horn Type 5W

3 Watt - $6.00
4W or 5W $8.00
4 Watt
3 Watt
5 Watt

Min. Order $5.00 - Orders under $10.00 add $1.50 handling.
CALIF. RESIDENTS ADD 6% SALES TAX
Please add $1.00 for postage inside Calif., $2.00 for Out of State, Overseas add 10% of order.
STORE HOURS: Mon.-Sat., 10-7, Sun. 10-3

PHONE 714/821-0234

TRICO ELECTRONIC SUPPLIES
2669 W. LINCOLN AVE., ANAHEIM, CA. 92801

CIRCLE 19 ON FREE INFORMATION CARD

COMPUTER
DISPLAY
TERMINAL
$180.00

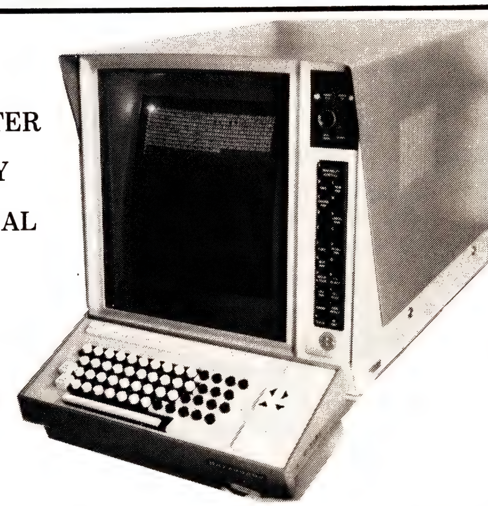

Unused computer terminals in original factory boxes. Made for airline ticketing & seating reservations. 17 inch B/W CRT in modernistic housing. 41 lines of data, 52 characters per line, generated by diode matrix (graphic) technique. Self contained power supply. Keyboard, free standing, reed switches, 54 data keys, 28 special keys. Logic unit (not shown) 1024 by 6 bit core memory, printer I/O interface, communications I/O interface. Due to several years storage, though unused, you may have to tinker, clean contacts on circuit boards, etc. We furnish free with each, one operational manual, one book of schematics. Sold "as is", all sales final. The price is a give-a-way. Check with order please (for immediate shipping certify your check. Shipped truck (238 lbs) you pay shipping on arrival. These have been interfaced by local customers with KIM-1 and IMSAI (no doubt can be interfaced with many others.

$180.00

JOHN MESHNA JR, PO BOX 62, E.LYNN MASS 01904

CIRCLE 37 ON FREE INFORMATION CARD

Radio Hut

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under $15.00 add 75 cents. Foreign orders add 10% for postage.

For your convenience, call your BankAmericard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.

master charge THE INTERBANK CARD

P. O. Box 64783
Dallas, Texas 75206

Your BANKAMERICARD welcome here

PLASMA DISPLAY KIT

Kit Includes: 12 digit display .4" Character Power supply for display above Complete specs for hookup.

Line cord Not Included. **ONLY $3.95**

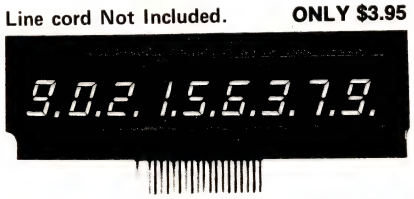

UNSCRAMBLER KIT

for all Scanners

- Tunes easily
- Full instructions included
- Easy to install
- 3½" x 3½" x 1½"

ONLY $14.95

CLOCK KIT

Kit includes
- LT701 clock module
- Power Supply
- Punched case
- 12 or 24 hour operation

Complete except for line cord

LT701E 12 hour clock
LT701G 24 hour clock

ONLY $14.95

CMOS SALE

CD4000	.16	CD4040	1.00
CD4001	.16	CD4041	.69
CD4002	.16	CD4042	.59
CD4007	.16	CD4043	.60
CD4009	.45	CD4044	.59
CD4010	.45	CD4047	.59
CD4011	.16	CD4049	.35
CD4012	.16	CD4050	.35
CD4013	.29	CD4051	.90
CD4014	.75	CD4053	.90
CD4015	.75	CD4056	1.00
CD4016	.29	CD4058	.90
CD4017	.80	CD4060	1.00
CD4018	.80	CD4066	.69
CD4019	.39	CD4069	.30
CD4021	.90	CD4071	.16
CD4022	.90	CD4076	.99
CD4024	.70	CD4077	.39
CD4025	.19	CD4102	.68
CD4027	.39	CD4116	.39
CD4028	.75	CD4507	.40
CD4029	.99	CD4512	.50
CD4030	.16	CD4516	.85
CD4034	2.30	CD4518	.85
CD4035	.99	CD4520	.85

Memorex computer boards with IC's, diodes, transistor, etc.
5 Boards containing
100 – 200 IC's
ONLY $4.25

BRIDGE RECTIFIERS

1 Amp	50V	.85
6 Amp	50V	1.10
10 Amp	50V	1.25
25 Amp	50V	1.39

TRANSISTORS - DIODES

*MJE1103	3/1.00
MJ3001	1.30
2N2222	6/1.00
2N2369	6/1.00
2N2905	4/1.00
*2N2907	15/1.00
2N3906	6/1.00
2N4400	6/1.00
2N4443 SCR	3/1.00
RCA 200V 115W NPN	.95
1N4004	15/1.00
1N4007	10/1.00
1N4148 (1N914)	20/1.00
3N201 VHF Pre amp	.80
D40C1 Power Darl	5/1.00

*House numbered and P.C. Lead

WATERGATE SPECIAL

Telephone Relay automatically starts and stops tape recorder. No batteries required. Kit complete with drilled P.C. Board.

Parts and Case **ONLY $9.95**

TI CALCULATOR CHIPS

TMS103 w/specs. .99
TMS107 w/specs. .99

HARDWARE

New, includes 2-56, 4-40, 6-32 and 8-32 screws and nuts. A very usable selection.

½ pound $1.50
1 pound $2.60

PROJECT CASES

SMALL $1.50	MEDIUM $2.00	LARGE $2.75
D - 2-1/2"	D - 2"	D - 2-1/2"
W - 4-3/4"	W - 4-7/8"	W - 7"
H - 1-7/8"	H - 3-1/2"	H - 4"

All cases have a sloped front, white with black wrinkle finish.

LOW POWER SCHOTTKY

74LS00	.25	74LS74	.49
74LS02	.25	74LS90	.85
74LS04	.30	74LS132	.90
74LS08	.25	74LS138	.89
74LS10	.25	74LS139	.89
74LS11	.32	74LS155	.90
74LS20	.31	74LS157	1.00
74LS21	.33	74LS162	1.39
74LS22	.33	74LS163	1.39
74LS27	.30	74LS175	1.09
74LS30	.31	74LS193	1.09
74LS32	.33	74LS258	1.09
74LS37	.40	74LS367	.70
74LS38	.35	74LS368	.70

ORDER BY PHONE. Charge your order to BankAmericard or Master Charge.
Use our Toll Free Watts
1-800-527-2304

READOUTS

FND70	.4" C.C.	.59
FND800	.8" C.C.	1.69
TI 6 digit array	C.C.	3/1.00
MAN 8	.3" CA Yellow	.89
LT767	.7" C.C. 4 digit stick	3.25

POSITIVE VOLTAGE REGULATORS

LM340-5 LM340-15
LM340-6 LM340-18
LM340-8 LM340-24
LM340-12

To-220 case. **Your Choice .75 Each**

NEGATIVE REGULATORS

7905 7915
7912

To-220 case. **Your Choice .75 Each**

FINNED HEATSINK for above regulators

2-3/4" High 2-1/2" Wide
1" Depth **ONLY .39 Each**

HEATSINK with pass transistor to increase regulator to 5 amps.
ONLY .99 Each

BATTERY CLIPS

Standard 9V battery clip with 4½" tinned leads. **25/$1.00**

LINEARS

LM309K	.95
LM380 (8 Pin)	.75
LM380 (14 Pin)	1.00
LM3900	.30
LM710	.25
LM711	.25
LM723	.40
LM748	.25
NE555	.35
NE556	.95
NE565	.95
NE566	.95
NE567	1.10
1458	.49
RCA 3043	.75
75491	.25
75492	.25

60Hz Crystal Time Base Kit – Kit enables a MOS clock circuit to operate from a DC power source. Ideal for car, camper, van, boat, etc.

60Hz output with an accuracy of .005% (typ.) Low power consumption 2.5 ma (typ.). Small size will fit most any enclosure. Single MOS IC oscillator/divider chip 5-15 volts DC operation.

ONLY $4.95
2 for $9.00

RESISTORS

Over 50,000,000 in stock

330	ohm 1/8W	20K	ohm 1/4W
470	ohm 1/4W	22K	ohm 1/4W
680	ohm 1/2W	27K	ohm 1/4W
1K	ohm 1/4W	33K	ohm 1/4W
1.2K	ohm 1/4W	39K	ohm 1/4W
2.2K	ohm 1/4W	43K	ohm 1/4W
3.3K	ohm 1/4W	47K	ohm 1/4W
4.7K	ohm 1/4W	82K	ohm 1/4W
6.8K	ohm 1/4W	100K	ohm 1/4W
10K	ohm 1/4W	150K	ohm 1/4W
		220K	ohm 1/4W

All resistors are PC lead, but are not pull offs. 100 min. order for each value. No Mix. **100/.99 Cents**

RADIO HUT GUARANTEE

If you are not satisfied with any of our products NO MATTER WHAT THE REASON we offer you a full money back guarantee if the product or products are returned within 14 days after you receive them.

CIRCLE 73 ON FREE INFORMATION CARD

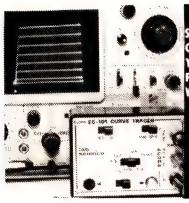

EC-101 CURVE TRACER
STILL BY FAR THE LOWEST COST FULL FUNCTION CURVE TRACER ON THE MARKET. ATTACHES TO YOUR SCOPE IN SECONDS. USED BY EDUCATORS, PROFESSIONALS AND HOBBYISTS ALL OVER THE WORLD. 30 DAY MONEYBACK GUARANTEE.

lab science | STILL ONLY $39.50 ADD $2 P&H | COLO. RES. ADD 3½% SALES TAX

PO BOX 1972, BOULDER, COLO. 80306

CANADIANS! AP Superstrip II universal breadboard, $18.95 postpaid. B.C. add 7%. Money order to **WOLVERTON ENTERPRISES** (Dept. RE), 5, South Hyte Avenue, Burnaby, B.C. V5B 3H6 U.S. inquiries invited.

MAKE professional-quality PC boards with silkscreen techniques. Complete step by step information, $4.95 Postpaid. **TERRATRONIC RESEARCH,** Box 513M, Quincy, IL 62301

BACK issue magazines. Over 200 titles, 1890 to 1976. Send stamped envelope. Free list. **EVERYBODY'S BOOKSHOP,** Dept. RE, 317 West 6th, Los Angeles, CA 90014

Looking for **BIRD** RF PRODUCTS?

AMATEUR RADIO SUPPLY
SEATTLE
6213 13th Ave. So., 98108
(206) 767-3222

60/600MHz 7-digit portable frequency counter battery or electric $299.00. 500MHz prescaler +10 or +100 $59.95. **CBS,** Box 1356, Cocoa Beach, FL 32931

Introducing
Equinox 100
computer kit

EQUINOX 100

THE FRONTRUNNER

Equinox 100: the 8080 CPU/S-100 Bus computer kit that's years in front of Altair* and IMSAI in design, function, and front programming capability.
At $599, it's clearly **the Frontrunner.**
Write for free specs to **PARASITIC ENGINEERING** P.O. Box 6314, Albany California 94706
*Altair is a trademark of M.I.T.S. Inc.

WIRE-Hookup, wire-wrap, ribbon cable, connectors, etc. Send 13¢ stamp for complete list. **RAM ELECTRONICS,** Box 336-R, Brookhaven, NY 11719

FREE catalog. Solar cells, NiCad's, kits, calculators, digital watch modules, ultrasonics, strobes, LED's, transistors, IC's, unique components. **CHANEYS,** Box 27038, Denver, CO 80227

PARTS! CORNELL TUBES!
FREE Send For FREE CORNELL'S New Color Catalog 48 Pgs. New Items
33¢ per tube IN LOTS OF 100
36¢ per tube ORDER FREE IF NOT SHIPPED IN 24 HOURS
4215 E UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

JAPANESE transistors, IC's, parts. Original parts at reduced prices. Free list. **ORA ELECTRONICS,** Box 7548, Van Nuys, CA 91409

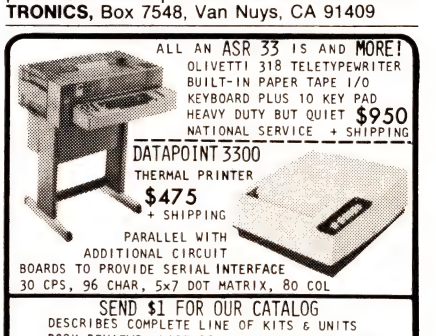

SUPERSCREEN lenses $99 to $199. Send $1 for plans and details. **PROJECTAPIX,** 300 West 53 Street, New York City, 10019

12 volt DC battery, Globe Union Gel Cell, sealed 4.5 Amps $33.95 with charger. GE nickel-cadmium batteries. **ROVA DISTR. CO.,** Hwy. F, Pewaukee, WI 53072

P.O. Box 4430E Santa Clara, CA 95054
(408) 988-1640

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

Quest ELECTRONICS

INTEGRATED CIRCUITS

7400TTL		74LS00 TTL		LM309K	.95
7400N	.17	74LS00N	.28	LM311H	.90
7402N	.17	74LS02N	.28	LM311N	.90
7403N	.17	74LS04N	.34	LM317T	2.95
7404N	.19	74LS05N	.34	LM318	1.35
7405N	.22	74LS08N	.28	LM320K-5	1.35
7407N	.42	74LS10N	.28	LM323K-5	6.95
7409N	.23	74LS13N	.67	LM302K-12	1.35
7410N	.17	74LS14N	1.30	LM320K-15	1.35
7411N	.28	74LS20N	.28	LM320T-5	1.60
7413N	.78	74LS22N	.34	LM320T-9	1.60
7414N	.63	74LS28N	.41	LM320T-12	1.95
7420N	.17	74LS30N	.28	LM320T-15	1.60
7422N	1.39	74LS33N	.39	LM324N	1.45
7430N	.20	74LS38N	.39	LM339N	1.55
7433N	.39	74LS74N	.46	LM340K-5	1.60
7438N	.25	74LS75N	.65	LM340K-8	1.60
7440N	.17	74LS90N	1.10	LM340K-12	1.60
7442N	.78	74LS93N	1.10	LM340K-15	1.60
7445N	.85	74LS95N	1.89	LM340K-24	1.60
7446N	1.04	74LS107N	.52	LM340T-5	1.50
7447N	.60	74LS112N	.52	LM340T-8	1.70
7448N	.78	74LS113N	.52	LM340T-12	1.70
7450N	.17	74LS132N	1.15	LM340T-15	1.50
7473N	.36	74LS136N	.59	LM340T-18	1.50
7474N	.32	74LS151N	1.60	LM340T-24	1.70
7475N	.49	74LS155N	1.50	LM343H	4.25
7482N	1.75	74LS157N	1.40	LM348	2.40
7483N	.70	74LS162N	2.05	LM350	1.00
7485N	.99	74LS163N	2.05	LM351	.60
7489N	2.00	74LS174N	1.85	LM358N	2.40
7490N	.45	74LS190N	2.60	LM370	1.15
7492N	.45	74LS221N	1.95	LM377	4.50
7493N	.49	74LS258N	2.20	LM379	5.00
7495N	.75	**74L00**		LM380N	1.00
74100N	.90	74L00	.30	LM381	1.60
74107N	.39	74L02	.30	LM382	1.60
74109N	.85	74L74	.60	LM386	1.75
74121N	.39	74L85	1.60	LM703H	.40
74123N	.87	74L86	1.60	LM709H	.28
74125N	.45	74L89	3.75	LM723H	.50
74132N	1.25	**74S00 TTL**		LM723N	.44
74145N	.89	74S00	.29	LM733N	1.00
74150N	.95	74S02	.29	LM741CH	.35
74151N	.75	74S04	.30	LM741N	.25
74154N	1.10	74S10	.90	LM747H	.62
74155N	.95	74S74	.68	LM747N	.62
74157N	.95			LM748N	.80
74161N	.95	**LINEAR**		LM1303N	.80
74162N	1.35	CA3026	1.00	LM1304	1.10
74163N	1.35	CA3045	.90	LM1305	.27
74174N	1.19	CA3046	.95	LM1307	2.00
74175N	.90	CA3049	.85	LM1310	2.75
74181N	2.40	CA3054	1.00	LM1458	.59
74190N	1.15	CA3081	1.80	LM1800	.75
74192N	1.25	CA3082	1.90	LM1812	7.50
74193N	.85	CA3086	1.40	LM1889	3.00
74221N	1.55	CA3089	2.95	LM2111	1.75
74285N	6.00	CA3090AQ	4.75	LM2902	1.50
74298N	1.65	LM301AN	.35	LM3900N	.55
74365N	2.00	LM301AH	.35	LM3905	1.75
74366N	2.00	LM305H	.87	LM3909N	.69
74367N	2.00	LM307N	.35	MC1458V	.59
74368N	2.00	LM308N	.89	NE540L	3.90
		LM309H	1.15	NE550N	.65
				NE555V	.43
				NE556A	1.00
				NE565A	1.00
				NE566V	1.85
				NE567V	1.25
				78L05	.90
				78L08	.90
				79L05	1.00
				75107	.50
				75108	1.75
				75451CN	.39
				75452CN	.39
				75453CN	.37
				75454CN	.37
				75491CN	.50
				75492CN	.55
				75494CN	.89
		DISCRETES		IN4001	.08
				IN4002	.08
				IN4003	.08
				IN4004	.08
				IN4005	.08
				IN4006	.08
				IN4733A	25
				IN4734A	25
				IN4736A	25
				IN4738A	25
				IN4739A	25
				IN4742A	25
				IN4744A	25
				IN4746A	25
				IN4749A	25
				IN4751A	25
				IN4752A	25
				IN4764A	25
				2N3904	25
				2N3906	25
		A to D CONVERTER		8700CJ	13.95
				8701CN	22.00
				LD130	13.75
		CMOS		CD3401 Fair.	.50
				CD4001	.25
				CD4002	.25
				CD4006	1.35
				CD4007	.25
				CD4008	1.50
				CD4009	.80
				CD4010	.53
				CD4011	.25
				CD4012	.25
				CD4013	.40
				CD4014	1.25
				CD4015	1.25
				CD4016	.50
				CD4017	1.00
				CD4018	2.75
				CD4019	2.00
				CD4020	1.35
				CD4021	1.20
				CD4022	1.40
				CD4023	.25
				CD4024	.85
				CD4025	.25
				CD4026	3.85
				CD4027	.55
				CD4028	1.50
				CD4029	1.70
				CD4030	.42
				CD4035	2.00
				CD4040	1.35
				CD4042	1.50
				CD4043	2.00
				CD4044	2.00
				CD4046	2.90
				CD4049	.62
				CD4050	.55
				CD4051	2.10
				CD4060	2.10
				CD4066	.85
				CD4068	.25
				CD4069	.40
				CD4070	.40
				CD4071	.40
				CD4072	.40
				CD4073	.40
				CD4075	.40
				CD4076	1.75
				CD4078	.40
				CD4081	.40
				CD4082	.45
				CD4116	1.30
				CD4490	5.50
				CD4508	4.25
				CD4510	2.00
				CD4511	2.20
				CD4515	4.00
				CD4516	2.00
				CD4518	2.45
				CD4520	2.90
				CD4527	4.75
				CD4528	1.50
				CD4553	5.75
				CD4566	2.25
				CD4583	4.50
				CD4585	2.10
				CD40192	3.00
				74C00	.28
				74C04	.33
				74C10	.28
				74C14	2.10
				74C20	.28
				74C30	.28
				74C48	2.95
				74C74	.75
				74C76	1.40
				74C90	1.15
				74C93	1.40
				74C106	2.10
				74C107	.85
				74C154	3.00
				74C160	1.44
				74C192	2.40
				74C221	2.75
				74C905	3.00
				74C906	1.50
				74C925	10.50
				74C926	10.50
				74C927	10.50
				INTERFACE	
				8095	.75
				8096	.75
				8097	.75
				8098	.75
				BT09	1.25
				BT10	4.50
				BT20	5.50
				BT23	3.10
				BT24	3.50
				BT25	3.20
				BT26	2.75
				BT28	2.75
				BT97	2.45
				BT98	2.45
		MOS/MEMORY RAM		2101-1	4.50
				2102-1	1.80
				2107B	8.00
				2111-1	7.00
				2112-2	7.90
				2513B	8.75
				2102-1	2.50
				MM5058	2.20
				MM5060	3.20
				MM5262	.90
				MM5320	5.95
				MM5330	9.75
				PD411D-3	7.00
				PD411D-4	8.00
		CLOCKS		MM5309	3.90
				MM5311	3.60
				MM5312	4.80
				MM5313	3.60
				MM5314	3.90
				MM5315	4.00
				MM5316	5.00
				MM5318	8.95
				MM5369	2.10
				MM5377N	5.95
				MM5841	10.80
				CT7001	5.80
				MM5375AA/N	3.90
				MM5375AB/N	4.90
				7205	16.50
				DS0026CN	3.75
				DS0056CN	3.75
				MM5314	3.75
		MICROPROCESSOR		8080 with data	19.00
				8080A with data	23.50
				8212	4.50
				8224	8.50
				8228	8.50
				CDP1802CD	29.50
				CDP1802D	35.00
		KEYBOARDS		63 Key Keyboard with HD0165 encoder add	$18.95 6.95

IC SOCKETS

Solder Tail		Low Profile	
PIN	1UP	PIN	1UP
8	.15	24	.36
14	.18	28	.43
16	.20	36	.58
18	.27	40	.61
22	.35		

PROM

1702A	7.95
N82S23	3.25
N82S123	4.00
N82S126	4.85
N82S129	4.85
2708	35.00
DM8577	2.90

SPECIAL PRODUCTS

LM1812N Ultrasonic Transceiver 7.50
LM3909N LED Flasher/Oscillator .69

Switches
Mom. Pushbutton .50
On off on toggle 1.35
On none on toggle 1.15

Encoder
HD0165-5 7.50

3 Digit Universal Counter Board Kit
Operates 5–18 Volt DC to 5 MHz typ. .125"LED display **10.50**

UART/FIFO

AYS-1013	6.20
3341	6.95

RESISTORS
¼ watt 5%

10 per type	.05
25 per type	.03
100 per type	.025
1000 per type	.02

MISCELLANEOUS
12 Volt 300 ma transformer 1.25

LEDS

Red T018	.15
Green T018	.20
Orange T018	.20
Yellow T018	.20
Jumbo Red	.20
Jumbo Green	.25
Jumbo Yellow	.25
Jumbo Orange	.25

Cliplite LED mounting Clips 8/$1.25
(specify red, amber, green, yelow, clear)

CRYSTALS

1 MHz	4.50	6.5536 MHz	4.50
2 MHz	4.50	1.8432 MHz	4.50
4 MHz	4.25	2.0100 MHz	2.95
5 MHz	4.25	2.097152 MHz	7.75
10 MHz	4.25	2.4576 MHz	7.50
18 MHz	3.90	3.2768 MHz	7.50
20 MHz	3.90	5.0688 MHz	4.50
32 MHz	3.90	5.185 MHz	4.50
32768 Hz	4.00	5.7143 MHz	4.50
3.5795 MHz	1.50	18.432 MHz	4.50
		22.1184 MHz	4.50

DISPLAY LEDS

MAN1	CA	.270	2.90
MAN3	CC	.125	.39
MAN6640 Dual	CC	.500	3.50
MAN72	CA	.300	1.50
MAN74	CC	.300	1.50
DL704	CC	.300	1.25
DL707	CA	.300	1.50
DL727	CA	.500	2.55
DL747	CA	.600	2.25
FND359	CC	.357	.95
FND503	CC	.500	1.00
FND510	CA	.500	1.00
FND800	CC	.800	1.90
FND807	CA	.800	1.90
DG8 Fluorescent			1.75
DG10 Fluorescent			1.75
5 digit 14 pin display			2.50
NSN3M 3 digit 8 pin			.39
NSN69 9 digit display			.60
7520 Clarex photocells			.25
TIL311 Hex			8.00

TV GAME CHIPS

MM57100 6 Games Chip	$19.95
MM53104 Clock Driver	3.75
LM1889 Modulator	3.00
GI AY38500-1	24.50

COMPUTER BOARD KITS

8K RAM Board Kit	$225.00
2K EPROM Kit	135.00
I/O Board Kit	44.50
Extender Board with connector	12.50
Video Interface board	149.95

Data Access Arrangement Kit. Instr. Incl. 10.00

IC Test Clips

	1	10
Red	.50	.43
Black	.50	.43

Keyer 8043 14.50 complete with spec. and socket

SCMP Keyboard Kit $95.00

SCPMP Kit $99.00

Not a Cheap Clock Kit $17.45
Includes everything except case. 2-PC boards. 6-.50" LED Displays. 5314 clock chip, transformer, all components and full instructions. **Same clock kit with .80" displays. $22.75**

Digital Temperature Meter Kit
Indoor and outdoor. Automatically switches back and forth. Beautiful .50" LED readouts. Nothing like it available. Needs no additional parts for complete, full operation. Will measure −100° to +200°F, air or liquid. Very accurate. Complete instructions. **$39.95**

8080A Microcomputer Kit
8080A CPU, Crystal Clock, I/O Buffers, RAM and PROM. D/A—A/D converter. PROM Programmer. Memory expandable. Complete documentation incl. assembly instruct., programming etc. **$195.00**

1977 IC Update Master Manual Brand new. Complete integrated circuit data selector from all manufacturers. 1264 page master ref. guide to the latest IC's including microprocessors and consumer circuits. 17,000 cross references for easier sourcing of hard to get parts. **$30.00** with free update service thru 1977. Domestic postage add $2.00. Foreign $6.00.

Frequency Counter Kit
Covers audio, ultrasonic and low amateur band 10 Hz to 2.5 MHz typ. Dual channel high sensitivity ±25 millivolts. Crystal controlled clock. Can be prescaled for higher frequency. 6-.50" digits. Full instructions. Less power supply. **$40.00**

Stopwatch Kit $26.95
Full six digit battery operated. 2–5 volts. 3.2768 MHz crystal accuracy. Times to 59 minutes, 59 seconds, 99 1/100 hrs. Times standard, split and taylor. 7205 chip, all components minus case. Full instruct.

COSMAC 'ELF'
RCA CMOS Microcomputer
CDP1802 CD **$29.50** Users Manual **$7.50**
Complete kit of parts to build the "ELF" including CDP1802 and users manual as listed in August '76 Pop. Elect. minus power supply and board. **$92.00**

VOLUME SPECIALS

		1	100
MM5262	2K RAM	.90	.50
MM5369	Divider	2.10	1.40
2102-1	500 NS 1K RAM	1.80	1.30
FND503	.50" Display	1.00	.89
18MHz	Crystal	3.90	2.50
PD411-3	150 NS 4K RAM	8.00	5.75
MA1002E	5' Alarm Clock Mod.	8.95	7.60
MA1013E	7' Alarm Clock Mod.	10.95	8.95
MM5309	Clock	3.90	2.70
MM5314	Clock	3.90	2.70
Momentary Pushbutton Switch		.50	.29

Other parts also available

60 Hz Crystal Time Base Kit $4.75 Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy. Kit includes: PC board, MM5369, crystal, resistors, capacitors and trimmer.

Clock Modules
Complete alarm clocks ready to hook up with transformer and switches. Very compact with .50" and .84" digits.

MA1002A, C or E .50"	$ 8.95
102P3 Transformer	$ 2.25
MA1010A, C or E .84"	$11.95
102P2 Transformer	$ 2.25

Special transformer and six switches when purchased with module $ 2.95

Stopwatch/Timer Kit $55.00
4 Digit, 7 function programmable stopwatch/timer. Two PC boards, components and case. Crystal controlled, this kit is excellent for rally and events as well as navigational, photography and for appliance control.

Auto Clock Kit $15.95
DC clock with 4-.50" displays. Uses National MA1012 module with alarm option. Crystal time base PC boards and full instructions. Add $3.95 for a beautiful dark gray case ready to install. This is the best value available anywhere!

TERMS: $5.00 min. order U.S. Funds. Calif residents add 6% tax. BankAmericard and Master Charge accepted.

FREE: Send for your copy of our 1977 QUEST CATALOG. Include 13¢ stamp.

CIRCLE 55 ON FREE INFORMATION CARD

DIGI-KEY CORPORATION
Quality Electronic Components

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

PRICE BREAKTHROUGH ON 74LS'

74LS00	.28	74LS30	.28	74LS90	.57	74LS157	.75	74LS248	.79
74LS01	.28	74LS32	.33	74LS92	.57	74LS158	.75	74LS249	.79
74LS02	.28	74LS37	.33	74LS93	.57	74LS160	1.02	74LS253	.84
74LS03	.28	74LS38	.33	74LS107	.39	74LS161	1.02	74LS257	.75
74LS04	.29	74LS40	.28	74LS109	.39	74LS162	1.02	74LS258	.75
74LS05	.29	74LS42	.67	74LS112	.39	74LS163	1.02	74LS266	.39
74LS08	.29	74LS47	.79	74LS113	.39	74LS164	1.02	74LS283	.79
74LS09	.29	74LS48	.77	74LS114	.39	74LS168	1.14	74LS290	.65
74LS10	.28	74LS51	.28	74LS125	.49	74LS169	1.14	74LS293	.65
74LS11	.28	74LS54	.28	74LS126	.49	74LS170	1.73	74LS365	.67
74LS12	.28	75LS55	.28	74LS132	.81	74LS173	1.34	74LS366	.67
74LS13	.47	74LS73	.39	74LS136	.39	74LS174	1.06	74LS367	.67
74LS14	1.02	74LS74	.39	74LS138	.73	74LS175	.84	74LS368	.67
74LS15	.28	74LS75	.53	74LS139	.73	74LS190	1.18	74LS386	.39
74LS20	.28	74LS76	.39	74LS151	.75	74LS191	1.18	74LS670	2.34
74LS21	.28	74LS78	.39	74LS153	.75	74LS196	.86	71LS95	.77
74LS22	.28	74LS83	.79	74LS154	1.10	74LS197	.86	71LS96	.77
74LS26	.33	74LS86	.39	74LS155	.75	74LS247	.79	71LS97	.77
74LS27	.33			74LS156	.75			71LS98	.77

INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400	.21	7476	.32	74181	2.15	4012	.23	4520	1.14
7401	.21	7480	.70	74182	.79	4013	.40	4527	1.68
7402	.21	7482	.70	74184	2.19	4014	.96	4528	.88
7403	.21	7483	.70	74185	2.19	4015	.96	4585	1.23
7404	.21	7485	.89	74188	3.50	4016	.40	2102-1	1.99
7405	.21	7486	.28	74189	3.50	4017	1.05	8080A	24.95
7406	.25	7489	2.19	74190	1.23	4018	1.05	CA3046	.75
7407	.25	7490	.44	74191	1.23	4019	.23	LM2111N	1.25
7408	.21	7491	.70	74192	.88	4020	1.14	LM309K	1.80
7409	.21	7492	.44	74193	.88	4021	1.14	LM324A	1.28
7410	.21	7493	.44	74194	.88	4022	.96	LM340T-5	1.25
7411	.21	7494	.70	74195	.88	4023	.23	LM340T-6	1.25
7412	.21	7495	.70	74196	.88	4024	.84	LM340T-8	1.25
7413	.25	7496	.70	74197	.88	4025	.23	LM340T-12	1.25
7414	.89	74100	1.28	74198	1.49	4026	1.68	LM340T-15	1.25
7416	.25	74107	.30	74199	1.49	4027	.40	LM340T-18	1.25
7417	.25	74109	.33	74251	1.09	4028	.89	LM340T-24	1.25
7420	.21	74121	.35	74279	.55	4029	1.14	LM3900N	.88
7421	.25	74122	.44	74365	.67	4030	.23	LM309N	.69
7423	.35	74123	.61	74366	.67	4033	1.51	MC1456V	1.00
7425	.35	74125	.40	74367	.67	4034	3.50	MC1458V	.53
7426	.25	74126	.40	74368	.67	4035	1.14	MC3302P	1.15
7427	.33	74132	.70	8093	.40	4040	1.14	NE536T	3.24
7428	.28	74141	.88	8094	.40	4041	.79	NE540L	2.04
7430	.21	74145	.70	9095	.67	4042	.79	NE555V	.48
7432	.25	74147	1.63	8096	.67	4043	.70	NE556A	.88
7433	.30	74148	1.30	8097	.67	4044	.70	NE560B	3.83
7437	.25	74150	1.16	8098	.67	4046	1.86	NE561B	3.83
7438	.25	74151	.70	75150	1.16	4049	.40	NE562B	3.83
7440	.21	74153	.65	75450	.88	4050	.40	NE565A	1.25
7442	.53	74154	1.03	75451	.61	4051	1.26	NE566V	1.28
7443	.63	74155	.70	75452	.61	4052	1.26	NE567V	1.36
7445	.70	74156	.70	75453	.61	4053	1.26	uA709CV	.44
7446	.70	74157	.70	75454	.61	4060	1.58	uA710CA	.44
7447	.70	74160	.88	75491	.81	4066	.79	uA711CA	.53
7448	.70	74161	.88	75492	.84	4071	.23	uA723CA	.60
7450	.21	74162	.88	75493	1.09	4072	.23	uA733CA	.75
7451	.21	74163	.88	75494	1.19	4073	.23	uA741CV	.44
7453	.21	74164	.96	82525	2.19	4075	.23	uA747CA	.70
7454	.21	74165	1.15	4000	.23	4081	.23	uA748CV	.49
7459	.21	74166	1.26	4001	.23	4082	.23	uA7805CU	1.25
7460	.21	74170	2.64	4002	.23	4502	.79	uA7806CU	1.25
7470	.30	74173	1.42	4006	1.23	4510	1.14	uA7808CU	1.25
7472	.30	74174	.98	4007	.23	4511	1.05	uA7812CU	1.25
7473	.30	74175	.93	4008	.79	4514	2.80	uA7815CU	1.25
7474	.30	74176	.79	4009	.44	4515	2.80	uA7818CU	1.25
7475	.49	74177	.79	4010	.44	4516	1.23	uA7824CU	1.25
		74180	.70	4011	.23	4518	1.14		

NEW

HOBBY-WRAP Model BW-630

Battery **wire wrapping** tool

ONLY **$34.95** (batteries not included)

COMPLETE WITH BIT AND SLEEVE

WIRE WRAPPING WIRE IN BULK

Red or Black 30 ga. Kynar

100' $2.00 500' $8.50 1000' $15.00

SILICON DIODES

1N4001	.64/10	5.50/C	$49/M
1N4002	.66/10	5.60/C	$51/M
1N4003	.68/10	5.80/C	$52/M
1N4004	.70/10	5.95/C	$54/M
1N4005	.82/10	7.05/C	$63/M
1N4006	.90/10	7.75/C	$69/M
1N4007	.99/10	8.60/C	$77/M
1N4148	.40/10	3.50/C	$29/M

Double Digit Discounts Save You Even More!

½ WATT ZENER DIODES

1N5226B 3.3v .15 $11/C	1N5236B 7.5v .15 $11/C
1N5227B 3.6v .15 $11/C	1N5237B 8.2v .15 $11/C
1N5228B 3.9v .15 $11/C	1N5238B 8.7v .15 $11/C
1N5229B 4.3v .15 $11/C	1N5239B 9.1v .15 $11/C
1N5230B 4.7v .15 $11/C	1N5240B 10v .15 $11/C
1N5231B 5.1v .15 $11/C	1N5241B 11v .15 $11/C
1N5232B 5.6v .15 $11/C	1N5242B 12v .15 $11/C
1N5233B 6.0v .15 $11/C	1N5243B 13v .15 $11/C
1N5234B 6.2v .15 $11/C	1N5244B 14v .15 $11/C
1N5235V 6.8v .15 $11/C	1N5245B 15v .15 $11/C

BUY A-P PRODUCTS & BISHOP GRAPHICS FROM DIGI-KEY

PLESSEY SAMPLER

An Assortment of Metalized Polyester Capacitors

300 Caps 18 Values **$26.00**

LED LAMPS

NSL5053 T-1¾	.18	$15/C
NSL5056 T-1¾	.18	$15/C

LED DUAL DIGITS

PRICED PER PAIR OF 2 DIGITS

NEW!

NSN373 0.3" CC . $2.20/Pair
NSN374 0.3" CA . $2.20/Pair
NSN584 0.5" CC . $2.60/Pair
NSN584 0.5" CA . $2.60/Pair
NSN783 0.7" CC . $3.00/Pair
NSN784 0.7" CA . $3.00/Pair

ALL LEADS BROUGHT OUT FOR EASE OF APPLICATION

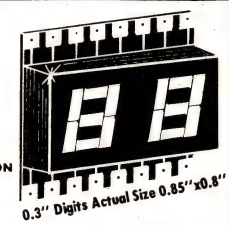

0.3" Digits Actual Size 0.85"x0.8"

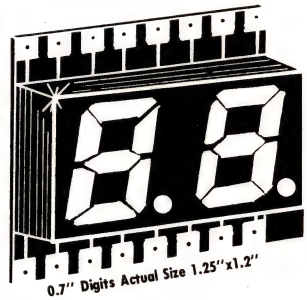

0.7" Digits Actual Size 1.25"x1.2"

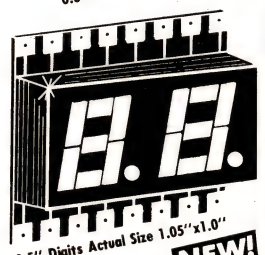

0.5" Digits Actual Size 1.05"x1.0"

NEW!

MA1003 CAR CLOCK

12 Hour Only
12 Volt DC
Crystal Time Base
Bright Green Digits
Assembled and Tested

NEW!

NEW — FOR CAR OR BOAT!

The MA1003 bright green flourescent display offers a brilliance that cannot be achieved by LED displays, a feature that sold Detroit!

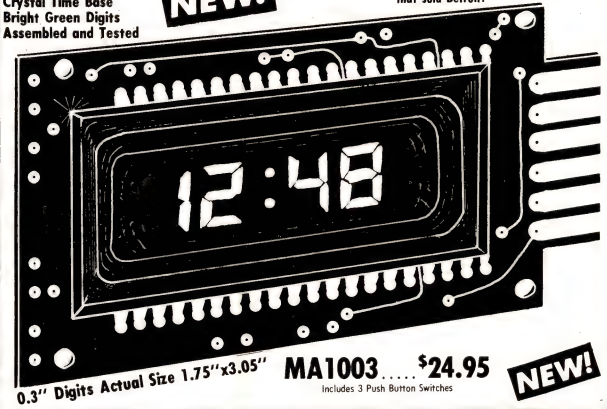

0.3" Digits Actual Size 1.75"x3.05"

MA1003 ..... $24.95

Includes 3 Push Button Switches

NEW!

MA1002 0.5" High Digits

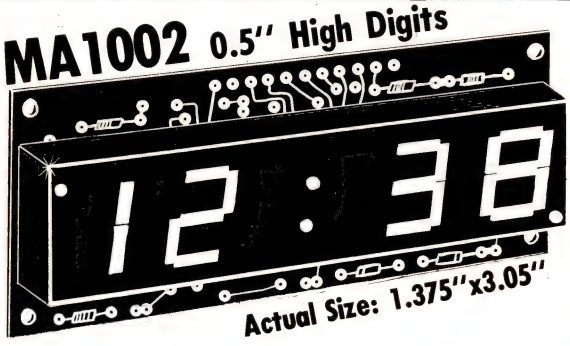

Actual Size: 1.375"x3.05"

MA1002A 12 Hour AM-PM **$10.50**
MA1002C 24 Hour **$10.50**
SPECIAL TRANSFORMER & SWITCHES $3.45

ABOUT OUR CLOCKS

The MA1002 and MA1010 series clock modules by National Semiconductor are fully assembled and tested clocks using a 4 digit LED display and an MOS integrated circuit on the same board. Simply connect switches and our special transofmer and you have a fully functioning clock.

The MA1003 clock module is a fully assembled and tested 12 hour clock using a high brilliance green flourescent display and crystal time base making it perfect for car, boat or other portable use. It operates directly from 12 volts DC so no transformer is needed. Our price includes three push button switches for setting the time.

MA1002A .5" LED 12 Hour AM-PM Clock Module **$10.50**
MA1002A SET Module with Transformer & Switches .. **$13.95**
MA1002C .5" LED 24 Hour Clock Module **$10.50**
MA1002C SET Module with Transformer & Switches .. **$13.95**
MA1003 12 Volt Car Clock with Switches **$24.95**
MA1010A .84" LED 12 Hour AM-PM Clock Module **$13.00**
MA1010A SET Module with Transformer & Switches .. **$16.45**
MA1010C .84" LED 24 Hour Clock Module **$13.00**
MA1010C SET Module with Transformer & Switches .. **$16.45**

RADIAL ELECTROLYTICS

.47/50V . . .08	.65/10	22/50V . . . 12	1.00/10	330/25V . . 23	1.86/10
1/50V 08	.65/10	100/6.3V . . 09	.75/10	470/10R . . 21	1.71/10
2.2/50V. . .08	.65/10	100/10V . . . 10	.77/10	470/16V . . 23	1.81/10
3.3/50V. . .08	.65/10	100/16V . . .11	.85/10	470/25V . . 29	2.35/10
4.7/35V. . .08	.65/10	100/25V . . 13	1.10/10	1000/10V . 24	1.96/10
4.7/50V. . .08	.68/10	100/50V . . 21	1.71/10	1000/16V . 29	2.35/10
10/16V 08	.65/10	220/10V . . 13	1.08/10	1000/25V . 42	3.33/10
10/25V . . .08	.65/10	220/16V . . 15	1.16/10	2200/10V . 42	3.33/10
10/50V . . .10	.75/10	220/25V . . 21	1.71/10	2200/16V . 54	4.30/10
22/16V . . .08	.67/10	220/50V . . 29	2.35/10	2200/25V . 58	4.67/10
22/25V . . .09	.70/10	330/10V . . 15	1.16/10	3300/16V . 89	7.14/10
		330/16V . . 21	1.66/10		

AXIAL ELECTROLYTICS

.47/10V . . 11	.90/10	33/25V. . . 14	1.15/10	330/16V . . 29	2.35/10
1/30V . . . 11	.90/10	33/50V. . . 19	1.52/10	330/25V . . 32	2.54/10
3.3/35V . . 12	.95/10	47/16V. . . 14	1.15/10	470/16V . . 32	2.55/10
3.3/50V . . 12	1.00/10	47/25V. . . 17	1.30/10	470/25V . . 37	3.00/10
4.7/25V . . 11	.90/10	47/50V. . . 21	1.17/10	1000/10V . 33	2.65/10
4.7/35V . . 12	.95/10	100/10V . . 14	1.13/10	1000/16V . 39	3.15/10
4.7/50V . . 12	1.00/10	100/16V . . 17	1.30/10	1000/25V . 56	4.50/10
10/25V. . . 12	1.00/10	100/25V . . 20	1.55/10	2200/10V . 50	3.96/10
10/50V. . . 14	1.15/10	100/50V . . 29	2.30/10	2200/16V . 62	4.95/10
22/16V. . . 12	1.00/10	220/10V . . 18	1.42/10	2200/25V . 79	6.36/10
22/25V. . . 13	1.05/10	220/16V . . 20	1.55/10	3300/16V . 95	7.63/10
22/50V. . . 17	1.32/10	220/25V . . 29	2.35/10	4700/16V 1.09	8.70/10
33/16V. . . 12	1.00/10	220/50V . . 40	3.23/10	10000/10V 1.15	9.19/10
		330/10V . . 14	1.16/10		

MA1010 0.84" High Digits

Actual size: 1.75"x3.75"

MA1010A 12 Hour AM-PM **$13.00**
MA1010C 24 Hour **$13.00**
SPECIAL TRANSFORMER & SWITCHES $3.45

Double Digit Discounts Save You Even More!

DATA BOOKS

TTL IC's 595 p.	$4.00
Linear IC's 957 p	$5.00
CMOS 74C 256 p	$3.00
Memory IC's 592 p	$3.00
Interface IC's 464 p	$4.00
Volt. Regs. 128 p.	$3.00
Linear Appl. 1 432 p.	$4.00
Linear Appl. 2 246 p.	$3.00
Audio 196 p	$3.00
MOS/LS1 IC's 713 p	$4.00
CMOS 4000 278 p	$3.25
Analog Manual 637 p	$5.95

SLIDE SWITCHES

SPST	.15	1.20/10	10.00/C
SPDT	.19	1.70/10	13.00/C
DPDT	.23	2.00/10	19.00/C

STRANDED HOOK UP WIRE

20 ga PVC . .	2.50/100' 10.00/500'
22 ga PVC . .	2.80/100' 11.25/500'
24 ga PVC . .	2.10/100' 8.50/500'
26 ga PVC . .	2.10/100' 8.50/500'

50 VOLT DISCS

100 pf.	.40/10	3.50/C
220 pf.	.40/10	3.50/C
470 pf.	.40/10	3.50/C
.001 uf	.40/10	3.50/C
.0022 uf	.40/10	3.50/C
.0047 uf	.40/10	3.50/C
.01 uf	.45/10	3.65/C
.022 uf	.50/10	4.00/C
.047 uf	.70/10	5.60/C
.1 uf	1.35/10	11.50/C

WIRE-WRAPPING TOOL

$5.95

Wraps, Unwraps & Strips 30 ga. Wire

¼ & ½ WATT 5% CARBON FILM RESISTORS

5c each in multiples of 5 per value
$1.70/100 & $12.00/1000 of same value

1 ohm thru 1.0 megohm

I.C. SOCKETS

8 Pin Solder	.17	1.60/10
14 Pin Solder	.20	1.90/10
16 Pin Solder	.22	2.10/10
18 Pin Solder	.29	2.75/10
24 Pin Solder	.38	3.60/10
28 Pin Solder	.45	4.25/10
40 Pin Solder	.63	6.00/10
8 Pin W-W	.24	2.30/10
14 Pin W-W	.26	2.50/10
16 Pin W-W	.30	2.85/10
18 Pin W-W	.60	5.70/10
24 Pin W-W	.96	9.10/10
28 Pin W-W	1.12	10.00/10
40 Pin W-W	.92	8.75/10

HARDWARE

2-56 1/4 Screw	.99/C	7.20/M
2-56 1/2 Screw	.99/C	7.65/M
4-40 1/4 Screw	.55/C	3.60/M
4-40 1/2 Screw	.60/C	4.05/M
6-32 1/4 Screw	.65/C	4.40/M
6-32 1/2 Screw	.75/C	4.85/M
8-32 3/8 Screw	.90/C	5.85/M
8-32 5/8 Screw	.99/C	7.00/M
2-56 Hex Nut	.55/C	3.60/M
4-40 Hex Nut	.55/C	3.75/M
6-32 Hex Nut	.60/C	4.00/M
8-32 Hex Nut	.60/C	4.15/M
No. 2 Lockwasher	.85/C	5.75/M
No. 4 Lockwasher	.45/C	3.00/M
No. 6 Lockwasher	.45/C	3.00/M
No. 8 Lockwasher	.45/C	3.00/M

DOUBLE-DIGIT DISCOUNT SCHEDULE

Merchandise	Discount	Merchandise	Discount
$ 0.00-$24.99	NET	$100.00-$499.99	Less 15%
		$500.00-$999.99	Less 20%
$25.99-$99.99	Less 10%	$1000.00 & Up	Less 25%

Then Add the Standard Charge Below

STANDARD SHIPPING/HANDLING CHARGE

If your merchandise total after discount is between

$ 0.00-$ 4.99	. . add $2.00
$ 5.00-$24.99	. . add $0.75
$25.00-$49.99	. . add $0.50
$ 50.00-$99.99	. . add $0.25
$100.00 & up	. . No Charge

Includes shipping and insurance to USA & Canada

COD ORDERS ACCEPTED FOR SAME DAY SHIPMENT — CALL 218-681-6674

SEND FOR OUR FREE CATALOG

WE STOCK A WIDE VARIETY OF PARTS NOT IN THIS AD PLUS MANY SPECIALLY PRICED BARGAINS!

Send for free catalog or mail reader's service card

"Only Quality Components Sold!"

DON'T FORGET TO APPLY DISCOUNT SCHEDULE

DIGI-KEY CORPORATION

Box 677, Thief River Falls, MN 56701 218-681-6674

CIRCLE 71 ON FREE INFORMATION CARD

SUPER VALUE!

- ICS Socketed
- Push button Switches on Main PC Board
- Open chassis for Easy Assembly
- Deluxe Metal Cabinet
- Complete Step-by-step Instruction & Diagrams
- .3 in. 7-Seg. LED Readouts

2 IN 1 DMM-COUNTER

FCM-8
8 DIGIT
250 MHz KIT
$219.95

Size 10W x 3-1/2H x 9D

Meter: Auto polarity and overrange indicator. 11 Meg. Ohm input impedance. Four overlapping ranges on AC-DC volts and current to 1KV and 1 AMP and five ranges on ohms to 1 Meg. Ohm. 500% overrange capability, except current. Accuracy: ±1%, ±1 count DC, ±1.5%, ±1 count AC and Ohms. Counter: Same as FCC-8.

CAPACITANCE COUNTER

NOW, IT IS A DREAM TO MEASURE YOUR CAPACITORS.

$89.95 KIT

Size 7W x 3H x 8D

±1% ±1 count (±1 pfd. below 100 pfd.) Four ranges from pico farads to several thousand microfarads. Features crystal timebase reference for stability. Auto-cycling.

FREQUENCY COUNTER

FC-6
30 MHz KIT
$89.95

FC-6H
250 MHz KIT
$129.95

Size 7W x 3H x 8D

Perfect for CBers, hams, hobbyists, technicians. Hi Z input, 50MV sensitivity. Frequency 10 Hz to over 30 Mhz. (FC-6) and 100 Hz to over 250 Mhz. (FC-6H). Crystal timebase. 5 ppm.

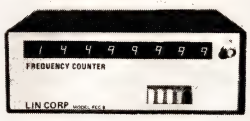

FCC-8
8 DIGIT
250 MHz KIT
$149.95

Size 10W x 3-1/2H x 9D

Hi Z input. Sensitivity 50 millivolts at 250 Mhz. Readout Hz., Khz., or Mhz. Resolution 1 Hz. to 10 Mhz. and 10 Hz above Crystal time base — 5 ppm.

Add $2.50 Shipping/Handling Each
California Residents Add 6% Sales Tax

master charge

your BANKAMERICARD welcome

LIN CORP. 15311 S. Broadway, Gardena, California 90248 (213) 532-8809

CIRCLE 49 ON FREE INFORMATION CARD

We have 400,000 reels of great recording tape to unload.

$30.00 gets you thirty reels ($225 value); or $12.50 gets you ten reels ($80 value). Call for quantity prices. These are government surplus, and fully guaranteed, professional quality mylar tapes on 10½ plastic reels, ¼" wide, 1 MIL with 3600 feet per reel.

Sounds crazy? We can sell brand name tapes at these ridiculous prices because we're the only supplier who bought up 400,000 reels.

Mail your order, name and address, with check or money order (N.Y. residents: add tax) to:

AMERICAN SURPLUS TRADING
Dept. R2
332 Canal Street
New York, N.Y. 10013
(212) 966-5650

CB SPECIALS–R.F. DRIVERS–R.F. POWER OUTPUTS–FETS

2SC481	1.85	2SC767	15.75	2SC866	5.85	2SC1449-1	1.60	40081	1.50
2SC482	1.75	2SC773	.85	2SC1013	1.50	2SC1475	1.50	40082	3.00
2SC495	1.10	2SC774	1.75	2SC1014	1.50	2SC1678	5.50	2SC608	4.85
2SC502	3.75	2SC775	2.75	2SC1017	1.50	2SC1679	4.75	SK3046	2.15
2SC517	4.75	2SC776	3.00	2SC1018	1.50	2SC1728	2.15	SK3047	3.75
2SC614	3.80	2SC777	4.75	2SC1173	1.25	2SC1760	2.15	SJ2095	3.50
2SC615	3.90	2SC778	3.25	2SC1226A	1.25	2SC1816	5.50	SK3048	3.25
2SC616	4.15	2SC797	2.50	2SC1237	4.50	2SC1908	.70	SK3054	1.25
2SC617	4.25	2SC798	3.10	2SC1239	3.50	2SC1957	1.50		
2SC699	4.75	2SC781	3.00	2SC1243	1.50	2SF8	3.00	2SK19	1.75
2SC710	.70	2SC789	1.00	2SC1306	4.75	HEP-S 3001	3.25	2SK30	1.00
2SC711	.70	2SC796	3.15	2SC1306-1	4.90	2SD235	1.00	2SK33	1.20
2SC735	.70	2SC799	4.25	2SC1307	5.75	MRF8004	3.00		
2SC756	3.00	2SC802	3.75	2SC1307-1	6.00	4004	3.00	3SK40	2.75
2SC765	9.50	2SC803	4.00	2SC1377	5.50	4005	3.00	3SK45	2.75
2SC766	10.15	2SC839	.85	2SC1449	1.30	40080	1.25	3SK49	2.75

JAPANESE TRANSISTORS

2SA52	.60	2SB187	.60	2SC458	.70	2SC815	.75	2SC1569	1.25
2SA316	.75	2SB235	1.75	2SC460	.70	2SC828	.75	2SC1756	1.25
2SA473	.75	2SB303	.65	2SC478	.80	2SC829	.75		
2SA483	1.95	2SB324	1.00	2SC491	2.50	2SC830	1.60	2SD30	.95
2SA489	.80	2SB337	2.10	2SC497	1.60	2SC839	.85	2SD45	2.00
2SA490	.70	2SB367	1.60	2SC515	.80	2SC945	.65	2SD65	.75
2SA505	.70	2SB370	.65	2SC535	.75	2SC1010	.80	2SD68	.90
2SA564	.50	2SB405	.85	2SC536	.65	2SC1012	.80	2SD72	1.00
2SA628	.65	2SB407	1.65	2SC537	.70	2SC1051	2.50	2SD88	1.50
2SA643	.85	2SB415	.85	2SC563	2.50	2SC1061	1.65	2SD151	2.25
2SA647	2.75	2SB461	1.25	2SC605	1.00	2SC1079	3.75	2SD170	2.00
2SA673	.85	2SB463	1.65	2SC620	.80	2SC1096	1.20	2SD180	2.75
2SA679	3.75	2SB471	1.75	2SC627	1.75	2SC1098	1.15	2SD201	1.95
2SA682	.85	2SB474	1.50	2SC642	3.50	2SC1115	2.75	2SD218	4.75
2SA699	1.30	2SB476	1.25	2SC643	3.75	2SC1166	.70	2SD300	2.50
2SA699A	1.75	2SB481	2.10	2SC644	.70	2SC1170	4.00	2SD313	1.10
2SA705	.55	2SB492	1.25	2SC681	2.50	2SC1172B	4.25	2SD315	.75
2SA815	.85	2SB495	.95	2SC684	2.10	2SC1209	.55	2SD318	.95
2SA816	.85	2SB507	.90	2SC687	2.50	2SC1213	.75	2SD341	.95
		2SB511	.70	2SC696	2.35	2SC1226	1.25	2SD350	3.25
2SB22	.65			2SC712	.70	2SC1243	1.50	2SD352	.80
2SB54	.70	2SC206	1.00	2SC713	.70	2SC1293	.85	2SD380	5.70
2SB56	.70	2SC240	1.10	2SC732	.70	2SC1308	4.75	2SD389	.90
2SB77	.70	2SC261	.65	2SC733	.70	2SC1347	.80	2SD-390	.75
2SB128	2.25	2SC291	.65	2SC739	.70	2SC1383	.75	2SD437	5.50
2SB135	.95	2SC320	2.00	2SC715	1.75	2SC1409	1.25		
2SB152	4.50	2SC352	.75	2SC762	1.90	2SC1410	1.25	MPS-U31	4.00
2SB173	.55	2SC353	.75	2SC783	1.00	2SC1447	1.25	MPS8000	1.25
2SB175	.55	2SC371	.70	2SC784	.70	2SC1448	1.25		
2SB178	1.00	2SC372	.70	2SC785	1.00	2SC1507	1.25		
2SB186	.60	2SC394	.70	2SC793	2.50	2SC1509	1.25		

POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204	1300V	3.90	BU207	1300V	5.40	2SC1172B	1100V	4.25
BU205	1500V	4.70	BU208	1500V	6.25	2SC1308	1100V	4.95
BU206	1700V	5.90	2SC1170	1100V	4.00	2SC1325	1100V	4.95

OEM SPECIALS

1N270	.10	2N960	.55	2N2219A	.30	2N2913	.75	2N3740	1.00	2N4401	.20
1N914	.10	2N962	.40	2N2221	.25	2N2914	1.20	2N3771	1.75	2N4402	.20
		2N967	.50	2N2221A	.30	2N2916A	3.65	2N3772	1.90	2N4403	.20
2N173	1.75	2N1136	1.35	2N2222	.25	3N3019	.50	2N3773	3.00	2N4409	.20
2N178	.90	2N1142	2.25	2N2222A	.30	2N3053	.30	2N3819	.32	2N4410	.25
2N327A	1.15	2N1302	.25	2N2270	.40	2N3054	.70	2N3823	.70	2N4416	.75
2N334	1.20	2N1305	.30	2N2322	1.00	2N3055	.75	2N3856	.20	2N4441	.85
2N336	.90	2N1377	.75	2N2323	1.00	2N3227	1.00	2N3866	.85	2N4442	.90
2N338A	1.05	2N1420	.20	2N2324	1.35	2N3247	3.40	2N3903	.20	2N4443	1.20
2N398B	.90	2N1483	.95	2N2325	2.00	2N3250	.50	2N3904	.20	2N4852	.55
2N404	.30	2N1540	.90	2N2326	2.85	2N3375	6.50	2N3905	.20	2N5061	.30
2N443	1.75	2N1543	2.70	2N2327	3.80	2N3393	.20	2N3906	.25	2N5064	.50
2N456	1.10	2N1544	.80	2N2328	4.20	2N3394	.17	2N3925	3.75	2N5130	.20
2N501A	3.00	2N1549	1.25	2N2329	4.75	2N3414	.17	2N3954	3.50	2N5133	.15
2N508A	.45	2N1551	2.50	2N2368	.25	2N3415	.18	2N3954A	3.75	2N5138	.15
2N555	.45	2N1552	3.25	2N2369	.25	2N3416	.19	2N3955	2.45	2N5198	3.75
2N652A	.85	2N1554	1.25	2N2484	.32	2N3417	.20	2N3957	1.25	2N5294	.50
2N677C	6.00	2N1557	1.15	2N2712	.18	3N3442	1.85	2N3958	1.20	2N5296	.50
2N706	.25	2N1560	2.80	2N2894	.40	2N3553	1.50	2N4037	.60	2N5306	.20
2N706B	.40	2N1605	.35	2N2903	3.30	2N3563	.20	2N4093	.85	2N5354	.20
2N711	.50	2N1613	.30	2N2904	.25	2N3565	.20	2N4124	.20	2N5369	.20
2N711B	.60	2N1711	.30	2N2904A	.30	2N3638	.20	2N4126	.20	2N5400	.40
2N718	.25	2N1907	4.10	2N2905	.25	2N3642	.20	2N4141	.20	2N5401	.50
2N718A	.30	2N2060	1.85	2N2905A	.30	2N3643	.15	2N4142	.20	2N5457	.35
2N720A	.50	2N2102	.40	2N2906	.25	2N3645	.15	2N4143	.20	2N5458	.30
2N918	.35	2N2218	.25	2N2906A	.30	2N3646	.14	2N4220A	.45	C103y	.25
2N930	.25	2N2218A	.30	2N2907	.25	2N3730	1.50	2N4234	.95	C103d	.40
2N956	.30	2N2219	.25	2N2907A	.30	2N3731	2.75	2N4400	.20	C106b1	.50
										C106di	.75

SILICON UNIJUNCTIONS

2N2646	.50	2N4871	.50
2N2647	.60	2N4891	.50
2N6027	.55	2N4892	.50
2N6028	.70	2N4893	.50
D5E37	.25	2N4894	.50
2N2160	.65	MU10	.40
2N4870	.50		

INTEGRATED CIRC.

UA703C	.40
709C OP. AMP.	.25
741C OP. AMP.	.25
7400	.15
TA7061P	3.50
TA7205P	8.00
UPC1001h2	6.00
Ne555	1.25

RECTIFIERS

	10	100
IN4001	.60	5.00
IN4002	.70	6.00
IN4003	.80	7.00
IN4004	.90	8.00
IN4005	1.00	9.00
IN4006	1.10	10.00
IN4007	1.20	11.00

nte

New-Tone Electronics
P.O. Box 1738 A
Bloomfield, N.J. 07003
Phone: (201) 748-6171
748-6172
748-6173

ALL PARTS GUARANTEED

N.J. residents add 5% sales tax. Minimum order $5.00. All orders add $1.00 postage. Dealers write or phone for discount prices.

CIRCLE 38 ON FREE INFORMATION CARD

Data sheets. Specifications. Applications information.

New TTL Data Book. Only $4.95

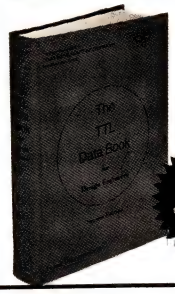

The TTL Data Book, second edition, 832 pages. $4.95

Five more valuable reference aids.

The Optoelectronics Data Book, 368 pages, $2.95.

The Semiconductor Memory Data Book, 272 pages, $2.95.

The Transistor and Diode Data Book, 1,248 pages, $4.95.

The Linear Control Circuits Data Book, 368 pages, $2.95.

The Power Semiconductor Data Book, 816 pages, $3.95.

The newest edition of the TTL Data Book for Design Engineers. Detailed specifications on over 900 TTL device types. Standard TTL, high-technology Schottky-clamped TTL. Pin assignment drawings of all TTL types. The most complete book on TTL logic written by the same company that invented the IC.

A must for every scientist, engineer, and technician!!!!!

REL

REL PRINTED CIRCUIT BOARD PROJECTS

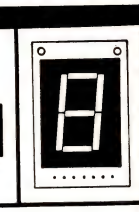

MODU-CLOCK

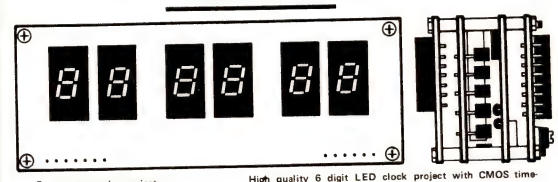

Our most popular project

- 1.5" x 4"
- 6 digit LED
- 4 stackable boards
- CMOS timebase for DC operation
- Drilled, etched, plated boards

High quality 6 digit LED clock project with CMOS timebase. Comes with readout board (DL-707, MAN-1 type etc.), clock board (MM5314), power board, CMOS timebase board. All boards stack behind each other. 4 board set. Clock may be constructed for AC or DC operation.

ONLY.....$5.95

DECADE COUNTER MODULE

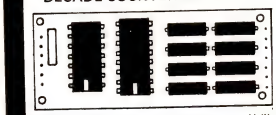

Decade counter board for building counters. Utilizes a 7447 decode driver and a 7490 decade counter. Directly drives common anode LED readouts. Use with our DM-5 and DM-8 Digit Modules. ONLY 70¢ ea 10 for $6.00

6 DIGIT READOUT BOARDS

Multiplexed connections for clocks, counters, etc. Corner holes for mounting.

Part NO.	Use with	price	Dim.
DB-63	FND 357	$2.25	1.5" x 4"
DB-67	DL-707, MAN-1 type etc.		1.5" x 4" $2.25
DB-65	FND 500/507/510	$3.00	1.5" x 5"

CMOS COOKBOOK

new

A complete and detailed guide to CMOS. Theory and applications. 414 p. $9.95

DIGIT-MODULE STRIP

DM-5 STRIP
5 digit strip for use with FND 500/507 LED readouts. Dim 1" x 3.5"

$2.25/ strip

DIGIT-MODULES

Versatile boards for mounting and wiring LED displays. For clocks, counters, timer etc.

Part No.	Use with	Price	Dim.
DM-5	FND 500/507	.50	.7" x 1"
DM-8	FND 800/807	.70	1" x 1.5"

UNIVERSAL BREADBOADING ELEMENT WITH SOLDERLESS, PLUG-IN TIE POINTS

SUPER-STRIPS

FREE FREE FREE

Free interconnect wire bundle with every super strip.

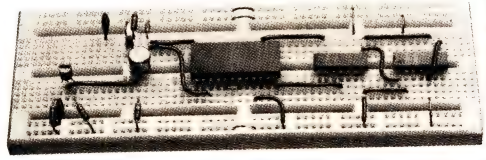

- Combine distribution system with universal .1" x .1" matrix
- 840 solderless, plug-in tie-points
- Accommodates up to 9 14-pin DIPs
- Compatible with all DIP's and discretes with lead diameters to .032"
- Require no special patch cords

SS-2 (Nickel/silver terminals). . . . 923252 $17.00

POTENTIOMETER HEX NUTS

Standard hex nuts for all 3/8" potentiometer bushings. High quality, chrome plated.

25 FOR $1.00

DIGITAL INTEGRATED CIRCUITS

TTL

7400	.20
7401	.20
7402	.20
7403	.20
7404	.20
7405	.20
7406	.24
7407	.24
7408	.20
7409	.20
7410	.20
7411	.20
7412	.20
7413	.24
7414	.88
7416	.24
7417	.24
7420	.20
7421	.24
7423	.34
7425	.34
7426	.24
7427	.32
7428	.27
7430	.20
7432	.24
7433	.29
7437	.24
7438	.24
7440	.20
7442	.52
7443	.62
7445	.69
7446	.69
7447	.69
7448	.69
7450	.20
7451	.20
7453	.20
7454	.20
7459	.20
7460	.20
7470	.29
7472	.29
7473	.29
7474	.29
7475	.48
7476	.31
7480	.69
7482	.69
7483	.69
7485	.89
7486	.27
7489	2.18
7490	.43
7491	.69
7492	.43
7493	.43
7494	.69
7495	.69
7496	.69

74100	1.27
74107	.29
74109	.32
74121	.34
74122	.43
74123	.60
74125	.39
74126	.39
74132	.69
74141	.87
74145	.69
74147	1.62
74148	1.29
74150	1.15
74151	.69
74153	.64
74154	1.02
74155	.69
74156	.69
74157	.69
74160	.87
74161	.87
74162	.87
74163	.87
74164	.95
74165	1.14
74166	1.25
74170	2.63
74173	1.41
74174	.97
74175	.92
74176	.78
74177	.78
74180	.69
74181	2.14
74182	.78
74184	2.18
74185	2.18
74188	3.49
74189	3.49
74190	1.22
74191	1.22
74192	.87
74193	.87
74194	.87
74195	.87
74196	.87
74197	.87
74198	1.48
74199	1.48
74251	1.08
74279	.54
74365	.66
74366	.66
74367	.66
74368	.66
8093	.39
8094	.39
8095	.66
8096	.66
8097	.66
8098	.66

75450	.87
75451	.60
75452	.60
75453	.60
75454	.60
75491	.80
75492	.83
75493	1.08
75494	1.18
82S25	2.18

CMOS

4000	.22
4001	.22
4002	.22
4006	1.22
4007	.22
4008	.78
4009	.43
4010	.43
4011	.22
4012	.22
4013	.39
4014	.95
4015	.95
4016	.39
4017	1.04
4018	1.04
4019	.23
4020	1.13
4021	1.23
4022	.95
4023	.22
4024	.83
4025	.22
4026	1.67
4027	.39
4028	.87
4029	1.13
4030	.22
4033	1.50
4034	3.49
4035	1.13
4040	1.13
4041	.78
4042	.78
4043	.69
4044	.69
4046	1.85
4049	.39
4050	.39
4051	1.25
4052	1.25
4053	1.25
4060	1.57
4066	.78
4071	.22

4072	.22
4073	.22
4075	.22
4081	.22
4082	.22
4502	.78
4510	1.13
4511	1.04
4514	2.79
4515	2.79
4516	1.22
4518	1.13
4520	1.13
4527	1.67
4528	.87
4585	1.22

HEP CROSS REFERENCE GUIDE

Only..... $1.00

HEP

A complete line of Motorola HEP is available from J. B. Saunders Company. Write or call our order desk for assistance when specifying your semiconductor needs.

To help in your needs, a valuable HEP cross reference guide is available.

RUBBER FEET

3M BRAND

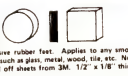

Moulded, adhesive rubber feet. Applies to any smooth, flat unflued surface such as glass, metal, wood, tile, etc. Non-skid, non mar. Peel off sheets from 3M. 1/2" x 1/8" thick. 1/2" round..... 8¢ 12 for..... 75¢ square..... 6¢ 12 for..... 55¢

HEP R0170 DIODE

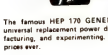

1000 PIV 2.5 A

The famous HEP 170 GENERAL PURPOSE DIODE. A universal replacement power diode. For TV's, audio, manufacturing, and experimenting. Brand new. Now at lowest prices ever.

20¢ EA. 100 for..... $14.50

OPTO ISOLATOR 4N27

NPN phototransistor and PN infrared emitting diode. 1500V isolation. 3ma collector output current. Excellent frequency response to 300khz. 2.1 microsecond switching time. Brand new MOTOROLA 6 pin DIP. With specs.

$1.00 10 for.. $9.00

1N4004 DIODE

400 PIV
1A

400 PIV @ 1A. Manufacturer prebent these units to .5 inches but did not cut leads. Straighten leads and save!!!

10 FOR $1.00

wire wrapping center

your one stop shopping for quality electronic parts and tools.

KYNAR WIRE WRAP

AWG	COLOR	100 FT.	1000 FT.
30 AWG	BLUE	$3.00	$14.95

NEW FROM ok®

Model BW-630

THE HOBBY-WRAP

COMPLETE WITH BIT AND SLEEVE

ONLY $34.95

Now you, the hobbyist, can do wire-wrapping professionally with our easy to use Hobby-Wrap gun.

FREE FREE

Order a BW-630 battery wire wrap tool and get a FREE 100 ft. roll of 30 ga. Kynar wire wrap wire.

.025 sq. post. AWG 30 wire (batteries not included)

HOBBY-WRAP-30 WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)

$5.95

FREE FREE

Order a HW-30 and get a FREE 25 ft. roll of 30 ga. Kynar wire wrap wire.

STRIP WRAP UNWRAP

TERMS

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE
ALL MERCHANDISE SUBJECT TO PRIOR SALE
24 HR SHIPMENT FOR CASHIERS CHECK OR MONEY ORDER
PERSONAL CHECKS ALLOW TIME FOR CLEARANCE
MINIMUM ORDER $5.00
NO COD'S
POSTAGE & HANDLING ADD $1
3 1/2% STATE TAX (COLO. RES.)

Customer Satisfaction Guarantee

We specialize in fast, prompt service with total customer satisfaction!! All items are guaranteed for 30 days from date of shipment, providing that no user inflicted damage has occured.

J. B. SAUNDERS CO.

STORE HOURS: 9:30 -- 5:30 Weekdays
9:30 -- 3:00 Saturdays

3050 VALMONT
BOULDER, COLO.
80301
(303) 442-1212

CIRCLE 63 ON FREE INFORMATION CARD

HOCKEY/SOCCER TV GAME

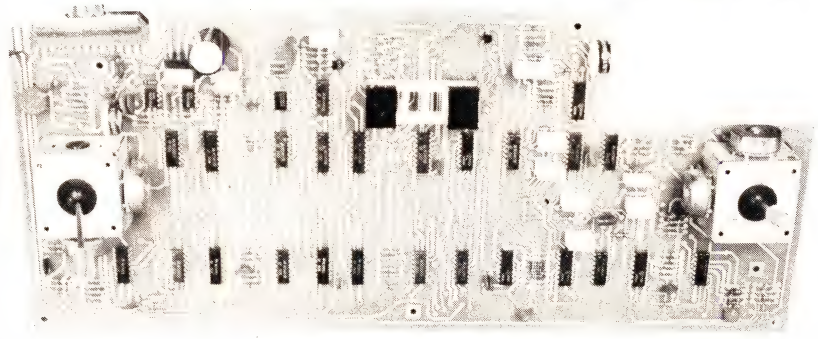

Complete kit of 4 TV games, and all necessary parts to display on your TV set.The games are HOCKEY & SOCCER, at 2 levels of skill. The display on the TV screen is on channel 3 or 4. It shows a field, either hockey or soccer, and 2 players. The puck or ball is set in motion, and the players attempt to move the ball or puck to the enemy goal. The players are controlled by 2 joy sticks, one for each player. In the hockey game,the puck stays with the player who gets it, and can be moved by moving the player, or pushing the 'shoot' button, which then shoots the puck in the direction it was going. The other player attempts to block the shot, and shoot it in the other direction. Each time the puck hits the the wall, it 'pings', and when a goal is scored, it 'pongs'. The score is displayed by 2 LED readouts, which automaticaly score up to 8 each. Scoreboard can be reset at any time by pushing the reset button. The skill needed can be controlled by pushing the 'novice or skilled' button

The soccer game is played the same as above, except that the ball goes as if it were kicked each time it touches a player. Scoring and skill is controlled the same as the hockey game above.

We provide the logic board, shown in the upper left photo, the LED READOUTS,the power transformer, the speaker, the line cord, the case and interface cube, shown in the photo to the right. The interface cube is actually a miniature TV transmitter, which puts the games on your TV set. This interface meets FCC requirements. In short, we provide everything you need to put this game on your TV set. An hour with some wire, solder and soldering iron is all you need We have about 2000 sets, but only about 1000 bases for the case, so the first 1000 orders get the base. Otherwise, you will need a piece of masonite or ply wood 7½"x 17 5/8"

STOCK NO.M5495 $27.50 complete kit as above 2/50.00

DELTA ELECTRONICS CO.

P.O. BOX 2,AMESBURY MA 01913
Phone (617) 388—4705

MINIMUM ORDER $5.00. Include sufficient postage, excess refunded. Send for new 88 page Catalog 15, bigger than ever.

BANKAMERICARD and MASTERCHARGE now accepted, minimum charge $15.00. Please include all numbers. Phone orders accepted.

CIRCLE 27 ON FREE INFORMATION CARD

2708-8K EPROM $45.00
2522 STATIC SHIFT REG . . . . . $ 1.95
2513 CHARACTER GEN . . . . . $ 9.95
2518-HEX 32 BIT SR . . . . . $ 3.50
2102-1 1024 BT RAM . . . . . $ 1.49
5280-4K DYNAMIC RAM . . . . . $ 6.95
5202A UV PROM . . . . . $ 6.95
MM5203 UV PROM . . . . . $ 6.95
1702A UV PROM . . . . . $ 6.95
5204-4K PROM $10.95

MINIATURE MULTI-TURN TRIM POTS
100,500,1K,2K,5K,10K,100K,200K, 1 Meg.
$.75 each . . . . . .3/$2.00

MULTI-TURN TRIM POTS Similar to Bourns 3010 style 3/16"x5/8"x1-1/4"; 50, 100, 1K, 10K, 50K ohms
$1.50 ea. . . . . .3/$4.00

LIGHT ACTIVATED SCR's
TO-18, 200V 1A. . . . . $ 1.75

TRANSISTOR SPECIALS

2N3585 NPN Si TO-66 . . . . . $ .95
2N3772 NPN Si TO-3 . . . . . $ 1.60
2N456A PNP GE . . . . . $ .75
2N4908 PNP Si TO-3 . . . . . $ 1.00
2N6056 NPN Si TO-3 Darlington . $ 1.70
2N5086 PNP Si TO-92 . . . . . 4/$ 1.00
2N4898 PNP TO-66 . . . . . $ .60
2N404 PNP GE TO-5 . . . . . 5/$ 1.00
2N3919 NPN Si TO-3 RF . . . . . $ 1.50
MPSA 13 NPN Si TO-92 . . . . . 3/$ 1.00
2N3767 NPN Si TO-66 . . . . . $ .70
2N2222 NPN Si TO-18 . . . . . 5/$ 1.00
2N3055 NPN Si TO-3 . . . . . $ .80
2N3904 NPN Si TO-92 . . . . . 5/$ 1.00
2N3906 PNP Si TO-92 . . . . . 5/$ 1.00
2N5296 NPN Si TO-220 . . . . . $ .50
2N6109 PNP Si TO-220. . . . . $ .55
2N3638 PNP Si TO-5 . . . . . 5/$ 1.00
2N65l 7 NPN TO-92 Si . . . . . 3/$ 1.00

C/MOS (DIODE CLAMPED)

74C02— .22	4015— .95	4029—1.10
74C10— .22	4016— .40	4030— .22
74C193-1.50	4017—1.05	4033—1.50
4001— .22	4018—1.00	4035—1.10
4002— .22	4019— .25	4042— .78
4006—1.20	4020—1.05	4047—2.00
4007— .22	4022— .95	4049— .40
4009— .42	4023— .22	4050— .40
4010— .42	4024— .75	4055—1.50
4011— .22	4025— .22	4066— .80
4012— .22	4026—1.25	4071— .22
4013— .40	4027— .40	4076—1.05
	4028— .88	

MCA-81 OPTICAL LIMIT SWITCH. $1.50

LED READOUTS

FND 500-.5" C.C. $1.25
HP 7740-.3" C.C. . . . . $ .95
MAN-7-.3" C.A. . . . . $ .95
NS 33-3 dig. array . . . . . $ .75
DL 747 . . . . . $1.60

PRINTED CIRCUIT BOARD

4-1/2"x6-1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched
$.50 ea. . . . . 5/$2.20

7 WATT LD-65 LASER DIODE IR $8.95

2N 3820 P FET . . . . . $ .45
2N 5457 N FET . . . . . $ .45
TIS 43 UJT . . . . . $ .35
ER 900 TRIGGER DIODES . . 4/ $1.00
2N 6028 PROG. UJT . . . . . $ .65
8 PIN DIP SOCKETS . . . . . $ .24
14 PIN DIP SOCKETS . . . . . $ .25
16 PIN DIP SOCKETS . . . . . $ .28
18 PIN DIP SOCKETS . . . . . $ .30
24 PIN DIP SOCKETS . . . . . $ .40
40 PIN DIP SOCKETS . . . . . $ .60

VERIPAX PC BOARD

This board is a 1/16" single sided paper epoxy board, 4½"x6½" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with busses for power supply connector. $4.00

MV 5691 YELLOW-GREEN BIPOLAR LED $1.25
FP 100 PHOTO TRANS . . . . . $ .50
RED, YELLOW, GREEN OR AMBER LARGE LED's . . . ea. $ .20
MOLEX PINS . . . . . 100/$1.00
1000/$7.50
10 WATT ZENERS 3.9, 4.7, 5.6, 8.2,10, 12, 15,18, 22, 100, 150 or 200V ea. $ .60
1 WATT ZENERS 4.7, 5.6, 18 OR 22V . . . . . ea. $ .25
MC6860 MODEM CHIP. $9.95

Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A
100	.06	.14	.30	.80	3.70
200	.07	.20	.35	1.15	4.25
400	.09	.25	.50	1.40	6.50
600	.11	.30	.70	1.80	8.50
800	.15	.35	.90	2.30	10.50
1000	.20	.45	1.10	2.75	12.50

SILICON SOLAR CELLS

2¼" diameter
.4V at 500 ma. $4.00 / .2V at 200 mils $2.00

REGULATED MODULAR POWER SUPPLIES

+ – 15 VDC AT 100ma 115VAC INPUT $27.95
5VDC AT 1A. 115VAC INPUT . . . $24.95
12 VDC AT .5 AMP $24.95
IN 4148 (IN914) . . . . . 15/$1.00

Send 25¢ for our catalog featuring Transistors and Rectifiers
145 Hampshire St., Cambridge, Mass.

TANTULUM CAPACITORS

.22UF 35V 5/$1.00	6.8UF 35V 3/$1.00
.47UF 35V 5/$1.00	22UF 35V $ .40
.68UF 35V 5/$1.00	30UF 6V $ .40
1UF 35V 5/$1.00	33UF 35V $ .40
2.20UF 20V5/$1.00	47UF 20V 5/$1.00
3.3UF 35V 4/$1.00	100UF 35V $ .35
4.7UF 35V 4/$1.00	150UF 15V $ .50

M7001 ALARM CLOCK CHIP. . . . $5.75

NATIONAL MOS DEVICES

MM1402— 1.75	MM5057— 2.25
MM1403— 1.75	MM5058— 2.75
MM1404— 1.75	MM5060— 2.75
MM5013— 2.50	MM5061— 2.50
MM5016— 2.50	MM5555— 4.75
MM5017— 2.70	MM5556— 4.75
MM5055— 2.25	MM5210— 1.95
MM5056— 2.25	MM5260— 1.75

#24, EIGHT CONDUCTOR SPECTRA FLAT CABLE 10'/$1.50 100'/$13.50

#30 WIRE WRAP WIRE SINGLE STRAND 100'/$1.40

TTL IC SERIES

7400— .15	7445— .70	74151— .70
7401— .15	7446— .70	74153— .65
7402— .15	7447— .70	74154—1.10
7403— .15	7448— .70	74155— .70
7404— .20	7450— .20	74157— .70
7405— .20	7472— .33	74161— .85
7406— .25	7473— .35	74163— .80
7407— .25	7474— .35	74164— .95
7408— .25	7475— .49	74165—1.05
7409— .21	7476— .35	74173—1.40
7410— .15	7480— .35	74174— .95
7411— .20	7483— .70	74175— .92
7412— .20	7485— .88	74176— .75
7413— .45	7486— .30	74177— .79
7414— .70	7489—1.85	74180 .70
7416— .25	7490— .45	74181—2.10
7417— .25	7491— .70	74190—1.20
7420— .20	7492— .50	74191—1.20
7425— .28	7493— .45	74192— .85
7426— .25	7494— .70	74193— .85
7427— .30	7495— .70	74194— .85
7430— .20	7496— .70	74195— .75
7432— .25	74107— .32	74196— .88
7437— .25	74121— .38	74257—1.25
7438— .25	74123— .65	74279— .90
7440— .16	74125— .40	75324—1.75
7441— .85	74126— .40	75491— .65
7442— .52	74132— .82	75492— .65

MINIATURE DIP SWITCHES
CTS-206-4 Four SPST switches in one minidip package. . . $1.75
CTS-206-8 Eight SPST switches in a 16 pin DIP package. $1.95

5-8V SPST Miniature reed, relay., normally open, 330 Ohm coil resistance. $.75, 3/$2.00

ALCO MINIATURE TOGGLE SWITCHES
MTA 106 SPDT $1.20
MTA 206 DPDT $1.70

Full Wave Bridges

PRV	2A	6A	25A
200	.75	1.25	2.00
400	.95	1.50	3.00
600	1.20	1.75	4.00

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS. . . . . $ 7.95
Si 1020 G 20 WATTS $15.95
Si 1050 G 50 WATTS $27.95

CCD 110 LINEAR 256 XI BIT SELF SCANNING CHARGED COUPLED DEVICE $65.00

CCD 201 — 100 x 100 CHARGE COUPLED DEVICE $99.00

LINEAR CIRCUITS

LM307 —Op. Amp. . . . . $ .30
LM 309K 5V 1A REGULATOR . . $ .95
723 — 40 + 40VV REGULATOR . . $ .50
301/748-Hi Per. Op. Amp. . . . . $ .31
320T 5,12,15, or 24V NEG REG . . $1.25
709C Op. Amp. . . . . $ .31
78MGS-Pos 5 to 30V, 500 ma reg. $1.35
79MGS-Neg 5 to 30V, 500 ma reg. $1.35
CA 3047 Hi Pef. Op. Amp. . . . . $ .95
340T 5, 6, 8, 12, 15, 18, 24V POS REG. TO-220 . . . . . $1.10
741A or 741C OP AMP . . . . . $ .31
LM 308 Oper. Amp., Low Power . . $ .95
747 — DUAL 741 . . . . . $ .65
556 — DUAL TIMER $1.00
1456 — Oper. Amp. . . . . $ .95
LM 3900 — QUAD OP. AMP . . . . $ .49
LM 324 — QUAD 741 . . . . . $1.50
560 — PHASE LOCK LOOP $2.00
561 — PHASE LOCK LOOP $2.00
565 — PHASE LOCK LOOP $1.25
566 FUNCTION GEN. $1.65
567 — TONE DECODER $1.50
LM 1310N FM STEREO DEMOD. . $2.75
8038 IC VOLTAGE CONT. OSC. . $3.90
LM 370 — AGC SQUELCH AMP. . $1.15
555 — 2µs — 2 HR. TIMER. . . . . $ .45
553 QUAD TIMER . . . . . $ .45
IL5 (MCT-2) OPTO-ISOLATOR . . $ .80
1458 DUAL OP AMP. . . . . $ .60
LM 380 — 2W AUDIO AMP. . . . $ .95
LM 377 — 2W Stereo Audio Amp. . $2.50
LM 381 — STEREO PREAMP. . . . $1.50
LM 382 — DUAL AUDIO PREAMP $1.50
LM 311 — HI PER. COMPARATOR $ .90
LM 319 — Dual Hi Speed Comp. . . $1.25
LM 339 — QUAD COMPARATOR $1.50

TRIACS

PRV	1A	10A	25A
100	.40	.70	1.30
200	.70	1.10	1.75
400	1.10	1.60	2.60
600	1.70	2.30	3.60

SCR'S

PRV	1.5A	6A	35A
100	.40	.50	1.20
200	.60	.70	1.60
400	1.00	1.20	2.20
600		1.50	3.00

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage, Minimum Order $5.00, COD'S $20.00

SOLID STATE SALES
P.O. BOX 74D
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

CIRCLE 47 ON FREE INFORMATION CARD

S.D. SALES CO.

P. O. BOX 28810 – C
DALLAS, TEXAS 75228

JUMBO LED CAR CLOCK

$16.95

KIT

Alarm Option – $1.50
AC XFMR – $1.50

THE HOTTEST SELLING KIT WE EVER PRODUCED!

You requested it! Our first D.C. operated clock kit. Professionally engineered from scratch. Not a makeshift kluge as sold by others.

Features:

A. Bowmar Jumbo –.5 inch LED array.
B. MOSTEK – 50250 – Super Clock Chip.
C. On board precision crystal time base.
D. 12 or 24 Hr. Real Time Format.
E. Perfect for cars, boats, vans, etc.
F. P.C. Board and all parts (less case) included.

50,000 SATISFIED CLOCK KIT CUSTOMERS CANNOT BE WRONG!

THIS MONTH'S SPECIALS

AMD – 8080A	$14.95
Z-80 CPU	49.95
82S129 1K PROM	2.50

1702A 2K EPROM

We tell it like it is. We could have said these were factory new, but here is the straight scoop. We bought a load of new computer gear that contained a quantity of 1702 A's in sockets. We carefully removed the parts, verified their quality, and are offering them on one heck of a deal. First come, first served. Satisfaction guaranteed! U.V. Eraseable. $6.95 ea. 4/$25

UP YOUR COMPUTER!

21L02-1 1K LOW POWER 500 NS STATIC RAM Time is of the essence!

And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02 1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off.

8 for $12.95

60 HZ CRYSTAL TIME BASE
S.D. SALES EXCLUSIVE!

$5.95

KIT FEATURES:

A. 60HZ output with accuracy comparable to a digital watch.
B. Directly interfaces with all MOS Clock Chips.
C. Super low power consumption (1.5 ma typ.)
D. Uses latest MOS 17 stage divider IC.
E. Eliminates forever the problem of AC line glitches.
F. Perfect for cars, boats, campers, or even for portable clocks at ham filed days. 2/$10.00
G. Small size; can be used in existing enclosures.

Kit includes Crystal, Divider IC, PC Board, Plus all necessary parts and specs. At last count - over 20,000 sold!

S.D. SALES EXCLUSIVE

$12.95 MOS 6 DIGIT UP–DOWN COUNTER $12.95

40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYPE.), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare output, BCD and seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking. 1MHZ. count input frequency. Very limited quantity! WITH DATA SHEET

7400–19c	7411–29c	7451–19c	7490–65c	74153–75c
74LS00–49c	7413–50c	7453–19c	74LS90–95c	74154-1.00
7402–19c	7416–69c	7473–39c	7492–75c	74157–75c
74LS02–49c	7420–19c	7474–35c	7493–69c	74161–95c
7404–19c	7430–19c	74LS74-59c	7495–75c	74164-1.10
74L04–29c	7432–34c	7475–69c	7496–89c	74165-1.10
74S04–44c	7437–39c	7476–35c	74121-38c	74174–95c
74LS04-49c	7438–39c	7480–49c	74123-65c	74181-2.50
7406–29c	7440–19c	7483–95c	74132-1.70	74191-1.25
7408–19c	7447–85c	7485–95c	74S138-1.95	74192-1.25
7410–19c	7448–85c	7486–45c	74141-75c	74193-1.00

TTL INTEGRATED CIRCUITS — 74195–69c

1000 MFD Filter Caps

Rated 35 WVDC Upright style with PC leads. Most popular value for hobbyists. Compare at up to $1.19 ea. from franchise type electronic parts stores. S.D. Special 4/$1.

Slide Switch Assortment

Our best seller. Includes miniature and standard sizes; single and multi-position units. All new, first name brand. Try one package and you'll reorder more! Special 12/$1.00

RESISTOR ASSORTMENT

¼W 5% & 10% PC leads. A good mix of values. 200/$2.

P.C. LEAD DIODES

1N4148/1N914
100/$2.00
1N4002-1A.
100 PIV 40/$1.

HEAVY DUTY Full Wave Bridge

25 AMP 50 PIV
$1.25

DISC CAP ASSORTMENT

PC leads. At least 10 different values. Includes .001, .01, .05, plus other standard value.
60/$1.00

TRANSISTOR SPECIALS

EN2222 NPN	8 for $1.00
EN2907 PNP	8 for $1.00
2N3904 NPN	8 for $1.00
2N4400 NPN	10 for $1.00
2N4402 PNP	8 for $1.00

LED's WITH CLIPS

Jumbo Red. RL-2 by Litronix. With plastic mtg. clips which are very scarce.
4 for $1.00

C&K MINI TOGGLE SWITCH

No. 7101. S.P.D.T. Panel mount or P.C. mount. 79c
3 for $2.

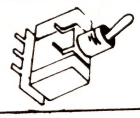

SIX DIGIT LED ALARM CLOCK KIT

We made a fantastic kit even better. Redesigned to take advantage of the latest advances in I.C. Clock technology. Features: Litronix Dual ½ inch displays, Mostek 50250 super clock chip, Single I.C. segment driver, SCR ditit drivers. Greatly simplified construction. More reliable and easier to build. Kit includes all necessary parts (except case). P.C.B. or XFMR optional.
ALL NEW DESIGN! P.C. Board – 3.00 AC XFMR – $1.50 KIT $9.95

Motorola SCR

2N4443. 8 AMP 400 PIV. P.C. Leads 3/$1.

FAIRCHILD - TBA 641

4W. Audio power Amp. Just out! In special heat sink DIP. One super audio IC.
$1.50 with data

FND-359 -Led Readout

.4 IN. Common Cathode. High effeciency. Has FND-70 PIN OUT. 59c

OUR CATALOG

is chocked full of rare parts bargains, deals, RAM or CPU kits, plus much more. Yours FREE!

PRICES SHOWN SUBJECT TO CHANGE WITHOUT NOTICE.

$15.95

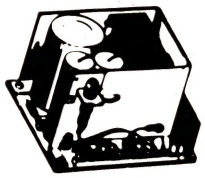

COMPUTER POWER SUPPLY

A very fortunate purchase. One of the best industrial quality REGULATED supplies we have seen. High performance, small size. Input is 120 VAC 60 HZ. Has the following regulated outputs: –5VDC@800MA; –15VDC @ 1.25 AMP; –25VDC @ 180 MA. Sold at a fraction of original cost. Do yourself a favor and order NOW. We expect a quick sellout.

NEXT MONTH:

S.D. will have music for your ears. Watch our ads.

For your Imsai or Altair 8080 Computer:
Z–80 CPU Kit – $149. 4K Low Power Ram Kit – $89.95

Terms: Money back guarantee. No COD. Texas residents add 5% sales tax. Add 5% of order for postage & handling. Orders under $10. add 75c. Foreign orders: US funds only!

Call your Bankamericard or Master Charge order in on our continental United States toll free Watts:
1–800–527-3460
Texas Residents Call Collect:
214/271-0022

Special Thanks to:
Dennis, Fred, Abe, Bill, Sam, Hal, Tom, Alex, John, Ely, and Larry

S.D. SALES CO.
P. O. BOX 28810
Dallas, Texas 75228

ORDERS OVER $15.00 – CHOOSE $1.00 FREE MERCHANDISE

CIRCLE 72 ON FREE INFORMATION CARD

AMAZING & HARD-TO-FIND SCIENCE BUYS!
ALTERNATE ENERGY
SPACE AGE • HOBBIES

SUPER POWER FOR ANY AM RADIO

Antenna assist has pulled in stations up to 1000 miles* off! No wires, clips, grounding. Solid state—no elec., batts., tubes.
No. 72,095EH $19.95 Ppd.
ULTRA SELECT-A-TENNA (OVER 1000* MILES)
No. 72,147EH $24.95
SUBJ. TO LOCAL COND.

SAVE 50%! 8 x 20 MONOCULAR

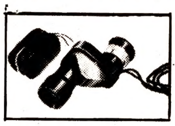

Top quality Spy Scope, a $30 value, now $14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box.
No.1568EH .. $14.95 Ppd.

SEE MUSIC IN PULSATING COLOR

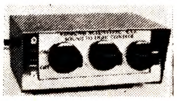

3-Channel Color Organ lets you modulate 3 independ. strings of colored lamps w/ intensity of your music. "Audio light show" flashes, responds to rhythm, pitch!
No. 42,309EH (ASSEMBLED).............$18.50 Ppd.
No. 42,336EH (UNASSEMBLED)........$15.95 Ppd.

NASA-CHOSEN FOR APOLLO/SOYUZ

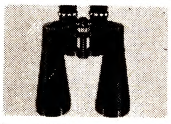

The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses; 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!
No. 1556EH ....(9¼x8½"; 47.5 oz) $99.95 Ppd.

110V FUEL MISER RECLAIMS HEAT

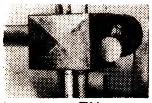

Save your 40% wasted heat to warm a basement, garage, rec rm. at no extra cost! Direct it your way instead of **up the chimney**. Fan-forced clean hot air via easy ducting!
No. 19,194EH (5" DIA.) Shpg. 17 lb. ..$121.50 FOB
No. 19,195EH (6" DIA.)

BUILD ALPHA MONITOR: $37.50!

All you need w/ your basic electronics knowledge (excl. 9v tr. batt.) for port. **biofeedback** unit, an aid to relaxation, concentration. 5 microvolt sensitivity; self-cont.
No. 61,069EH (KIT)..............................$37.50 Ppd.
No. 71,809EH (FULLY ASSEMBLED)..$59.95 Ppd.

PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18¾" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100X over omni-direction mikes. Catch sounds never bef. heard; highest signal to noise ratio poss. 5½ lb.
No. 1649EH (REQ. 2 9V BATT.)............$299.00 Ppd.

15% EFFICIENT SOLAR CELL!

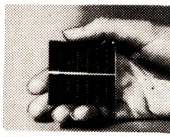

Largest, most powerful ever for terrestrial use, to build solar panels where max. power per unit area is req. Output up to 12w per sq. ft. Produces .8A @ .45 v; .38w output. 2" x 2" sq. 2 OZ.
No. 42,514EH.$39.95 Ppd.

CAN'T SLEEP, RELAX? TRY THIS!

Electronic sound conditioner simulates 4 kinds of soothing sounds of ocean surf & rain; "white" sound helps mask unwanted noise. Medical tests proved analgesic effects!
No. 71,997EH $89.95 Ppd.

QUALITY DETECTOR UNDER $40

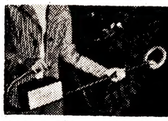

Our fully transistorized BFO unit can locate a quarter at 18". Powerful 6 trans.-oscillator-amplifier circuit. Comp. to others priced 50% more! Aluminum, just 2 lb.
No. 80,222EH $39.95 Ppd.

THERE IS NO OTHER TELESCOPE LIKE IT!

THE NEW EDMUND 4¼", f/4 NEWTONIAN WIDE FIELD REFLECTOR TELESCOPE

Patent Pending

Clear, bright, spectacular wide angle views of stars, moon, comets . . . easy to use . . . ***portable!***

IN SECONDS YOU'RE SCANNING THE ASTOUNDING UNIVERSE, able to see and study the breath-taking cosmos as perhaps you never have before . . . awesome vastness, unbelievable orderliness, stark silent beauty. All the fascinating heavenly mysteries are yours to enter and explore. This new reflector telescope makes it easy for everyone to span a thousand light-years to space-age enjoyment of the heavens and outdoors. No complicated set up! Just insert the eyepiece, focus, and its big 3½° field of view gives you more stars in a single view than any other type of telescope. Bright, crisp, finely resolved images to capture your interest and imagination. It's probably the easiest to use telescope ever . . . over your shoulder, in your lap, on a tripod. Or just rotate the spherical base on its own mount for use on a table, car hood. Take it anywhere (only 17", 10 lb.). Top quality optical system: 4¼", f/4 parabolic primary mirror (⅛ wave, 17" F.L.); prealigned ⅛ wave diagonal on a coated optical window seals optics from moisture and dust; 28mm Kellner eyepiece (gives 15X, higher without other eyepiece or Barlow). Fast focusing (25' to infinity). Bright Scharfanian red (doesn't impair night vision); adj. carrying strap. A "first" scope "must". an ideal second scope!
There is no other telescope like it. NO. 2001EH **$149.95 Ppd.**

FOR GREATER RELAXATION, CONCENTRATION,
listen to your Alpha and Theta brainwaves!

COMPARES WITH UNITS SELLING FOR $150 UP.

No. 1689EH

Do it with an amazing biofeedback monitor. This ultra-sensitive sensor detects brain signals, lets you monitor (hear and **see!**) your Alpha and Theta brainwaves. Great aid to relaxation, concentration. This portable (8 x 3 x 4") lightweight (24 oz.) metal unit has a unique electrode headband to slip on or off in seconds without messy creams or solutions. Hooked to amplifier, it filters brainwaves, and signals an audible beep for each Alpha or Theta wave passed. You get both audio and visual (L.E.D.) feedback with this reliable, completely safe unit. It operates on two 9v transistor batteries, offers features comparable to many costlier models. A comprehensive instruction booklet is included.

Do-It-Yourself Kit #61069EH .... $37.50 ppd.
Low Cost 'Starter' Unit #71809EH .... $59.95 ppd.

No. 1689EH JUST $99.95 Ppd.

LOW COST, HIGH QUALITY INFRA-RED EYE

BINOCULAR STYLE $329.95

STANDARD STYLE $299.95

A must for Infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, night-time wildlife study—any work requiring I.R. detection and conversion to the visible spectrum. Self-contained scope (11 x 14¼ x 3") includes I.R. light source (for up to 90' sight at night!), 6032 I.R. converter tube, f/3.5 telephoto lens, adjustable triplet eyepiece, an adapter for use with your car's cigarette lighter—more! Bright 1.6X image **(Binocular style gives super-bright 2.5X).** Focuses from 10' to infinity, runs on 6 or 12v DC.

Not for sale to Cal. residents other than authorized by U.S. Armed Forces, law enforcement agencies or solely for scientific research and education purposes.

STANDARD STYLE, STOCK NO. 1683EH ...... ONLY $299.95 Ppd.
BINOCULAR STYLE, STOCK NO. 1685EH ...... JUST $329.95 Ppd.

GIANT *FREE* 164 PG. CATALOG

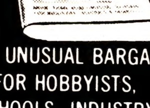

4000 UNUSUAL BARGAINS FOR HOBBYISTS, SCHOOLS, INDUSTRY

COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007

AMERICAN EXPRESS · Your BANKAMERICARD welcome here · master charge THE INTERBANK CARD

☐ SEND FREE 164 PG. CATALOG "EH"

Charge my ☐ American Exp. ☐ BankAmericard ☐ Master Chg.

Interbank No.__________

Card No.__________

Expiration Date__________

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.

Send me the following:

Stock No.	Quantity	Price Ea.

Add handling charge $_____1.00
Enclosed is ___check, ___M.O. in amount of $_____

Signature__________

Address__________

City, State, Zip__________

EDMUND SCIENTIFIC CO.
300 Edscorp Bldg., Barrington, N.J. 08007 • (609) 547-3488
America's Greatest Science • Optics • Hobby Center

CIRCLE 26 ON FREE INFORMATION CARD

Spring Specials

CB TRANSCEIVER
PORTABLE CB ANTENNA
UNIVERSAL LOCK MOUNT
OUTDOOR REFLEX HORN

FACTORY WARRANTY

direct from factory

Celebrate! Enjoy Year round, Springtime pleasure with these special spring factory offerings in top quality CB equipment. Buy the Deluxe PT-23 Transceiver and all the trimmings, or pick up any accessory you want. Our Spring specials include...

Deluxe Pt-23 CB Transceiver

- RF gain - Delta Tuning
- 23 Channel Mobile Radio
- ANL switch - Squelch Control
- 'S' - RF output meter
- CP - PA switch
- On-the-Air indicator
- Special Price $49.95 (Retail $129.95)
- 40 Channel unit also available . . . $69.95

Mobile CB Antenna

- Powerful heavy duty magnet...mount anywhere on car.
- Water proof coil-Center load
- For 23 or 40 channel
- Stainless steel whip, chrome plate
- Frequency range 26.965 - 27.255 mhz.
- Stand up to 100 mph.
- Special Price $9.95 (Retail $17.95)

CT-8 5" Outdoor Reflex Horn

- Available in black or copper color
- 10 watt power rating
- 8 ohm voice coil impedance
- 5 inch horn opening
- Special Price $3.95 (Retail $9.95)

Gs-10 CB Universal Lock Mount

- Easy to install
- Built-in lock
- Universal Slide mount
- Positive or Negative ground
- Special Price $3.45 (Retail $8.95)

EASTERN INDUSTRIAL CORP. INC.
1380 Jarvis Ave., Elk Grove Village, Illinois 60007
(312) 640-8737 Call Toll Free 800-323-0661

Please send:

☐ ___ PT-23 CB Tranceiver @ $49.95
☐ ___ CT-8 5" Reflex Horn @ $3.95
☐ ___ Gs-10 CB Lock Mount @ $3.45
☐ ___ CB Antenna @ $ 9.95

Illinois Residents add 5% Sales Tax

Enclosed please find ☐*Check* ☐*Money Order for $* .....

Add $2.00 shipping and handling charge for PT-23 Transceiver
Add 50 cents shipping and handling charge for each accessory item

☐ **Master Charge** ☐ **Bank Americard**

Account Number _____ **Expiry Date** _____

eic **EASTERN INDUSTRIAL CORP. INC.**
1380 Jarvis Ave., Elk Grove Village, Illinois 60007
(312) 640-8737

CIRCLE 87 ON FREE INFORMATION CARD

The 40-channel Cobra 29XLR. From the sleek brushed chrome face to the matte black housing, it's a beauty. But its beauty is more than skin deep. Because inside, this CB has the guts to pack a powerful punch.

The illuminated 3-in-1 meter tells you exactly how much power you're pushing out. And pulling in. It also measures the system's efficiency with an SWR check. In short, this Cobra's meter lets you keep an eye on your ears.

The Digital Channel Selector shows you the channel you're on in large LED numerals that can be read clearly in any light. There's also switchable noise blanking to reject short-pulse noise other systems can't block. The built-in power of DynaMike Plus. Automatic noise limiting and Delta Tuning for clearer reception.

And the added protection of Cobra's nationwide network of Authorized Service Centers with factory-trained technicians to help you with installation, service and advice.

The Cobra 29XLR. It has 40 channels. And it has what it takes to improve communications by punching through loud and clear on every one of them. That's the beauty of it.

Cobra

Punches through loud and clear.

Cobra Communications Products
DYNASCAN CORPORATION
6460 W. Cortland St., Chicago, Illinois 60635
Write for color brochure
EXPORTERS: Empire • Plainview, N.Y. • CANADA: Atlas Electronics • Toronto

PUNCH AND BEAUTY

CIRCLE 8 ON FREE INFORMATION CARD